

$$1. \quad \frac{v_1}{3} + \frac{v_1 - 2}{1} = 2$$

$$v_1 + 3(v_1 - 2) = 6$$

$$4v_1 = 12$$

$$v_1 = 3V$$

$$v_x = v_1 - v_2$$

$$v_x = 3V - 2V$$

$$v_x = 4V$$

$$2. \quad 20\Omega + 40\Omega = 60\Omega$$

$$\frac{v_p - 200}{60} + \frac{v_p}{100} + \frac{v_p - v_3}{50} = 0$$

$$= 5(v_p - 200) + 3v_p + 6(v_p - v_3) = 0$$

$$\Rightarrow 7v_p - 3v_3 = 500$$

$$(v_3 - v_p) + 25 + 5v_3 - 5v_4 = 0 \rightarrow -v_p + 6v_3 - 5v_4 = -25$$

$$v_3 = \frac{7v_p - 500}{3}$$

$$-20v_3 + 21v_4 = 600$$

$$v_p = \frac{31600}{181}$$

$$v_p = 171.5V$$

$$3. \quad \frac{V_L - V_M}{3} + \frac{V_L - V_R}{3} = 8 + 4 = 12$$

$$\frac{V_M - V_L}{3} + \frac{V_M - V_R}{1} + \frac{V_M}{5} + 4 = 0$$

$$\frac{V_R - V_L}{3} + \frac{V_R - V_M}{1} + \frac{V_R}{7} + 5 = 0$$

$$V_L = \frac{401}{15} \text{ V}, \quad V_M = \frac{53}{6} \text{ V}, \quad V_R = \frac{259}{30} \text{ V}$$

↓

$$V_M = \frac{53}{6} \text{ V} \rightarrow \begin{matrix} 1 \\ 2 \end{matrix} \boxed{8.33 \text{ V}}$$

$$P_D = \frac{V_R^2}{R} = \frac{\left(\frac{259}{30}\right)^2}{7} = \boxed{10.647 \text{ W}}$$

$$4. \quad \frac{12-V}{4} + \frac{12-V}{5} = V$$

$$5(12-V) + 4(12-V) = 20V$$


$$60 - 5V + 48 - 4V = 20V$$

$$108 = 29V$$

$$\frac{108}{29} = V$$

$$\frac{12 - \frac{108}{29}}{4} = \frac{60}{29} = \boxed{2.06A} \quad \leftarrow \text{For } u_1 (2V)$$
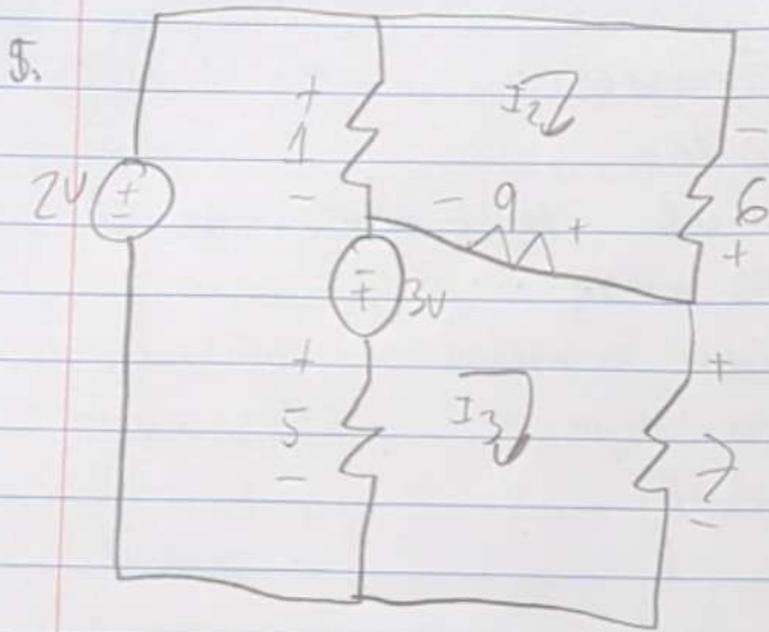
$$\frac{12 - \frac{108}{29}}{5} = \frac{48}{29} = \boxed{1.65A} \quad \leftarrow \text{For } u_2 (1V)$$



$$\begin{bmatrix} -(R_1 + R_5) & R_1 & -R_5 \\ -R_1 & (R_1 + R_2 + R_3) & -R_2 \\ -R_5 & -R_2 & (R_5 + R_4 + R_2) \end{bmatrix} \rightarrow \begin{bmatrix} -6 & 1 & -5 \\ -1 & 16 & -9 \\ -5 & -9 & 21 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ -3 \end{bmatrix}$$

$\begin{matrix} R & & I \end{matrix}$

$$A = \text{inv}(R) \times I$$

$$A = \begin{bmatrix} -0.55 \\ -0.24 \\ -0.38 \end{bmatrix}$$

7. a. The 1mA source is in an op amp that isn't ideal for input current of ϕ .

b. Each voltage source is a different voltage which can't be in the op amp.

8.

$$V_{out} = R_f \frac{-V_i}{R_x} = 2\text{k}\Omega \cdot \frac{-(-1)}{1\text{M}} = \boxed{2\text{V}}$$