

EXAM RULES

- 1) One 8.5" x 11" sheet permitted;
otherwise closed books, closed notes, open minds!
- 2) Scientific calculator is permitted; no computers and no phone!
- 3) **NO PHONES !!!**
Phones should not be visible at all!
A visible phone will result in a zero grade for the exam!
- 4) Write FULL NAME legibly on each page provided.
- 5) **PLEASE SHOW ALL WORK !!!**
This is essential to receive partial credit!
- 6) Please do not submit multiple answers. You must pick an answer!!
- 7) Write your solutions on the sheets provided.
No other paper/sheets/pages should be used!
- 8) Clearly label voltages and currents on the circuits provided.
- 9) Use the variables provided!
No additional variables should be used!
- 10) Unreadable work will receive NO CREDIT.
- 11) Please place important equations and answers within boxes as we have
done in lecture.
- 12) Please be careful with your algebra, signs, etc.
- 13) Please turn in your solutions to me at the end of the period!
- 14) **PLEASE DO NOT CHEAT !!!**


From the desk of Dr. A.A. Rodriguez

Problem # 1

Determine H , diff eq, t_s , y_{ss} , y ; Plot $|H(j\omega)|$ & $\angle H(j\omega)$


(All $R, L = 1$)

$$u = -3 + 7\cos\left(\frac{\pi}{4}t - 45^\circ\right)$$

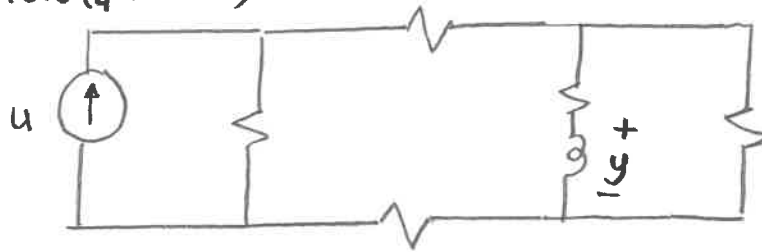


Problem 1

Problem 2

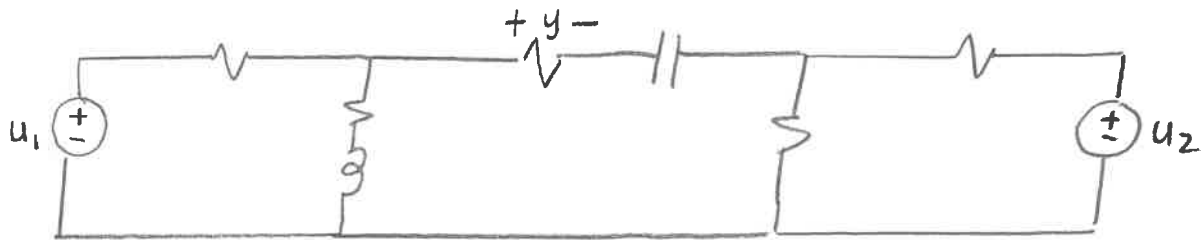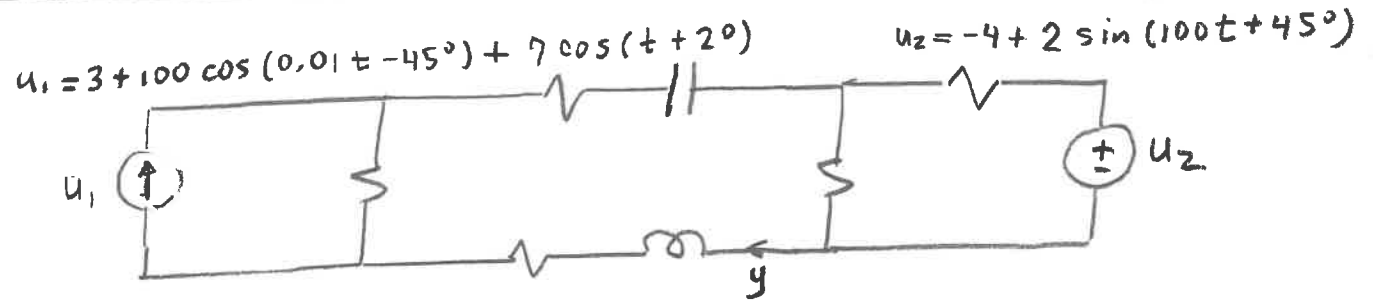Determine poles, t_s , $H_i(0)$, $H_i(\infty)$ $i=1,2$ (All $R,L,C=1$)

Problem 2

Problem 3


Determine $H_{1,2}$, diff eq, t_s , y_{ss} (All $R, L, C=1$)

Problem 3

Problem 4

Determine H , diff eq, y , y_{ss} (All $R, L = 1$)

Hint: Use KVL, KCL, Ohm!

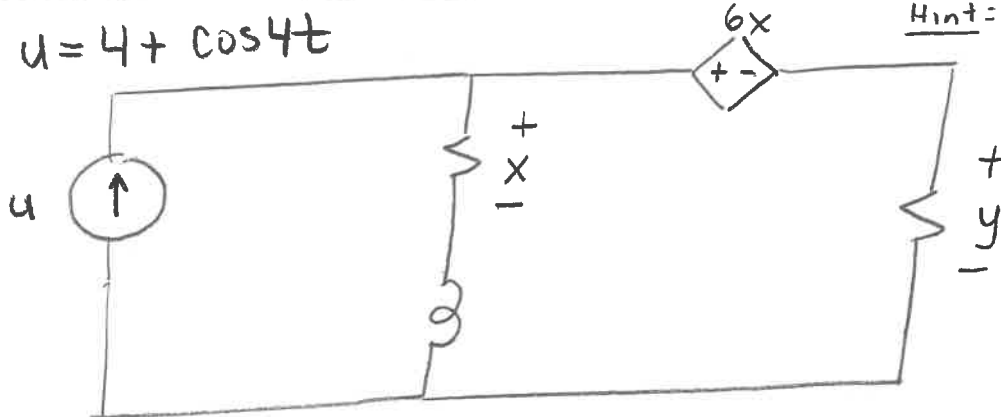

Problem 4

Problem 5

Determine t_s , y_{ss} , y

$$H(s) = \frac{s^2 + 1}{(s+2)(s^2 - 6s + 25)(s^2 + 2s + 4)}$$

$$u(t) = 5 - 60 \sin(t + 30^\circ) + 7 \cos(100t + 45^\circ)$$


Note:

Show how to calculate all coefficients associated with constants, sinusoids, & instabilities in y .

You are expected to do the easy calculations!

Problem 5

Problem 6

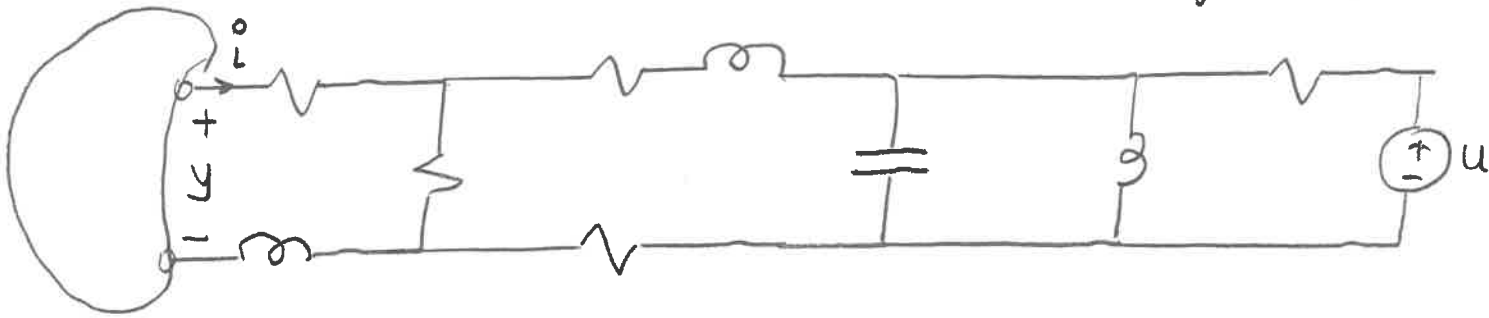Determine an s-domain Thevenin equivalent circuitMust specify Z_{th} & V_{th} ... emphasize process
... NOT algebra !!!


Problem 6

Problem 7

Determine H , y_{ss} , t_s


Note: (All $R, L, C = 1$)
Determine all coefficients in
 y_{ss} (approximately)

$$u(t) = 7 + 8 \sin(t + 45^\circ) - 50 \cos(100t - 80^\circ)$$

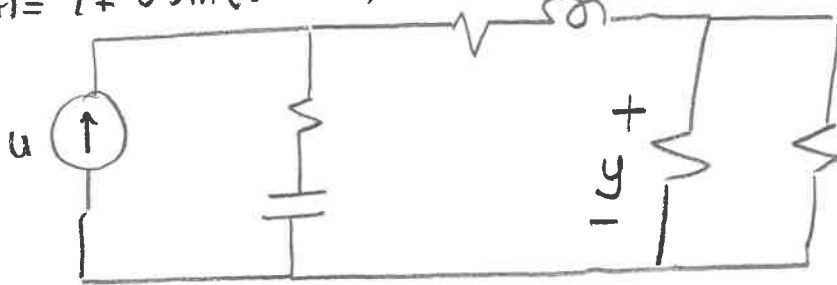

Problem 7

Problem 8

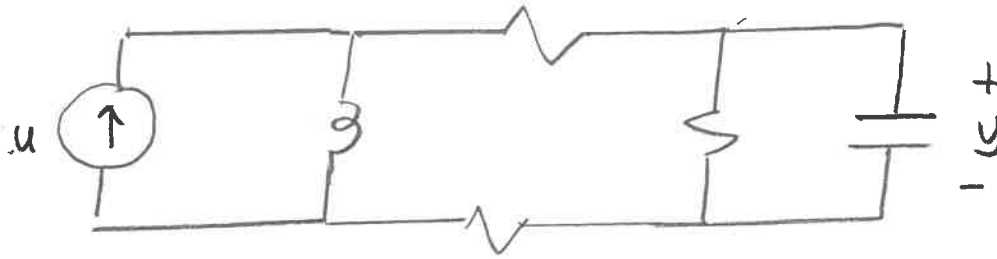Determine \mathcal{Z} , plot $|H(j\omega)|$ & $\angle H(j\omega)$ (All $R, L, C = 1$)

Problem 8

Problem 1

Determine H , diff eq, t_s , y_{ss} , y ; Plot $|H(j\omega)|$, $\angle H(j\omega)$

$$u = -3 + 7\cos(\frac{7}{4}t - 45^\circ)$$




(All $R, L = 1$)

$$M \leftrightarrow M/s$$

$$M \sin \omega_0 t \leftrightarrow \frac{M \omega_0}{s^2 + \omega_0^2}$$

$$M \cos \omega_0 t \leftrightarrow \frac{M s}{s^2 + \omega_0^2}$$

solution via source transformations

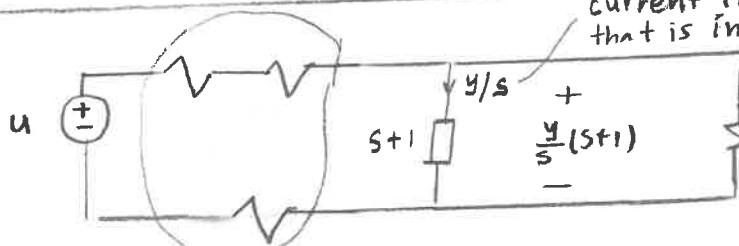

current through inductor is in series with it


$$\cos(x-y) = \cos x \cos y + \sin x \sin y$$

Note =

$$u(t) = -3 + 7(\cos(\frac{7}{4}t) \cos 45^\circ + \sin(\frac{7}{4}t) \sin 45^\circ)$$



$$U(s) = -\frac{3}{s} + 7 \left(\frac{s}{s^2 + (\frac{7}{4})^2} \right) \frac{1}{\sqrt{2}} + 7 \left(\frac{7/4}{s^2 + (\frac{7}{4})^2} \right) \frac{1}{\sqrt{2}}$$
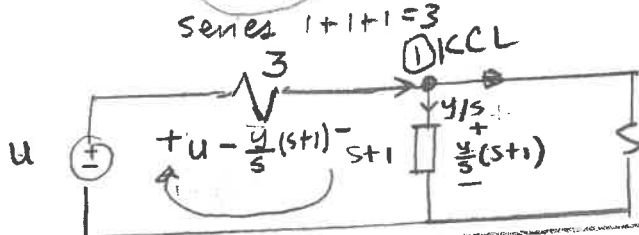
$$= \frac{\text{num}}{s(s^2 + (\frac{7}{4})^2)}$$



$$\text{KCL} \Rightarrow \left(\frac{u - \frac{y}{s}}{3} \right) = \left(\frac{y}{s} \right) + \left(\frac{y}{s} (s+1) \right)$$
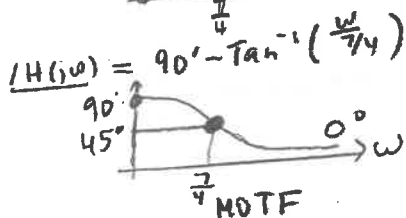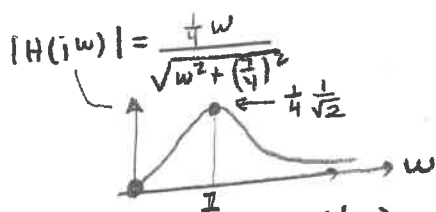
$$H(j\omega) = \frac{\frac{1}{4}j\omega}{j\omega + \frac{7}{4}}$$



$$y \left[\frac{1}{3} \left(\frac{s+1}{s} \right) + \frac{1}{s} + \frac{s+1}{s} \right] = \frac{1}{3} u$$

$$y [s+1 + 3 + 3s+3] = s u$$

$$4s+7 = 4(s + \frac{7}{4})$$

$$H(s) = \frac{y}{u} = \frac{\frac{1}{4}s}{s + 7/4}$$

$$\Rightarrow \dot{y} + \frac{7}{4}y = \frac{1}{4}\dot{u}$$

$$\Rightarrow \Phi(s) = s + \frac{7}{4} = 0$$

$$\Rightarrow \text{pole at } s = -\frac{7}{4}$$

$$\Rightarrow t_s = \frac{5}{|\text{pole}|} = \frac{5}{\frac{7}{4}} = \frac{20}{7} \text{ sec}$$

$$y_{ss} = -3H(0) + 7|H(j\frac{7}{4})| \cos(\frac{7}{4}t - 45^\circ + \angle H(j\frac{7}{4}))$$

$$H(0) = 0 \quad H(j\frac{7}{4}) = \frac{1}{4} \left[\frac{j\frac{7}{4}}{j\frac{7}{4} + \frac{7}{4}} \right] = \frac{1}{4} \left[\frac{1e^{j90^\circ}}{\sqrt{2}e^{j45^\circ}} \right] = \frac{1}{4\sqrt{2}} e^{j(90-45)}$$

$$Y = H U = \left[\frac{\frac{1}{4}s}{s + \frac{7}{4}} \right] \left[\frac{\text{num}}{s(s^2 + (\frac{7}{4})^2)} \right] = \frac{A}{s} + \frac{B}{s + \frac{7}{4}} + \left[\frac{C}{s - j\frac{7}{4}} + * \right]$$

$$A = \lim_{s \rightarrow 0} s Y(s) = s H(s) \left[\frac{-3}{s} + \frac{7}{s^2 + (\frac{7}{4})^2} \right] \Big|_{s=0} = -3H(0)$$

$$B = \lim_{s \rightarrow -\frac{7}{4}} (s + \frac{7}{4}) Y(s)$$

$$C = \lim_{s \rightarrow j\frac{7}{4}} (s - j\frac{7}{4}) Y(s) = \frac{7|H(j\frac{7}{4})|}{2} e^{j(-45^\circ + \angle H(j\frac{7}{4}))}$$


$$y = A + B e^{-\frac{7}{4}t} + 2|C| \cos(\frac{7}{4}t + \angle C)$$

$$y_{ss} \text{ (MOTF)}$$

Note: You need to compute num in $U(s)$ to actually show that the right hand side holds!

Problem 1

pole check:
set $u=0$

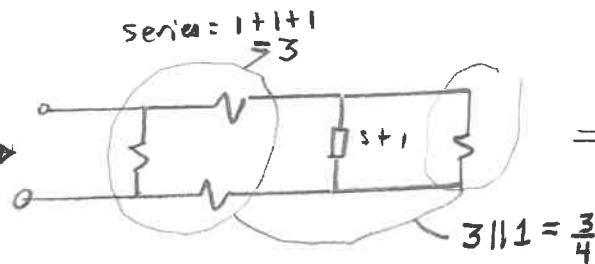


$$Z = s + 1 + \frac{3}{4}$$

$$= s + \frac{7}{4} = 0$$



$$\Rightarrow \text{pole} = -\frac{7}{4}$$

Gain Checks:

Analysis at $s=0$ | $Z_L = sL = 0$ (short)

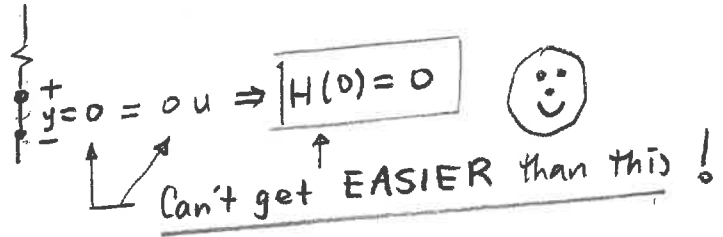


Analysis at $s=\infty$ | $Z_L = sL = \infty$ (open)

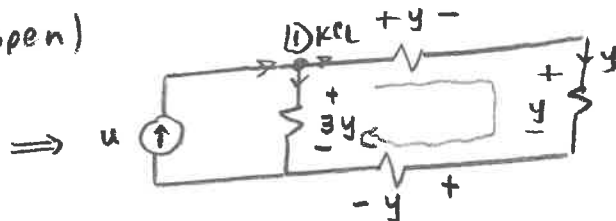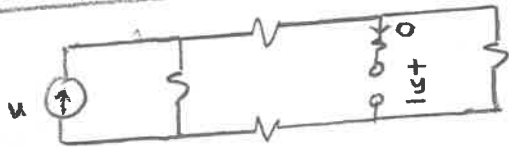

$$\Rightarrow H(\infty) = \frac{1}{4}$$

\Rightarrow Good to always check gains at dc ($s=0$) & $s=\infty$!

solution via KVL, KCL, Ohm:

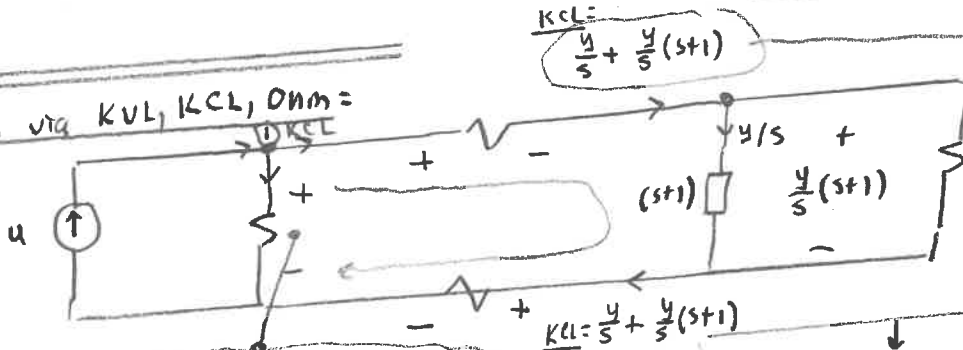

$$\left[\frac{y}{s} + \frac{y}{s}(s+1) \right] + \left[\frac{y}{s}(s+1) \right]$$

$$+ \left[\frac{y}{s} + \frac{y}{s}(s+1) \right]$$

$$= \frac{2y}{s} + \frac{3y}{s}(s+1)$$

$$\text{KCL: } u = \left[\frac{2y}{s} + \frac{3y}{s}(s+1) \right] + \left[\frac{y}{s} + \frac{y}{s}(s+1) \right]$$

$$\Rightarrow y [2 + 3s + 3 + 1 + s + 1] = su$$



$$\Rightarrow y [4s + 7] = su$$

$$\Rightarrow H(s) = \frac{\frac{1}{4}su}{s + \frac{7}{4}}$$

Just like what we got before!


2113

Problem 2

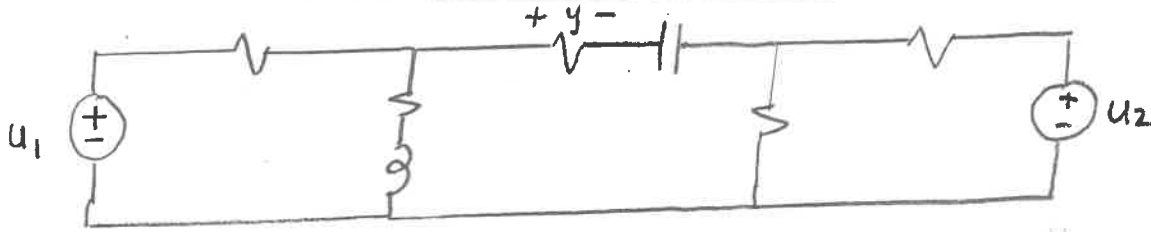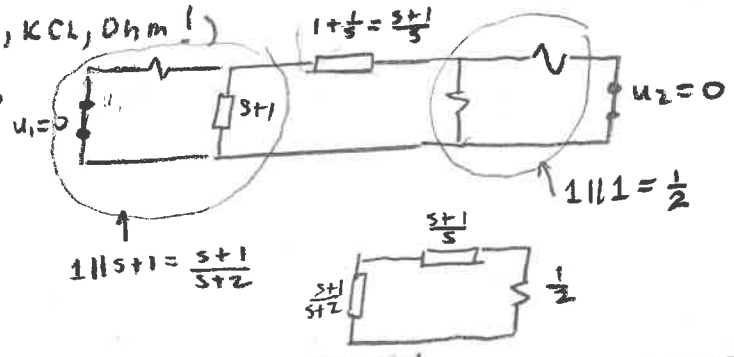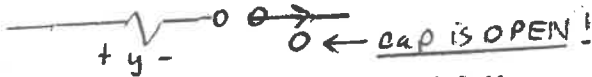Determine poles, t_s , $H_i(0)$, $H_i(\infty)$ $i=1,2$ (All $R, L, C=1$)solution for poles, t_s (without KVL, KCL, Ohm!)Set $u_1 = 0$ (short), $u_2 = 0$ (short) \Rightarrow 


$$Z = \frac{s+1}{s+2} + \frac{s+1}{s} + \frac{1}{2} = \frac{s(s+1) + (s+1)(s+2) + \frac{1}{2}s(s+2)}{s(s+2)} = \frac{s^2 + s + s^2 + 3s + 2 + \frac{1}{2}s^2 + s}{s(s+2)}$$

$$\frac{5}{2}s^2 + 5s + 2 = \frac{5}{2} \left[s^2 + 2s + \frac{4}{5} \right]$$

Analysis at $s=0$
 $Z_L = sL = 0$ (short)
 $Z_C = \frac{1}{sC} = \infty$ (open)


$$\Rightarrow y = 0 = 0u_1 + 0u_2$$

$$\Rightarrow H_1(0) = H_2(0) = 0$$

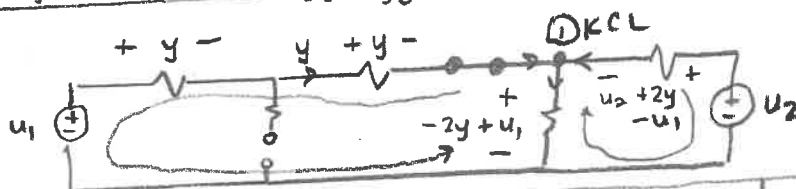Analysis at $s=\infty$
 $Z_L = sL = \infty$ (open)
 $Z_C = \frac{1}{sC} = 0$ (short)


$$\textcircled{1} \text{ KCL: } \bar{y} + (u_2 + 2y - u_1) = (-2y + u_1)$$

$$\Rightarrow y[1+2+2] = u_1[1+1] - u_2$$


$$\Rightarrow y = \left(\frac{2}{5}\right)u_1 + \left(-\frac{1}{5}\right)u_2 \Rightarrow H_1(\infty) = \frac{2}{5} \quad H_2(\infty) = -\frac{1}{5}$$

$$\Rightarrow \Phi = s^2 + 2s + \frac{4}{5} = 0$$

$$\text{poles} \Rightarrow s_{1,2} = \frac{-2 \pm \sqrt{4 - \frac{16}{5}}}{2}$$

$$= -1 \pm \sqrt{1 - \frac{4}{5}}$$

$$= -1 \pm \frac{1}{\sqrt{5}}$$

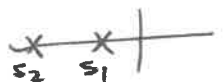


stable




$$t_s = \frac{5}{|s_1|} = 1 - \frac{1}{\sqrt{5}}$$

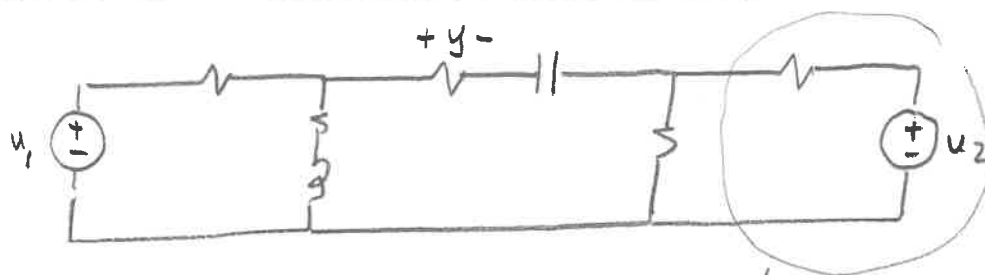Problem 2

Determine poles, t_s , $H_i(0)$, $H_i(\infty)$ $i=1,2$ (All $R,L,C=1$)



Long Solution = Find $H_{1,2}$!

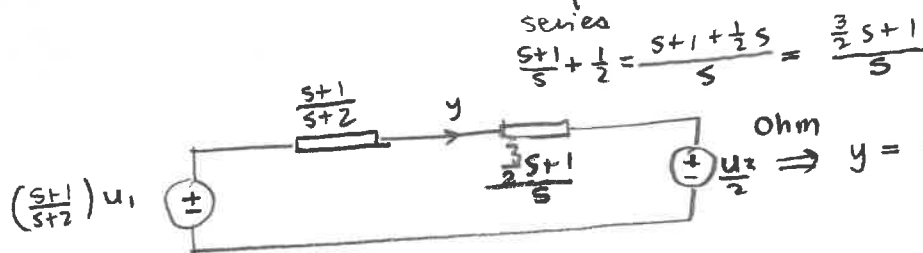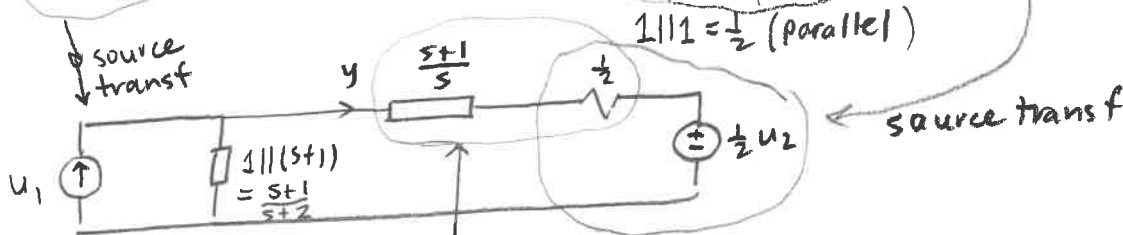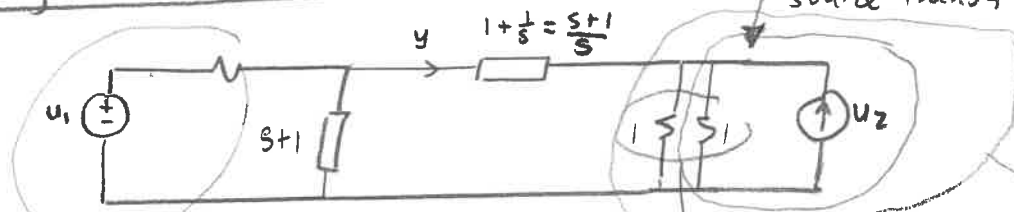

$$y = \frac{\left(\frac{s+1}{s+2}\right)u_1 - \frac{u_2}{2}}{\frac{s+1}{s+2} + \frac{\frac{3}{2}s+1}{s}}$$

$$= \frac{s(s+1)u_1 - \frac{1}{2}s(s+2)u_2}{s(s+1) + (\frac{3}{2}s+1)(s+2)}$$

$$\frac{\frac{1}{2}[s^2 + 2s + \frac{4}{5}]}{\frac{1}{2}s^2 + 5s + 2}$$

$$\frac{1}{s^2 + s + \frac{3}{2}s^2 + 3s + s + 2}$$

$$\Rightarrow y = \left[\frac{\frac{2}{5}s(s+1)}{s^2 + 2s + \frac{4}{5}} \right] u_1 + \left[\frac{-\frac{1}{5}s(s+2)}{s^2 + 2s + \frac{4}{5}} \right] u_2$$

$$\Rightarrow \Phi = s^2 + 2s + \frac{4}{5} \dots \text{just like before!} \quad \text{😊}$$

$$\Rightarrow H_1(0) = H_2(0) = 0 \dots$$

$$\Rightarrow H_1(\infty) = \frac{2}{5} \quad H_2(\infty) = -\frac{1}{5} \dots \quad \text{😊}$$


\Rightarrow The previous method used is a great way to get poles, t_s , & $H_i(0)$, $H_i(\infty)$ quickly!!!

Problem 3

Determine $H_{1,2}$, diff eq, t_s , y_{ss}

$$u_1 = 3 + 100 \cos(0.01t - 45^\circ) + 7 \cos(t + 2^\circ)$$

$$u_2 = -4 + 2 \sin(100t + 45^\circ)$$

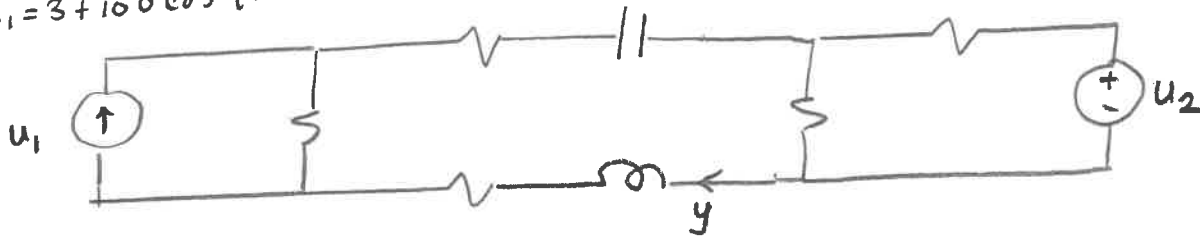

solution =

Since circuit consists of R, L, C & independent sources ($u_{1,2}$),
it MUST BE STABLE; i.e. all poles in left half s -plane!
(we'll show this below)

$$\Rightarrow y_{ss} = y_{1ss} + y_{2ss}$$


\downarrow MTF
 $y_{1ss} = 3 H_1(0) + 100 |H_1(j0.01)| \cos(0.01t - 45^\circ + \angle H_1(j0.01))$
 $+ 7 |H_1(j1)| \cos(t + 2^\circ + \angle H_1(j1))$

\downarrow -MTF
 $y_{2ss} = -4 H_2(0) + 2 |H_2(j100)| \sin(100t + 45^\circ + \angle H_2(j100))$

... we'll compute the required magnitudes & angles below ---

Now for the circuit analysis -

Will use some source transformations.

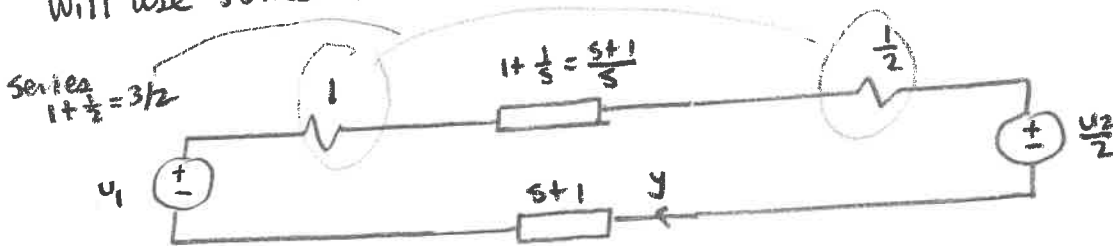

$$y \stackrel{\text{ohm}}{=} \frac{u_1 - \frac{u_2}{2}}{\frac{3}{2} + \left(\frac{s+1}{s}\right) + (s+1)} = \frac{s(u_1 - \frac{u_2}{2})}{\frac{3}{2}s + s+1 + s^2 + s}$$

\uparrow $s^2 + \frac{7}{2}s + 1$

because capacitor is open at DC

$$H_1(0) = H_2(0) = 0$$

$$y = \left[\frac{s}{s^2 + \frac{7}{2}s + 1} \right] u_1 + \left[\frac{-\frac{1}{2}s}{s^2 + \frac{7}{2}s + 1} \right] u_2$$

\uparrow H_1 \uparrow H_2 poles

$$\ddot{y} + \frac{7}{2}\dot{y} + y = \ddot{u}_1 - \frac{1}{2}\ddot{u}_2$$

$$H_1(j0.01) \cong j0.01 = 0.1 e^{j90^\circ}$$

$$H_2(j100) \cong \frac{-1/2}{j100} = \frac{1}{190} e^{j180^\circ} = \frac{1}{190} e^{j(180-90^\circ)}$$

$$H_1(j1) = \frac{j1}{1 + \frac{7}{2}j1 + 1} = \frac{2}{7} e^{j0^\circ}$$

$$\Rightarrow t_s = \frac{5}{|s_1|} = \frac{5}{\frac{7}{4} - \frac{\sqrt{33}}{4}}$$

$$s_{1,2} = \frac{-\frac{7}{2} \pm \sqrt{\frac{49}{4} - 4}}{2} = \frac{-\frac{7}{2} \pm \sqrt{\frac{49}{4} - \frac{16}{4}}}{2} = \frac{-\frac{7}{2} \pm \frac{\sqrt{33}}{2}}{2}$$

slow pole



$$s_2, s_1$$

5113

Problem 3

pole check =

Set $u_1 = 0$ (open)
 $u_2 = 0$ (short)

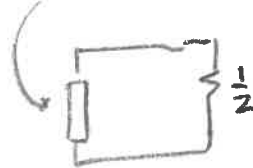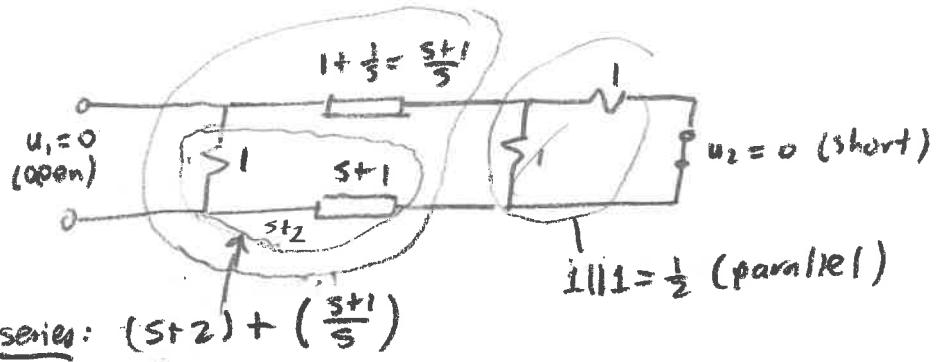

$$Z = (s+2) + \left(\frac{s+1}{s}\right) + \frac{1}{2}$$

$$= \frac{s^2 + 2s + s + 1 + \frac{1}{2}s}{s} = s^2 + \frac{7}{2}s + 1$$


$\Rightarrow \Phi = s^2 + \frac{7}{2}s + 1$... just like before!



Gain checks =

Analysis at dc ($s=0$)

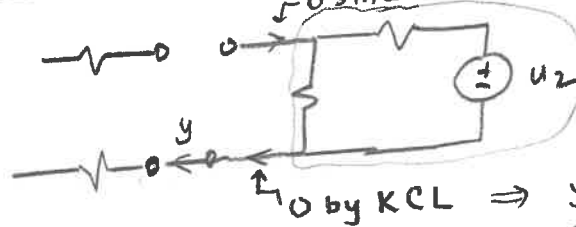$Z_L = sL = 0$ (short)
 $Z_C = \frac{1}{sC} = \infty$ (open)
since cap is OPEN




by KCL $\Rightarrow y = 0 = 0u_1 + 0u_2$
 $\Rightarrow H_1(0) = H_2(0) = 0$

... just like before!



Analysis at $s=\infty$

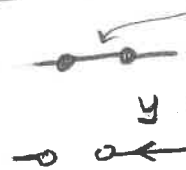$Z_L = sL = \infty$ (open)
 $Z_C = \frac{1}{sC} = 0$ (short)



$\Rightarrow y = 0 = 0u_1 + 0u_2$
 $\Rightarrow H_1(\infty) = H_2(\infty) = 0$



\Rightarrow Yes ... our H_1 & H_2 satisfy these!

\Rightarrow Based on the above 3 smiley faces, it is reasonable to believe that we computed H_1 & H_2 correctly?


\Rightarrow Should try to always do these pole & gain checks!

Problem 4


Determine H , diff eq, y , y_{ss} (All $R, L = 1$)

$$u = 4 + \cos 4t$$

Hint: Use KVL, KCL, Ohm!

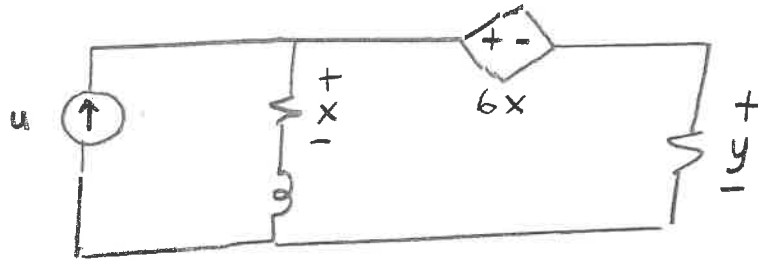

solution via KVL, KCL, Ohm:

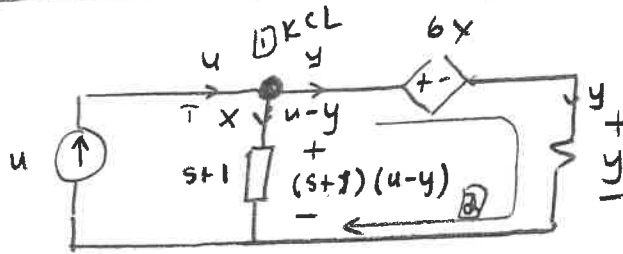

$$\textcircled{1} \text{ KCL} = \boxed{x = u - y} \quad \leftarrow \text{this was easy to get! (Not always the case!!!)}$$

$$\textcircled{2} \text{ KVL} = \boxed{(s+1)(u-y) = 6(u-y) + y}$$

$$\Rightarrow y \left[\underbrace{s+1-6}_{s-4} + 1 \right] = u \left[\underbrace{s+1-6}_{s-5} \right]$$

$$\Rightarrow \boxed{H = \frac{y}{u} = \frac{s-5}{s-4}} \quad \bar{y} - 4\bar{y} = \bar{u} - 5\bar{u}$$

$$\hookrightarrow \Phi = s-4=0 \Rightarrow \text{pole} = \text{pole at } s=4$$


4
X
unstable

components of y that can be computed using MOTF!

$$y_{\text{MOTF}} = 4H(0) + |H(j4)| \cos(4t + \angle H(j4))$$

$$H(0) = \frac{5}{4}$$

$$H(j4) = \frac{-5+j4}{-4+j4}$$

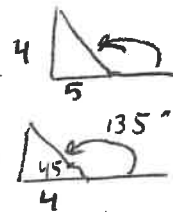

$$= \sqrt{16+25} e^{j(180 - \tan^{-1}(\frac{4}{5}))}$$

$$\sqrt{2} e^{j135^\circ}$$

$$= \frac{\sqrt{16+25}}{\sqrt{2}} e^{j(180 - \tan^{-1}(\frac{4}{5}) - 135^\circ)}$$

$$B = \frac{(-1)(16+64)}{4(16+16)}$$

$$U(s) = \frac{4}{s} + \frac{s}{s^2+16} = \frac{5s^2+64}{s(s^2+16)}$$

$$Y(s) = H(s)U(s)$$

$$= \left[\frac{s-5}{s-4} \right] \left[\frac{5s^2+64}{s(s^2+16)} \right]$$

$$= \frac{A}{s} + \frac{B}{s-4} + \left[\frac{C+j4}{s-j4} + \frac{C-j4}{s+j4} \right]$$

$$\Rightarrow y(t) = A + Be^{4t} + 2|C| \cos(4t + \angle C)$$

$$A = \lim_{s \rightarrow 0} sY(s) \stackrel{\text{MOTF}}{=} 4H(0)$$

$$C = \lim_{s \rightarrow j4} (s-j4)Y(s) \stackrel{\text{MOTF}}{=} \frac{1H(j4)}{2} e^{j\angle H(j4)} \quad y_{\text{MOTF}} = |C| e^{j\angle C}$$


$$B = \lim_{s \rightarrow 4} (s-4)Y(s) = \frac{(-1)(16+64)}{4(16+16)} \quad s=4$$

17/13


Problem 4

Determine H , diff eq, y , y_{ss} (All $R, L = 1$)

$$u = 4 + \cos 4t$$

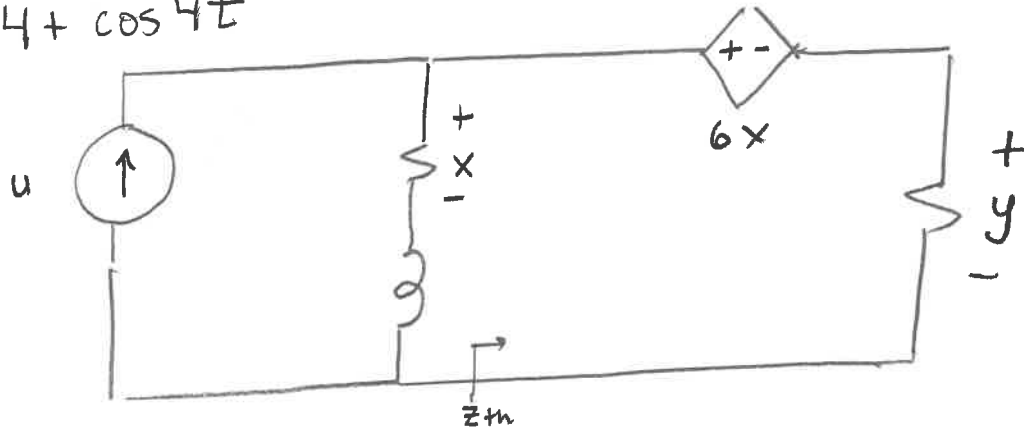

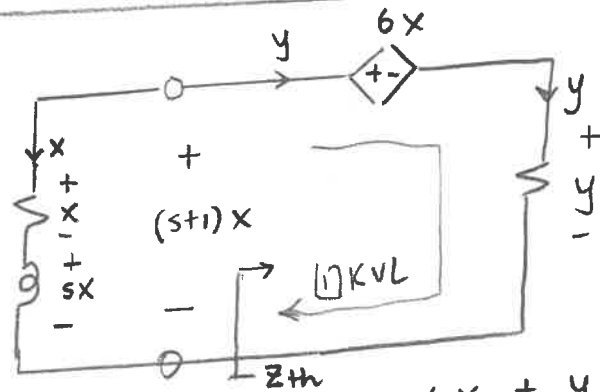Alternate solution via Thevenin Equivalent



$$\text{KVL} = (s+1)x = 6x + y$$


$$\Rightarrow x[s+1-6] = y$$

$$\Rightarrow x[s-5] = y$$

$$\Rightarrow x = \frac{y}{s-5}$$

$$\Rightarrow (s+1)x = \left[\frac{s+1}{s-5} \right] y$$
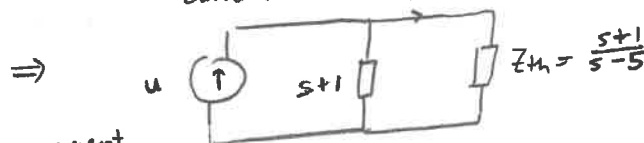
$$\Rightarrow \tilde{Z}_{th} = \frac{\text{voltage } (s+1)x}{\text{current } y} = \frac{s+1}{s-5} \leftarrow \text{seems complicated but it will yield correct result!}$$



$$\Rightarrow y = \left[\frac{s+1}{s+1 + \frac{s+1}{s-5}} \right] u = \left[\frac{1}{1 + \frac{1}{s-5}} \right] u = \left[\frac{s-5}{s-4} \right] u$$


😊 same as before!

8/13

Problem 4

Pole check:

Set $u = 0$
(open)

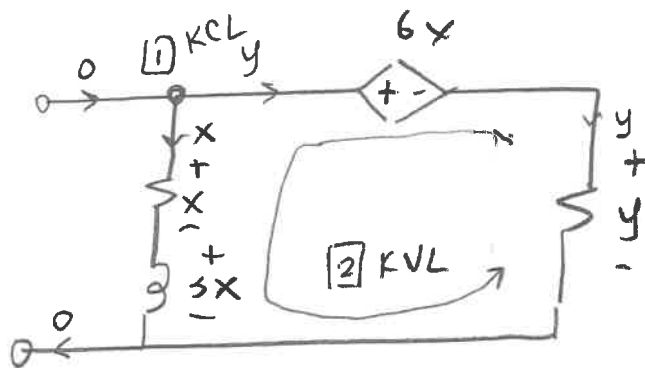

$$\textcircled{1} \text{ KCL} = x = -y$$

$$\begin{aligned} \textcircled{2} \text{ KVL} = y &= -6x + x + 5x \\ &= [-6 + 1 + 5]x \\ &\quad \uparrow x = -y \\ &= -[-6 + 1 + 5]y \end{aligned}$$

$$\Rightarrow y[1 - 6 + 1 + 5] = 0$$


$$\Rightarrow y[s - 4] = 0$$

$$\Rightarrow \Phi = s - 4 = 0 \leftarrow \text{Agrees with what we got in } H(s)!$$



Analysis at dc ($s=0$)

$Z_L = sL = 0$ (short)

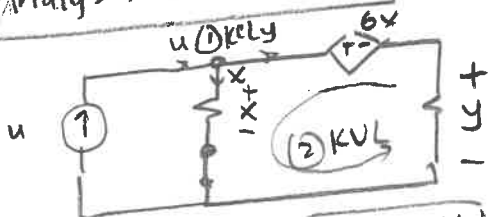


$$\textcircled{1} \text{ KCL} = x = u - y$$

$$\textcircled{2} \text{ KVL} = y = -6x + x = -5x = -5(u - y) = -5u + 5y$$

$$\Rightarrow 4y = 5u \Rightarrow y = \left(\frac{5}{4}\right)u \Rightarrow H(0) = \frac{5}{4} \text{ --- just like what we got before!}$$

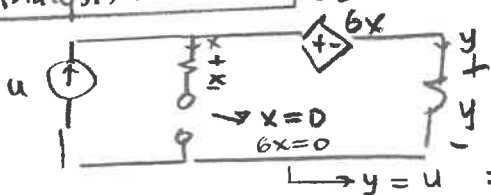Analysis at $s = \infty$ $Z_L = sL = \infty$ (open)



$$y = u \Rightarrow H(\infty) = 1 \text{ --- just like we got before!}$$

9113



Problem 5

Determine t_s , y_{ss} , y

Note:

Show how to compute all coefficients associated with constants, sinusoids, & instabilities in y

Note: You are expected to do the easy calculations.

$$H(s) = \frac{s^2 + 1}{(s+2)(s^2 - 6s + 25)(s^2 + 25 + 4)}$$

$$u(t) = 5 - 60 \sin(t + 30^\circ) + 7 \cos(100t + 45^\circ)$$

Solution:

$$H(j1) = 0 \quad (\text{since } s^2 + 1|_{s=j1} = (j1)^2 + 1 = -1 + 1 = 0)$$


zero since $H(j1) = 0$!!!

$$y_{\text{MOTF}} = 5 H(0) - 60 |H(j1)| \sin(t + 30^\circ + \angle H(j1)) + 7 |H(j100)| \cos(100t + 45^\circ + \angle H(j100))$$

$$H(0) = \frac{(1)}{(2)(25)(4)}$$

$$H(j100) \approx \frac{1}{s^3} \Big|_{s=100e^{j90^\circ}} = \frac{1}{(10^2 e^{j90})^3} = 10^{-6} e^{j(-270^\circ)}$$

poles of H : -2 stable
 $3 \pm j4$ unstable
 $-1 \pm j\sqrt{3}$ stable

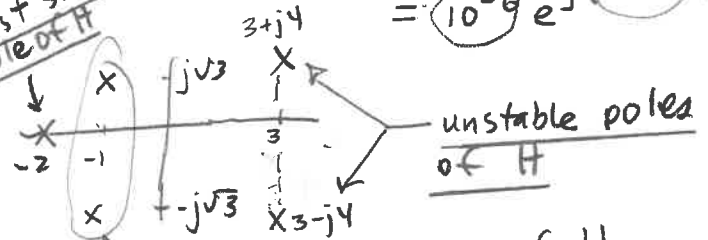fast stable pole of H slow stable poles of H

$$\Rightarrow t_s = \frac{5}{|\text{Re slow poles}|}$$

$$= \frac{5}{1-1}$$

$$= 5 \text{ sec}$$

$$U(s) = \frac{5}{s} + \frac{\text{num1}}{s^2 + 1} + \frac{\text{num2}}{s^2 + 104}$$

$$= \frac{\text{num}}{s(s^2 + 1)(s^2 + 104)}$$

$$Y = HU = \left[\frac{s^2 + 1}{(s+2)(s^2 - 6s + 25)(s^2 + 25 + 4)} \right] \left[\frac{\text{num}}{s(s^2 + 1)(s^2 + 104)} \right]$$

$$= \frac{A}{s} + \frac{B}{s+2} + \left[\frac{C}{s-3-j4} + \frac{D}{s-3+j4} \right] + \left[\frac{E}{s-j100} + \frac{F}{s+j100} \right]$$

$$y = A + B e^{-2t} + 2|C| e^{3t} \cos(4t + \angle C) + 2|D| e^{-t} \cos(\sqrt{3}t + \angle D)$$

stable with $t_s = 5 \text{ sec}$ y_{ss} unstable

$$+ 2|E| \cos(100t + \angle E)$$

MOTF

$$y_{\text{MOTF}} \quad A = \lim_{s \rightarrow 0} s Y(s) = 5 H(0)$$

$$E = \lim_{s \rightarrow j100} (s-j100) Y(s) = \frac{7 |H(j100)|}{2} e^{j(45^\circ + \angle H(j100))} = 1E e^{j \angle E}$$

10/13


$$C = \lim_{s \rightarrow 3-j4} (s-3-j4) Y(s)$$

MOTF


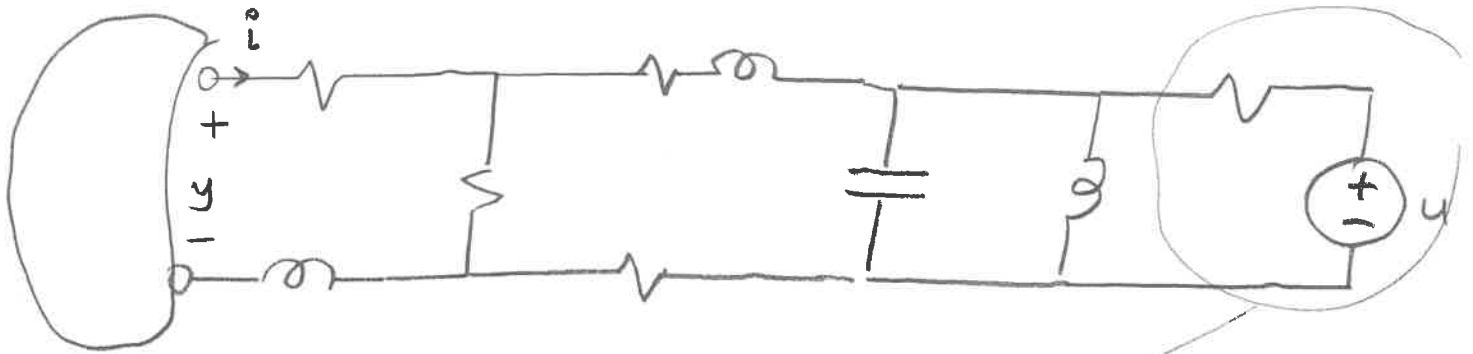
Problem 6

Determine an s-domain Thevenin equivalent at y




Must specify Z_{th} & V_{th} --- emphasize process
... NOT algebra !!!




solution =

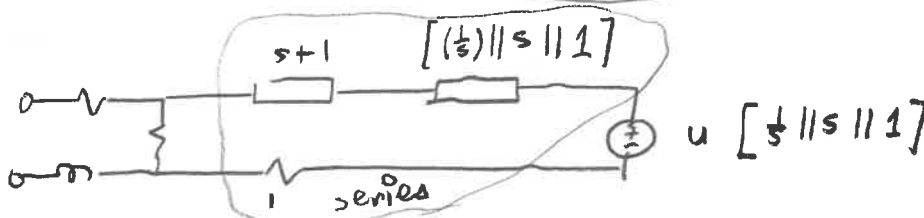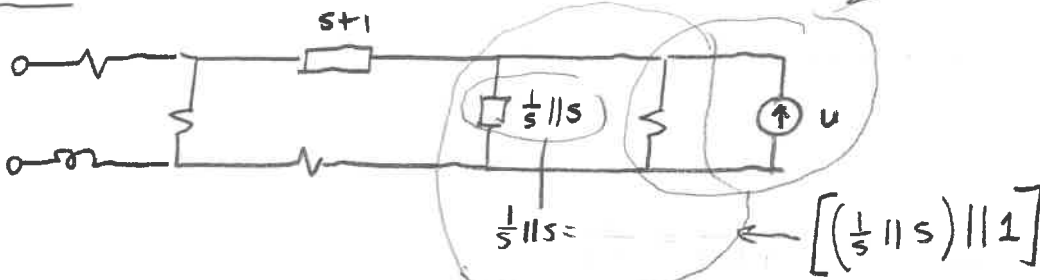

$$Z = (s+2) + \left[\frac{1}{s} || s || 1 \right]$$

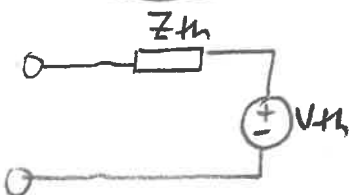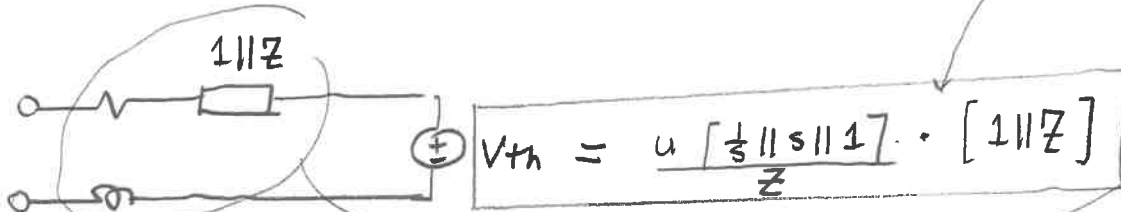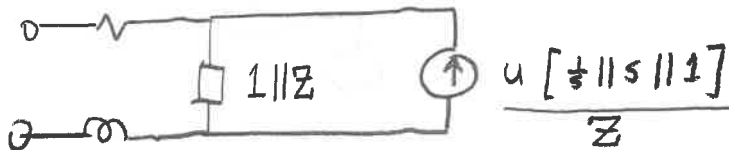

$$Z_{th} = s+1 + 1 || Z$$

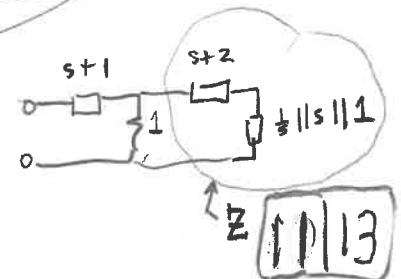

Problem 7

Determine H , y_{ss} , t_s


$$u = 7 + 8 \sin(t + 45^\circ) - 50 \cos(100t - 80^\circ)$$



Note:

Determine all coefficients in y_{ss} (approximately).

solution:

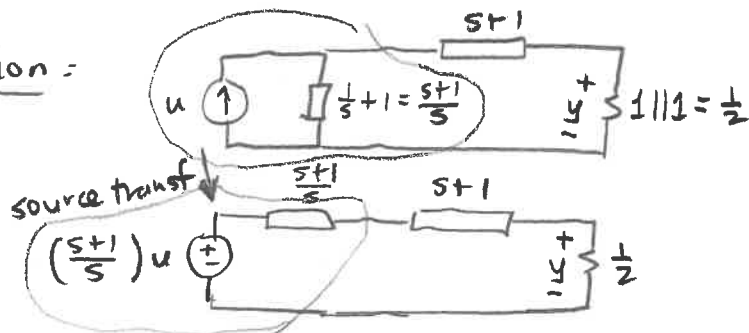

voltage division

$$y \stackrel{!}{=} \left[\frac{\frac{1}{s+1}}{\frac{s+1}{s} + s+1 + \frac{1}{s}} \right] \left(\frac{s+1}{s} \right) u = \left[\frac{\frac{1}{2}(s+1)}{s^2 + \frac{5}{2}s + 1} \right] u$$

$$H = \frac{y}{u} = \frac{\frac{1}{2}(s+1)}{s^2 + \frac{5}{2}s + 1}$$

poles

$$s_{1,2} = \frac{-\frac{5}{2} \pm \sqrt{\frac{25}{4} - 4}}{2}$$

→ MoTF

$$y_{ss} = 7H(0)$$

$$+ 8|H(j1)| \sin(t + 45^\circ + \angle H(j1))$$

$$- 50|H(j100)| \cos(100t - 80^\circ + \angle H(j100))$$

$$H(0) = \frac{1}{2} \text{ (dc gain)}$$

$$H(j1) = \frac{\frac{1}{2}(j1+1)}{-1 + \frac{5}{2}j1 + 1} = \frac{1}{5} \frac{(1+j1)}{j1}$$

$$= \frac{1}{5} \frac{\sqrt{2} e^{j45^\circ}}{1 e^{j90^\circ}}$$

$$= \left(\frac{\sqrt{2}}{5} \right) e^{j(45-90^\circ)}$$


$$H(j100) \approx \frac{1/2}{s} \Big|_{s=100} e^{j90^\circ} = \frac{1/2}{100 e^{j90^\circ}} = \frac{1}{200} e^{j(-90^\circ)}$$

$$= -\frac{5}{4} \pm \sqrt{\frac{25}{16} - \frac{16}{16}} - \frac{9}{16}$$

$$= -\frac{5}{4} \pm \frac{3}{4}$$

$$= -\frac{8}{4}, -\frac{2}{4}$$

$$= -2, -\frac{1}{2}$$

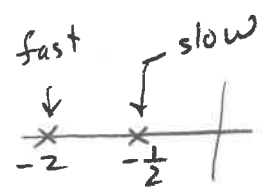


$$t_s = \frac{5}{|\text{slow pole}|} = \frac{5}{\frac{1}{2}} = 10 \text{ sec}$$


Problem 8

Determine and
Plot $|H(j\omega)|$, $\angle H(j\omega)$

(All $R, L, C = 1$)

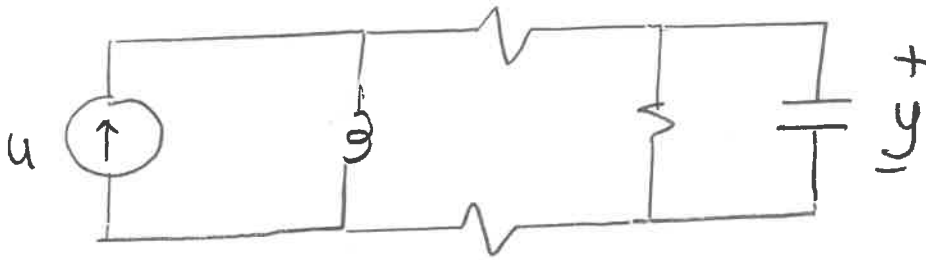

solution via source transf =

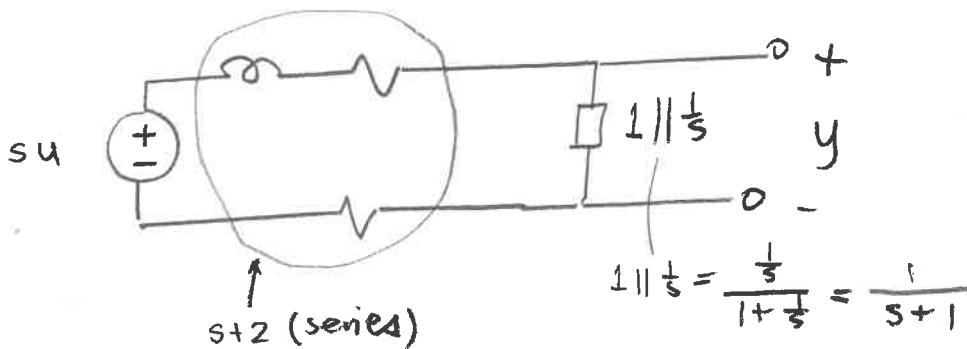

$$\begin{aligned} \text{voltage division} \\ U &= \left[\frac{\frac{1}{s+1}}{s+2 + \frac{1}{s+1}} \right] (su) \\ &= \left[\frac{1}{(s+2)(s+1) + 1} \right] su \\ &= \left[\frac{s}{s^2 + 3s + 3} \right] u \end{aligned}$$

$$H(s) = \frac{s}{s^2 + 3s + 3}$$

$$\begin{aligned} H(j\omega) &= \frac{j\omega}{3 - \omega^2 + j3\omega} \\ |H(j\omega)| &= \frac{\omega}{\sqrt{(3 - \omega^2)^2 + (3\omega)^2}} \end{aligned}$$

$$\angle H(j\omega) = 90^\circ - \begin{cases} \tan^{-1}\left(\frac{3\omega}{3 - \omega^2}\right) & \omega \in [0, \sqrt{3}] \\ 180 - \tan^{-1}\left(\frac{3\omega}{\omega^2 - 3}\right) & \omega \in [\sqrt{3}, \infty) \end{cases}$$

