

EEE 202 Exam #2 Spring 2021

A.A. Rodriguez


For each of the following circuits:

(a) Relate y to input(s) in s -domain

Specify/address (b) transfer functions (c) differential equation

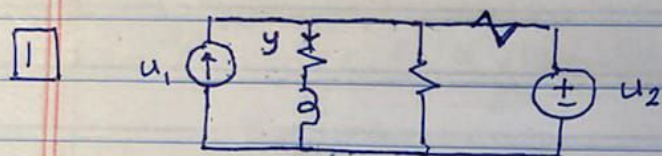
(d) stability (e) poles (f) settling time

(Note: All $R=L=C=1$!) (g) $y(t)$ (h) $y_{ss} = \lim_{t \rightarrow \infty} y(t)$ (y for large t)




$$u_1 = (1 + \sin 100t) 1(t)$$

$$u_2 = 10 1(t)$$

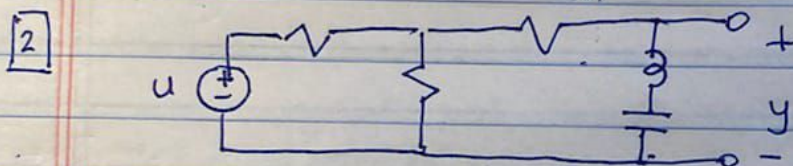


$$u = 1 + \sin(t + 30^\circ)$$

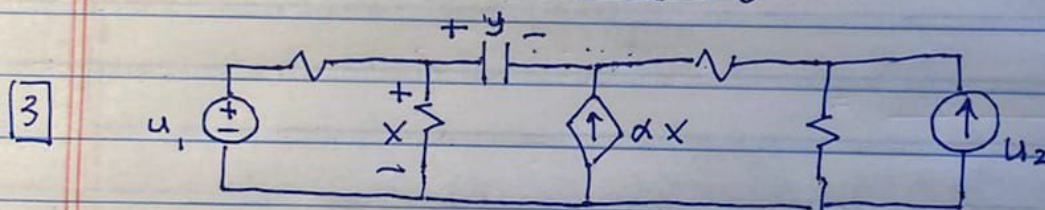

Use $\alpha = 3$

$$u_1 = 1(t)$$

$$u_2 = -2.9 1(t)$$

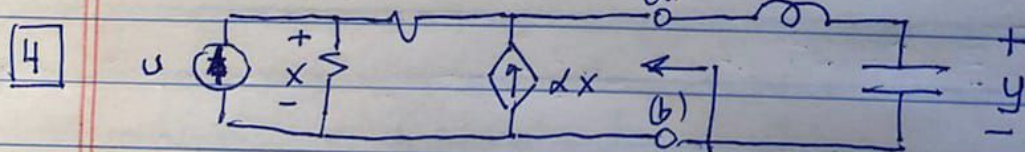


Use $\alpha = 3$

$$u = -\frac{1}{2} 1(t)$$

Hint: Find Thevenin Equivalent to left of terminals (a),(b)



$$u = [1 + \sin 100t] 1(t)$$

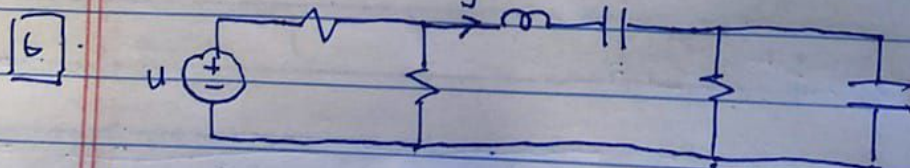

$$u = [1 + \sin t$$

$$+ \cos(100t + 30^\circ)] 1(t)$$