


# Example 32

(Switching <sup>RLC</sup> Circuit)

3010

A

Assume  $M > 0$

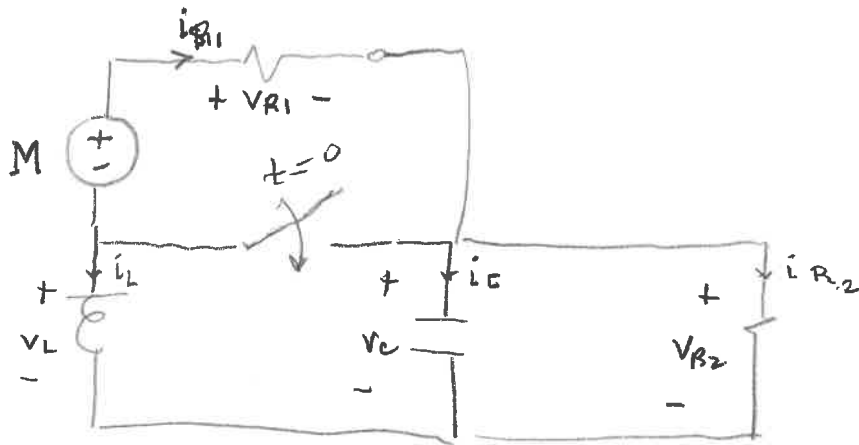

(All  $R=L=C=1$ )

- 1 Find  $i_{R1}, i_L, i_C, i_{R2}$  at  $t=0^-$   
 $V_{R1}, V_L, V_C, V_{R2}$
- 2 " " " "  $t=0^+$
- 3 for  $t \geq 0^+$


1  $t=0^-$

$$V_{R1} = i_{R1} = i_{R2} = \frac{M}{1+1} = \frac{1}{2} M$$

$$i_L = -i_{R1} = -\frac{1}{2} M$$


$$V_L = 0$$
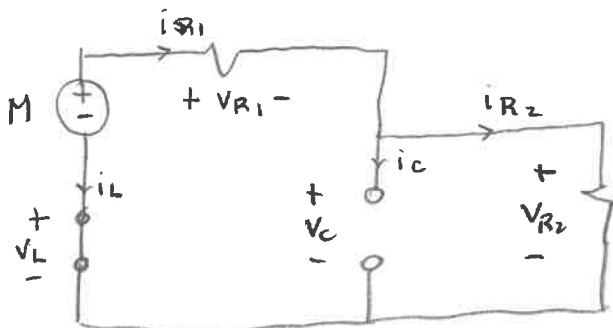
$$V_C = V_{R2} = i_{R2} = \frac{1}{2} M$$



Summary =

At  $t=0^-$ , we have

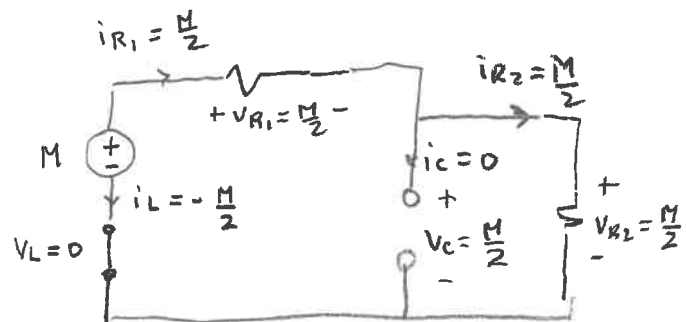

# Example 32

3020

Remember:

$$i_C = C \frac{dv_C}{dt}$$


Capacitor voltages can't jump  
(would result in  $\infty$   $i_C$ !!!)

Inductor currents " " (would result in  $\infty$   $v_L$ !!!)

$$v_L = L \frac{di_L}{dt}$$

- capacitor currents & inductor voltages can jump!

- resistor voltages & currents can jump

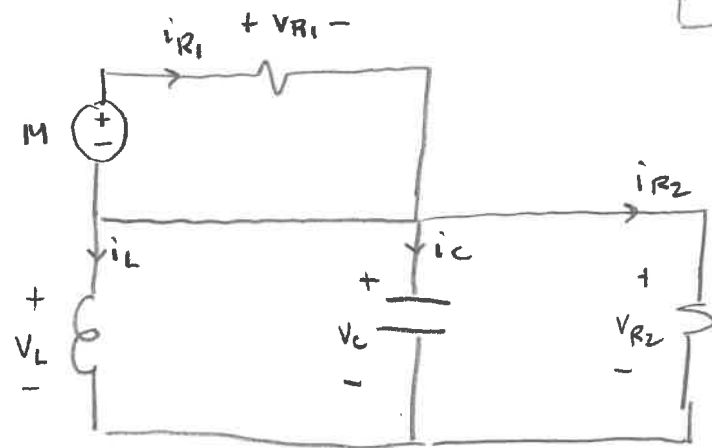

1st things 1st: Capacitor voltages & inductor currents can't jump!

$$\Rightarrow i_L(0^+) = i_L(0^-) = -\frac{1}{2} M$$


$$v_C(0^+) = v_C(0^-) = \frac{1}{2} M \Rightarrow v_L(0^+) = v_{R2}(0^+) = i_{R2}(0^+) = v_C(0^+) = \frac{1}{2} M$$

$$v_{R1}(0^+) = v_{R1}(0^-) = M$$

Note:  $\frac{di_L}{dt}(0^+) = \frac{v_L(0^+)}{L} = \frac{v_C(0^+)}{L} = \frac{M}{2L}$   
 $\frac{dv_C}{dt}(0^+) = \frac{i_C(0^+)}{C} = \frac{0}{C} = 0$

Summary:

At  $t = 0^+$ , we have

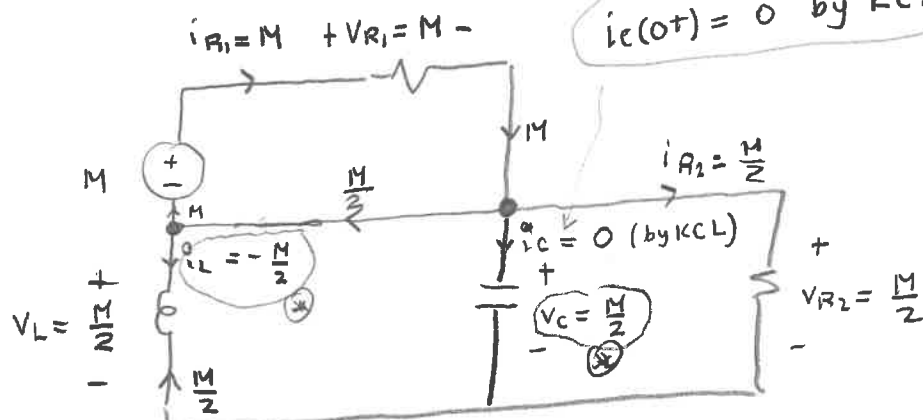

⊗ inductor current  $i_L$  & capacitor voltage  $v_C$  can't jump at  $t = 0$ !

# Example 32

3030

3  $t \geq 0^+$


$v_{R1} = i_{R1} = M$  for  $t \geq 0^+$

$\{v_L, v_C, v_{R2}, i_L, i_C, i_{R2}\}$  all have the form  $A_1 e^{s_1 t} + A_2 e^{s_2 t}$

where  $s_1, s_2$  are roots of the characteristic eq  $\Phi$ .

Lets find  $\Phi$ 's roots  $s_{1,2}$ !

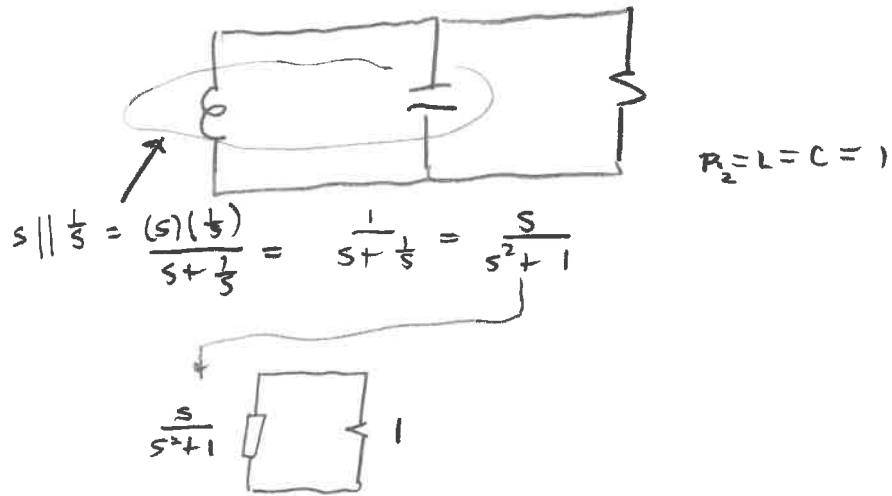
Finding  $\Phi$ 's Characteristic Roots  
for  $t \geq 0^+$  we have



$Z = \frac{s}{s^2 + 1} + 1 = \frac{s + s^2 + 1}{s^2 + 1} = 0$

$\Rightarrow \Phi_{CL} = s^2 + s + 1 = 0$

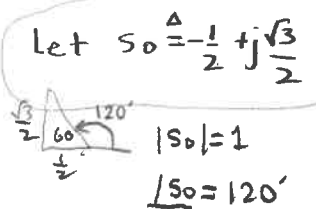
$\Rightarrow s_{1,2} = -\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$



Lets now find  $\{i_L, i_C, i_{R2}, v_L, v_C, v_{R2}\}$  - - -

# Example 32

Inductor

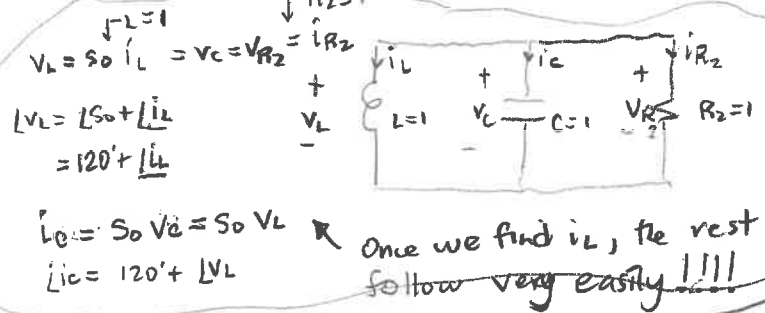

$$i_L(0^+) = -\frac{M}{2} \quad \frac{di_L}{dt}(0^+) = \frac{M}{2}$$

3040

$$i_L(t) = A e^{(-\frac{1}{2} + j\frac{\sqrt{3}}{2})t} + \bar{A} e^{(-\frac{1}{2} - j\frac{\sqrt{3}}{2})t} = 2 \operatorname{Re} [A e^{(-\frac{1}{2} + j\frac{\sqrt{3}}{2})t}]$$

$$= |A| e^{-\frac{1}{2}t} e^{j(\frac{\sqrt{3}}{2}t + \angle A)} + \bar{A}$$

$$= 2 \operatorname{Re} |A| e^{-\frac{1}{2}t} \cos(\frac{\sqrt{3}}{2}t + \angle A)$$

$$\Rightarrow i_L(t) = 2 |A| e^{-\frac{1}{2}t} \cos(\frac{\sqrt{3}}{2}t + \angle A)$$

$$i_L(0^+) = -\frac{M}{2} = 2 |A| \cos \angle A \Rightarrow |A| \cos \angle A = -\frac{M}{4}$$

Re A

$$i_L = A e^{(-\frac{1}{2} + j\frac{\sqrt{3}}{2})t} + \bar{A} e^{(-\frac{1}{2} - j\frac{\sqrt{3}}{2})t}$$

$$\frac{di_L}{dt} = A e^{(-\frac{1}{2} + j\frac{\sqrt{3}}{2})t} [j\frac{\sqrt{3}}{2}] + \bar{A} e^{(-\frac{1}{2} - j\frac{\sqrt{3}}{2})t} [-j\frac{\sqrt{3}}{2}]$$

$$\frac{di_L}{dt}(0^+) = \frac{M}{2} = A [j\frac{\sqrt{3}}{2}] - \bar{A} [j\frac{\sqrt{3}}{2}] = j\frac{\sqrt{3}}{2} [A - \bar{A}]$$

$$= j\frac{\sqrt{3}}{2} [j2 \operatorname{Im} A]$$


$$= j\frac{\sqrt{3}}{2} [j2 |A| \sin \angle A]$$

$$= -\sqrt{3} |A| \sin \angle A$$

$$\Rightarrow |A| \sin \angle A = -\frac{M}{2\sqrt{3}}$$

Im A
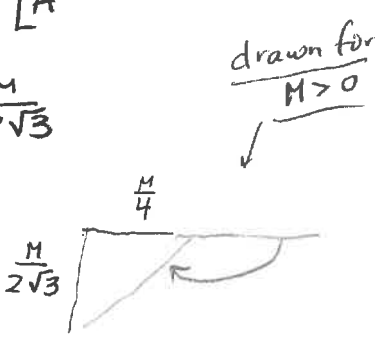
$$\begin{cases} \operatorname{Re} A = -\frac{M}{4} \\ \operatorname{Im} A = -\frac{M}{2\sqrt{3}} \end{cases} \Rightarrow A = -\frac{M}{4} - j\frac{M}{2\sqrt{3}}$$



# Example 32

3050

$$\Rightarrow |A| = M \sqrt{\frac{1}{16} + \frac{1}{4(3)}} = M \sqrt{\frac{12 + 16}{(16)(12)}} \leftarrow 28$$

$$= M \sqrt{\frac{(4)(7)}{(4)(4)(4)(3)}}$$

$$= \frac{M}{4} \sqrt{\frac{7}{3}} \quad (\text{OK since } M > 0)$$

$$\angle A = -180 + \tan^{-1}\left(\frac{\frac{M}{2\sqrt{3}}}{\frac{M}{4}}\right)$$

$$= -180' + \tan^{-1}\left(\frac{2}{\sqrt{3}}\right) = 49.1066^\circ$$

$$\approx -130.8934^\circ$$

$$i_L(t) = \frac{M}{2} \sqrt{\frac{7}{3}} e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t - 130.8934^\circ\right)$$

$$= \frac{M}{2} \sqrt{\frac{7}{3}} e^{-\frac{1}{2}t} \sin\left(\frac{\sqrt{3}}{2}t - 40.8934^\circ\right)$$

$\cos(x - 90) = \sin x$

↑ easier to differentiate complex exponential!

$$v_L = L \frac{di_L}{dt} = \frac{di_L}{dt} = \frac{d}{dt} \left[ 2 \operatorname{Re} A e^{(-\frac{1}{2} + j\frac{\sqrt{3}}{2})t} \right]$$

$$= 2 \operatorname{Re} \left\{ \frac{d}{dt} \left( A e^{(-\frac{1}{2} + j\frac{\sqrt{3}}{2})t} \right) \right\}$$

$$= 2 \operatorname{Re} \left\{ A e^{(-\frac{1}{2} + j\frac{\sqrt{3}}{2})t} (-\frac{1}{2} + j\frac{\sqrt{3}}{2}) \right\}$$

$$= 2 \operatorname{Re} \left\{ |A| e^{j\angle A} e^{-\frac{1}{2}t} e^{j\frac{\sqrt{3}}{2}t} \frac{\sqrt{3}}{2} \angle 120^\circ \right\}$$

$$= 2 \operatorname{Re} \left\{ |A| e^{-\frac{1}{2}t} e^{j(\frac{\sqrt{3}}{2}t + \angle A + 120^\circ)} \right\}$$

# Example 32

3060

$$V_L = S_0 I_L \Rightarrow \underline{V}_L = \underline{I}_L + \angle 50^\circ = -130.8934 + j120 = -10.8934 - j130.8934$$

Note that  $V_L$  differs from  $i_L$  by just  $\angle 50^\circ = 120^\circ$ . This is because


$$V_L = S_0 L I_L = S_0 I_L \Rightarrow S_0 = -\frac{1}{2} + j\frac{\sqrt{3}}{2} \Rightarrow |S_0| = 1, \angle S_0 = 120^\circ$$

A

$$\Rightarrow V_L(t) = 2(1A)e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t + \angle A + 120^\circ\right) = \frac{M}{2}\sqrt{\frac{1}{3}}e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t - 10.8934^\circ\right)$$

Note:
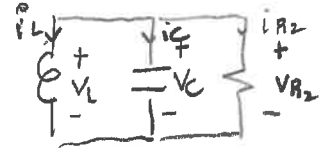
$$V_{R_2}(t) = i_{R_2}(t) = V_C(t) = V_L(t)$$



$$i_C(t) = -i_L(t) - i_{R_2}(t)$$

$$= -\frac{M}{2}\sqrt{\frac{1}{3}}e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t - 130.8934^\circ\right) - \frac{M}{2}\sqrt{\frac{1}{3}}e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t - 10.8934^\circ\right)$$

$$= -\frac{M}{2}\sqrt{\frac{1}{3}}e^{-\frac{1}{2}t} \left\{ \text{Re} \left[ \left( 1e^{-j130.8934^\circ} + 1e^{-j10.8934^\circ} \right) e^{j\frac{\sqrt{3}}{2}t} \right] \right\}$$

MATLAB

$$0.9999e^{-j70.8934^\circ}$$

$$= -\frac{M}{2}\sqrt{\frac{1}{3}}e^{-\frac{1}{2}t} (1) \cos\left(\frac{\sqrt{3}}{2}t - 70.8934^\circ\right)$$

$$-\cos x = \cos(x + 180^\circ)$$

$$= \frac{M}{2}\sqrt{\frac{1}{3}}e^{-\frac{1}{2}t} (1) \cos\left(\frac{\sqrt{3}}{2}t + 110.8934^\circ\right)$$

Note:

$$i_C = S_0 V_C$$

$= S_0 V_L \Rightarrow$  It follows that  $i_C$  will differ from  $V_L$  just by  $\angle S_0 = 120^\circ$

$$\angle i_C = \angle S_0 + \angle V_L$$

$$= 120^\circ - 10.8934^\circ$$

$$= 110.8934^\circ$$


3060

# Example 32

3070

B


Assume  $M > 0$

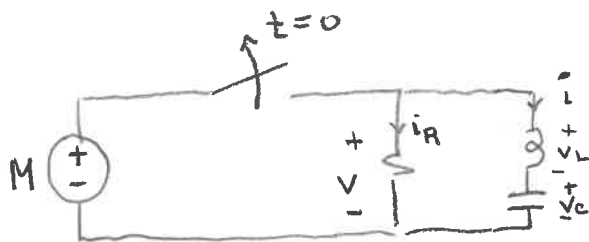

(All  $R=L=C=1$ )

- Find  $V, i_R, i, V_L, V_C$
- ① at  $t=0^-$
  - ② at  $t=0^+$
  - ③ for  $t > 0^+$


①  $t=0^-$

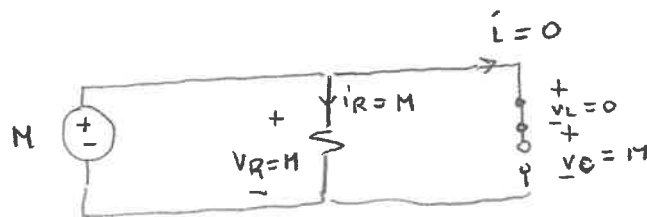

②  $t=0^+$

$$\frac{dV_C(0^+)}{dt} = \frac{i(0^+)}{C} = 0$$
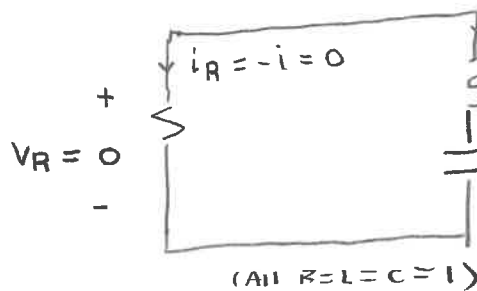
$$\frac{di_L(0^+)}{dt} = \frac{V_L(0^+)}{L} = \frac{-M}{1} = -M$$



(All  $R=L=C=1$ )

since inductor current can't jump!

$$i(0^+) = i(0^-) = 0$$

$$V_L = V_R - V_C = 0 - M = -M$$

$$V_C(0^+) = V_C(0^-) = M$$

↑  
since capacitor voltage can't jump!

③  $t > 0^+$

$V, i_R, i, V_L, V_C$  all have the form  $A_1 e^{s_1 t} + A_2 e^{s_2 t}$

where  $s_{1,2}$  are roots of the characteristic eq  $\Phi$ .

Let's find  $\Phi$  & the roots  $s_{1,2}$ !

# Example 32



3080

## Finding $\Phi$ & Characteristic Roots

$$Z = 1 + s + \frac{1}{s} = \frac{s^2 + s + 1}{s}$$

$$\Rightarrow \Phi = \frac{\text{numerator}}{\text{denominator}} = s^2 + s + 1 = 0 \Rightarrow s_{1,2} = -\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$$
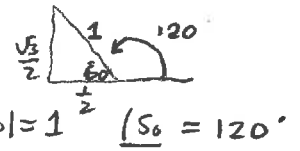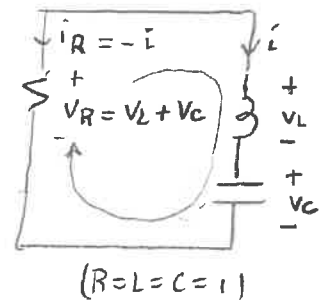
$$\Rightarrow s_0 \triangleq -\frac{1}{2} + j\frac{\sqrt{3}}{2}$$



Note:

Suppose we find  $V_C \Rightarrow$  Since  $i = s_0 V_C \Rightarrow \angle i = \angle s_0 + \angle V_C = 120^\circ + \angle V_C$

$$V_L = s_0 i \Rightarrow \angle V_L = \angle s_0 + \angle i = 120^\circ + \angle i$$

Multiplying by  $s_0$  is simpler than differentiation & greatly simplifies our arithmetic/algebraic steps!!!!

$\Rightarrow$  By finding  $V_C$ , it will be easy to determine

$$i, i_R = -i, \text{ \& } V_L$$

from  $V_C$ !

Lets find  $V_C$ .

Finding  $V_C$  from initial conditions

$$\begin{aligned} V_C(t) &= A e^{s_0 t} + * = 2 \operatorname{Re} [A e^{s_0 t}] \\ &= 2 \operatorname{Re} [ |A| e^{-\frac{1}{2}t} e^{j(\frac{\sqrt{3}}{2}t + \angle A)} ] \\ &= 2 |A| e^{-\frac{1}{2}t} \cos \left( \frac{\sqrt{3}}{2}t + \angle A \right) \end{aligned}$$

To find  $A$  ( $|A|$  &  $\angle A$ ) we use

$$V_C(0^+) = M$$

$$\dot{V}_C(0^+) = 0$$

found earlier (previous page)

$$\begin{aligned} \text{Noting that } \dot{V}_C &= s_0 A e^{s_0 t} + * = 2 \operatorname{Re} [s_0 A e^{s_0 t}] \\ &= 2 \operatorname{Re} [ |s_0| e^{j\angle s_0} |A| e^{j\angle A} e^{(-\frac{1}{2} + j\frac{\sqrt{3}}{2})t} ] \\ &= 2 \operatorname{Re} [ \downarrow |1| |A| e^{-\frac{1}{2}t} e^{j(\frac{\sqrt{3}}{2}t + \angle A + \angle s_0)} ] \\ &= 2 |A| e^{-\frac{1}{2}t} \cos \left( \frac{\sqrt{3}}{2}t + \angle A + 120^\circ \right) \end{aligned}$$

From the above we have

$$V_C(0^+) = M = 2 |A| \cos(\angle A) \Rightarrow |A| \cos(\angle A) = \frac{M}{2}$$

$$\dot{V}_C(0^+) = 0 = 2 |A| \cos(\angle A + 120^\circ) \Rightarrow \cos(\angle A + 120^\circ) = 0$$



# Example 32

3090

B

$$V_L(0+) = -M = 2|C| \cos(LC) \quad \leftarrow \text{This tells us that } LC \text{ must be a 2nd or 3rd Quadrant angle}$$

$$\dot{V}_L = s_0 C e^{s_0 t} + * = 2 \operatorname{Re} [s_0 C e^{s_0 t}]$$

$$= 2 \operatorname{Re} [(s_0) |C| e^{-\frac{1}{2}t} e^{j(\frac{\sqrt{3}}{2}t + LC + \frac{s_0}{1})}]$$

$$= 2|C| e^{-\frac{1}{2}t} \cos(\frac{\sqrt{3}}{2}t + LC + 120^\circ)$$

$$|V_L| + 120^\circ$$

because  $\cos LC < 0 \Leftrightarrow LC$  is in 2nd or 3rd Quad



For either of these  $\cos LC < 0$

$$\dot{V}_L(0+) = M = 2|C| \cos(LC + 120^\circ)$$

$$= 2|C| [\cos LC \cos 120^\circ - \sin LC \sin 120^\circ]$$


$$= 2|C| [\cos LC (-\frac{1}{2}) - \sin LC (\frac{\sqrt{3}}{2})]$$

$$M = -2|C| \cos LC = 2|C| [-\frac{1}{2} \cos LC - \frac{\sqrt{3}}{2} \sin LC]$$

$$\Rightarrow 2 \cos LC = \cos LC + \sqrt{3} \sin LC$$

$$\Rightarrow \cos LC = \sqrt{3} \sin LC$$
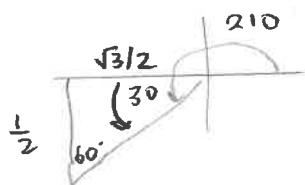
$$\Rightarrow \tan LC = \frac{1}{\sqrt{3}} > 0 \Rightarrow \tan > 0 \text{ in 3rd Quad} \Rightarrow LC \text{ is a 3rd Quad angle}$$



$$\Rightarrow LC = 210^\circ$$

Why?

$$\frac{1}{\sqrt{3}} = \tan LC = \tan(180^\circ + \theta)$$

$$= \tan \theta \Rightarrow \theta = 30^\circ$$

$$\Rightarrow LC = 180^\circ + 30^\circ = 210^\circ$$

$$\Rightarrow -M = 2|C| \cos LC$$

$$= 2|C| \cos 210^\circ$$

$$= 2|C| (-\frac{\sqrt{3}}{2})$$

$$= -\sqrt{3}|C| \Rightarrow |C| = \frac{M}{\sqrt{3}}$$

$$\Rightarrow C = \frac{M}{\sqrt{3}} e^{j210^\circ}$$


$$V_L = 2|C| e^{-\frac{1}{2}t} \cos(\frac{\sqrt{3}}{2}t + LC)$$

$$\Rightarrow V_L = \frac{2M}{\sqrt{3}} e^{-\frac{1}{2}t} \cos(\frac{\sqrt{3}}{2}t + 210^\circ)$$

$$= -\frac{2M}{\sqrt{3}} e^{-\frac{1}{2}t} \cos(\frac{\sqrt{3}}{2}t + 30^\circ)$$

agrees with what we found earlier above!

**B**

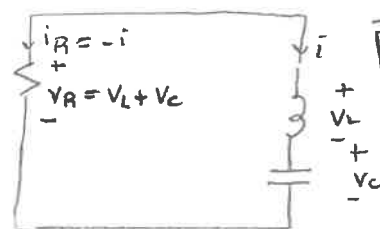
$$(R=L=C=1)$$

[3100

Finding 1 (from  $V_c$ )

$$i = i_L = i_C = C \frac{dv_C}{dt} = \frac{0}{V_C} \Rightarrow i = 0 \text{ so } V_C$$

$$\Rightarrow |I_L| = 15.0 \text{ A} \quad |V_C| = |V_C|$$

$$\underline{I_c} = I_{s0} + I_{vc}$$

$$V_c(t) = \frac{21}{\sqrt{3}} e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t - 30^\circ\right) \Rightarrow$$

$$i(t) = \frac{2M}{\sqrt{3}} e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t - 30^\circ + 120^\circ\right)$$
  

$$= -\frac{2M}{\sqrt{3}} e^{-\frac{1}{2}t} \sin\left(\frac{\sqrt{3}}{2}t\right)$$

Finding  $i$  (from  $i_L$  initial conditions)

$$i_L = i = B e^{s_0 t} + * = 2 \operatorname{Re} [B e^{s_0 t}] = 2 \operatorname{Re} [ |B| e^{-\frac{1}{2}t} e^{j(\frac{\sqrt{3}}{2}t + \angle B)} ]$$

$$= 2 |B| e^{-\frac{1}{2}t} \cos(\frac{\sqrt{3}}{2}t + \angle B)$$

Now we can find  $B$  ( $|B| \leq |B|$ ) from the initial conditions =

$$i_L(0^+) = 0$$

$$\frac{di_L}{dt}(0^+) = -M$$

(found earlier!)

$$\begin{aligned} \frac{di_L}{dt} &= s_0 B e^{s_0 t} + * = 2 \operatorname{Re} [s_0 B e^{s_0 t}] = 2 \operatorname{Re} \left[ \underbrace{s_0}_{1} |B| e^{-\frac{1}{2}t} e^{j(\frac{\sqrt{3}}{2}t + \underbrace{135^\circ}_{11+120^\circ})} \right] \\ &= 2 |B| e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t + \underbrace{135^\circ}_{11+120^\circ}\right) \end{aligned}$$

$$\Rightarrow i_L(0^+) = 0 = 2|B| \cos LB \Rightarrow \operatorname{Re} B = |B| \cos LB = 0 \Rightarrow LB = \pm 90^\circ$$

$$\frac{d_i L}{dt}(0^+) = -M = 2|B| \cos(LB + 120^\circ) \Rightarrow |B| = \frac{-M}{2 \cos(LB + 120^\circ)} \stackrel{LB = 90^\circ}{=} \frac{-M}{2 \cos 210^\circ}$$

$$= \frac{-M}{2(-\frac{\sqrt{3}}{2})} = \frac{M}{\sqrt{3}} > 0 \quad \text{😊}$$

with  $B = -90^\circ$ , we get  $|B| = \frac{-M}{2\cos(30)} = \frac{-M}{2(\frac{\sqrt{3}}{2})} = \frac{-M}{\sqrt{3}} < 0 \Rightarrow$  can't be since  $M > 0 \Rightarrow |B|$  must be  $\geq 0$ !

# Example 32

3110

B

$$\operatorname{Re} A = |A| \cos \angle A = \frac{M}{2}$$

$$\cos(\angle A + 120^\circ) = 0$$

↓

lets determine  $\angle A$  2 ways ...

i


Trig Formula

$$\cos(x+y) = \cos x \cos y - \sin x \sin y$$

$$\cos(\angle A + 120^\circ) = \cos \angle A \cos(120^\circ) - \sin \angle A \sin(120^\circ) = 0$$

$$\Rightarrow \sin \angle A \sin(120^\circ) = \cos \angle A \cos(120^\circ)$$
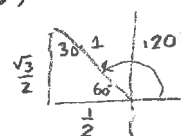
$$\Rightarrow \tan \angle A \tan 120^\circ = 1$$



$$\begin{aligned} \tan 120 &= \tan(180 - 60^\circ) \\ &= -\tan 60^\circ \\ &= -\sqrt{3} \end{aligned}$$

$$\Rightarrow \tan \angle A = \frac{1}{\tan 120} = -\frac{1}{\sqrt{3}}$$

$$\Rightarrow \angle A = -30^\circ$$

$$|A| \cos \angle A = \frac{M}{2} \Rightarrow |A| = \frac{M}{2 \cos \angle A} = \frac{M}{2 \cos(-30^\circ)} = \frac{M}{\sqrt{3}}$$

$$\Rightarrow A = \frac{M}{\sqrt{3}} e^{j30^\circ} \quad (|A| = \frac{M}{\sqrt{3}} \quad \angle A = -30^\circ)$$

$$\Rightarrow V_c = 2|A| e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t + \angle A\right) \Rightarrow V_c = \frac{2M}{\sqrt{3}} e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t - 30^\circ\right)$$

ii

Cosine Angle

$$\cos(\angle A + 120^\circ) = 0 \Rightarrow \angle A + 120^\circ = \pm 90^\circ \Rightarrow \angle A = -30^\circ, -210^\circ$$

$$\text{or } \angle A = \pm 270^\circ \Rightarrow \angle A = 150^\circ, -390^\circ$$

$\begin{aligned} &\text{or } -30^\circ \\ &\text{or } -210 + 360^\circ = 150^\circ \end{aligned}$

$$|A| = \frac{M}{2 \cos \angle A} \stackrel{\angle A = -30^\circ}{=} \frac{M}{2 \cos(-30^\circ)} = \frac{M}{\sqrt{3}} \quad (\text{OK since } M > 0)$$

$$|A| = \frac{M}{2 \cos \angle A} \stackrel{\angle A = -210^\circ}{=} \frac{M}{2 \cos(-210^\circ)} = \frac{M}{2 \cos(-30^\circ)} = \frac{M}{\sqrt{3}}$$



(NOT OK unless  $M < 0$ )

$\Rightarrow$  it must be that  $\angle A = -30^\circ$

$$\Rightarrow A = \frac{M}{\sqrt{3}} e^{-j30^\circ} \quad (\text{as we got above})$$

# Example 32

3120

[B] with  $\angle B = +90^\circ$ , we now have  $|B| = \frac{M}{\sqrt{3}}$  &

$$i_L = i = 2|B|e^{-\frac{t}{2}} \cos\left(\frac{\sqrt{3}}{2}t + \angle B\right)$$

$$\begin{aligned} i_L(t) = i(t) &= \frac{2M}{\sqrt{3}} \cos\left(\frac{\sqrt{3}}{2}t + 90^\circ\right) \\ &= -\frac{2M}{\sqrt{3}} \sin\left(\frac{\sqrt{3}}{2}t\right) \end{aligned}$$

which is precisely what we got earlier above! ☺

Find  $v_L$  from  $i_L$

$$v_L = L \frac{di_L}{dt} \Rightarrow v_L = s_0 L I_L = s_0 I_L \Rightarrow |v_L| = \overset{1}{s_0} |I_L| = |I_L|$$

$$\angle v_L = \angle s_0 + \angle I_L = 120^\circ + \angle I_L$$

$$\begin{aligned} \Rightarrow v_L(t) &= \frac{2M}{\sqrt{3}} \cos\left(\frac{\sqrt{3}}{2}t + 90^\circ + 120^\circ\right) \quad \text{cos}(180^\circ + x) = -\cos x \\ &= -\frac{2M}{\sqrt{3}} \cos\left(\frac{\sqrt{3}}{2}t + 30^\circ\right) \end{aligned}$$

Find  $v_L$  from Initial Conditions

We know  $v_L(0^+) = -M$  &  $i_L(0^+) = 0$

$$v_L = v_R - v_C$$

$$\dot{v}_L = \dot{v}_R - \dot{v}_C$$

$$= -\frac{di_L}{dt} - \dot{i}_L$$


$$\begin{aligned} \Rightarrow \dot{v}_L &= -v_L - \dot{i}_L \Rightarrow \dot{v}_L(0^+) = -v_L(0^+) - \dot{i}_L(0^+) \\ &= M - 0 \\ &= M \end{aligned}$$

$\Rightarrow$  We'll now use

$$\begin{aligned} v_L(0^+) &= -M \\ \dot{v}_L(0^+) &= M \end{aligned}$$

to determine  $e = |C|e^{j\omega t}$  in

$$\begin{aligned} v_L &= Ce^{s_0 t} + * = 2 \operatorname{Re}[Ce^{s_0 t}] \\ &= 2|C|e^{-\frac{t}{2}} \cos\left(\frac{\sqrt{3}}{2}t + \angle C\right) \end{aligned}$$

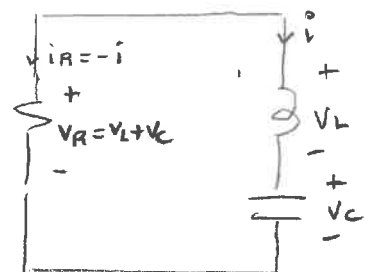


# Example 32

(Switching Circuits)

3/30

B

## Visual Summary

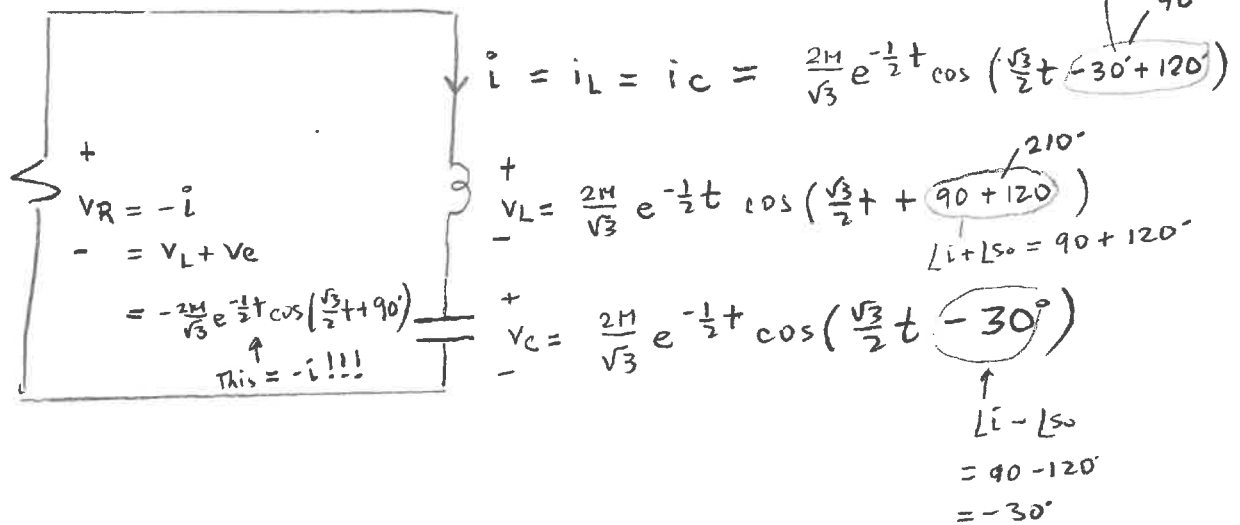

Now lets show that


$$V_R = -i = V_L + V_C$$

$$\begin{aligned}
 -\text{Re}\left[\frac{2M}{\sqrt{3}} e^{s_0 t} e^{j(-30 + 150)}\right] &= \text{Re}\left[\frac{2M}{\sqrt{3}} e^{s_0 t} e^{j(90 + 150)} + \frac{2M}{\sqrt{3}} e^{s_0 t} e^{-j30}\right] \\
 -e^{j(-30 + 120)} &\stackrel{?}{=} e^{j(90 + 120)} + e^{-j30} \\
 -e^{-j30} e^{j90} e^{j30} &= e^{j90} e^{j90} e^{j30} + e^{-j30} \\
 -j &= -e^{j30} + e^{-j30} \\
 j &= e^{j30} - e^{-j30} = j 2 \sin 30^\circ = j 1 \quad \checkmark \checkmark \checkmark
 \end{aligned}$$

# Problem 32

(Switching Circuits)

3140

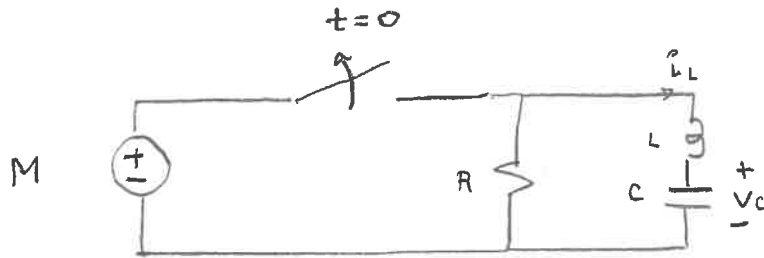

$$R=2, L=1, C=\frac{1}{2}$$

- Find  $i_L, V_C$
- ① at  $t=0^-$
  - ② at  $t=0^+$
  - ③ for  $t > 0^+$