

1 Compute transfer function  $H_C$  from  $u$  to  $y_C$ .

Hint: Voltage divider with

$$Z_C = \frac{1}{sC}$$

$$Z_L = sL$$

$$Z_R = R$$

$$H_C = \frac{y_C}{u} = \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}} = \frac{\frac{1}{sC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

2 Compute the transfer function  $H_R$  from  $u$  to  $y_R$

$$H_R = \frac{y_R}{u} = \frac{R}{R + sL + \frac{1}{sC}} = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

3 Compute the transfer function  $H_L$  from  $u$  to  $y_L$

$$H_L = \frac{y_L}{u} = \frac{sL}{R + sL + \frac{1}{sC}} = \frac{s^2}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Note:  $H_L + H_R + H_C = 1$

Why?  $\frac{y_L}{u} + \frac{y_R}{u} + \frac{y_C}{u} = 1$

Why? By KVL =  $u = y_R + y_L + y_C$

4 Compute the transfer function  $H_{LC}$  from  $u$  to  $y_{LC} = y_L + y_C$ .

$$H_{LC} = \frac{y_{LC}}{u} = \frac{sL + \frac{1}{sC}}{R + sL + \frac{1}{sC}} = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Note:  $H_R + H_{LC} = 1$

since  $\frac{y_R}{u} + \frac{y_{LC}}{u} = \frac{y_R}{u} + \frac{y_L + y_C}{u} = \frac{y_R}{u} + \frac{y_L}{u} + \frac{y_C}{u} = 1$

5 What is the differential equation associated with  $y_C, y_R, y_L, y_{LC}$

$$H_C = \frac{y_C}{u} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \Rightarrow (s^2 + \frac{R}{L}s + \frac{1}{LC}) y_C = \frac{1}{LC} u$$

$$\Rightarrow \ddot{y}_C + \frac{R}{L} \dot{y}_C + \frac{1}{LC} y_C = \frac{1}{LC} u$$

$$H_R = \frac{y_R}{u} = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \Rightarrow (s^2 + \frac{R}{L}s + \frac{1}{LC}) y_R = (\frac{R}{L}) u$$

$$\Rightarrow \dot{y}_R + \frac{R}{L} y_R + \frac{1}{LC} y_R = \frac{R}{L} u$$

$$H_L = \frac{y_L}{u} = \frac{s^2}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \Rightarrow (s^2 + \frac{R}{L}s + \frac{1}{LC}) y_L = (s^2) u$$

$$\Rightarrow \ddot{y}_L + \frac{R}{L} \dot{y}_L + \frac{1}{LC} y_L = \ddot{u}$$

$$H_{LC} = \frac{y_{LC}}{u} = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} \Rightarrow (s^2 + \frac{R}{L}s + \frac{1}{LC}) y_{LC} = (s^2 + \frac{1}{LC}) u$$

$$\Rightarrow \ddot{y}_{LC} + \frac{R}{L} \dot{y}_{LC} + \frac{1}{LC} y_{LC} = \ddot{u} + \frac{1}{LC} u$$

Recall =

$$\begin{aligned} y &\leftrightarrow Y \\ \dot{y} &\leftrightarrow sY \\ \ddot{y} &\leftrightarrow s^2Y \end{aligned}$$

(assuming zero initial conditions)

6 What is the system characteristic equation (polynomial)  $\Phi$ ?

$$\Phi = \text{denominator of any system transfer function } H$$

$$= s^2 + \frac{R}{L}s + \frac{1}{LC}$$

6 What are the system poles (characteristic roots)?

$$\Phi(s) = s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$\Rightarrow s_{1,2} = \frac{-\frac{R}{L} \pm \sqrt{(\frac{R}{L})^2 - 4(1)(\frac{1}{LC})}}{2(1)}$$

$$= -\frac{R}{2L} \pm \sqrt{(\frac{R}{2L})^2 - \frac{1}{LC}}$$

Recall =

$$\begin{aligned} &\text{Quadratic Formula:} \\ &as^2 + bs + c = 0 \\ &s_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} \end{aligned}$$

7 What is the system discriminant?

$$\begin{aligned}\text{discriminant} &= \text{quantity underneath radical } \sqrt{(\cdot)} \\ &= \left(\frac{R}{2L}\right)^2 - \frac{1}{LC}\end{aligned}$$

This is important because it determines the nature of the roots.

8 What can be said about the system poles (roots) when discriminant = 0? For what R is discriminant zero?

When discriminant = 0  $\Rightarrow$  system poles (roots) are =

$$s_{1,2} = -\frac{R}{L} \pm \frac{R}{L}$$

Note:

In this case,  
system's time constant  
or 1% settling time is:


$$t_s = \frac{5}{|\text{Re poles}|} = \frac{5}{1 - \frac{R}{L}} = 5\left(\frac{L}{R}\right)$$

$\Rightarrow$  They are therefore

real

repeated

stable (in left half plane)

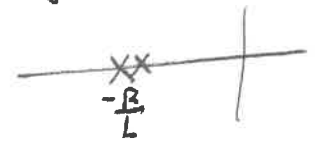

Critical Value of R:

$$\text{discriminant} = \left(\frac{R}{2L}\right)^2 - \frac{1}{LC} = 0 \Leftrightarrow \left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$$

$$\Leftrightarrow \frac{R}{2L} = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow \boxed{R = R_c \triangleq 2\sqrt{\frac{L}{C}}}$$

For this value of R, we say that the system

is Critically Damped

$\uparrow$  (a "critical" level of resistance (damping))

# Example 33

3/80

9

What can be said about the system poles (roots) when  $\text{disc} < 0$ ?  
For what  $R$  is  $\text{disc} < 0$ ?

discriminant  $< 0 \Rightarrow$  system poles (roots) are

$$s_{1,2} = -\frac{R}{2L} \pm j \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

Note=

In this case,  
system 5 time constant  
or 1% settling time is:


$$t_s = \frac{5}{|\text{Re poles}|} = \frac{5}{|-\frac{R}{2L}|} = \frac{5}{\frac{R}{2L}} = \frac{10L}{R}$$

$\Rightarrow$  They are therefore

complex

conjugates

stable (in left half plane)

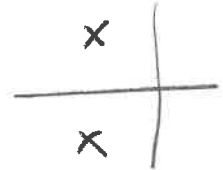

$$\text{disc} < 0 \Leftrightarrow R < R_c \triangleq 2\sqrt{\frac{L}{C}}$$

For these values of  $R$ , we say that the system is

**Underdamped**

$\uparrow$  (a "low" level of resistance (damping))

Note:

If  $R = 0$ , then the system poles (roots)


$$\text{are} = s_{1,2} = \pm j \frac{1}{\sqrt{LC}}$$

i.e. they are

purely imaginary

conjugates

marginally stable

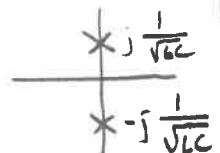

We shall assume

$R > 0$  so that

system is stable !!!

### Example 33

3190

10 What can be said about the system poles (roots) when  $\text{disc} > 0$ ?  
For what  $R$  is  $\text{disc} > 0$ ?

$\text{disc} > 0 \Rightarrow$  system poles (roots) are

$$s_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Note:

In this case,

system 5 time constant  
or 1% settling time is:


$$t_s = \frac{5}{|\text{Re slow pole}|} = \frac{5}{|s_2|}$$
$$= \frac{5}{\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}}$$

$\Rightarrow$  They are therefore

real

distinct (different)

stable (in left half plane)

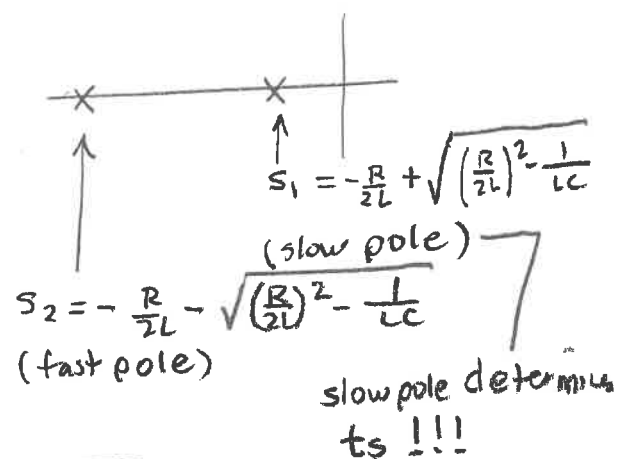

$$\text{disc} > 0 \Leftrightarrow R > R_c \triangleq 2\sqrt{\frac{L}{C}}$$

For these values of  $R$ , we say that the system is

**Overdamped**

$\uparrow$  (a "high" level of resistance (damping))


II

Assuming stability ( $R > 0$ ) for the transfer function  $H$ , determine

$$y_{ss} \text{ when } u(t) = A + B \sin(\omega_0 t + \theta)$$

steady  
state  
output  $y$ 

Answer =

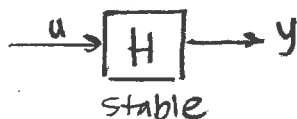

$$u = A + B \sin(\omega_0 t + \theta)$$

$$\Rightarrow y_{ss} = A H(0) + B |H(j\omega_0)| \sin(\omega_0 t + \theta + \angle H(j\omega_0))$$

Note: The above very concisely summarized all of the work in our texts' Chapter 9!

This is why the following are so EXTREMELY IMPORTANT!

- a) transfer function  $H$
- b) magnitude response  $|H(j\omega)|$
- c) phase response  $\angle H(j\omega)$

### Example 33

3210

12 From now on, we assume that our system is  
Very Underdamped; i.e.

$$R \ll R_c \triangleq 2\sqrt{\frac{L}{C}}$$

(little resistance or damping)

Note =

For  $R=0$ , the system poles are

$$s_{1,2} = \pm j \frac{1}{\sqrt{LC}}$$

i.e. they are  
purely imaginary  
conjugates  
marginally stable

$$\begin{array}{c} * j \frac{1}{\sqrt{LC}} \\ \hline * -j \frac{1}{\sqrt{LC}} \end{array}$$

$$H_c = \frac{1}{s^2 + \frac{1}{LC}}$$

$$H_R = 0$$

$$H_L = \frac{s^2}{s^2 + \frac{1}{LC}}$$

$$H_{LC} = H_L$$

Lets use the following numbers moving forward =

$$R = 20 \Omega$$

$$L = 10 \text{ mH} = (10)(10^{-3}) \text{ H} = 10^{-2} \text{ H}$$

$$C = 1 \mu\text{F} = 10^{-6} \text{ F}$$

In such a case:  $\frac{R}{L} = \frac{20}{10^{-2}} = 2000$

$$\frac{1}{LC} = \frac{1}{(10^{-2})(10^{-6})} = 10^8$$

### Example 33

3220

13 Determine the system poles -

$$\Phi(s) = s^2 + \frac{R}{L}s + \frac{1}{LC} = s^2 + 2000s + 10^8 = 0$$

$$\Rightarrow s_{1,2} = \frac{-2000 \pm \sqrt{(2 \times 10^3)^2 - 4(1)(10^8)}}{2(1)}$$


$$= -1000 \pm \sqrt{\frac{1}{4}(4)(10^6) - (10^8)}$$

$$= -1000 \pm \sqrt{10^6(1 - 10^2)}$$

$$= -1000 \pm 1000 \sqrt{-99}$$

$$= -1000(-1 \pm j\sqrt{99})$$

$$\approx 1000(-1 \pm j10)$$

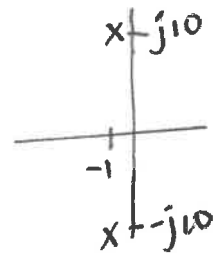

14 Let's compute each of the transfer functions  $H$  & plot  $|H(j\omega)|$  &  $\angle H(j\omega)$ .


$H_c$

$$H_c(s) = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{10^8}{s^2 + 2000s + 10^8}$$

Resonant Low Pass System

$$H_c(j\omega) = \frac{10^8}{10^8 - \omega^2 + j2000\omega}$$

$$|H_c(j\omega)| = \frac{10^8}{\sqrt{(10^8 - \omega^2)^2 + (2000\omega)^2}}$$

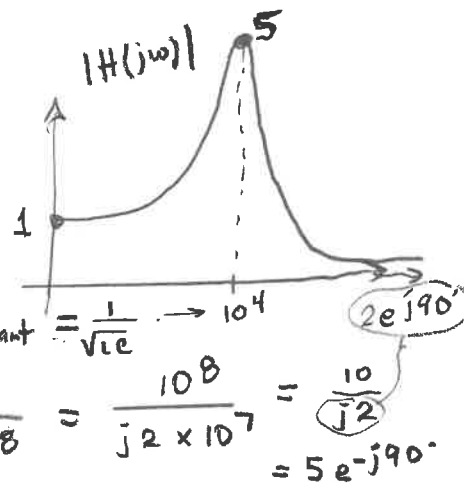

Note:

$H_c \approx 1$  small  $s$

$H_c \approx \frac{1}{s^2}$  large  $s$

Near  $s = j10^4$

$H_c \approx 5e^{-j90^\circ}$

Note:

$$H(0) = 1 \quad |H(j\infty)| = 0$$

$$H(j10^4) = \frac{10^8}{-10^8 + j2000 \times 10^4 + 10^8} = \frac{10^8}{j2 \times 10^7} = \frac{10}{j2} = 5e^{-j90^\circ}$$



# Example 33

3230

$$\angle H_c(j\omega) = \angle \text{top} - \angle \text{bottom}$$


$$= \angle 10^8 - \angle 10^8 - \omega^2 + j 2000 \omega$$

$$= 0 - \left\{ \begin{array}{l} \text{triangle with base } 10^8 - \omega^2 \text{ and height } 2000\omega \\ \text{triangle with base } \omega^2 - 10^8 \text{ and height } 2000\omega \end{array} \right.$$

$$10^8 > \omega^2 \downarrow 10^4 > \omega \geq 0$$

$$\text{if } 10^4 \leq \omega < \infty$$
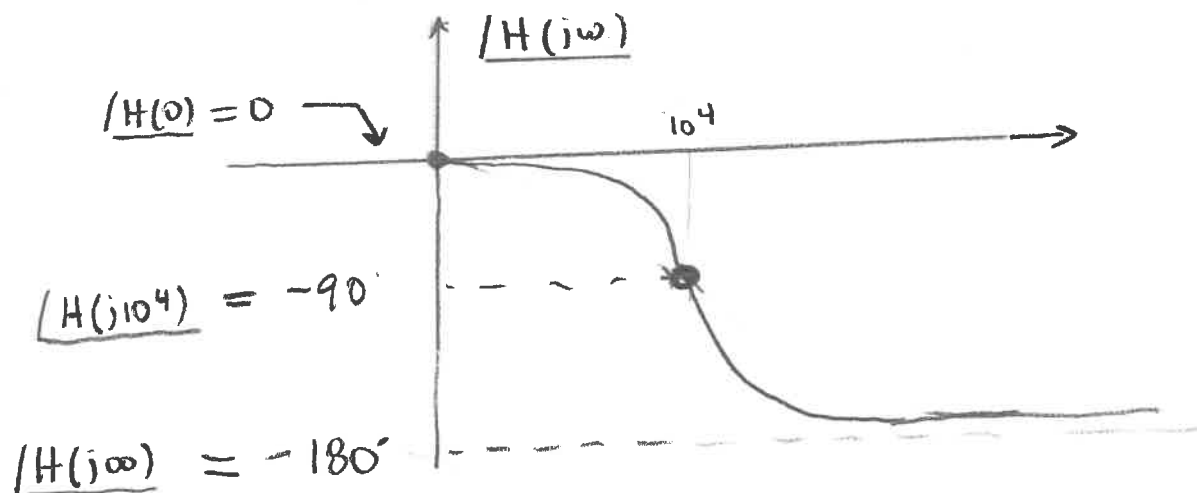
$$= \begin{cases} -\tan^{-1} \left( \frac{2000\omega}{10^8 - \omega^2} \right) & \text{if } \omega \in [0, 10^4) \\ -(180 - \tan^{-1} \left( \frac{2000\omega}{\omega^2 - 10^8} \right)) & \text{if } \omega \in [10^4, \infty) \end{cases}$$



# Example 33

3240

$H_R$

$$H_R(s) = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{2000s}{s^2 + 2000s + 10^8}$$

Note:


$$H_R \approx \frac{2000s}{10^8} \text{ small } s$$

$$H_R \approx 1 \text{ near } s = j10^4$$

$$H_R \approx \frac{2000}{s} \text{ large } s$$

$$H_R(j\omega) = \frac{j2000\omega}{10^8 - \omega^2 + j2000\omega}$$

$$|H_R(j\omega)| = \frac{2000\omega}{\sqrt{(10^8 - \omega^2)^2 + (2000\omega)^2}}$$

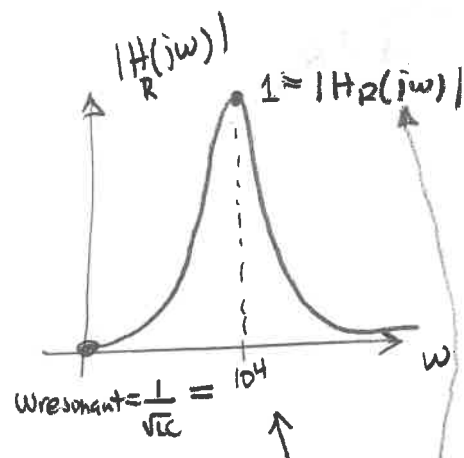

Note:  $H(0) = 0 = 0e^{j0^\circ}$   
 $|H(j\infty)| = 0$


Resonant Bandpass filter

$$H(j10^4) = \frac{2000j10^4}{-10^8 + j2000(10^4) + 10^8} = 1 = 1e^{j0^\circ}$$

$$\angle H_R(j\omega) = \angle \text{top} - \angle \text{bottom}$$

$$= \angle j2000\omega - \angle (10^8 - \omega^2 + j2000\omega)$$
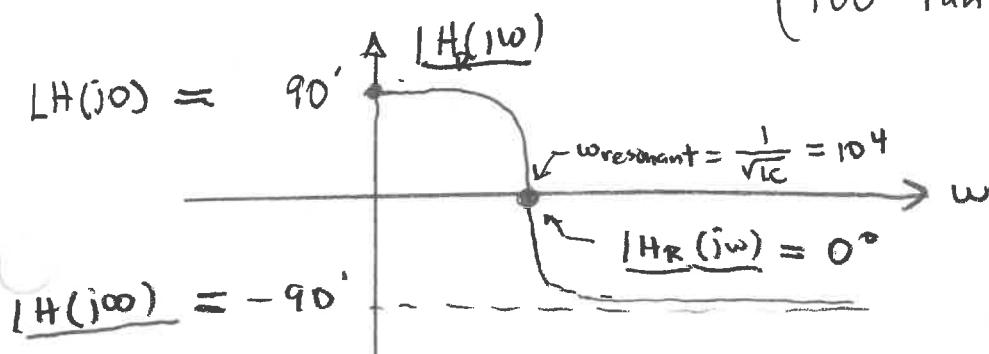
$$= 90^\circ - \begin{cases} \tan^{-1}\left(\frac{2000\omega}{10^8 - \omega^2}\right) & \text{if } \omega \in [0, 10^4) \\ 180 - \tan^{-1}\left(\frac{2000\omega}{\omega^2 - 10^8}\right) & \text{if } \omega \in [10^4, \infty) \end{cases}$$



# Example 33

3250

$H_L$

$$H_L(s) = \frac{s^2}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{s^2}{s^2 + 2000s + 10^8}$$

$$H_L(s) \approx \frac{s^2}{10^8} \quad s \text{ small}$$

$$H_L(s) \approx \frac{s}{2000} \quad \text{near } s \approx j10^4$$


$$H_L(s) \approx 1 \quad \text{large } s$$

$$H_L(j\omega) =$$

$$\frac{(j\omega)^2}{10^8 - \omega^2 + j2000\omega} \quad (we^{j90^\circ})^2 = \omega^2 e^{j180^\circ}$$

$$|H_L(j\omega)| =$$
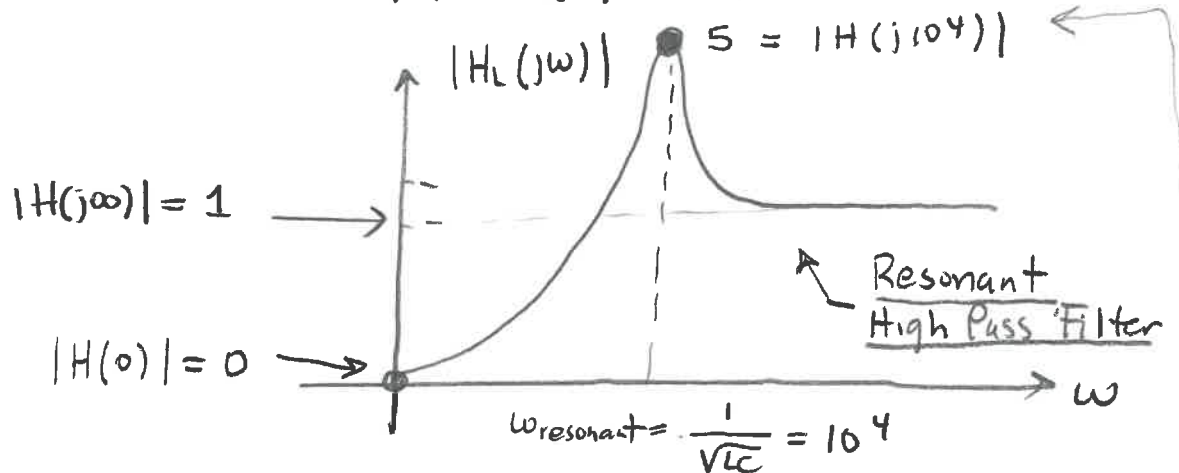
$$\frac{\omega^2}{\sqrt{(10^8 - \omega^2)^2 + (2000\omega)^2}}$$



Note:  $H(0) = 0 = 0 e^{j0^\circ}$

$$H(j\infty) = 1 = 1 e^{j0^\circ}$$

$$\begin{aligned} H(j10^4) &= \frac{(j10^4)^2}{\cancel{-10^8} + j(2000)(10^4) + \cancel{10^8}} \\ &= \frac{j10^4}{2000} \\ &= j5 = 5 e^{j90^\circ} \end{aligned}$$

# Example 33

3260


$$\angle H_L(j\omega) = \angle \text{top} - \angle \text{bottom}$$

$$= \angle (j\omega)^2 - \angle (108 - \omega^2 + j2000\omega)$$

$$(j\omega)^2 = (\omega e^{j90^\circ})^2 = \omega^2 e^{j180^\circ}$$

$$= 180^\circ - \begin{cases} \tan^{-1} \left( \frac{2000\omega}{108 - \omega^2} \right) & \omega \in [0, 104) \\ 180 - \tan^{-1} \left( \frac{2000\omega}{\omega^2 - 108} \right) & \omega \in [104, \infty) \end{cases}$$
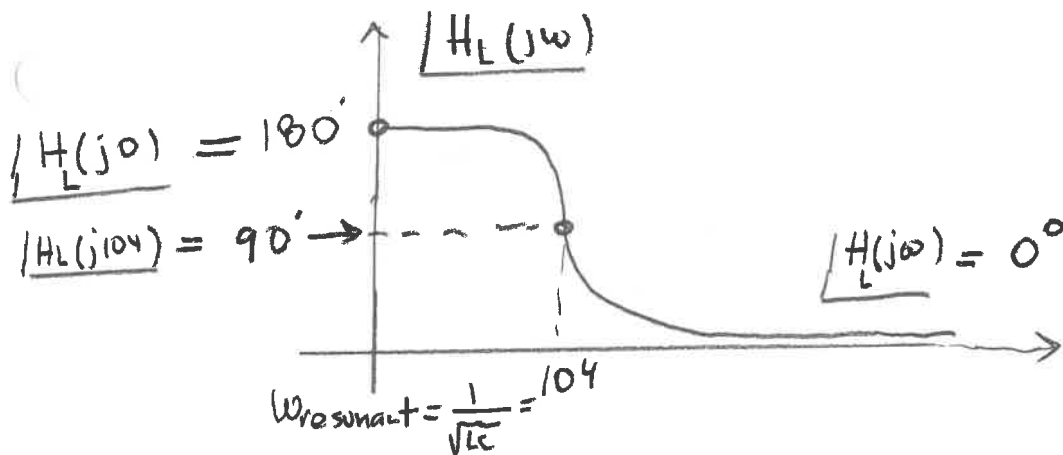
$$= \begin{cases} 180 - \tan^{-1} \left( \frac{2000\omega}{108 - \omega^2} \right) & \omega \in [0, 104) \\ \tan^{-1} \left( \frac{2000\omega}{\omega^2 - 108} \right) & \omega \in [104, \infty) \end{cases}$$



# Example 33

3270

$H_{LC}$

$$H_{LC}(s) = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{s^2 + 10^8}{s^2 + 2000s + 10^8}$$

$$H_{LC}(j\omega) = \frac{10^8 - \omega^2}{10^8 - \omega^2 + j2000\omega}$$

$$|H_{LC}(\omega)| = \frac{|top|}{|bottom|}$$


$$= \frac{|10^8 - \omega^2|}{\sqrt{(10^8 - \omega^2)^2 + (2000\omega)^2}}$$

Note:  $H_{LC}(0) = 1 = 1e^{j0^\circ}$

$$H_{LC}(j10^4) = 0 = 0e^{j0^\circ}$$

↑ since numerator of  $H_{LC}$   
has zeros at  $\pm j \frac{1}{\sqrt{LC}}$
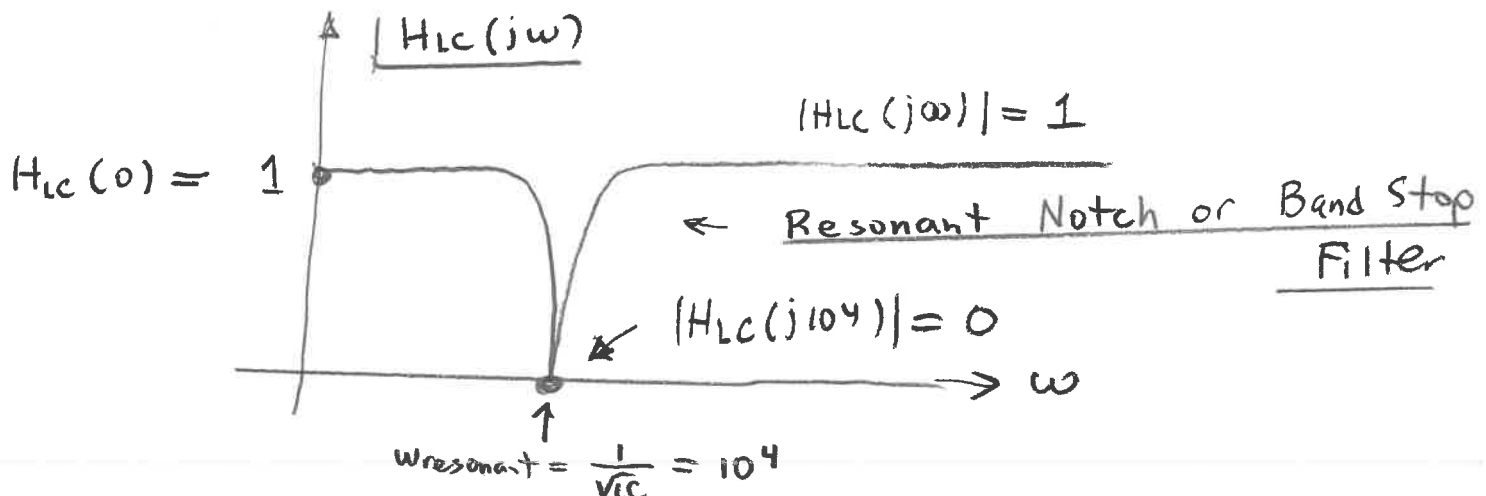
$$H_{LC}(j\infty) = 1 = 1e^{j0^\circ} = \pm j10^4$$



# Example 33


3280

$$\angle H_{LC}(j\omega) = \angle_{\text{top}} - \angle_{\text{bottom}}$$

$$= \angle 10^8 - \omega^2 - \angle 10^8 - \omega^2 + j 2000 \omega$$

$$= \begin{cases} 0^\circ - \tan^{-1} \left( \frac{2000\omega}{10^8 - \omega^2} \right) & \text{if } \omega \in [0, 10^4) \\ 180^\circ - (180 - \tan^{-1} \left( \frac{2000\omega}{\omega^2 - 10^8} \right)) & \text{if } \omega \in [10^4, \infty) \end{cases}$$
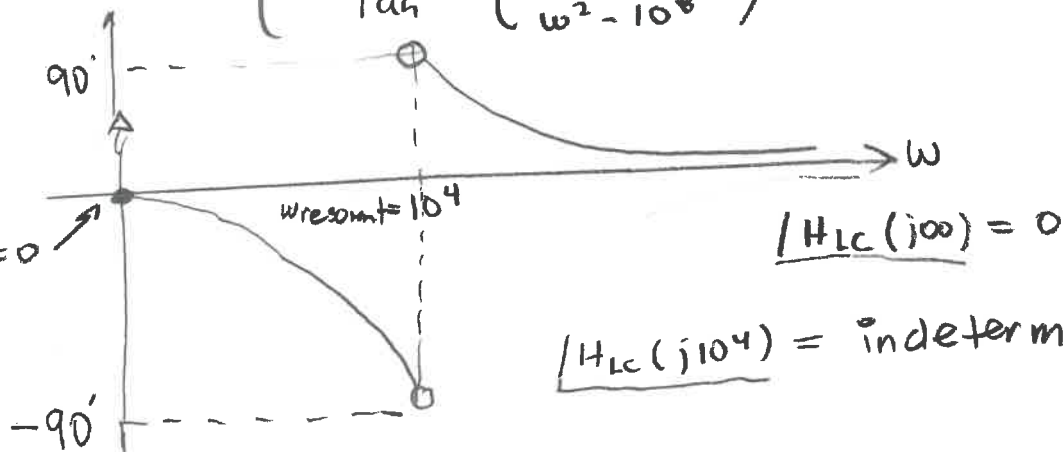
$$= \begin{cases} -\tan^{-1} \left( \frac{2000\omega}{10^8 - \omega^2} \right) & \omega \in [0, 10^4) \\ \tan^{-1} \left( \frac{2000\omega}{\omega^2 - 10^8} \right) & \omega \in [10^4, \infty) \end{cases}$$



$\angle H_{LC}(j10^4) = \text{indeterminate!}$

Note:  $H_{LC}(s) \cong 1 = 1 e^{j0}$   $s$  small

$H_{LC}(s) \cong 1 = 1 e^{j0}$   $s$  large


$H_L(s) \cong \frac{s^2 + 10^8}{2000s}$   $s \cong j \frac{1}{\sqrt{LC}}$

$$H_L(j\omega) = \begin{cases} \frac{10^8 - \omega^2}{2000\omega e^{j90^\circ}} = \left( \frac{10^8 - \omega^2}{2000\omega} \right) e^{-j90^\circ} & \omega \in [0, 10^4) \\ \frac{(\omega^2 - 10^8) e^{j180^\circ}}{2000\omega e^{j90^\circ}} & \omega \in (10^4, 10^4+) \\ \left( \frac{\omega^2 - 10^8}{2000\omega} \right) e^{j90^\circ} & \end{cases}$$

# Problem 33

3290

Consider the RLC circuit

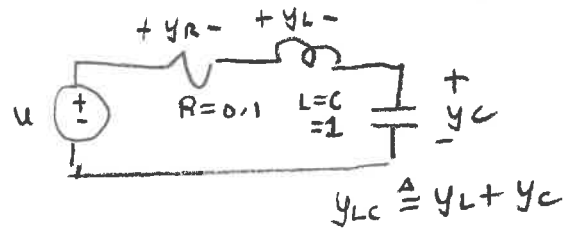

- 1 Compute  $H(s)$ ,  $H(j\omega)$ ,  $|H(j\omega)|$ ,  $\underline{|H(j\omega)|}$  for each of the transfer functions  $H_C$ ,  $H_R$ ,  $H_L$ ,  $H_{LC}$
- 2 Plot  $|H(j\omega)| \geq \underline{|H(j\omega)|}$  for each transfer function


Note: clearly indicate what the resonant frequency is in each plot!

# Example 34

## Average Power & RMS Values

3300

Consider a device :

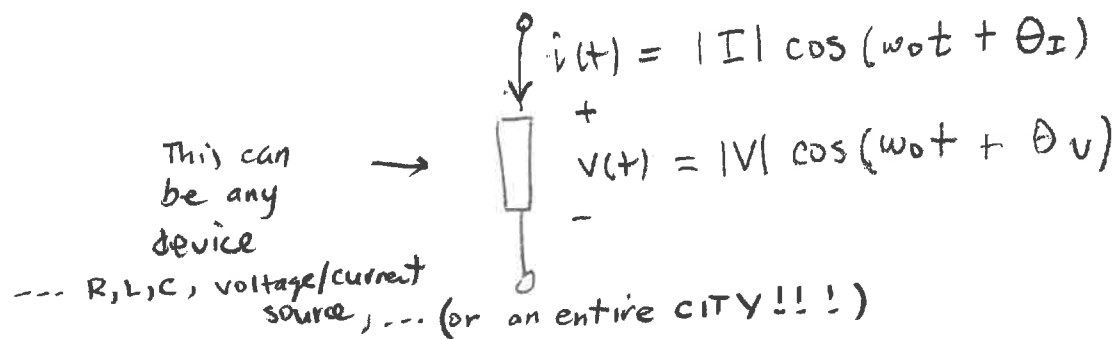

Using the trig identity

$$\cos x \cos y = \frac{1}{2} \cos(x+y) + \frac{1}{2} \cos(x-y)$$

yields =

$$\begin{aligned} p(t) &= v(t) i(t) \\ &= [|V| \cos(\omega_0 t + \theta_V)] [|I| \cos(\omega_0 t + \theta_I)] \\ &= \frac{1}{2} |V| |I| \cos(2\omega_0 t + \theta_V + \theta_I) + \frac{1}{2} |V| |I| \cos(\theta_V - \theta_I) \end{aligned}$$

↑  
sinusoid with frequency  $2\omega_0$  3 period  $\frac{2\pi}{2\omega_0} = \frac{\pi}{\omega_0}$

↑  
constant

If we define

$$\langle f \rangle \triangleq \frac{1}{T} \int_T f(x) dx$$

↑  
average of a periodic function  $f$  with period  $T$

Taking  $\langle p \rangle$  yields =

$$\begin{aligned} \langle p \rangle &= \langle \frac{1}{2} |V| |I| \cos(2\omega_0 t + \theta_V + \theta_I) \rangle \xrightarrow{\text{zero!}} \\ &\quad + \langle \frac{1}{2} |V| |I| \cos(\theta_V - \theta_I) \rangle \\ &= \frac{1}{2} |V| |I| \cos(\theta_V - \theta_I) \end{aligned}$$



Summary =



$$i(t) = |I| \cos(\omega_0 t + \theta_I)$$

$$v(t) = |V| \cos(\omega_0 t + \theta_V)$$

$$p(t) = v(t)i(t) = \frac{1}{2} |V| |I| \left\{ \cos(2\omega_0 t + \theta_V + \theta_I) + \cos(\theta_V - \theta_I) \right\}$$

$$\langle p \rangle = \frac{1}{2} |V| |I| \cos(\theta_V - \theta_I)$$

Lets examine  $\langle p \rangle$  for a resistor, inductor, capacitor =  
(same  $v$  &  $i$  above !!!)

Resistor

$$v = Ri \Rightarrow |V| = R |I| \quad \theta_V = \theta_I \quad (\cos(\theta_V - \theta_I) = 1)$$

$$\Rightarrow \langle P_R \rangle = \frac{1}{2} |V| |I| = \frac{1}{2} R |I|^2 = \frac{1}{2} \frac{|V|^2}{R}$$

Inductor

$$v = L \frac{di}{dt} \Rightarrow \frac{V}{I} = sL \Big|_{s=j\omega} = j\omega L$$

$$\Rightarrow \theta_V - \theta_I = 90^\circ$$

$$\cos 90 = 0 \Rightarrow$$

$$\langle P_L \rangle = 0$$

Capacitor

$$i = C \frac{dv}{dt} \Rightarrow \frac{V}{I} = \frac{1}{sC} \Big|_{s=j\omega} = \frac{1}{j\omega C}$$

$$\Rightarrow \theta_V - \theta_I = -90^\circ$$

$$\Rightarrow \langle P_C \rangle = 0$$

### Example 34

3320

root mean square  
RMS Values

Consider  $f(t) = A \cos(\omega_0 t + \theta)$

(angular) frequency  
 $\uparrow$   $T = \frac{2\pi}{\omega_0}$  (period)

We now compute =

$$f_{rms} = \sqrt{\frac{1}{T} \int_T f^2(t) dt}$$

$\uparrow$  any period

$$f_{rms}^2 = \frac{1}{T} \int_T f^2(t) dt$$

$$= \frac{\omega_0}{2\pi} \int_x^{x + \frac{2\pi}{\omega_0}} [A \cos(\omega_0 t + \theta)]^2 dt$$

$\cos^2 x = \frac{1}{2} [\cos 2x + 1]$

$$= \frac{\omega_0}{2\pi} \int_x^{x + \frac{2\pi}{\omega_0}} \frac{A^2}{2} [\cos(2\omega_0 t + 2\theta) + 1] dt$$

$$= \frac{\omega_0}{2\pi} \frac{A^2}{2} \left( \int_x^{x + \frac{2\pi}{\omega_0}} \cos(2\omega_0 t + 2\theta) dt \right) + \frac{\omega_0}{2\pi} \frac{A^2}{2} \int_x^{x + \frac{2\pi}{\omega_0}} dt$$

$\uparrow$   
we'll show this  
= zero below

$$= \frac{\omega_0}{2\pi} \frac{A^2}{2} \left( \frac{2\pi}{\omega_0} \right)$$

$$= \frac{A^2}{2}$$

$$\Rightarrow \boxed{f_{rms} = \frac{A}{\sqrt{2}} \quad \text{for } f(t) = A \cos(\omega_0 t + \theta)}$$

### Example 34

3330

Now let's show that

$$\int_x^{x + \frac{2\pi}{\omega_0}} \cos(2\omega_0 t + 2\theta) dt = 0$$

solution:

$$\int_x^{x + \frac{2\pi}{\omega_0}} \cos(2\omega_0 t + 2\theta) dt = \left. \frac{\sin(2\omega_0 t + 2\theta)}{2\omega_0} \right|_x^{x + \frac{2\pi}{\omega_0}}$$

$$= \frac{1}{2\omega_0} \left[ \sin(2\omega_0(x + \frac{2\pi}{\omega_0}) + 2\theta) - \sin(2\omega_0 x + 2\theta) \right]$$

$$= \frac{1}{2\omega_0} \left[ \sin(2\omega_0 x + 2\theta + 4\pi) - \sin(2\omega_0 x + 2\theta) \right]$$

$\sin(x + 2\pi n) = \sin x$   $\rightarrow$

$$= \frac{1}{2\omega_0} \left[ \sin(2\omega_0 x + 2\theta) - \sin(2\omega_0 x + 2\theta) \right]$$

$$= 0$$

$\uparrow$  as we wanted to show!



Why should anyone care about this RMS value stuff?

For a resistor  $\left[ \langle P_R \rangle = \frac{1}{2} |V| |I| = \frac{1}{2} R |I|^2 = \frac{1}{2} \frac{|V|^2}{R} \right]$

Noting that  $V_{rms} = \frac{V}{\sqrt{2}}$  &  $I_{rms} = \frac{I}{\sqrt{2}}$ , the above

becomes

$$\left[ \langle P_R \rangle = |V_{rms}| |I_{rms}| = R |I_{rms}|^2 = \frac{|V_{rms}|^2}{R} \right]$$




Now  $\langle P_R \rangle$  formulae look just like ohm's law for a resistor !!!

# Problem 34

3340

For the circuit in Problem 33 =

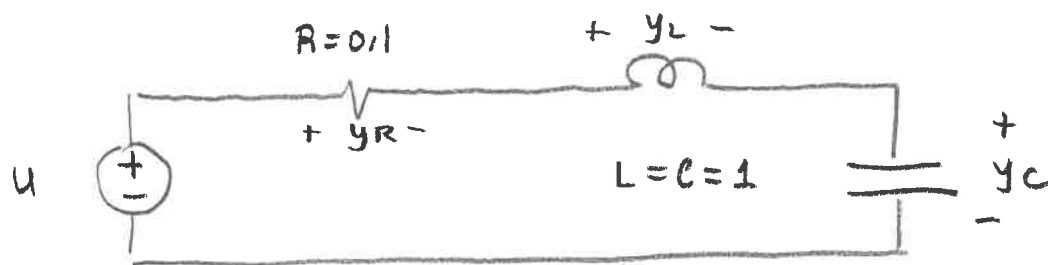

compute  $\langle P_R \rangle$ ,  $\langle P_L \rangle$ ,  $\langle P_C \rangle$

when  $u(t) = A \sin(\omega_0 t + \theta)$

$\omega_0$  = resonant frequency of the circuit!

Hint: What do  $H_R$ ,  $H_L$ ,  $H_C$  look like near  $s = j\omega_0$ ?

That will permit you to compute  $Y_{Rss}$ ,  $Y_{Lss}$ ,  $Y_{Css}$

Now you can find the steady state current  $i_{ss}$  passing through  $R$ ,  $L$ , &  $C$ .

Now you can compute  $\langle P_R \rangle$ ,  $\langle P_L \rangle$ ,  $\langle P_C \rangle$

↑  
This is  
the important  
one!

↑  
These are  
trivial!

