

EXAMS & EXAM SOLUTIONS

FALL 2023

Dr. A.A. Rodriguez

EE202

All rights reserved

Exam Rules

(As discussed in class & ^{formally} announced)

Exam # 1

Fall 2023

10-25-23

- 1 One $8\frac{1}{2}'' \times 11''$ sheet permitted;
otherwise closed books, closed notes, closed phones,
open minds!
- 2 Calculator permitted (no computer!!; no phone!!!)
- 3 NO PHONES ! Phones should not be visible at all!
A visible phone will result in a zero
grade for the exam!
- 4 Write full name legibly on each page provided.
- 5 Please show all work. Write your solutions on the pages
provided. (No other pages should be used!)
- 6 Clearly label voltages and currents on circuits provided.
- 7 Use variables provided! (No additional variables!)
- 8 Unreadable work will receive no credit.
- 9 Please place important equations and answers within boxes.
- 10 Please turn in solutions to me at end of period!
- 11 PLEASE DO NOT CHEAT!!!




-all rights reserved

Problem # 1

Relate y to u_1, u_2


(Propagate y)

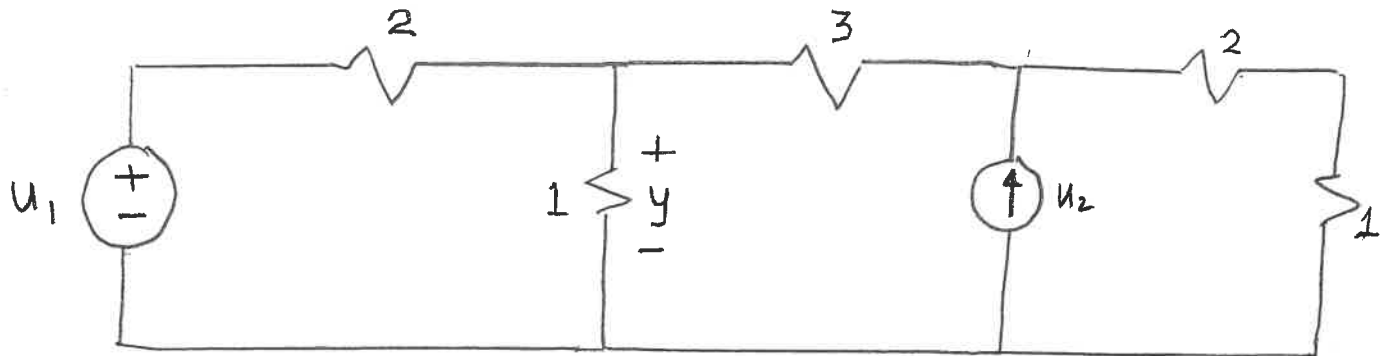

Problem #2

Relate w_1, w_2, w_3 to u_1, u_2, u_3


(Nodal Analysis)

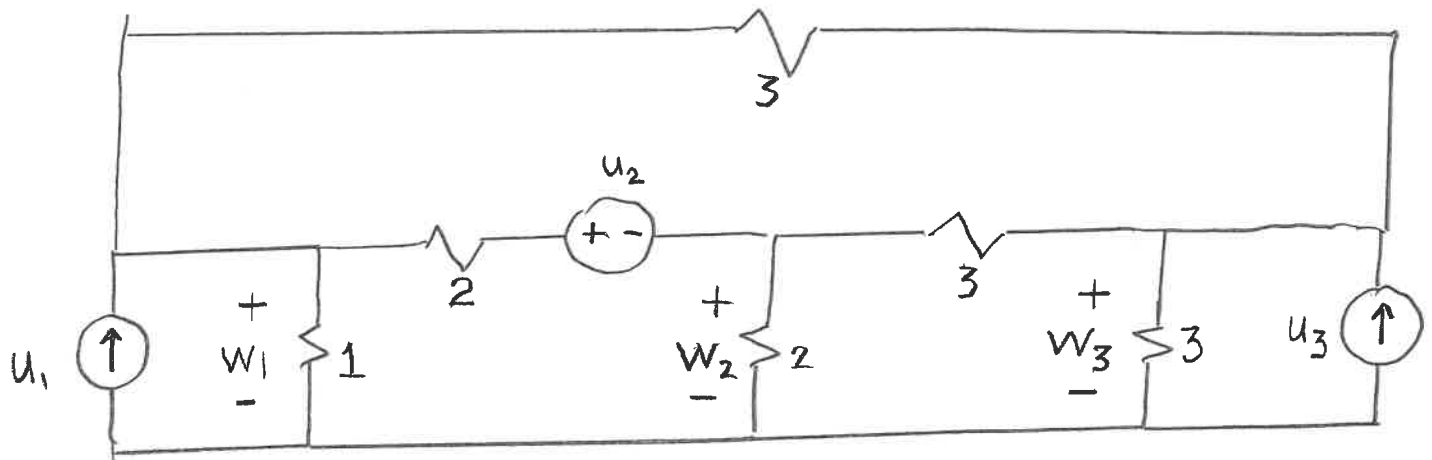

Problem # 3

Relate I_1, I_2, I_3, I_4 to u_1, u_2, u_3


(Mesh Analysis)

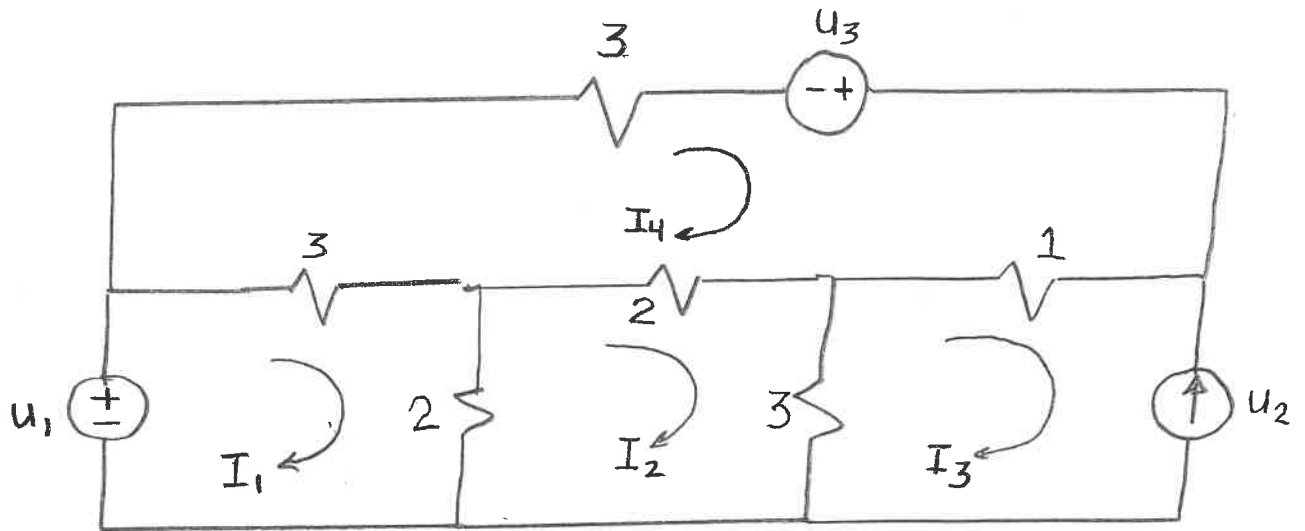

Problem # 4

Find a Thevenin equivalent at y
(looking leftward)

(Thevenin
Equivalent
at y)

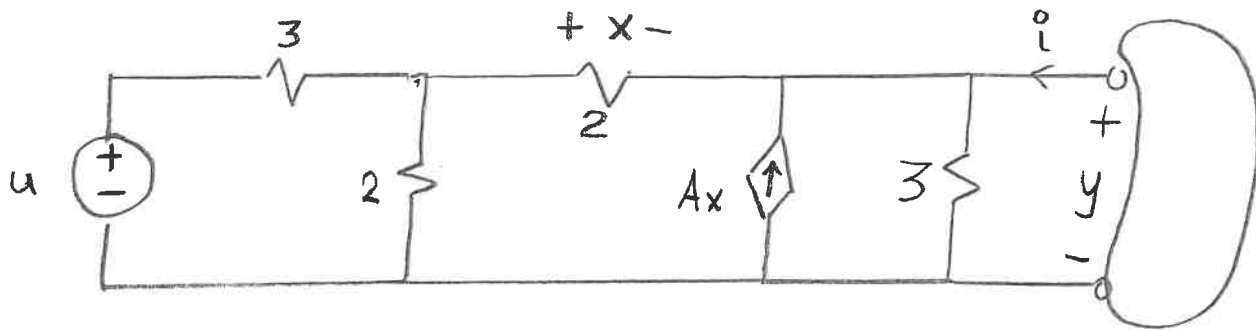


Problem # 5

Find a Thevenin equivalent at y

(looking rightward)


(Thevenin
Equivalent
at y)

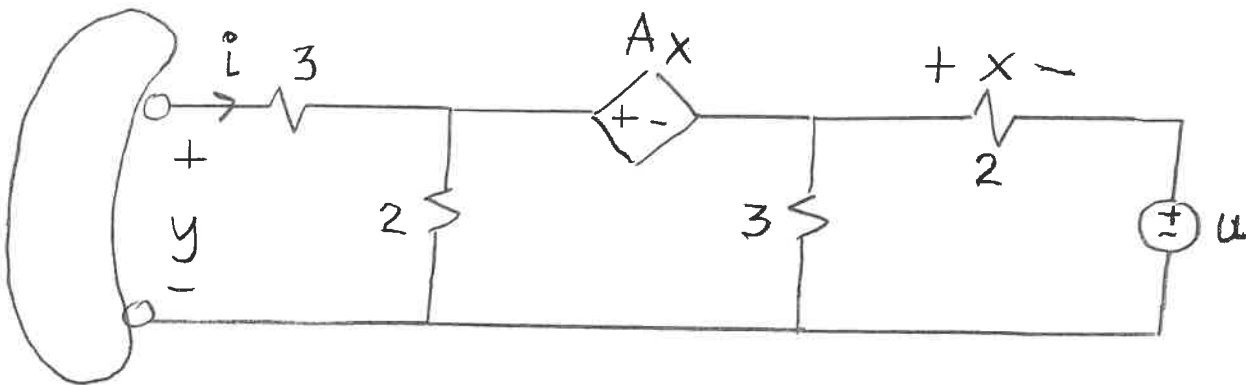

Problem #6

Find a Thevenin Equivalent at y
(looking leftward)

(Thevenin
Equivalent
at y)

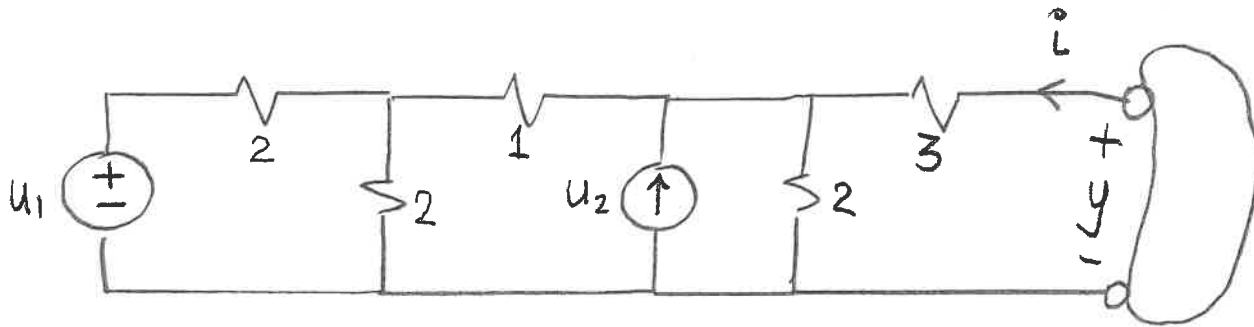

Exam Rules

Exam #2
Fall 2023
Fri 12-8-23

Dr. A.A. Rodriguez
EE202

- 1 One $8\frac{1}{2}'' \times 11''$ sheet permitted;
otherwise closed books, closed notes, closed phones
open minds!
- 2 calculator permitted (no computer!!; no phone!!!)
- 3 NO PHONES ! Phones should not be visible at all!
A visible phone will result in a zero grade
for the exam!
- 4 Write full name legibly on each page provided.
- 5 Please show all work. Write your solutions on the
pages provided. (No other pages/paper should be used!)
- 6 Clearly label voltage & currents on circuits provided.
- 7 Use variables provided! (No additional variables!)
- 8 Unreadable work will receive NO CREDIT.
- 9 Please place important equations & answers within box.
- 10 Please be careful with your algebra, signs, etc.
- 11 Please turn in solutions to me at end of period!
- 12 PLEASE DO NOT CHEAT!!! ☹️




Problem # 1

Determine H , diff eq , τ , t_s , y_{ss} , y

$$u = -3 + \cos 2t$$


(all $R=L=C=1$)

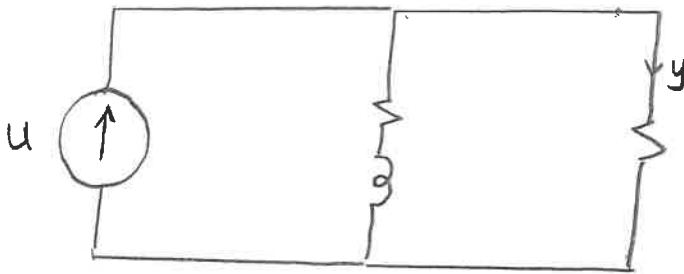

Problem #2

Determine $H_1(0)$, $H_2(0)$, $H_1(\infty)$, $H_2(\infty)$, τ , t_s

(all $R=L=C=1$)

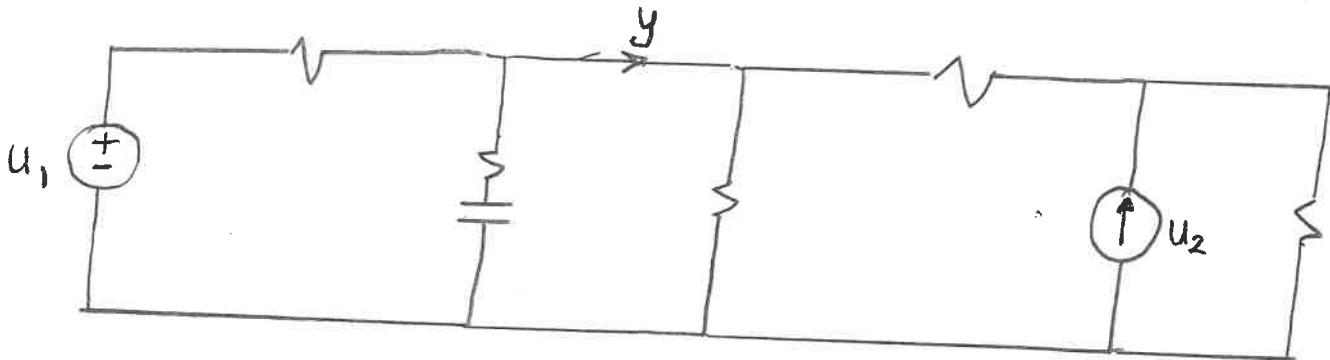


Problem # 3

Determine H , diff eq, T , t_s , y_{ss}



$$u = -5 + 10\sin(t + 30^\circ)$$

(all $R = L = C = 1$)

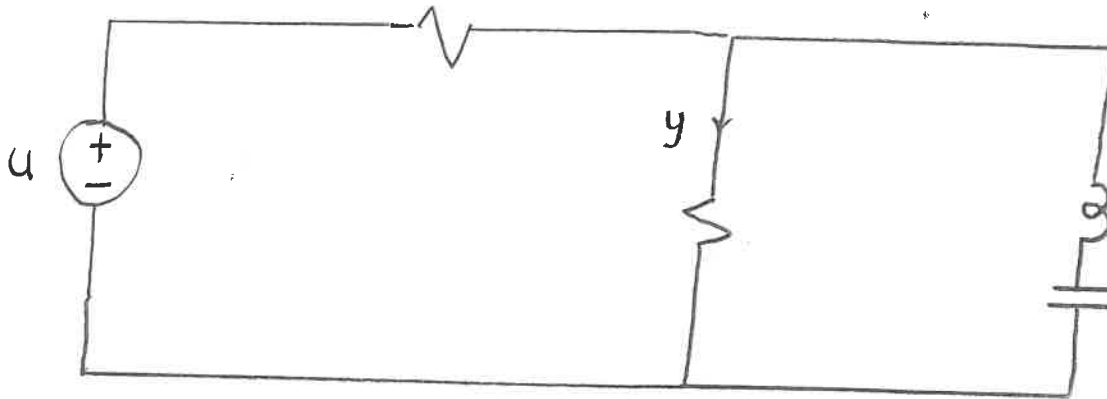

Problem # 4

Determine H , diff eq, y

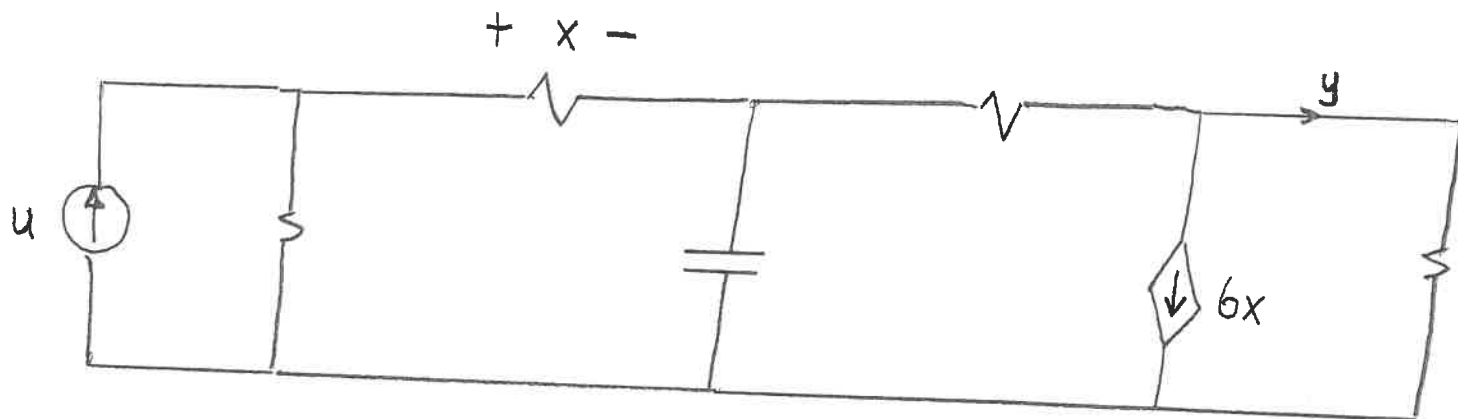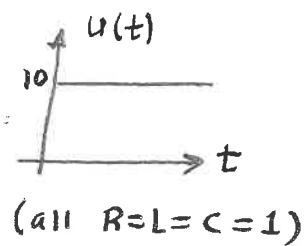

Problem #5

Determine y_{1ss} , y_1 , t_{s1} , y_{2ss} , y_2 , t_{s2}

$$H_1(s) = \frac{s}{(s+2)(s^2-6s+25)}$$

$$u_1(t) = -10 + 50 \cos(0.01t - 45^\circ) + 8 \sin(5t + 30^\circ)$$


$$H_2(s) = \frac{s^2 + 1}{(s+1)(s^2 + 10s + 100)}$$

$$u_2(t) = 7 - \cos(t + 20^\circ) + 6 \sin(100t + 135^\circ)$$

Problem #6

Determine an s-domain Thevenin Equivalent at y.

(all $R=L=C=1$)

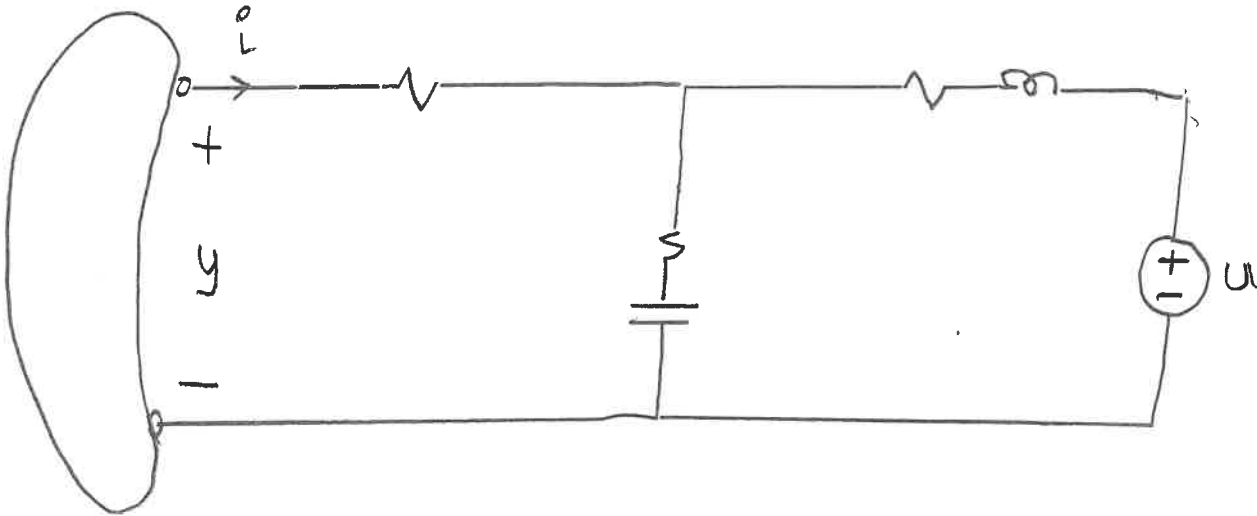


Problem # 7

Determine H & y_{ss}

$$u = -5 + 2\sin(t + 30^\circ)$$


$$-3\cos(100t - 135^\circ)$$

$$(all \ R=L=C=1)$$

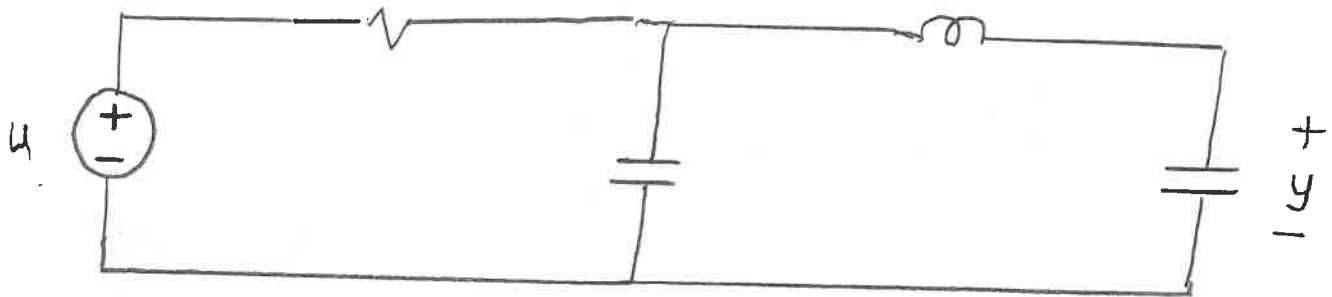

Problem # 8

Determine $H_1, H_2, t_{s1}, y_{1ss}$

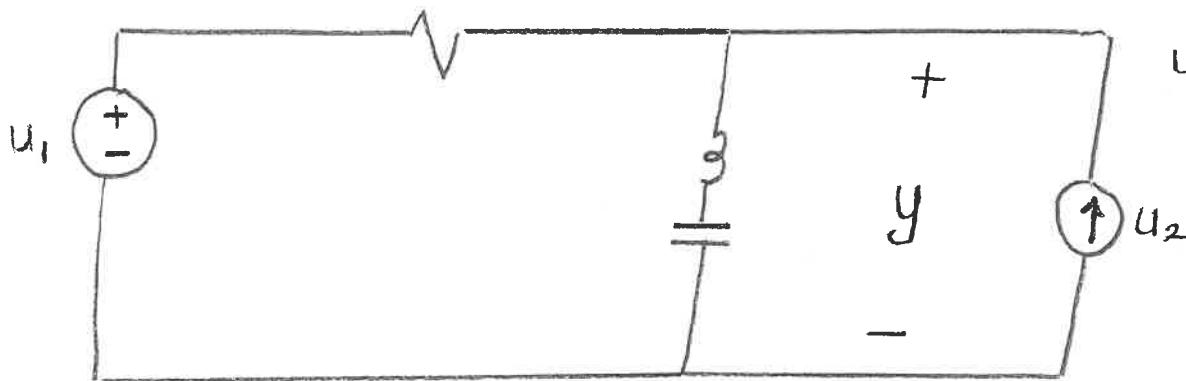

$$u_1 = 10$$

$$- 8 \sin(t + 30^\circ)$$

$$+ 7 \cos(100t + 45^\circ)$$

$$u_2 = 0$$

$$(all R=L=C=1)$$

Exam Rules

Final Exam

Fall 2023

Fri 12-15-23

Dr. A.A. Rodriguez
EE202

- 1 One $8\frac{1}{2}" \times 11"$ sheet permitted;
otherwise closed books, closed notes, closed phone:
open minds!
- 2 calculator permitted (no computer!!; no phone!!!)
- 3 NO PHONES ! Phones should not be visible at all!
A visible phone will result in a zero grad
for the exam!
- 4 Write full name legibly on each page provided.
- 5 Please show all work. Write your solutions on the
pages provided. (No other pages/paper should be used!)
- 6 Clearly label voltage & currents on circuits provided.
- 7 Use variables provided! (No additional variables!)
- 8 Unreadable work will receive NO CREDIT.
- 9 Please place important equations & answers within box
- 10 Please be careful with your algebra, signs, etc.
- 11 Please turn in solutions to me at end of period!
- 12 PLEASE DO NOT CHEAT!!! 😐




Problem #1

Determine H , diff eq, t_s , y_{ss} , y

(all $R=L=C=1$)


$$u = -6 - 2\cos(t - 45^\circ)$$

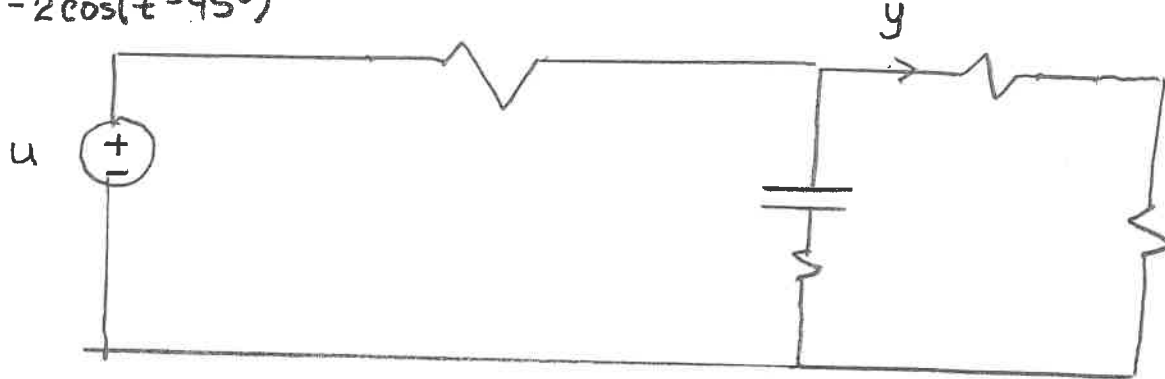

Problem # 2

Determine $H_1(0)$, $H_2(0)$, $H_1(\infty)$, $H_2(\infty)$, poles, t_s


(all $R=L=C=1$)

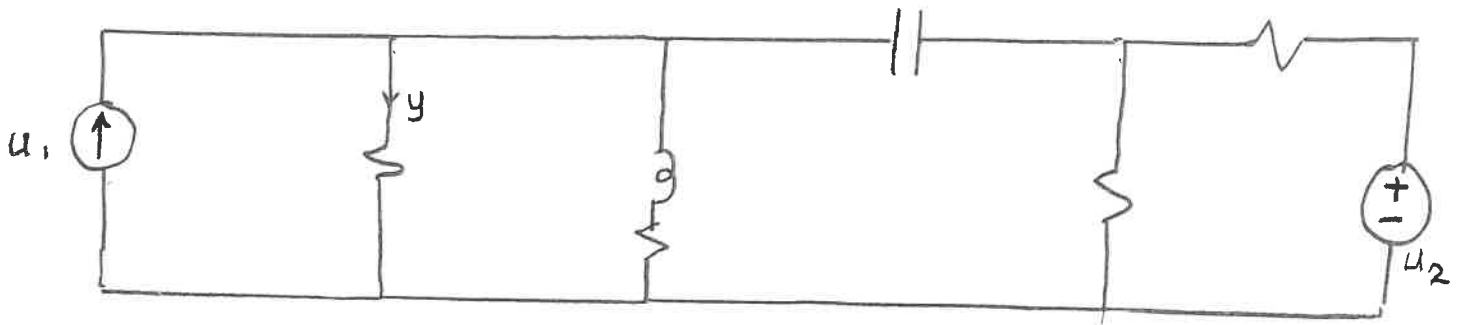

Problem # 3

Determine H , diff eq, t_s , y_{ss}



(all $R=L=C=1$)

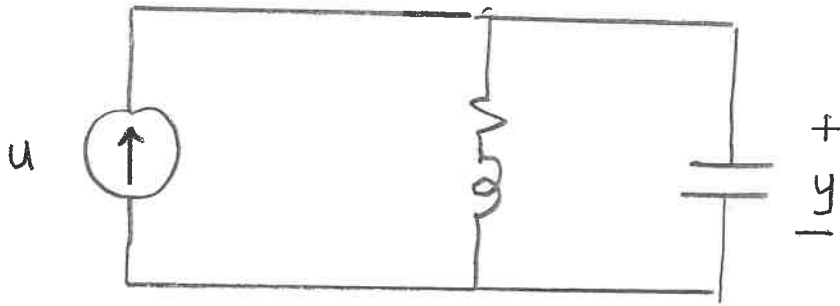

$$u = 4 - 3 \sin(t + 135^\circ)$$

Problem # 4

Determine H , diff eq, y

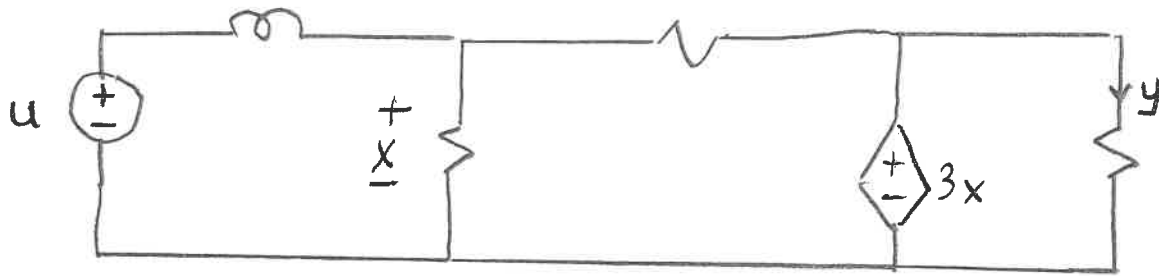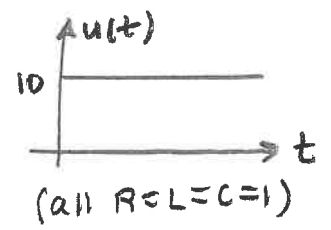

Problem # 5

Determine y_{ss} , y , t_s


$$H(s) = \frac{s(s^2 + 4)}{(s+2)(s^2 + 2s + 10)(s^2 - s + 1)}$$

$$u(t) = 5 - 6 \sin(2t + 45^\circ) + 7 \cos(100t + 270^\circ)$$

(compute all important coefficients as discussed in class)

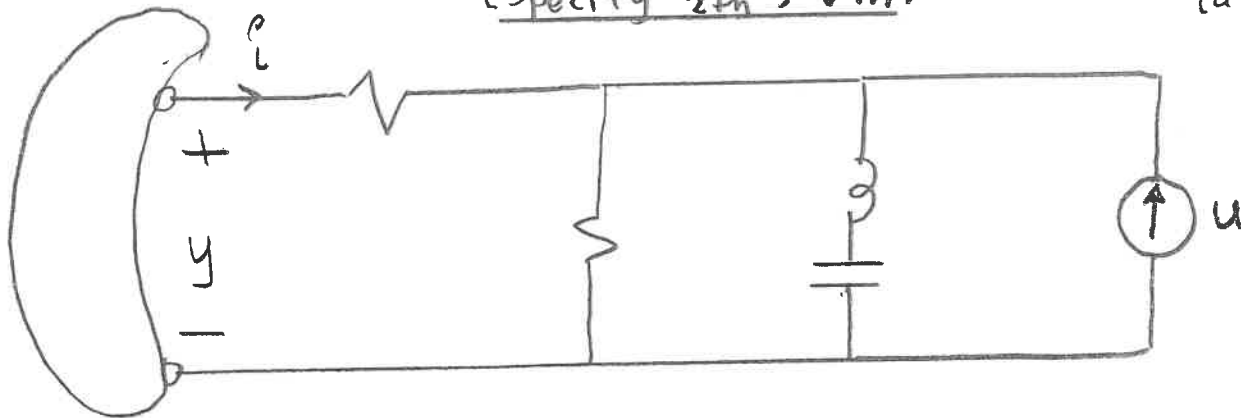Problem # 6

Determine an s-domain Thevenin Equivalent at y
(Specify Z_{th} & V_{th})
(all $R=L=C=1$)




Problem # 7

Determine $H \approx y_{ss}$

[compute all coefficients in y_{ss} (approximately)]

(all $R=L=C=1$)

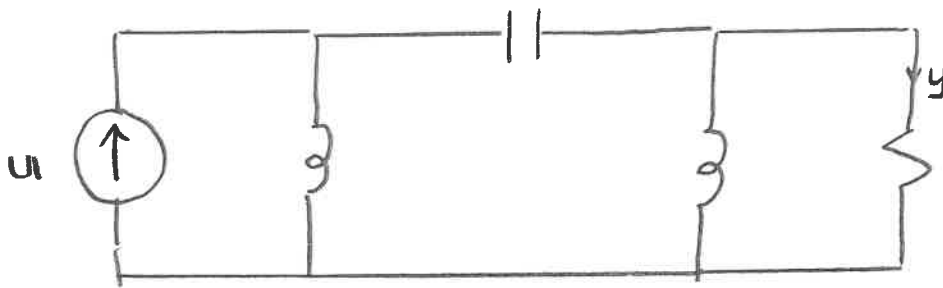


$$u = -7 + 8 \cos(0.01t - 180^\circ) - 9 \sin(100t + 20^\circ)$$

Problem #8

Determine H , t_s , y_{ss}

$$u = -8 + 9 \sin(t - 45^\circ)$$

(all $R=L=C=1$)

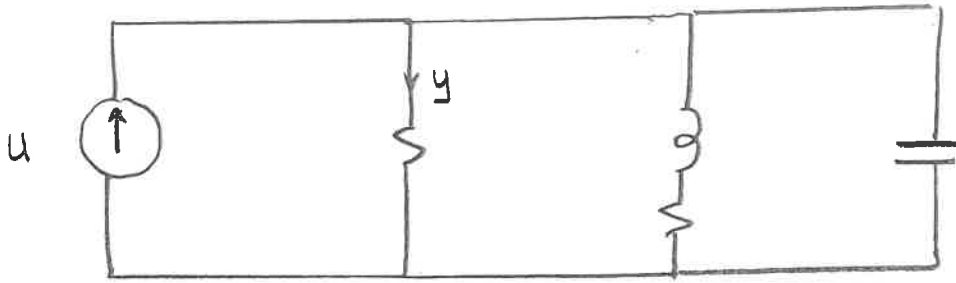

Final Fall 2023

9/9

Exam #1 Rules

(EE202)

wed 10-25-23

Exam 1


Fall 2023 Solutions

- 1) 1 8 1/2" x 11" sheet permitted - otherwise closed books, closed notes, open minds
- 2) calculator permitted (not really needed)
- 3) No phones - phones should not be visible at all! visible phones will result in a zero for the exam!!!
- 4) Write full name clearly on each page
- 5) Please show all work! Write your solutions clearly on the pages provided by me. clearly label voltages & currents on circuits provided.
- 6) Unreadable work will receive no credit.
- 7) place important equations & answers in a box
- 8) must turn in your solutions to me at the end of the period
- 9) PLEASE DO NOT CHEAT! 😊

AAR Solutions
Exam #1 Fall 2023

Dr. A.A. Rodriguez, EE202, all rights reserved

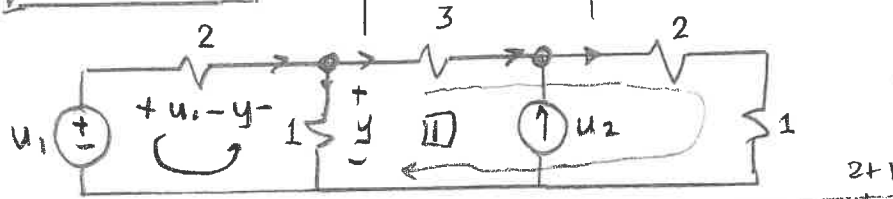Problem 1 $\left[\frac{u_1 - y}{2}\right] - y$ $\left[\frac{u_1 - y}{2}\right] - y + u_2$ (Propagate y)



Relate y to u_1, u_2


$$\text{① KVL} = \left\{ y = 3 \left[\frac{u_1 - y}{2} \right] - 3y + 3 \left\{ \left[\frac{u_1 - y}{2} \right] - y + u_2 \right\} \right.$$

$$y \left[\frac{1}{2} + \frac{3}{2} + \frac{3}{2} + \frac{3}{2} + \frac{3}{2} \right] = u_1 \left[\frac{3}{2} + \frac{3}{2} \right] + 3u_2$$

$$y \left[\frac{20}{2} \right] = \left(\frac{6}{2} \right) u_1 + \left(\frac{6}{2} \right) u_2 \Rightarrow y = \left(\frac{3}{10} \right) u_1 + \left(\frac{3}{10} \right) u_2$$


$$\frac{u_1}{2} - \frac{3}{2}y = \left(\frac{10}{20} \right) u_1 - \frac{9}{20} u_1 - \frac{9}{20} u_2 = \left(\frac{1}{20} \right) u_1 - \left(\frac{9}{20} \right) u_2$$

check:

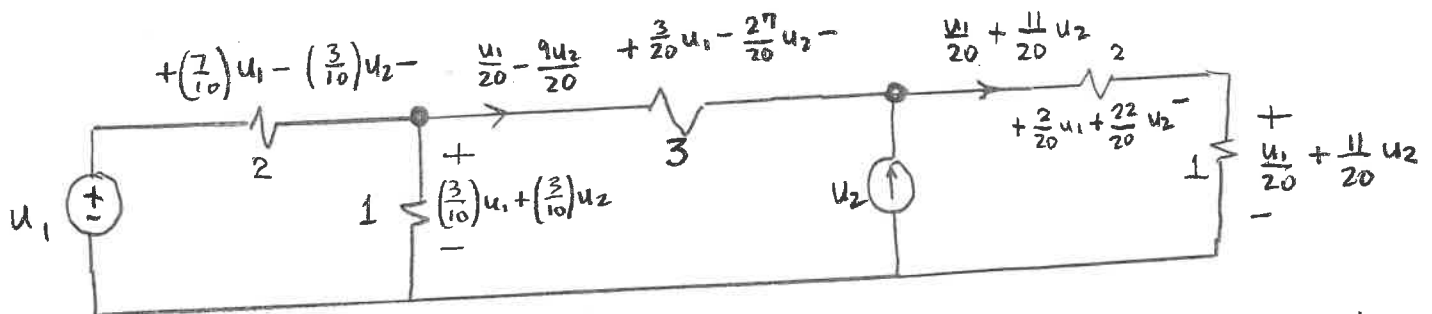

KVL & KCL check out everywhere!

Alternate:

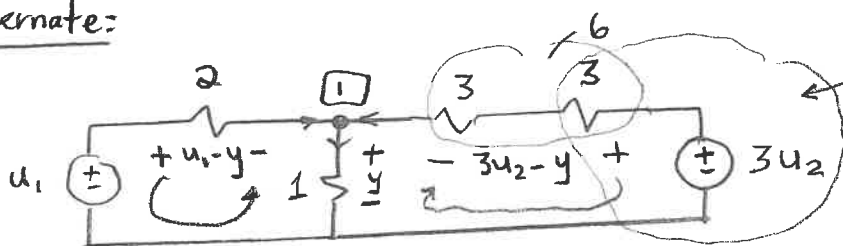


i to v
Source Transformation

$$\text{① KCL} = \left[\frac{u_1 - y}{2} \right] + \left[\frac{3u_2 - y}{6} \right] = \left[\frac{y}{1} \right]$$



$$6x \quad 3u_1 - 3y + 3u_2 - y = 6y$$

$$10y = 3u_1 + 3u_2$$
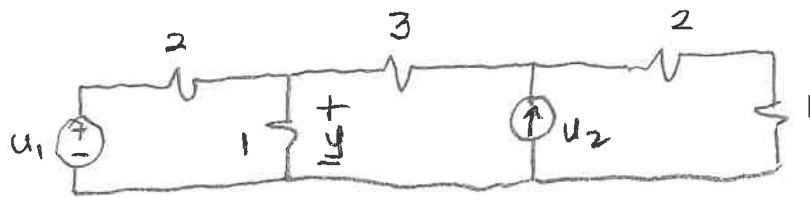
$$\Rightarrow y = \left(\frac{3}{10} \right) u_1 + \left(\frac{3}{10} \right) u_2 \quad \checkmark \quad \text{😊}$$



Sol via source trans f

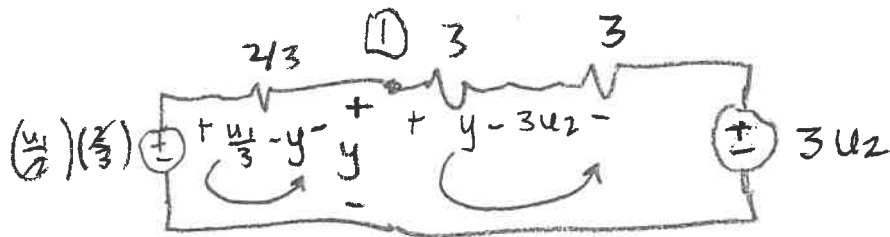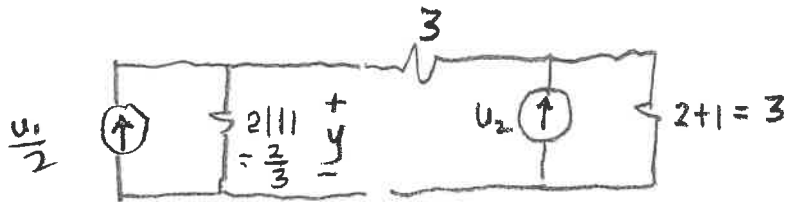

$$\textcircled{1} \text{ KCL} = \left(\frac{\frac{u_1}{3} - y}{\left(\frac{2}{3}\right)} \right) = \left(\frac{y - 3u_2}{\cancel{3+3}_6} \right)$$

$$\frac{u_1}{2} - \frac{3}{2}y = \frac{y}{6} - \frac{1}{2}u_2$$

$$3u_1 - 9y = y - 3u_2$$


$$10y = 3u_1 + 3u_2$$


$$\boxed{y = \left(\frac{3}{10}\right)u_1 + \left(\frac{3}{10}\right)u_2} \quad \checkmark$$


Problem # 2


Relate $w_{1,2,3}$ to $u_{1,2,3}$

(Nodal Analysis)

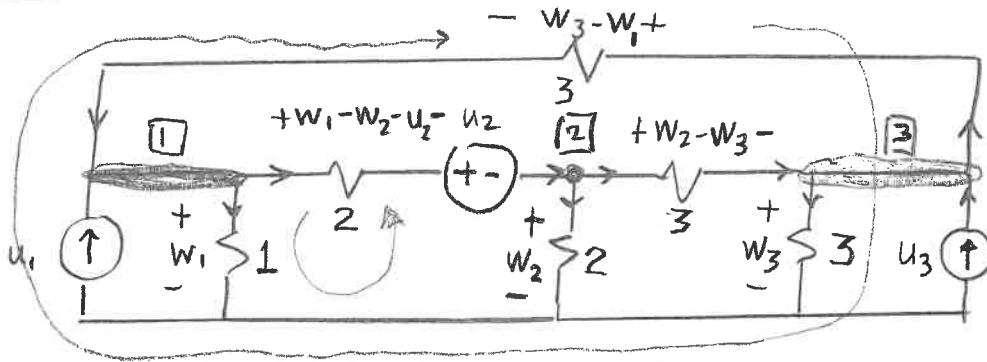

[1] KCL = 
$$\left(\frac{w_3 - w_1}{3} \right) + u_1 = \left(\frac{w_1}{1} \right) + \left(\frac{w_1 - w_2 - u_2}{2} \right)$$

[2] KCL = 
$$\left(\frac{w_1 - w_2 - u_2}{2} \right) = \left(\frac{w_2}{2} \right) + \left(\frac{w_2 - w_3}{3} \right)$$

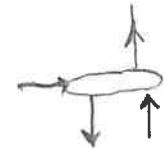[3] KCL = 
$$\left(\frac{w_2 - w_3}{3} \right) + (u_3) = \left(\frac{w_3}{3} \right) + \left(\frac{w_3 - w_1}{3} \right)$$

Matrix-Vector Form:

$$\begin{bmatrix} 1 + \frac{1}{2} + \frac{1}{3} & -\frac{1}{2} & \frac{1}{3} \\ \frac{1}{2} & -\frac{1}{2} - \frac{1}{2} - \frac{1}{3} & \frac{1}{3} \\ -\frac{1}{3} & -\frac{1}{3} & 1 \end{bmatrix} \begin{bmatrix} w_1 \\ w_2 \\ w_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix} u_1 + \begin{bmatrix} \frac{1}{2} \\ \frac{1}{2} \\ 0 \end{bmatrix} u_2 + \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix} u_3$$

\uparrow \uparrow \uparrow
 A x b_1 b_2 b_3


If x_i solves $Ax_i = b_i$ then by linearity:

$$X = \begin{bmatrix} 1 \\ x_1 \\ 1 \end{bmatrix} u_1 + \begin{bmatrix} 1 \\ x_2 \\ 1 \end{bmatrix} u_2 + \begin{bmatrix} 1 \\ x_3 \\ 1 \end{bmatrix} u_3$$

Problem # 3

Relate I_1, I_2, I_3, I_4 to u_1, u_2, u_3

(Mesh Analysis)

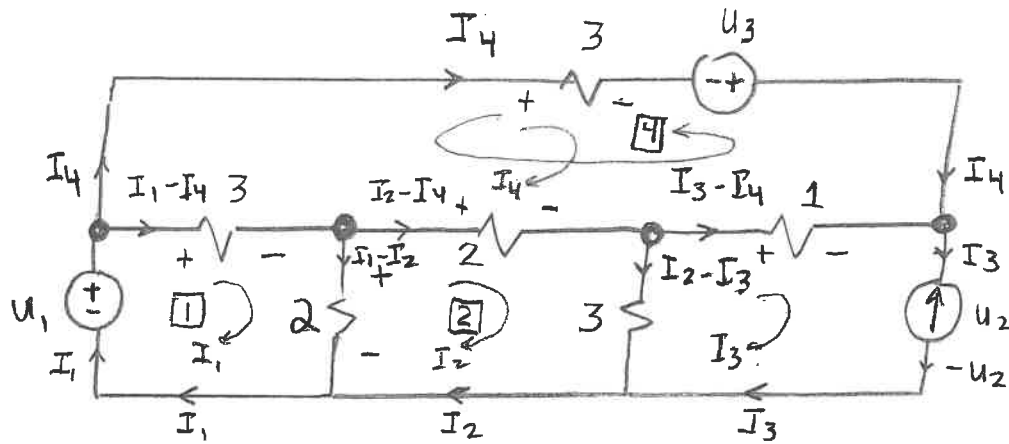

$$\boxed{1} \text{ KVL: } u_1 = 3(I_1 - I_4) + 2(I_1 - I_2)$$

$$\boxed{2} \text{ KVL: } 2(I_1 - I_2) = 2(I_2 - I_4) + 3(I_2 - I_3)$$



$$\boxed{3} \text{ KCL: } I_3 = -u_2$$

$$\boxed{4} \text{ KVL: } 3(I_4) - u_3 = 3(I_1 - I_4) + 2(I_2 - I_4) + 1(I_3 - I_4)$$

Problem #4


Find a Thevenin Equivalent at y
(looking leftward)

(Thevenin Equivalent at y)

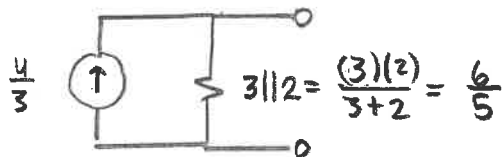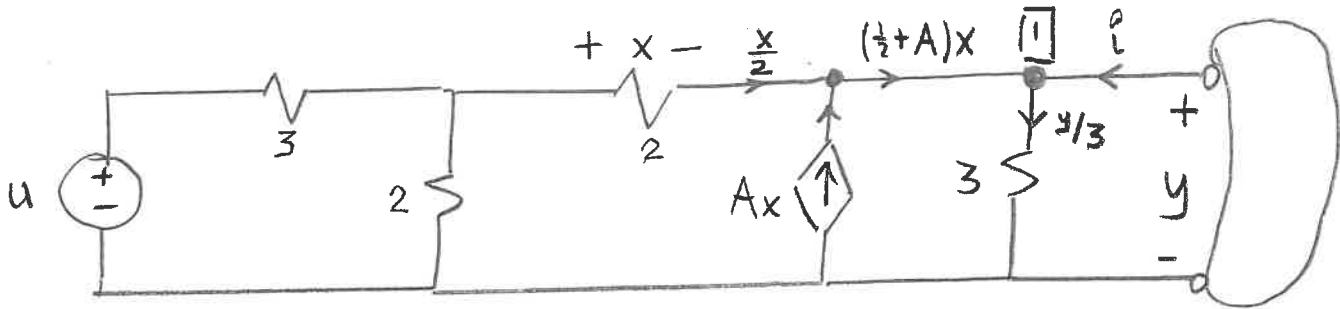

[1] KCL =
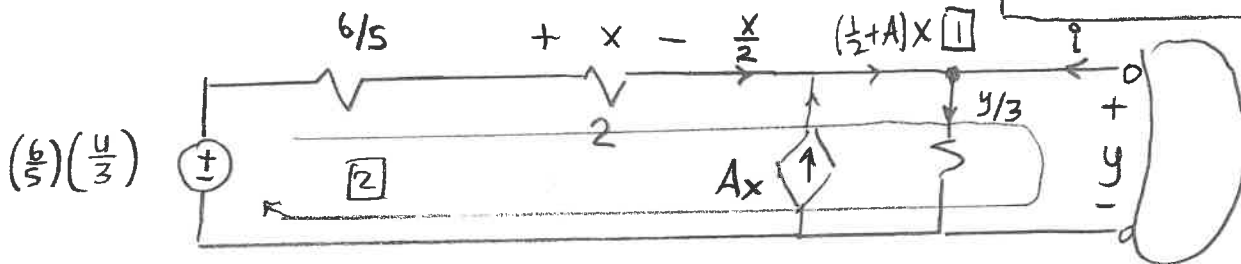
$$\left(\frac{1}{2} + A\right)x + i = \left(\frac{y}{3}\right)$$



[2] KVL = $\left(\frac{6}{5}\right)\left(\frac{u}{3}\right) = \left[\frac{6}{5} + 2\right]\left[\frac{x}{2}\right] + y$

$\left(\frac{2}{5}\right)u$ $\frac{10}{5}$

$$[1] \Rightarrow x = \left[\frac{y/3 - i}{A + \frac{1}{2}}\right] \quad [2] \Rightarrow \left(\frac{2}{5}\right)u = \left(\frac{8}{5}\right)\frac{1}{2} \left[\frac{y/3 - i}{A + \frac{1}{2}}\right] + y$$

$$y \left[\frac{8/5}{A + \frac{1}{2}} + 1 \right] = \left[\frac{8/5}{A + \frac{1}{2}} \right] i + \left(\frac{2}{5}\right)u$$

$$y \left[\frac{8}{15} + A + \frac{1}{2} \right] = \left[\frac{8}{5} \right] i + \left(\frac{2}{5}\right)(A + \frac{1}{2})u$$

$$y [0 + 15A + 7.5] = 24i + 6(A + \frac{1}{2})u$$

15.5

$$y = \left[\frac{24}{15A + 15.5} \right] i + 6 \left[\frac{A + \frac{1}{2}}{15A + 15.5} \right] u$$


R_{th} V_{th}

Problem #5

Find a Thevenin Equivalent at y


(looking rightward)

(Thevenin Equivalent at y)

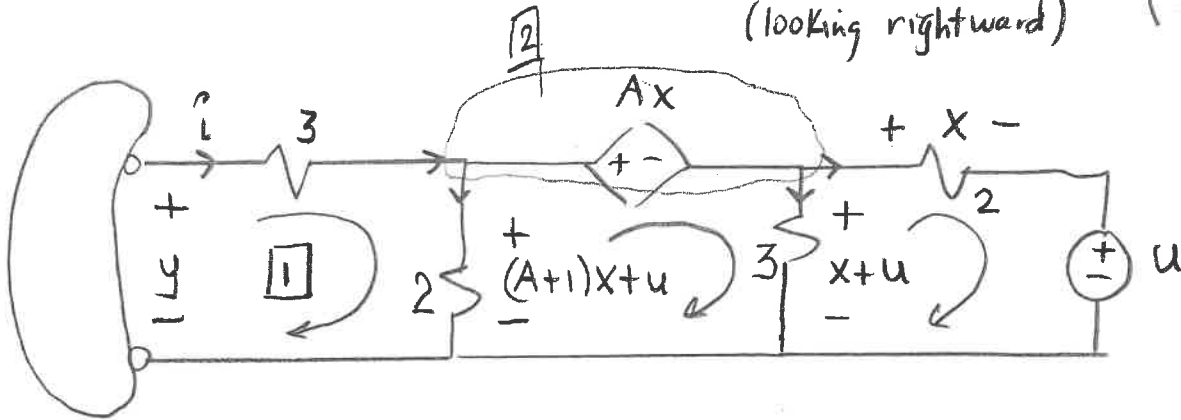

[1] KVL = $y = 3i + (A+1)x + u$

[2] KCL =

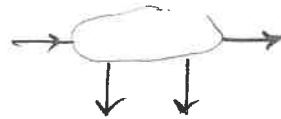

$$i = \left[\frac{(A+1)x + u}{2} \right] + \left[\frac{x+u}{3} \right] + \left[\frac{x}{2} \right]$$

6x

$$6i = 3(A+1)x + 3u + 2x + 2u + 3x$$

$$= x[3A + 8] + u[3 + 2]$$

$$\Rightarrow x = \frac{6i - 5u}{3A + 8}$$

$$\Rightarrow y = 3i + (A+1) \left[\frac{6i - 5u}{3A + 8} \right] + u$$



$$\Rightarrow (3A + 8)y = i[3(3A + 8) + (A+1)6] + u[(3A + 8) - 5(A+1)]$$

$$= i[9A + 24 + 6A + 6] + u[3A + 8 - 5A - 5]$$

$$y = \left[15 \left(\frac{A+2}{3A+8} \right) \right] i + \left(\frac{3-2A}{3A+8} \right) u$$

V_{th}

solution via source transf

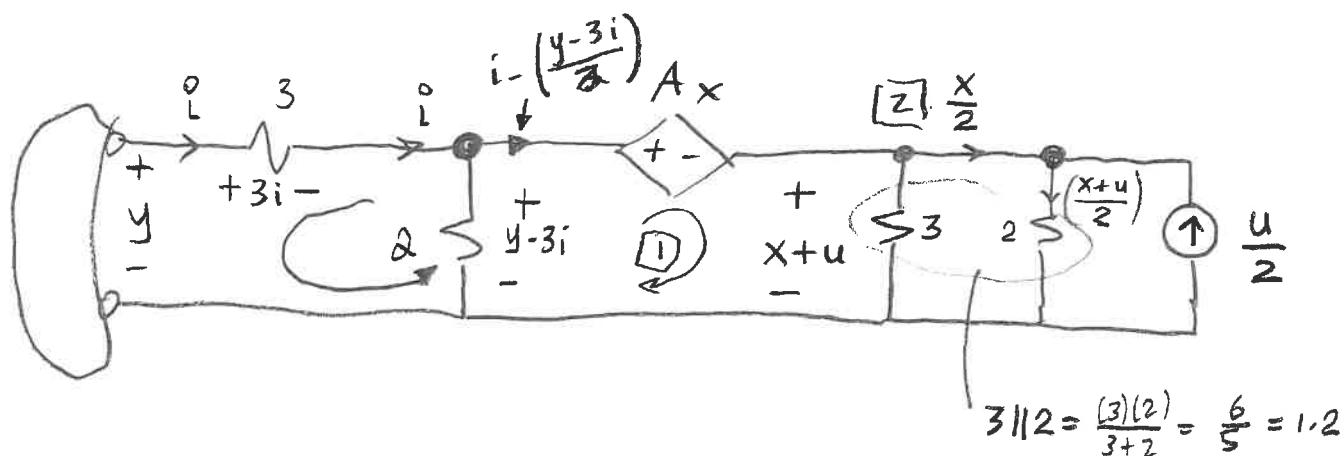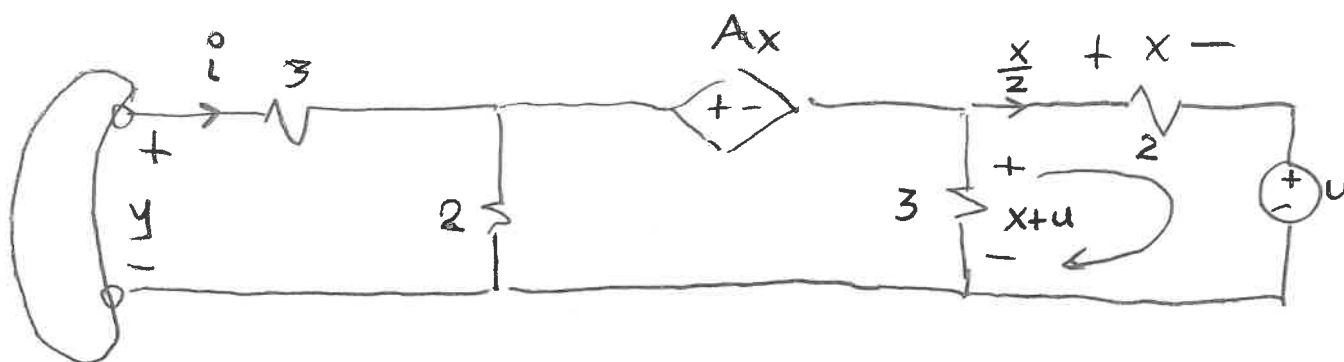

$$\textcircled{1} \text{ KVL} = (y - 3i) = (Ax) + (x + u)$$

or $y = 3i + (A+1)x + u$ as on reverse side



Also, KCL at $\textcircled{2}$ yields

$$i - \left(\frac{y-3i}{2}\right) = \left(\frac{x+u}{3}\right) + \left(\frac{x}{2}\right)$$


(same as on reverse side!)

Problem #5

(sol via Source transf)

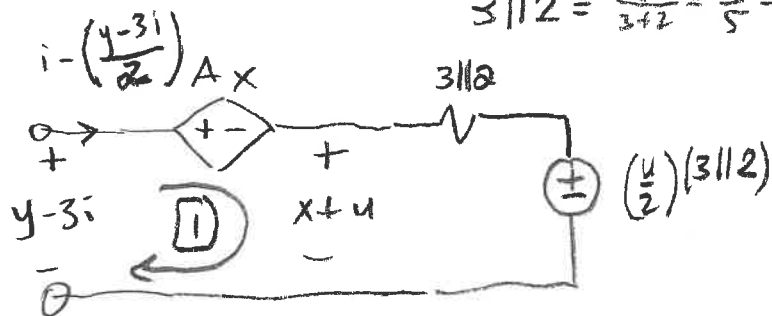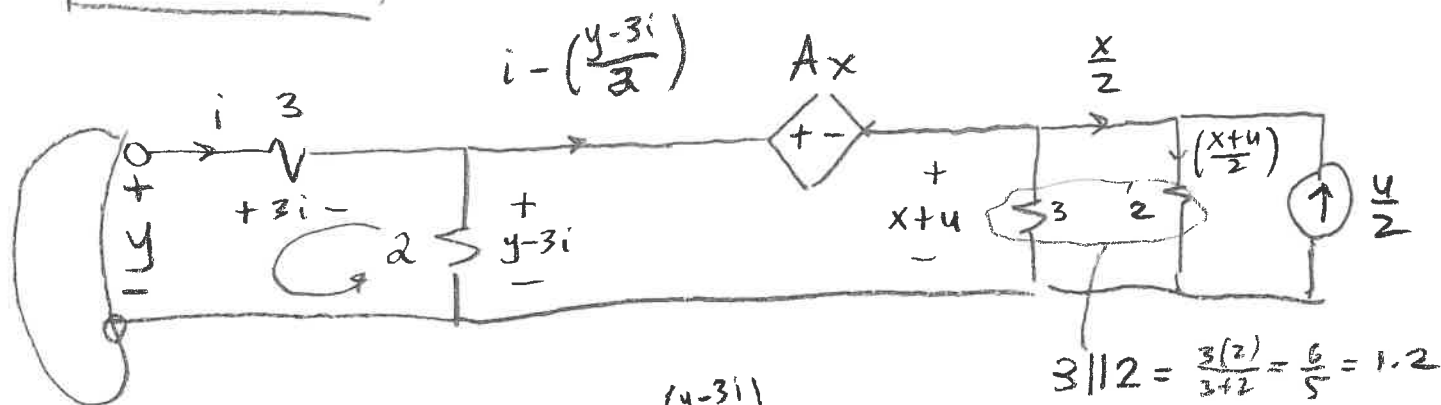

[1] KVL = $y - 3i = (A+1)x + u$

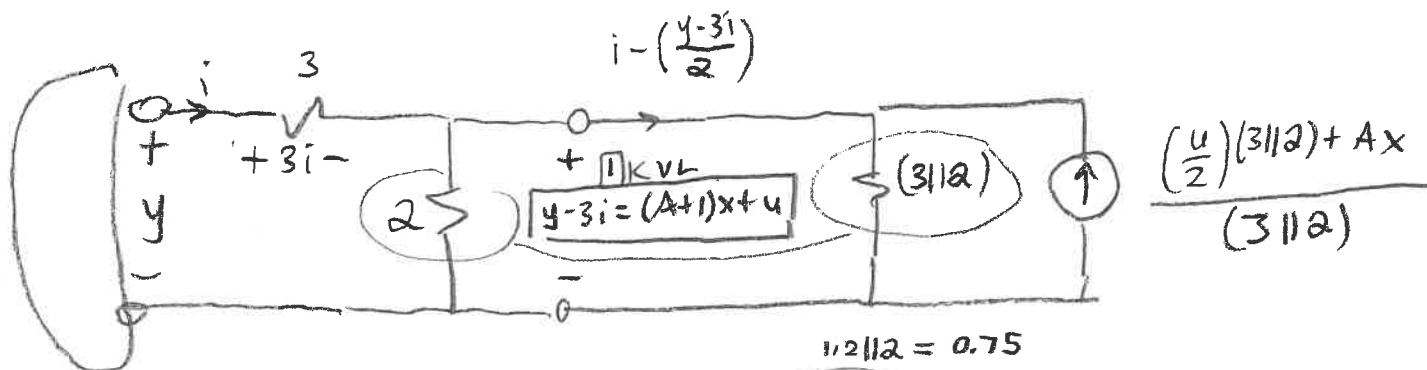


[2] KVL = $y = (3 + (3 \parallel 2) \parallel 2) i + \left[\frac{(\frac{u}{2})(3 \parallel 2) + Ax}{(3 \parallel 2)} \right] [(3 \parallel 2) \parallel 2]$

- We have 2 eq in 2 unknowns y, x !!!

Problem #6

Find a Thevenin Equivalent at y
(looking leftward)


(Thevenin Equivalent at y)

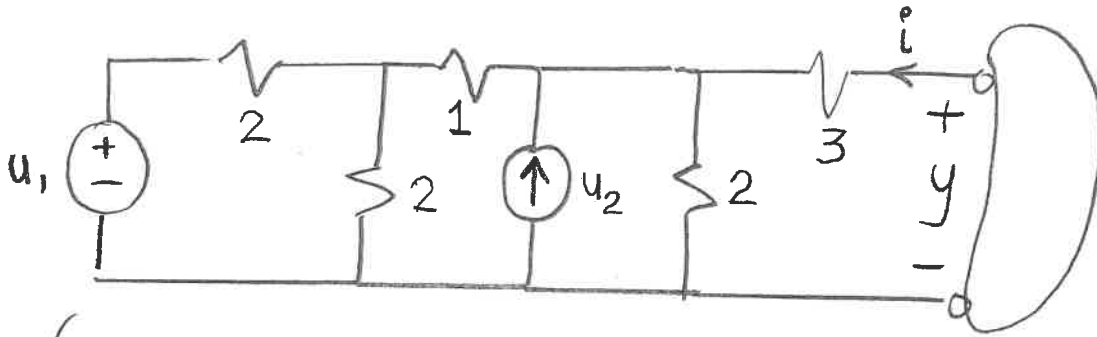

Source Transf

Note: $R_{eq} = 3 + \left[2 \parallel [1 + (2 \parallel 2)] \right] = 3 + 2 \parallel (1 + 1) = 3 + (2 \parallel 2) = 3 + 1$


Source Transf

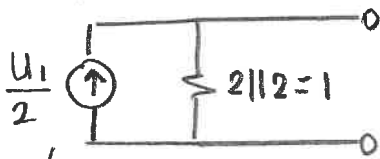


$R_{eq} = 4$

(best way to find R_{th} !!!)


Source Transf

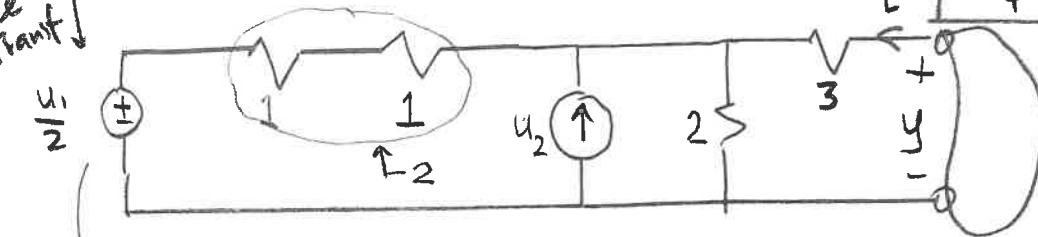


$\left(\frac{u_1}{2} \right)$

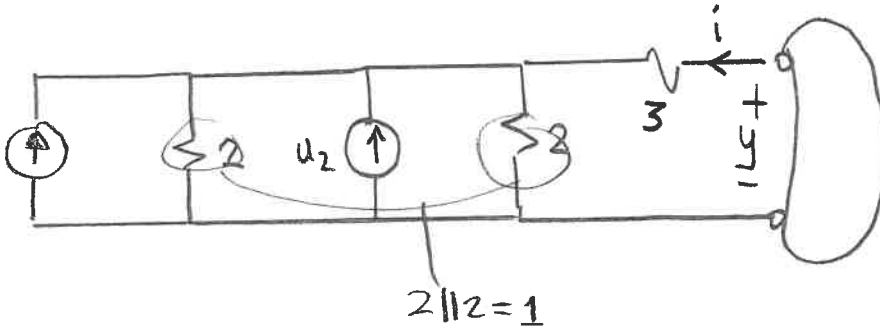

Source Transf

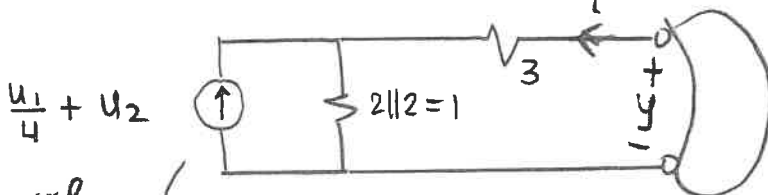






$\frac{u_1}{4} + u_2$

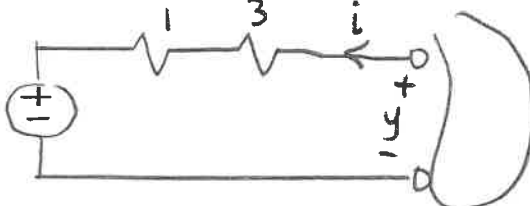

$R_{th} = 4$

$V_{th} = \frac{u_1}{4} + u_2$

Check on $V_{th} = y|i=0$ (Source transf)

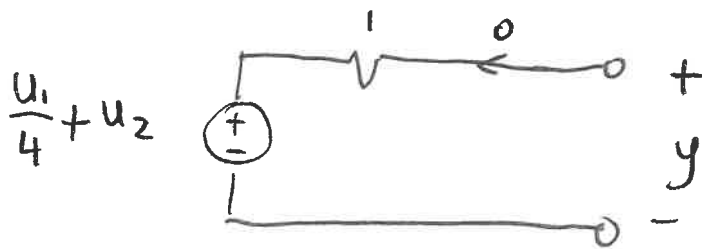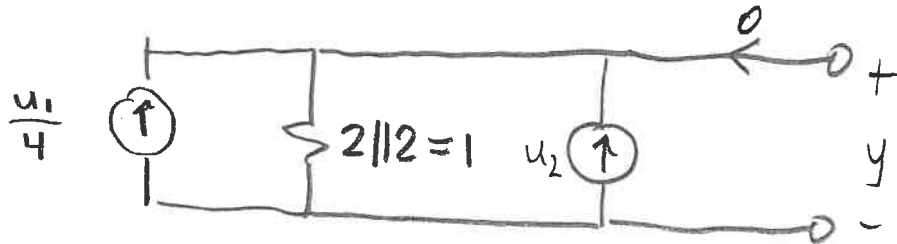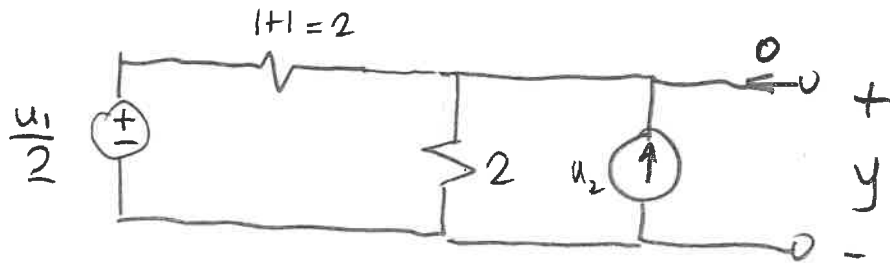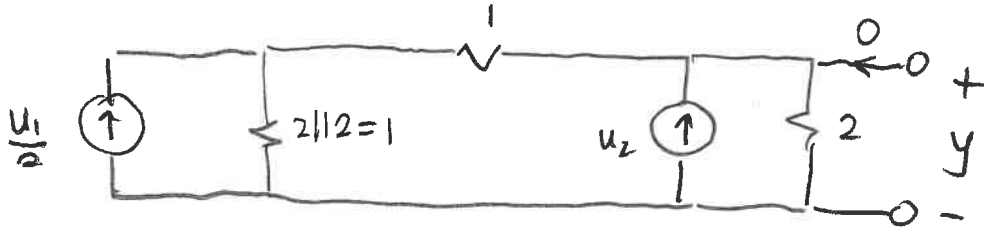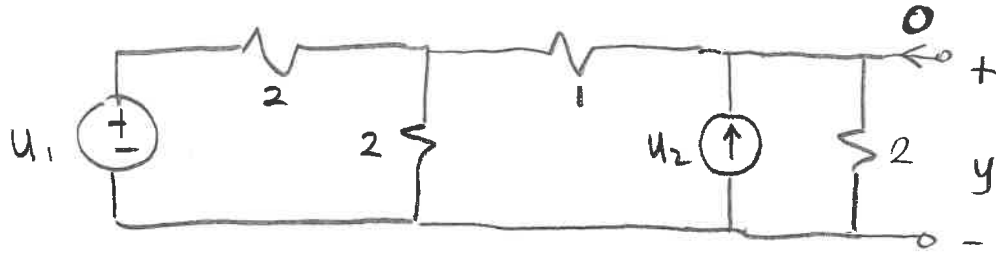


$$y|i=0 = V_{th} = \frac{u_1}{4} + u_2 \quad \checkmark$$

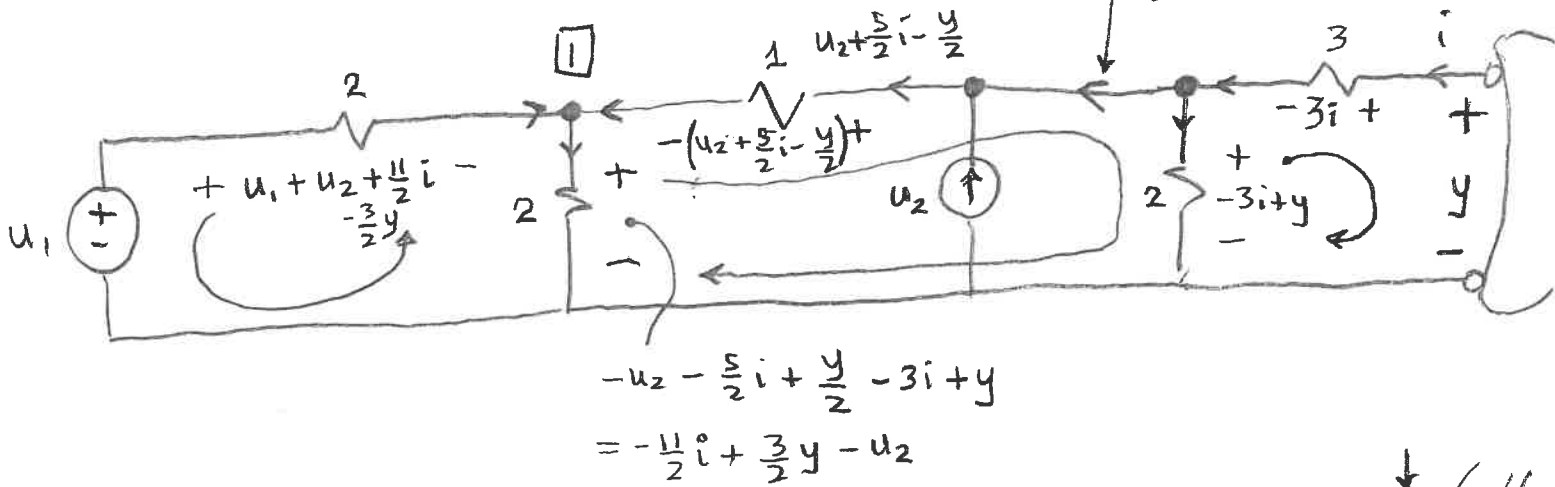Problem 6

(Thev equiv =
sol via KVL, KCL, etc.)

$$i_1 - \left(\frac{-3i + y}{2} \right) = \frac{5}{2}i - \frac{y}{2}$$



$$\boxed{1} \text{ KCL} = \left(\frac{u_1 + u_2 + \frac{11}{2}i - \frac{3}{2}y}{2} \right) + \left(\frac{u_2 + \frac{5}{2}i - \frac{y}{2}}{1} \right) = \left(\frac{-\frac{11}{2}i + \frac{3}{2}y - u_2}{2} \right)$$

Algebra:

$$y \left[\frac{3}{4} + \frac{1}{2} + \frac{3}{4} \right] = i \left[\frac{11}{4} + \frac{5}{2} + \frac{11}{4} \right] + u_1 \left[\frac{1}{2} \right] + u_2 \left[\frac{1}{2} + 1 + \frac{1}{2} \right]$$

$$y \left[\frac{8}{4} \right] = i \left[\frac{32}{4} \right] + \left[\frac{1}{2} u_1 + 2 u_2 \right]$$

$$y = (4)i + \left[\frac{1}{4} u_1 + u_2 \right]$$

$\boxed{R_{th} = 4}$
 $\boxed{V_{th} = \frac{1}{4} u_1 + u_2}$

Exam Rules

Fri 12-8-23

Fall 2023

AAR Exam #2
solutions


- 1 One $8\frac{1}{2}$ " x 11" sheet permitted;
otherwise closed books, closed notes, closed phone
open minds?
- 2 calculator permitted (no computer!!; no phone!!!)
- 3 NO PHONES ! Phones should not be visible at all!
A visible phone will result in a zero grade
for the exam!
- 4 Write full name legibly on each page provided.
- 5 Please show all work. Write your solutions on the
pages provided. (No other pages/paper should be used!)
- 6 Clearly label voltage & currents on circuits provided.
- 7 Use variables provided! (No additional variables!)
- 8 Unreadable work will receive NO CREDIT.
- 9 Please place important equations & answers within box
- 10 Please be careful with your algebra, signs, etc.
- 11 Please turn in solutions to me at end of period!
- 12 PLEASE DO NOT CHEAT!!! 😊

Problem # 1

Determine H , diff eq, τ , t_s , y_{ss} , y

$$u = -3 + \cos 2t$$

(all $R=L=C=1$)

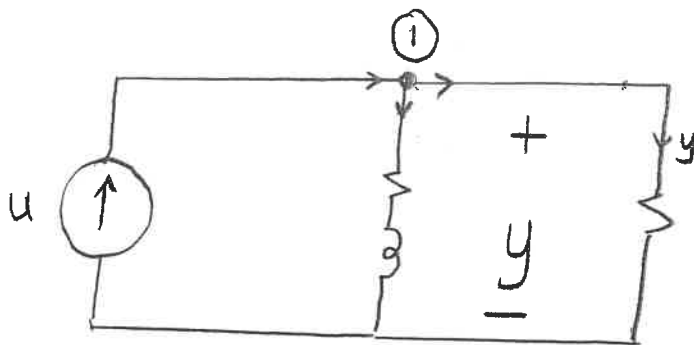

$$\textcircled{1} \text{ KCL} = \boxed{u = \frac{y}{s+1} + y} = y \left[\frac{1}{s+1} + 1 \right]$$

$$(s+1)u = y[1 + s+1] = y[s+2]$$

$$\boxed{H = \frac{y}{u} = \frac{s+1}{s+2}}$$

$$\boxed{\dot{y} + 2y = \dot{u} + u}$$

$$\text{pole} = -2 \Rightarrow \tau = \frac{1}{2}$$

(stable system)

$$t_s = 5\tau = \frac{5}{2}$$

$$\tau = \frac{1}{2}$$

$$t_s = \frac{5}{2}$$

MOTF

$$y_{ss} = -3H(0) + |H(j2)| \cos(2t + \angle H(j2))$$

$$H(0) = \frac{1}{2}$$

$$H(j2) = \frac{j2+1}{j2+2} = \frac{\sqrt{5} \angle 63.4^\circ}{\sqrt{5} \angle 45^\circ} = \frac{\sqrt{5}}{2} e^{j18.4^\circ}$$

$$= \frac{\sqrt{5}}{2\sqrt{2}} e^{j45^\circ}$$

$$= \left(\frac{\sqrt{5}}{2\sqrt{2}} \right) e^{j(\tan^{-1}(\frac{2}{1}) - 45^\circ)}$$

$$u = -\frac{3}{s} + \frac{s}{s^2+4} = \frac{s(s^2+4) - 3(s^2+4)}{s(s^2+4)}$$

$$Y = HU = \left[\frac{s+1}{s+2} \right] \left[\frac{s(s^2+4)}{s(s^2+4)} \right]$$

$$= \frac{A}{s} + \frac{B}{s+2} + \left[\frac{C}{s-j2} + \frac{C^*}{s+j2} \right]$$

$$y(t) = A + Be^{-2t} + 2|C| \cos(2t + \angle C)$$

$$y_{ss} = A + 2|C| \cos(2t + \angle C)$$

$$= -3H(0) + |H(j2)| \cos(2t + \angle H(j2))$$

$$\boxed{A = \lim_{s \rightarrow 0} sY = -3H(0)}$$



$$\boxed{C = \lim_{s \rightarrow j2} (s-j2)Y = \frac{|H(j2)|}{2} e^{j\angle H(j2)}}$$

$$B = \lim_{s \rightarrow -2} (s+2)Y$$

Problem #2

Determine $H_1(0)$, $H_2(0)$, $H_1(\infty)$, $H_2(\infty)$, τ .

(all $R=L=C=1$)

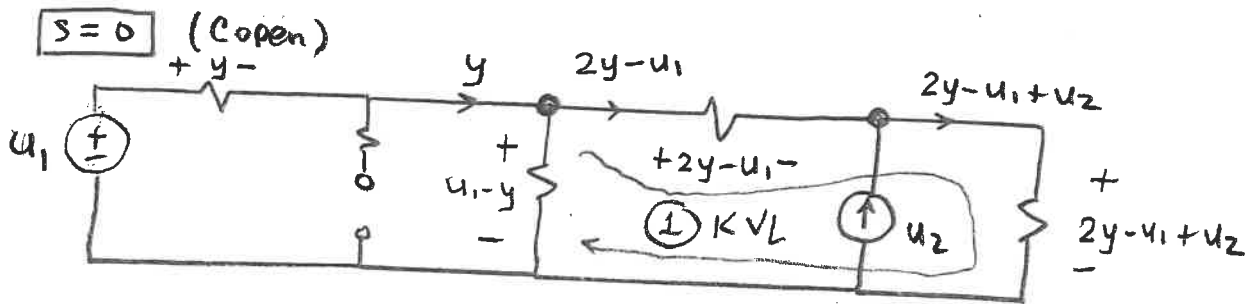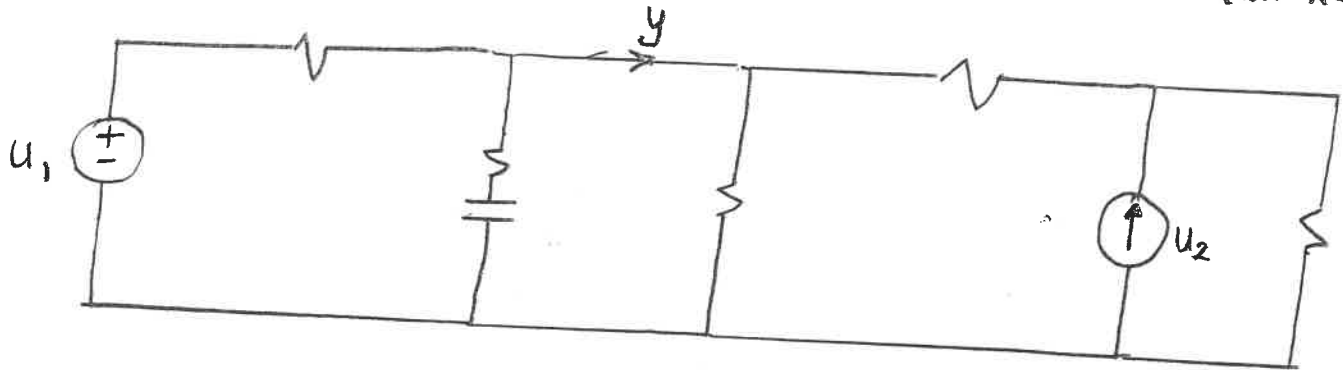


$$\textcircled{1} \text{ KVL} = u_1 - y = (2y - u_1) + (2y - u_1 + u_2)$$

$$3u_1 - u_2 = 5y$$

$$y = \left(\frac{3}{5}\right)u_1 + \left(-\frac{1}{5}\right)u_2$$


\uparrow $H_1(0)$ \uparrow $H_2(0)$

$s = \infty$

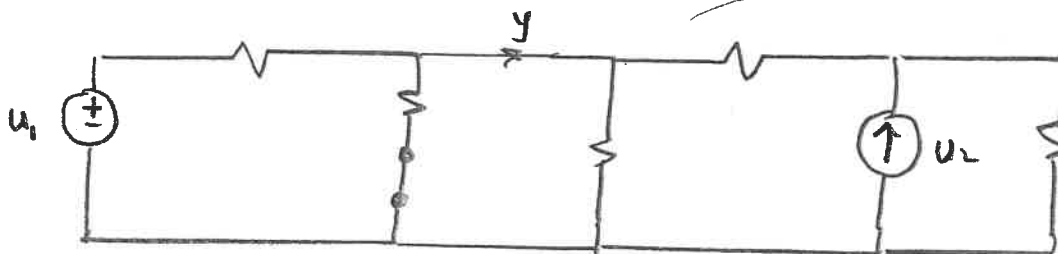

$$y = \left(\frac{3}{7}\right)u_1 + \left(-\frac{2}{7}\right)u_2$$

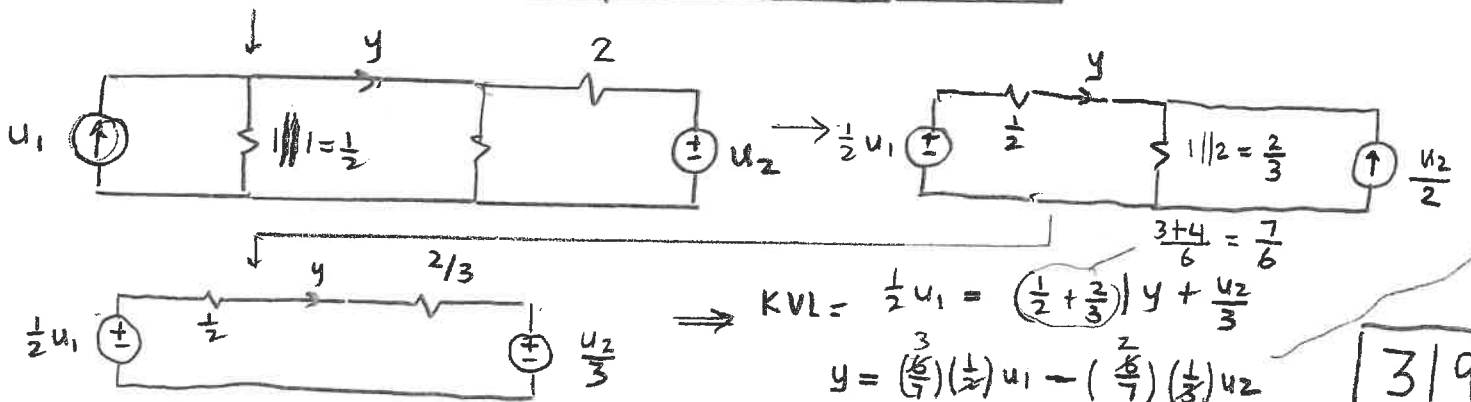\uparrow $H_1(\infty)$ \uparrow $H_2(\infty)$






$$\Rightarrow \text{KVL} = \frac{1}{2}u_1 = \left(\frac{1}{2} + \frac{2}{3}\right)y + \frac{u_2}{3}$$

$$y = \left(\frac{3}{7}\right)\left(\frac{1}{2}\right)u_1 - \left(\frac{2}{7}\right)\left(\frac{1}{3}\right)u_2$$

3/9

$$\tau, t_s = ?$$

$$\text{Set } u_1 = u_2 = 0$$

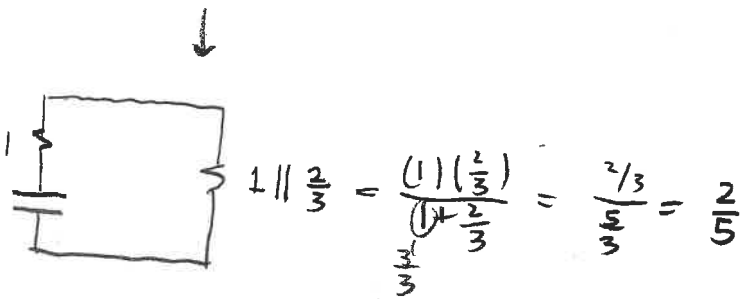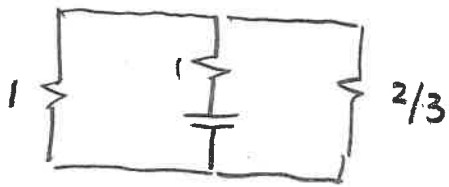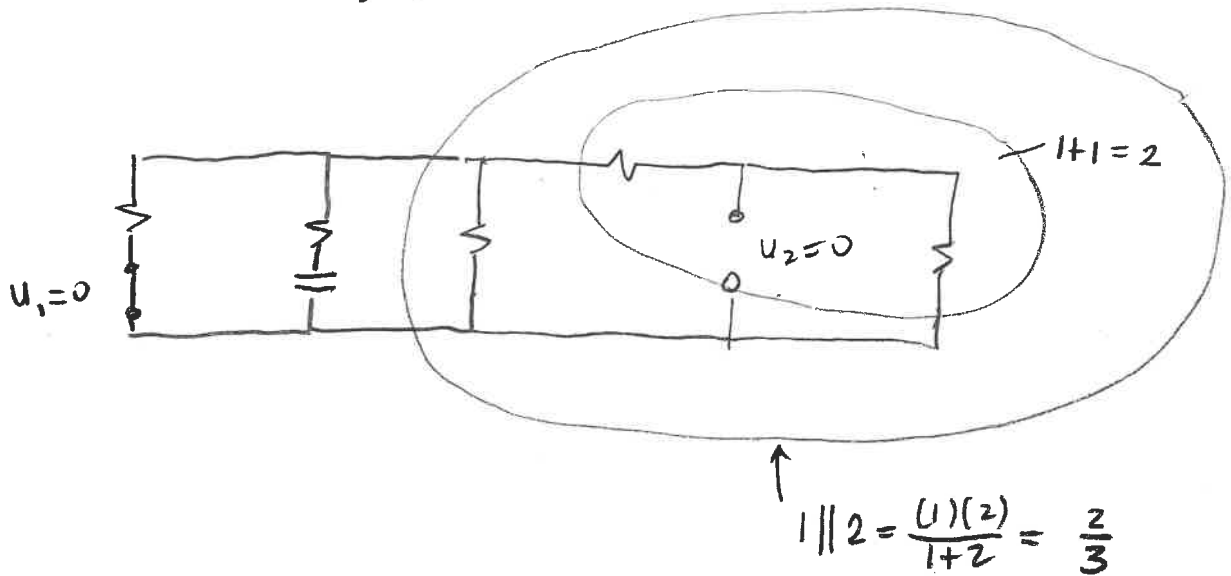

$$1 + \frac{2}{5} = \frac{7}{5}$$

$$\tau = R_{eq} C = \left(\frac{7}{5}\right)(1)$$

$$t_s = 5\tau = 7$$

$$\Rightarrow \begin{cases} \tau = 7/5 \\ t_s = 7 \end{cases}$$


Note: pole = $-\frac{1}{\tau} = -\frac{5}{7}$
 \Rightarrow stable system

Problem # 3

Determine H , diff eq, τ , t_s , y_{ss}

$$u = -5 + 10 \sin(t + 30^\circ)$$

(all $R=L=C=1$)

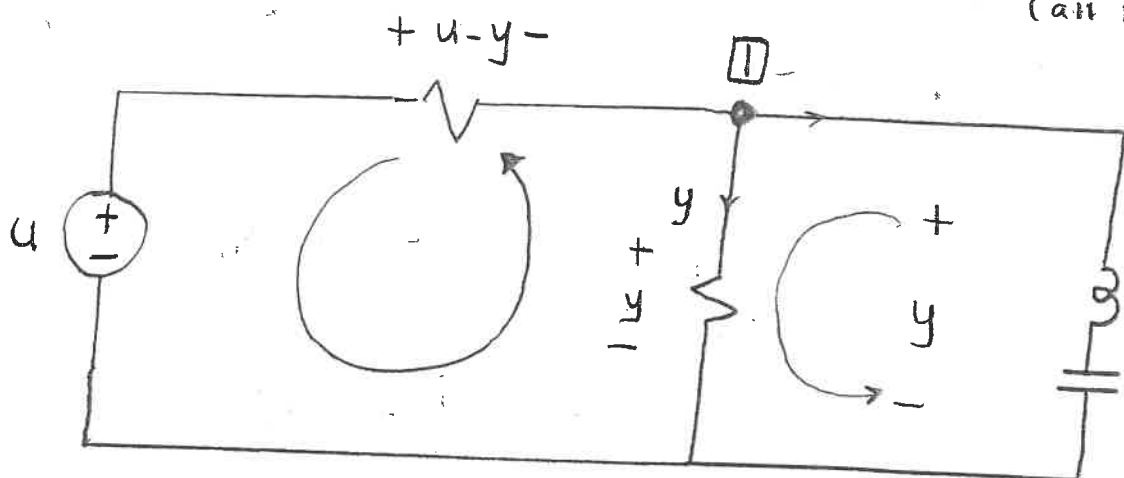

① KCL = $\left(\frac{u-y}{1} \right) = y + \frac{y}{s + \frac{1}{s}} \Rightarrow u - y = y + \frac{sy}{s^2 + 1}$

$$\Rightarrow u = y \left[1 + 1 + \frac{s}{s^2 + 1} \right]$$

$$\Rightarrow (s^2 + 1)u = y[2s^2 + 2 + s]$$

$$\Rightarrow H = \frac{y}{u} = \frac{\frac{1}{2}(s^2 + 1)}{s^2 + \frac{1}{2}s + 1}$$

char eq:

$$\Phi = s^2 + \frac{1}{2}s + 1 = 0 \Rightarrow s_{1,2} = \frac{-\frac{1}{2} \pm \sqrt{\frac{1}{4} - 4(1)(1)}}{2}$$

$$= -\frac{1}{4} \pm \sqrt{\frac{1}{16} - \frac{16}{16}}$$

$$= -\frac{1}{4} \pm j \frac{\sqrt{15}}{4}$$

↑
stable system

$$\Rightarrow \tau = \frac{1}{|\text{Re pole}|} = \frac{1}{|-\frac{1}{4}|} = 4$$

$$t_s = 5\tau = 5(4) = 20$$

$$\boxed{\tau = 4, t_s = 20}$$

MOTF

$$y_{ss} = -5 H(0) + 10 |H(j1)| \sin(t + 30^\circ + \angle H(j1))$$



$$H(0) = \frac{1}{2}$$

$$H(j1) = \frac{\frac{1}{2}(j1)^2 + 1}{\text{den}} = \frac{\frac{1}{2}(-1 + 1)}{\text{den}} = 0$$

since H has zeros at $\pm j1$

Problem # 4

Determine H , diff eq, y

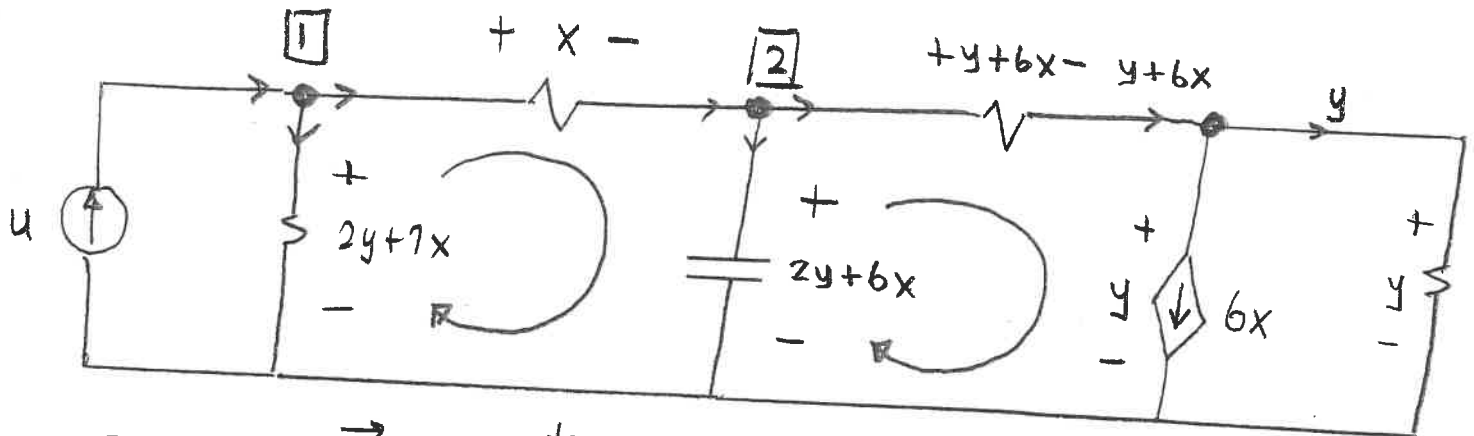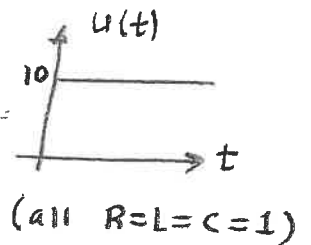

$$① \text{ KCL} = \begin{matrix} \rightarrow \\ u = \end{matrix} \begin{matrix} \downarrow \\ \left(\frac{2y+7x}{1} \right) \end{matrix} + \begin{matrix} \rightarrow \\ \left(\frac{x}{1} \right) \end{matrix} \Rightarrow \boxed{u = 2y + 8x} \quad (*)$$

$$② \text{ KCL} = \begin{matrix} \rightarrow \\ \left(\frac{x}{1} \right) \end{matrix} = \begin{matrix} \downarrow \\ s(2y+6x) \end{matrix} + \begin{matrix} \rightarrow \\ (y+6x) \end{matrix} \Rightarrow y[2s+1] = x[1-6s-6] = -x[6s+5]$$

$$\boxed{x = -\left(\frac{2s+1}{6s+5}\right)y} \quad (*)$$

$$(*) \Rightarrow u = 2y + 8 \left[-\left(\frac{2s+1}{6s+5}\right)y \right]$$

$$\Rightarrow (6s+5)u = [12s+10 - 16s-8]y = [-4s+2]y$$

$$\Rightarrow H = \frac{y}{u} = \frac{6(s+\frac{5}{6})}{-4(s-\frac{1}{2})}$$

\Rightarrow

$$\boxed{H = \frac{y}{u} = -\frac{3}{2} \left[\frac{s+\frac{5}{6}}{s-\frac{1}{2}} \right]}$$

pole at $s = \frac{1}{2} \Rightarrow$ unstable system (pole in RHP!)

$$\boxed{\dot{y} - \frac{1}{2}y = -\frac{3}{2} \left(\dot{u} + \frac{5}{6}u \right)}$$

growing exponential

$$Y = H U = -\frac{3}{2} \left[\frac{s+\frac{5}{6}}{s-\frac{1}{2}} \right] \left[\frac{10}{s} \right] = \frac{A}{s} + \frac{B}{s-\frac{1}{2}} \Rightarrow \boxed{y = A + B e^{\frac{1}{2}t}}$$

$$A = \lim_{s \rightarrow 0} s Y = s H(s) \frac{10}{s} \Big|_{s=0} = 10 H(0) = 10 \left(-\frac{3}{2} \left(\frac{5/6}{-1/2} \right) \right) = 10 \left(\frac{5}{2} \right)$$

$$\boxed{A = 25}$$

$$B = \lim_{s \rightarrow \frac{1}{2}} (s-\frac{1}{2}) Y = \left(-\frac{3}{2} \right) \left(s+\frac{5}{6} \right) \frac{10}{s} \Big|_{s=\frac{1}{2}} = \left(-\frac{3}{2} \right) \left(\frac{1}{2} + \frac{5}{6} \right) \left(\frac{10}{1/2} \right)$$


$$\boxed{B = -40}$$

$$\boxed{5/9}$$

(Problem 7.1)

Alternate =

via
source
transf

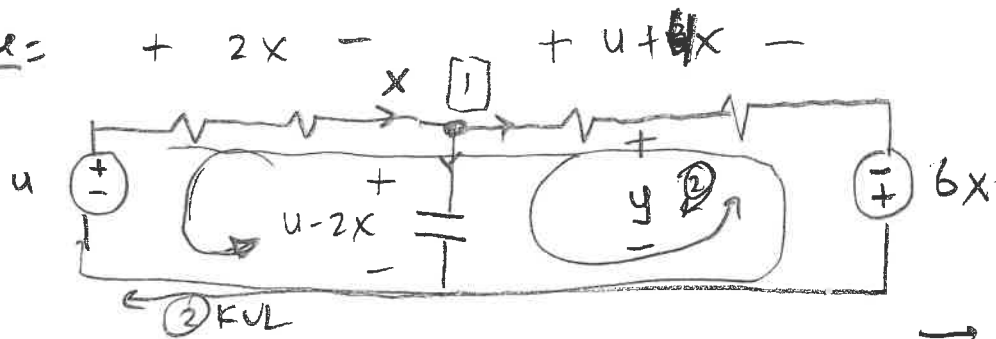

$$(1) \text{ KVL} = x = s(u - 2x) + \frac{(u + 4x)}{2}$$

$$x[1 + 2s - 2] = u[s + \frac{1}{2}]$$

$$x = \left[\frac{s + \frac{1}{2}}{2s - 1} \right] u$$

$$(2) \text{ KVL} = y = \left(\frac{u + 4x}{2} \right) (1) - 6x$$

$$= \frac{u}{2} + 2x - 6x$$

$$= \frac{u}{2} - 4x$$

$$= \frac{u}{2} - 4 \left[\frac{s + \frac{1}{2}}{2s - 1} \right] u$$

$$= \left[\frac{(2s - 1) - 8(s + \frac{1}{2})}{2(2s - 1)} \right] u$$

$$= \left[\frac{2s - 1 - 8s - 4}{4(s - \frac{1}{2})} \right] u$$

$$= \left[\frac{-6s - 5}{4(s - \frac{1}{2})} \right] u$$

$$= -\frac{3}{2} \left[\frac{s + 5/6}{s - 1/2} \right] u \quad \checkmark \checkmark \text{ -- same! } \left(\begin{smallmatrix} \tau \\ \vdots \\ \checkmark \end{smallmatrix} \right)$$

Problem #5

Sorry -- I know this is crowded! AAR

Determine y_{1ss} , y_1 , t_{s1} , y_{2ss} , y_2 , t_{s2}

$$H_1(s) = \frac{s}{(s+2)(s^2-6s+25)}$$

$$\begin{aligned} \tau_1 &= \frac{1}{2} \\ t_{s1} &= 5\tau_1 = \frac{5}{2} \\ 6 \pm \sqrt{36-4(1)(25)} &= 3 \pm j4 \\ &\uparrow \text{unstable} \\ &\text{(has poles in RHP)} \end{aligned}$$

$$u_1(t) = -10 + 50 \cos(0.01t - 45^\circ) + 8 \sin(5t + 30^\circ)$$

$$U_1 = \frac{-10}{s} + \frac{50}{s^2 + 10^{-4}} + \frac{8}{s^2 + 25}$$

$$y_{1ss} = -10 H_1(0) + 50 |H_1(j0.01)| \cos(0.01t - 45^\circ + |H_1(j0.01)|) + 8 |H_1(j5)| \sin(5t + 30^\circ + |H_1(j5)|) + \text{unstable term due to poles at } 3 \pm j4 \text{ (see PFE below)}$$

$$H_1(j0.01) \approx \frac{s}{(2)(25)} \Big|_{s=j0.01} = \frac{1}{50} (0.01 e^{j90^\circ}) = \frac{1}{5000} e^{j90^\circ}$$

$$H_1(0) = 0$$

since H_1 has a zero at $s=0$!

$$C = \lim_{s \rightarrow 3-j4} (s-3+j4) Y_1(s)$$

$$Y_1 = H_1 U_1 = \left[\frac{s}{(s+2)(s^2-6s+25)} \right] \left[\frac{-10}{s} + \frac{50}{s^2+10^{-4}} + \frac{8}{s^2+25} \right] = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{s-3+j4} + \frac{D}{s-j0.01} + \frac{E}{s-j5} + \dots$$

$$H_1(j5) = \frac{(j5)}{(j5+2)(-25-j6(5)+25)} = \frac{5e^{j90^\circ}}{(\sqrt{25+4} e^{j\arctan(\frac{5}{2})}) (30e^{-j90^\circ})} = \left(\frac{5}{\sqrt{29}} \left(\frac{1}{30} \right) \right) e^{j[90 - \arctan(\frac{5}{2}) - (-90^\circ)]}$$

$$y_1 = A + B e^{-2t} + 21C |e^{3t} \cos(4t + \angle C)| + 21D |\cos(0.01t + \angle D)| + 21E |\cos(5t + \angle E)|$$

$$H_2(s) = \frac{(s+1)(s^2+10s+100)}{(s+1)(s^2+10s+100)}$$

$$A = \lim_{s \rightarrow 0} s Y_1 = -10 H_1(0)$$

$$\begin{aligned} \tau_2 &= 1 \\ t_{s2} &= 5\tau_2 = 5(1) = 5 \end{aligned}$$

$$U_2(t) = 7 - \cos(t + 20^\circ) + 6 \sin(100t + 135^\circ)$$

$$U_2 = \frac{7}{s} - \frac{1}{s^2+1} + \frac{6}{s^2+104} = \frac{7}{s(s^2+1)} + \frac{6}{s(s^2+104)}$$

$$y_{2ss} = 7 H_2(0) - |H_2(j1)| \cos(t + 20^\circ + |H_2(j1)|) + 6 |H_2(j100)| \sin(100t + 135^\circ + |H_2(j100)|)$$

$$H_2(0) = \frac{1}{(1)(100)} \quad H_2(j1) = 0 = 0e^{j0} \quad \text{Since } H_2 \text{ has zero at } \pm j1$$

$$H_2(j100) \approx \frac{1}{s} \Big|_{s=j100} = \frac{1}{100} e^{j90^\circ} = 0.01 e^{j90^\circ}$$

$$Y_2 = H_2 U_2 = \left[\frac{s+1}{(s+1)(s^2+10s+100)} \right] \left[\frac{7}{s} - \frac{1}{s^2+1} + \frac{6}{s^2+104} \right] = \frac{A}{s} + \frac{B}{s+1} + \left[\frac{C}{s+5-j5\sqrt{3}} + \dots \right]$$

$$y_2 = A + B e^{-t} + 21C |e^{-5t} \cos(5\sqrt{3}t + \angle C)| + 21D |\cos(100t + \angle D)| + \dots$$

y_{2ss}


$$A = \lim_{s \rightarrow 0} s Y_2 = 7 H_2(0)$$

$$D = \lim_{s \rightarrow j100} (s-j100) Y_2 \leftarrow \text{related to } H_2(j100) = \frac{6 |H_2|}{2} e^{j[135 + \angle H_2 - 90^\circ]} = \frac{6 |H_2|}{2} e^{j[135 + \angle H_2 - 90^\circ]}$$

Problem #6

Determine an s-domain Thevenin Equivalent at y

(all $R=L=C=1$)

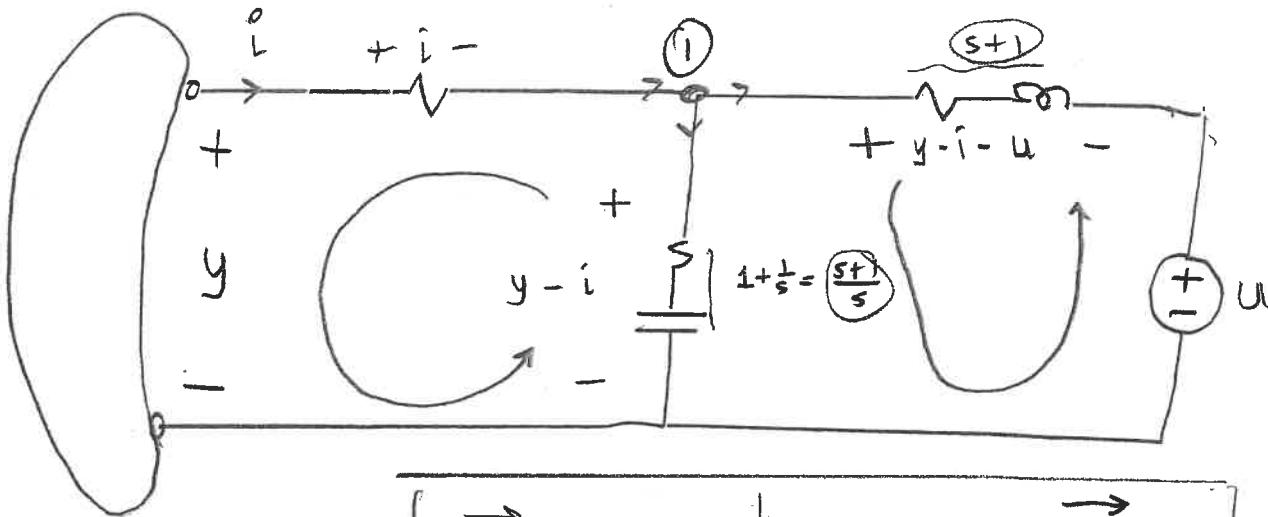

$$\textcircled{1} \text{ KCL} = \begin{matrix} \rightarrow \\ i \end{matrix} = \begin{matrix} \downarrow \\ s(y-i) \\ s+1 \end{matrix} + \begin{matrix} \rightarrow \\ (y-i-u) \\ s+1 \end{matrix}$$

$$y \left[\frac{s}{s+1} + \frac{1}{s+1} \right] = i \left[1 + \frac{s}{s+1} + \frac{1}{s+1} \right] + u \left[\frac{1}{s+1} \right]$$

$$y [s+1] = i [s+1 + s + 1] + u [1]$$

$$y = [2] i + \left[\frac{1}{s+1} \right] u$$


$$Z_{th} = 2$$

WOW!


admittances in parallel add

$$Y = \frac{1}{Z} = Y_1 + Y_2 = \frac{s}{s+1} + \frac{1}{s+1} = \frac{s+1}{s+1} = 1 \Rightarrow Z = 1$$

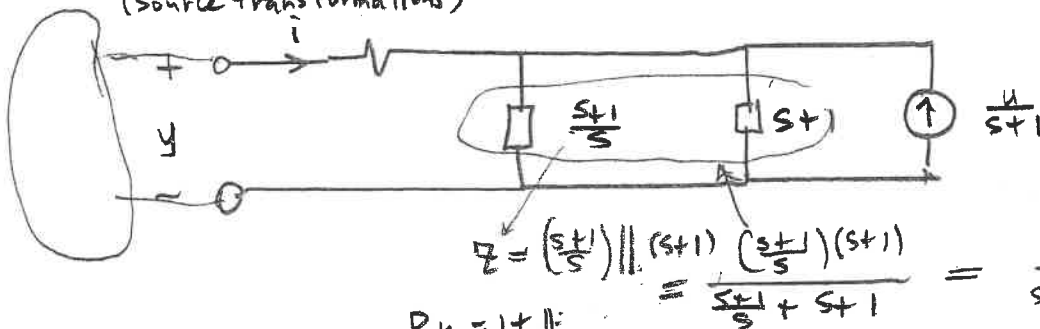Alternate Method:
(source transformations)


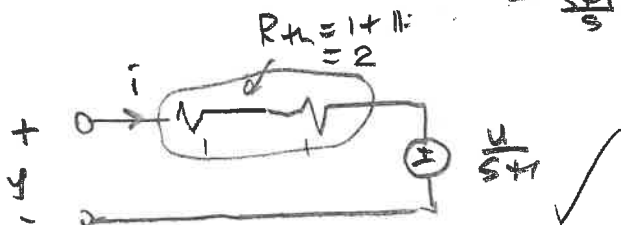
$$Z = \left(\frac{s+1}{s} \right) \parallel (s+1) = \frac{(s+1)(s+1)}{s+1+s^2+s} = \frac{(s+1)(s+1)}{s^2+2s+1} = \frac{s^2+2s+1}{s^2+2s+1} = 1$$



WOW!


Problem #7

Determine H & y_{ss}

$$u = -5 + 2 \sin(t + 30^\circ)$$

$$-3 \cos(100t - 135^\circ)$$

$$(a) R=L=C=1$$

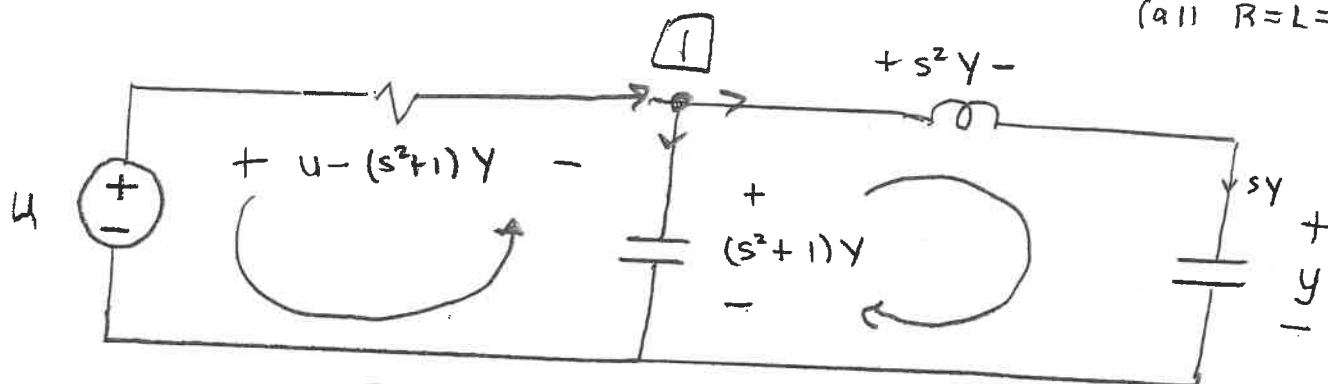

$$\textcircled{1} \text{ KCL} = \left(\frac{u - (s^2 + 1)y}{1} \right) = s[(s^2 + 1)y] + (sy)$$

$$y[s^2 + 1 + s^3 + s + s] = u$$

$$H = \frac{y}{u} = \frac{1}{s^3 + s^2 + 2s + 1}$$

$$y_{ss} = -5 \textcircled{H(0)} + 2 |H(j1)| \sin(t + 30^\circ + \textcircled{H(j1)} - 90^\circ) - 3 |H(j100)| \cos(100t - 135^\circ + \textcircled{H(j100)} - 270^\circ)$$


$$H(0) = 1$$

$$\begin{aligned} H(j1) &= \frac{1}{(j1)^3 + (j1)^2 + 2j1 + 1} = \frac{1}{-j1 + 1 + j2 + 1} = \frac{1}{1 + j1} \\ &= \frac{1}{\sqrt{2}} \angle -45^\circ = \frac{1}{\sqrt{2}} \angle -90^\circ = \textcircled{1} e^{-j90^\circ} \end{aligned}$$

$$\begin{aligned} H(j100) &\cong \frac{1}{s^3} \Big|_{s=j100} = \frac{1}{10^6 e^{j270^\circ}} = 10^{-6} e^{-j270^\circ} \end{aligned}$$

Problem #8

Determine $H_1, H_2, \tau_{s1}, y_{1ss}$

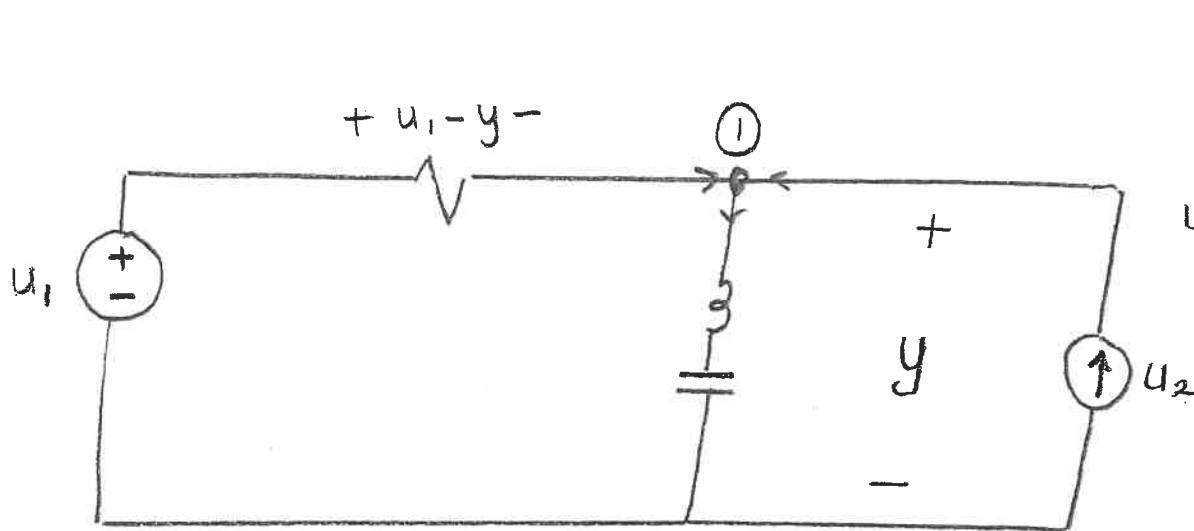

$$u_1 = 10$$

$$-8 \sin(t + 30^\circ)$$

$$+ 7 \cos(100t + 45^\circ)$$

$$u_2 = 0$$

$$(all R=L=C=1)$$

$$\textcircled{1} KCL = \left(\frac{u_1 - y}{1} \right) + \left(u_2 \right) = \frac{y}{s + \frac{1}{s}} = \frac{s^2 + 1}{s} = \frac{s y}{s^2 + 1}$$

$$u_1 + u_2 = y \left[1 + \frac{s^2}{s^2 + 1} \right]$$

$$y [s^2 + 1 + s] = (s^2 + 1)(u_1 + u_2)$$

$$y = \left[\frac{s^2 + 1}{s^2 + s + 1} \right] (u_1 + u_2)$$

\uparrow
 $H_1 = H_2$

$$poles = -\frac{1}{2} \pm j\frac{\sqrt{3}}{2} \Rightarrow \tau_1 = \frac{1}{|Re poles|} = \frac{1}{1 - \frac{1}{2}} = 2$$


$$\tau_{s1} = 5\tau_1 = 5(2) = 10$$

$$y_{1ss} = 10 H_1(0) - 8 |H_1(j1)| \sin(t + 30^\circ + \angle H_1(j1)) + 7 |H_1(j100)| \cos(100t + 45^\circ + \angle H_1(j100))$$

$H_1(0) = 1$ \rightarrow $H_1(j1) = 0$ since H_1 has zeros at $\pm j1$

$H_1(j100) \approx 1 = 1 \angle 0^\circ$

Problem #4 (Alternate Solution)

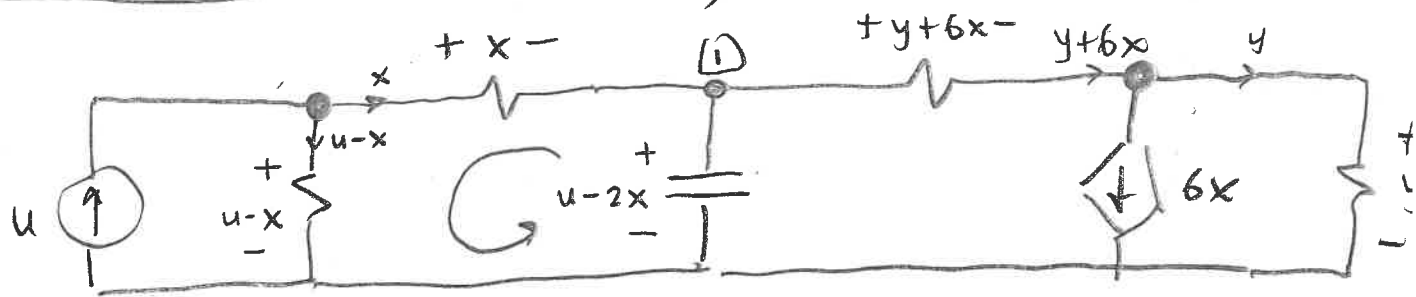

$$\textcircled{1} \text{ KCL} = x = s(u-2x) + (y+6x) \Rightarrow x(1+2s-6) = su+y$$

$$\Rightarrow x = \frac{y+su}{2s-5}$$

AAR SOLUTIONS'

EXAM #2

Fall 2023

Fri 12-8-23



Final Exam Rules

Final Exam
Fall 2023
Fri 12-15-23

- 1 One $8\frac{1}{2}'' \times 11''$ sheet permitted;
otherwise closed books, closed notes, closed phone,
open minds!
- 2 calculator permitted (no computer!!; no phone!!!)
- 3 NO PHONES ! Phones should not be visible at all!
A visible phone will result in a zero grad
for the exam!
- 4 Write full name legibly on each page provided.
- 5 Please show all work. Write your solutions on the
pages provided. (No other pages/paper should be used!)
- 6 Clearly label voltage & currents on circuits provided.
- 7 Use variables provided! (No additional variables!)
- 8 Unreadable work will receive NO CREDIT.
- 9 Please place important equations & answers within box
- 10 Please be careful with your algebra, signs, etc.
- 11 Please turn in solutions to me at end of period!
- 12 PLEASE DO NOT CHEAT!!! ☹️

Pr. A.A. Rodriguez
EE102
all rights reserved


AAR SOLUTIONS!

Final Exam
Fall 2023

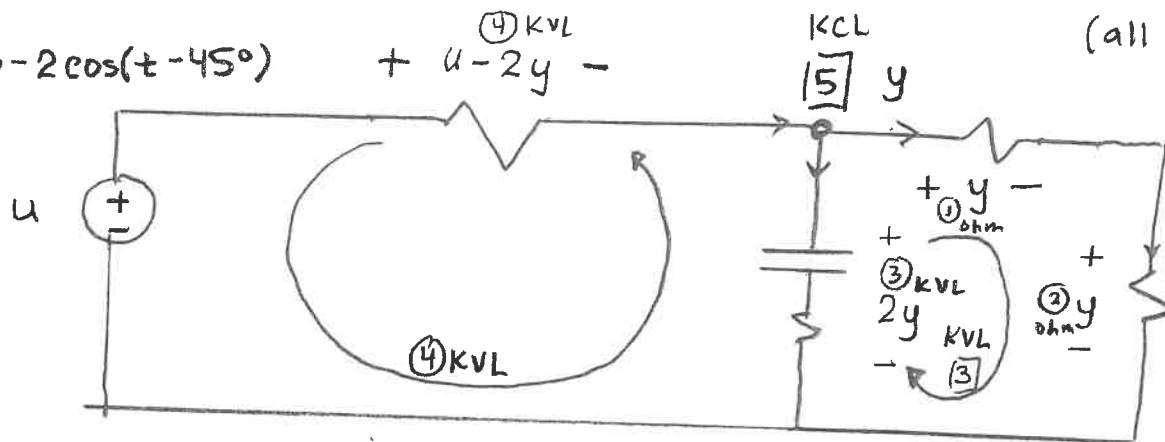Problem #1

Determine H , diff eq, t_s , y_{ss} , y

$u = -6 - 2\cos(t - 45^\circ)$ + $u - 2y$ - (all $R=L=C=1$)



⑤ KCL: $\left(\frac{u-2y}{1} \right) = (y) + \left(\frac{2y}{\frac{1}{s} + 1} \right) = y + \frac{2sy}{s+1}$

$u = y \left[2 + \frac{1}{s} + \frac{2s}{s+1} \right]$
 $\Rightarrow (s+1)u = y [3s+3+2s] = y [5s+3]$

$\Rightarrow H = \frac{y}{u} = \frac{\frac{1}{5}(s+1)}{(s+\frac{3}{5})} \Rightarrow \dot{y} + \frac{3}{5}y = \frac{1}{5}(\dot{u} + u)$

$\Rightarrow \text{pole} = -\frac{3}{5}$
 $\Rightarrow \text{stable} \Rightarrow \tau = \frac{1}{|\text{Re pole}|} = \frac{1}{|\frac{3}{5}|} = \frac{5}{3}$

$t_s = 5\tau = \frac{25}{3}$

NOTE

$y_{ss} = -6H(0) - 2|H(j1)|\cos(t-45^\circ + \angle H(j1))$

$H(0) = \frac{1}{3}$

$H(j1) = \frac{\frac{1}{5}(j1+1)}{(j1+\frac{3}{5})}$

$j1 = \sqrt{2}e^{j45^\circ}$

$\frac{3}{5} + j1 = \sqrt{\frac{9}{25} + 1} e^{j \tan^{-1}(\frac{1}{3/5})}$

$U = -\frac{6}{s} - \frac{2}{s^2+1} = \frac{1}{s(s^2+1)}$
 $Y = HU = \left[\frac{1}{s+\frac{3}{5}} \right] \left[\frac{1}{s(s^2+1)} \right] = \frac{A}{s} + \frac{B}{s+\frac{3}{5}} + \left[\frac{C}{s-j1} + \frac{C^*}{s+j1} \right] \Rightarrow y = A + Be^{-\frac{3}{5}t} + 2|C|\cos(t + \angle C)$

$A = \lim_{s \rightarrow 0} sY = -6H(0)$

$C = \lim_{s \rightarrow j1} (s-j1)Y$

$-6H(0)$

$-2|H(j1)|\cos(t-45^\circ + \angle H(j1))$


$= 2|H(j1)|\cos(t-45^\circ + \angle H(j1) \pm 180^\circ)$

$\Rightarrow C = |H(j1)| e^{j(-45^\circ + \angle H(j1) \pm 180^\circ)} \quad \text{Final Fall 2023}$

Note: $B = \lim_{s \rightarrow -\frac{3}{5}} (s+\frac{3}{5})Y$

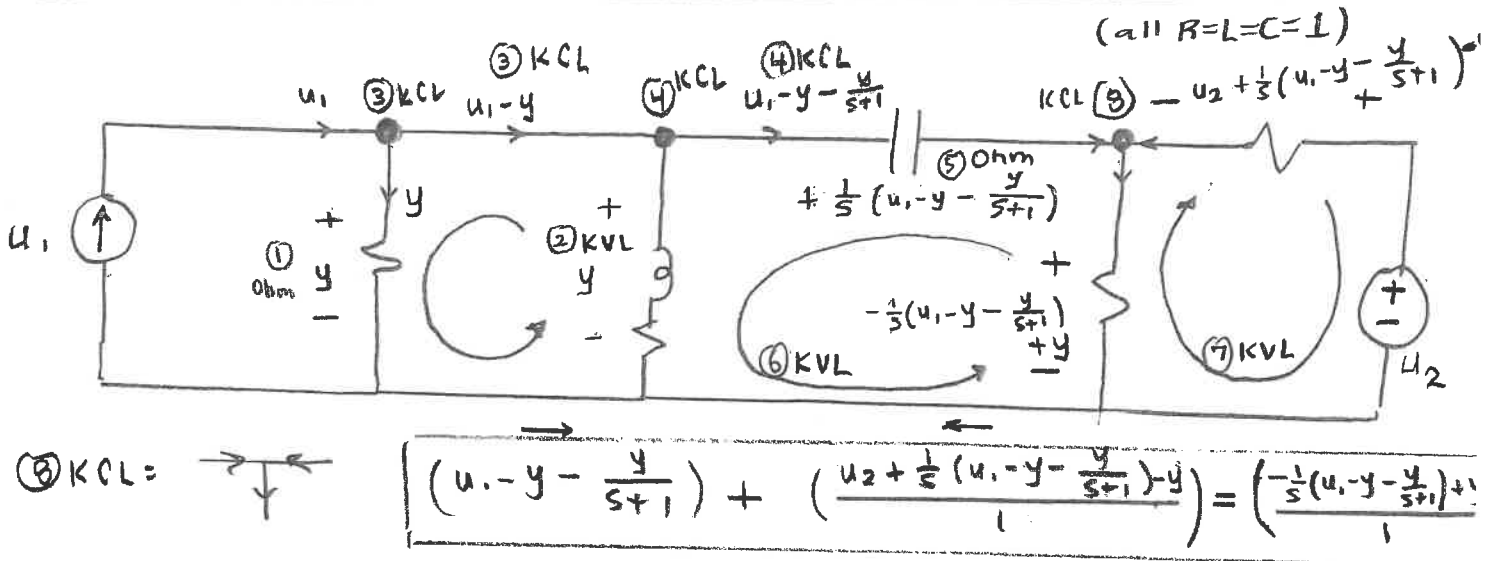Problem # 2

Determine $H_1(0)$, $H_2(0)$, $H_1(\infty)$, $H_2(\infty)$, poles, t_s



$$u_1 \left[1 + \frac{1}{s} + \frac{1}{s} \right] + u_2 [1] = y \left[1 + \frac{1}{s+1} + \frac{1}{s} + \frac{1}{s(s+1)} + 1 + \frac{1}{s} + \frac{1}{s(s+1)} \right]$$

$$u_1 \left[1 + \frac{2}{s} \right] + u_2 [1] = y \left[3 + \frac{1}{s+1} + \frac{2}{s} + \frac{2}{s(s+1)} \right]$$

$$X(s)(s+1)$$

$$u_1 [(s+2)(s+1)] + u_2 [s(s+1)] = y [3s(s+1) + s + 2(s+1) + 2]$$

$$u_1 [s^2 + 3s + 2] + u_2 s(s+1) = y [3s^2 + 3s + s + 2s + 2 + 2]$$

$$= 3y [s^2 + 2s + \frac{4}{3}]$$

$$\Rightarrow y = \left[\frac{\frac{1}{3}(s^2 + 3s + 2)}{s^2 + 2s + \frac{4}{3}} \right] u_1 + \left[\frac{\frac{1}{3}s(s+1)}{s^2 + 2s + \frac{4}{3}} \right] u_2$$

$$H_1(b) = \frac{1}{2} \quad H_2(b) = 0 \quad H_1(\infty) = H_2(\infty) = \frac{1}{3}$$

poles = $\bar{\varphi}(s) = s^2 + 2s + \frac{4}{3} = 0 \Rightarrow s_{1,2} = \frac{-2 \pm \sqrt{4 - 4(1)(\frac{4}{3})}}{2(1)} = -1 \pm \sqrt{1 - \frac{4}{3}} = -1 \pm j\frac{1}{\sqrt{3}}$

$$\tau = \frac{1}{|\text{Re poles}|} = \frac{1}{|-1|} = 1$$

$$t_5 = 5\tau = 5(1) = 5$$


NOTE:-

Above was the long (hard) way!

Lets see how to get answers

much faster --- without KVL, KCL, Ohm!

$s=0$ (Cap open, Inductor shorted)

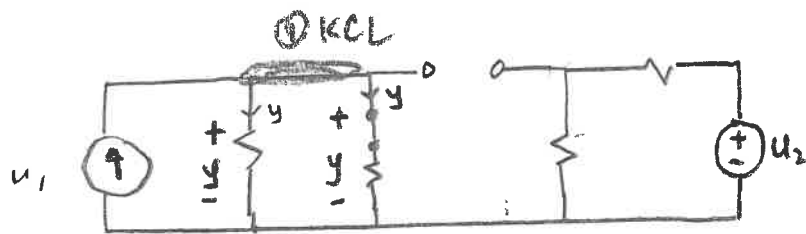


① KCL: $u_1 = y + y = 2y \Rightarrow y = \frac{1}{2} u_1 \Rightarrow$

$H_1(0) = \frac{1}{2} \quad H_2(0) = 0$

Agrees with what we got on reverse side!

$s=\infty$ (Cap shorted, Inductor open)

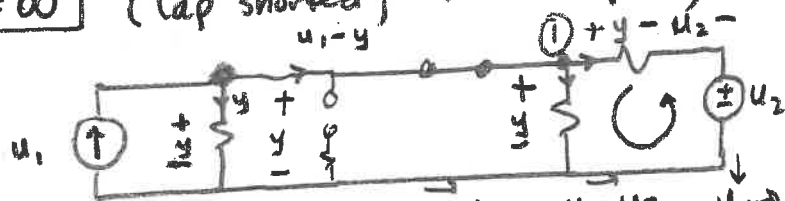


① KCL: $u_1 - y = \frac{y + u_2}{1} + y \Rightarrow u_1 + u_2 = 3y \Rightarrow y = \frac{1}{3} (u_1 + \frac{1}{3} u_2)$

$H_1(\infty) = H_2(\infty) = \frac{1}{3}$

Agrees with what we got on reverse side!

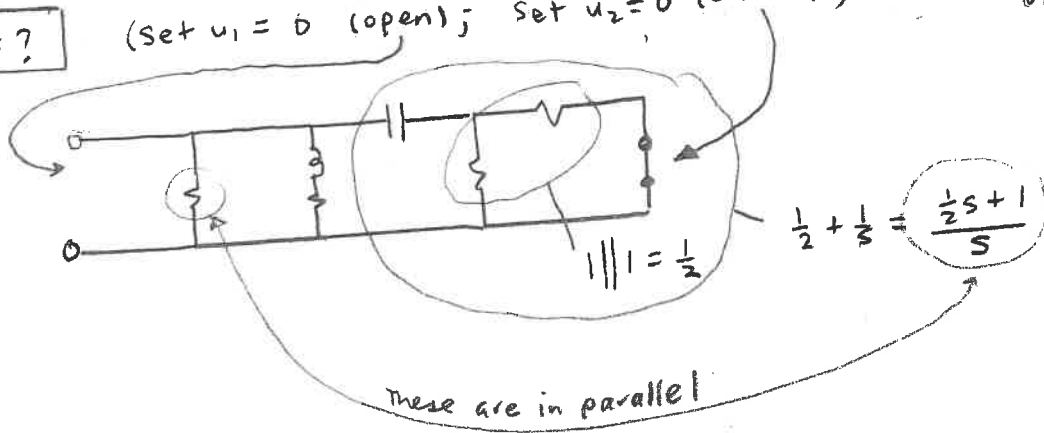$t_s = ?$ (set $u_1 = 0$ (open); set $u_2 = 0$ (short))



NOTE:
ALL THIS
IS MUCH EASIER
THAN WHAT WE
DID ON REVERSE
SIDE!

$Z_{total} = s+1 + \frac{\frac{1}{2}s+1}{1 + \frac{\frac{1}{2}s+1}{s}} = \frac{(s+1)(\frac{3}{2}s+1) + \frac{1}{2}s+1}{\frac{3}{2}s+1}$

$\frac{3}{2}s^2 + \frac{5}{2}s + 1 + \frac{1}{2}s + 1 = \frac{3}{2}s^2 + \frac{6}{2}s + 2 = \frac{3}{2} [s^2 + 2s + \frac{4}{3}]$

$\Phi(s) = s^2 + 2s + \frac{4}{3} = 0 \Rightarrow s_{1,2} = -1 \pm j\frac{1}{\sqrt{3}} \Rightarrow \tau = \frac{1}{|\text{Re pole}|} = 1$


$t_s = 5\tau = 5(1) = 5$

what we got on reverse side!

Problem #3

Determine H , diff eq, t_s , y_{ss}

(all $R=L=C=1$)

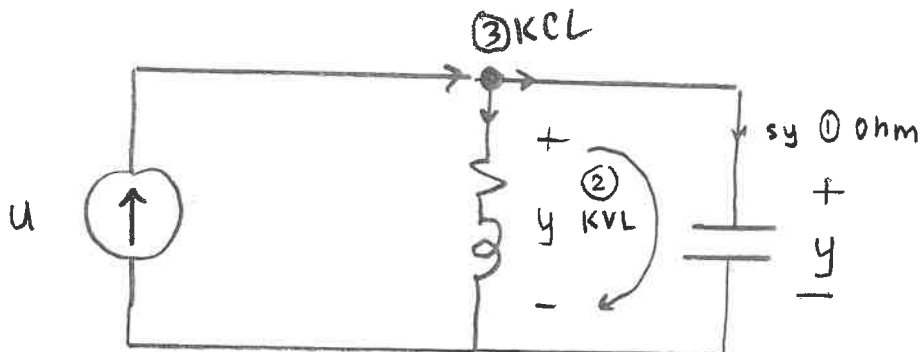

$$u = 4 - 3 \sin(t + 135^\circ)$$

given stability

↑

we know system (circuit) is stable since it consists only of independent sources & passive elements (i.e. R, L , & C s).

... we find H from ckt analysis!

$$\textcircled{3} \text{KCL} = \rightarrow y \quad \boxed{u = \frac{y}{1+s} + sy} = y \left[\frac{1}{s+1} + s \right] \quad \text{transf function}$$

$$\Rightarrow (s+1)u = y[1 + s^2 + s] \Rightarrow \boxed{H = \frac{y}{u} = \frac{s+1}{s^2+s+1}}$$

$$\text{diff eq: } \ddot{y} + \dot{y} + y = \dot{u} + u$$

$$\text{poles: } s_{1,2} = -\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$$

$$H(0) = 1$$

$$H(j\omega) = \frac{j\omega + 1}{-1 + j\omega + 1} = \frac{j\omega + 1}{j\omega} = 1 + \frac{1}{j\omega}$$

$$|H(j\omega)| = \frac{\sqrt{2}}{1} = \sqrt{2}$$

$$\angle H(j\omega) = 45^\circ - 90^\circ$$

all poles in LHP \Leftrightarrow system is stable



$$\Rightarrow T = \frac{1}{|\text{Re poles}|} = \frac{1}{\frac{1}{2}} = 2$$

$$t_s = 5T = 5(2) = 10$$

Final Fall 2023

Problem # 4

Determine H , diff eq, y

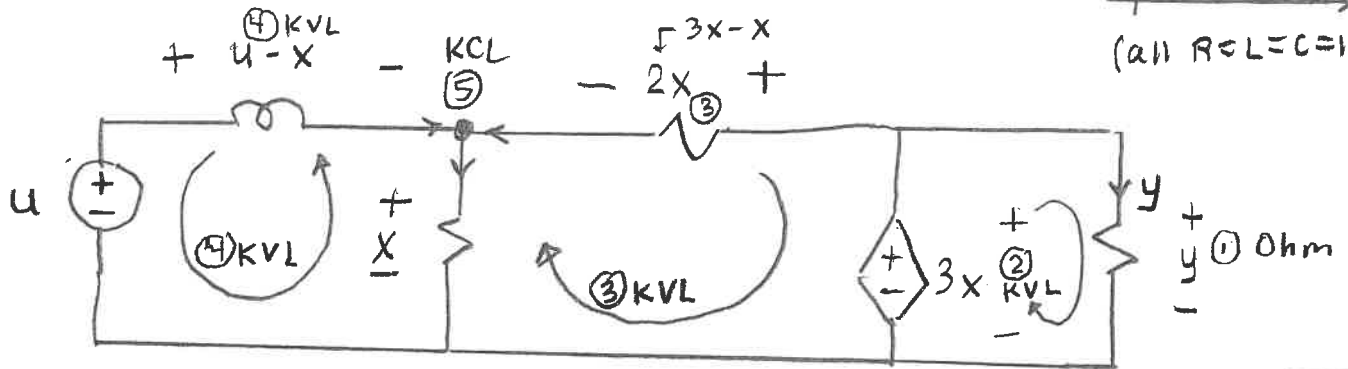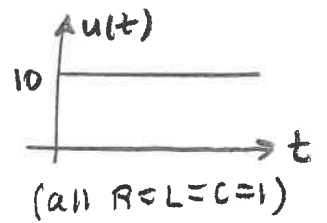


② KVL: $3x = y \Rightarrow \boxed{x = \frac{y}{3}}$

WOW!
That was easy!

⑤ KCL: $\left(\frac{u-x}{s}\right) + \left(\frac{2x}{1}\right) = \left(\frac{x}{1}\right)$

$\Rightarrow \frac{u}{s} = x \left[\frac{1}{s} - 2 + 1\right] = x \left[\frac{1}{s} - 1\right]$
 $= x \left[\frac{1-s}{s}\right]$
 $= \frac{y}{3} \frac{[1-s]}{s}$

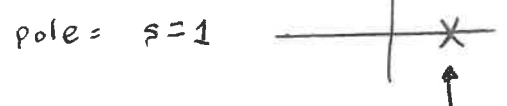$\Rightarrow H = \frac{y}{u} = \frac{-3}{s-1} \Rightarrow \text{diff eq: } \dot{y} - y = -3u$



pole in RHP \Rightarrow system is unstable
expected from MOTF

$Y = HU = \left[\frac{-3}{s-1}\right] \left[\frac{10}{s}\right] = \frac{A}{s} + \frac{B}{s-1}$

$\Rightarrow \boxed{y(t) = A + Be^t}$

$A = \lim_{s \rightarrow 0} sY = \cancel{s} H \frac{10}{\cancel{s}} \Big|_{s=0} = 10 H(0) = 10 \left(\frac{-3}{-1}\right) = (10)(3) = 30$

$B = \lim_{s \rightarrow 1} (s-1)Y = (s-1) \left(\frac{-3}{s-1}\right) \frac{10}{s} \Big|_{s=1} = (-3) \left(\frac{10}{1}\right) = -30$

Final Fall 2023

Problem # 5

Determine y_{ss} , y , t_s

$$H(s) = \frac{s(s^2 + 4)}{(s+2)(s^2 + 2s + 10)(s^2 - s + 1)}$$

$\text{pole} = -2$ (stable) poles = $\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$ (unstable)

$$u(t) = 5 - 6 \sin(2t + 45^\circ) + 7 \cos(100t + 270^\circ)$$

(compute all important coefficients as discussed in class)


$$\text{poles} = s_{1,2} = \frac{-2 \pm \sqrt{4 - 4(1)(10)}}{2(1)} = -1 \pm \sqrt{1-10}$$

$$U = \frac{5}{s} - \frac{1}{s^2 + 4} + \frac{1}{s^2 + 104} = \frac{5(s^2 + 4)(s^2 + 104)}{s(s^2 + 4)(s^2 + 104)}$$

$$= -1 \pm j3 \text{ (stable)}$$

$$Y = HU = \left[\frac{s(s^2 + 4)}{(s+2)(s+1+j\sqrt{3})(s-1-j\sqrt{3})} \right] \left[\frac{5(s-j2)(s+j100)}{s(s+j2)(s-j100)} \right]$$
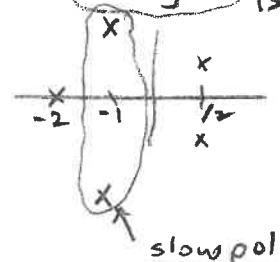
$$= \frac{A}{s} + \frac{B}{s+2} + \left[\frac{C}{s+1-j\sqrt{3}} + * \right] + \left[\frac{D}{s-1-j\sqrt{3}} + * \right] + \left[\frac{E}{s-j2} + * \right] + \left[\frac{F}{s-j100} + * \right]$$



$$\tau = \frac{1}{|Re \text{ poles}|} = \frac{1}{1-1} = 1$$

$$t_s = 5\tau = 5(1) = 5_{se}$$

Note: It will take 5sec for the output y of the unstable system H to reach y_{ss}

$$y(t) = A + B e^{-2t} + 2|C| e^{-t} \cos(\sqrt{3}t + \angle C) + 2|D| e^{\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t + \angle D\right) + 2|E| \cos(2t + \angle E) + 2|F| \cos(100t + \angle F)$$

stable stable unstable

$$y_{ss} = 5H(0) - 6|H(j2)| \sin(2t + 45^\circ + \angle H(j2)) + 7|H(j100)| \cos(100t + 270^\circ + \angle H(j100)) + 6|H(j2)| \cos(2t + 45^\circ + \angle H(j2) + 90^\circ)$$

from MOTF

$$A = \lim_{s \rightarrow 0} sY = sH(0) = 5(0) = 0$$

MOTF

$$D = \lim_{s \rightarrow \frac{1}{2} + j\frac{\sqrt{3}}{2}} (s - \frac{1}{2} - j\frac{\sqrt{3}}{2}) Y$$

$$E = \frac{6|H(j2)|}{2} e^{j(45^\circ + \angle H(j2) + 90^\circ)}$$

from PFE!


$$F = \lim_{s \rightarrow j2} (s - j2) Y$$

$$F = \lim_{s \rightarrow j100} (s - j100) Y = \frac{7|H(j100)|}{2} e^{j(270^\circ + \angle H(j100))}$$

Final Fall 2023

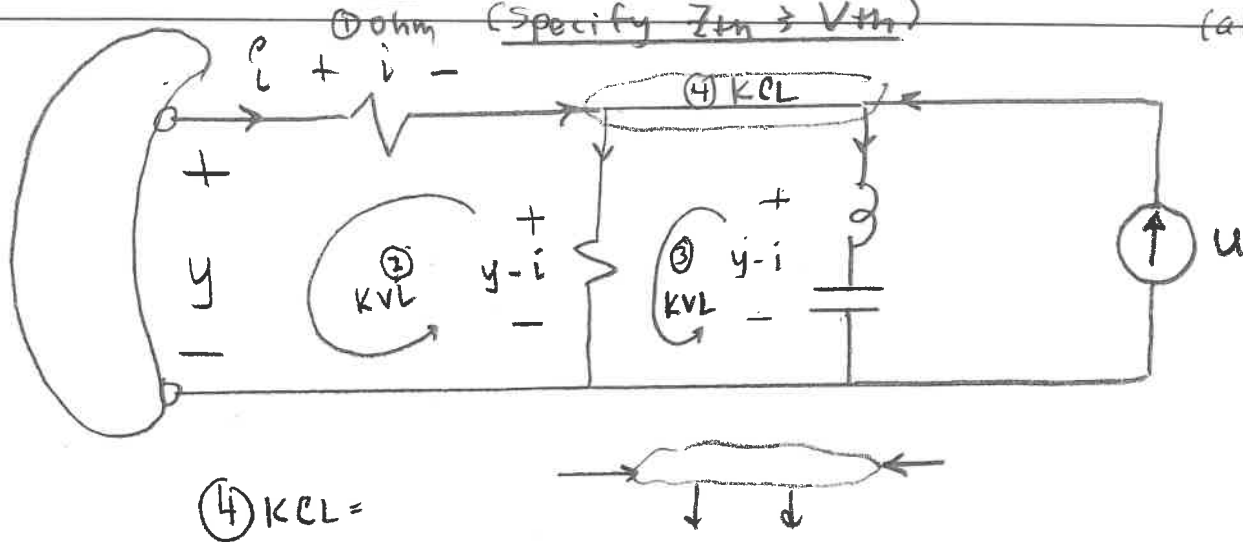Problem #6

Determine an s-domain Thevenin Equivalent at y
(Specify Z_{th} & V_{th})
(all $R=L=C=1$)




$$i + u = \left(\frac{y-i}{1} \right) + \left(\frac{y-i}{s+\frac{1}{s}} \right)$$

$$i \left[1 + 1 + \frac{1}{s+\frac{1}{s}} \right] + u = y \left[1 + \frac{1}{s+\frac{1}{s}} \right]$$

$$i \left[\frac{2s^2 + 2s + 1}{s^2 + 1} \right] + u \left[\frac{s^2 + 1}{s^2 + 1} \right] = y \left[\frac{s^2 + 1 + s}{s^2 + 1} \right]$$
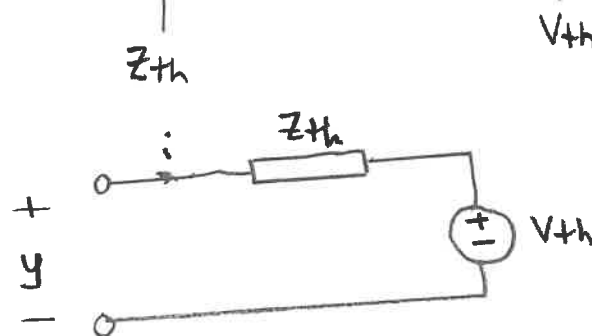
$$y = \left[\frac{2(s^2 + \frac{1}{2}s + 1)}{s^2 + s + 1} \right] i + \left[\frac{s^2 + 1}{s^2 + s + 1} \right] u$$




Problem # 7

Determine $H \hat{=} y_{ss}$

Compute all coefficients in y_{ss} (approximately)

(all $R=L=C=1$)

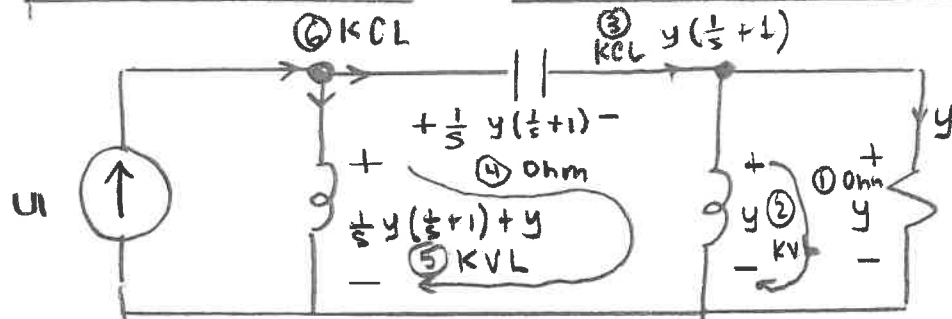

$$u = -7 + 8 \cos(0.01t - 180^\circ) - 9 \sin(100t + 20^\circ)$$

↓ MDTF

$$y_{ss} = -7H(0) + 8|H(j0.01)| \cos(0.01t - 180^\circ + \angle H(j0.01)) - 9|H(j100)| \sin(100t + 20^\circ + \angle H(j100))$$

Note: H is found from circuit analysis!

$$\textcircled{6} \text{ KCL} = \rightarrow y \rightarrow \boxed{u = \left(\frac{\frac{1}{5}y(\frac{1}{5}+1) + y}{s} \right) + \left(y(\frac{1}{3}+1) \right)}$$

$$= y \left[\frac{1}{s^3} + \frac{1}{s^2} + \frac{1}{s} + \frac{1}{s} + 1 \right]$$

$$s^3 u = y [1 + s + 2s^2 + s^3]$$

$$\boxed{H = \frac{y}{u} = \left[\frac{s^3}{s^3 + 2s^2 + s + 1} \right]}$$

$H(0) = 0$ (so dc term of u gets "killed" i.e. absorbed by H)

$$H(j0.01) \cong s^3 \Big|_{s=j0.01} = 10^{-6} e^{j270^\circ} \sim |H(j0.01)|$$

$$= 0.01 e^{j90^\circ}$$

$$= 10^{-2} e^{j90^\circ}$$

$$H(j100) \cong H(\infty) = 1 = 1 e^{j0^\circ} \sim |H(j100)|$$


Final Fall 2023

Problem #8

Determine H , t_s , y_{ss}

$$u = -8 + 9 \sin(t - 45^\circ)$$

(all $R=L=C=1$)

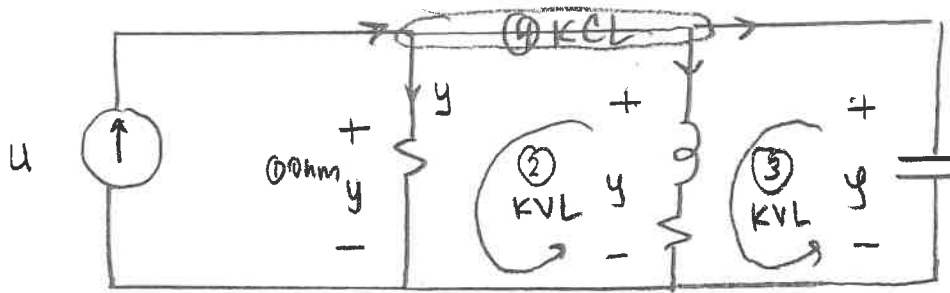

④ KCL =

$$\vec{u} = \left(\frac{y}{1} \right) + \left(\frac{y}{s+1} \right) + (sy)$$

$$= y \left[1 + \frac{1}{s+1} + s \right]$$

$$(s+1)u = y [\underbrace{s+1 + 1 + s^2 + s}_{s^2 + 2s + 2}]$$

$$H = \frac{y}{u} = \left[\frac{s+1}{s^2 + 2s + 2} \right]$$

$$H(0) = 1$$

$$H(j1) = \frac{j1 + 1}{-1 + 2j1 + 2} = \frac{1+j1}{1+j2}$$

$$|H(j1)| = \frac{|top|}{|bottom|} = \frac{\sqrt{2}}{\sqrt{5}}$$

$$\angle H(j1) = \angle top - \angle bottom = 45^\circ - \tan^{-1}\left(\frac{2}{1}\right)$$

$$y_{ss} = -8H(0) + 9|H(j1)|\sin(t - 45^\circ + \angle H(j1))$$

MOTF

His found from circuit analysis

$$\text{poles} = -1 \pm j1$$

$$T = \frac{1}{|\text{Re pole}|} = \frac{1}{1} = 1$$

$$t_s = 5T = 5$$

$$|H(j1)| = \sqrt{2} e^{j45^\circ}$$

$$\frac{\sqrt{2}}{1} \angle 45^\circ$$

$$1+j2 = \sqrt{5} e^{j \tan^{-1}(2/1)}$$

Final Fall 2023

9/9