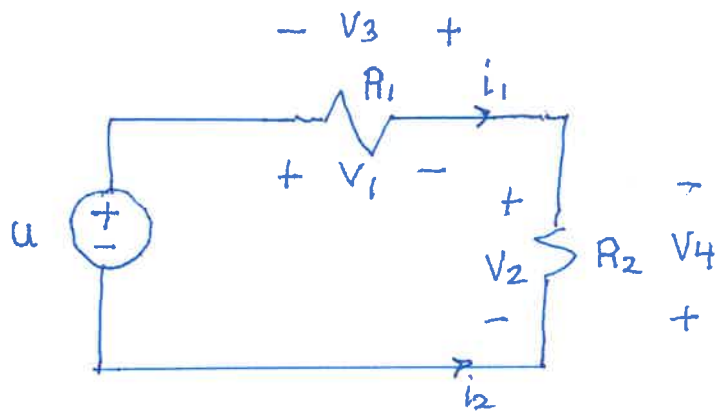


Everything Anyone Would Want 61 to Know About a Voltage Divider




Relate $V_{1,2,3,4}$, $i_{1,2}$ to the input u

I shall solve this many ways... to show you how KVL, KCL, & Ohm can be systematically applied to a ^{simple} circuit in many different ways!

Method


1

Find i_1 first

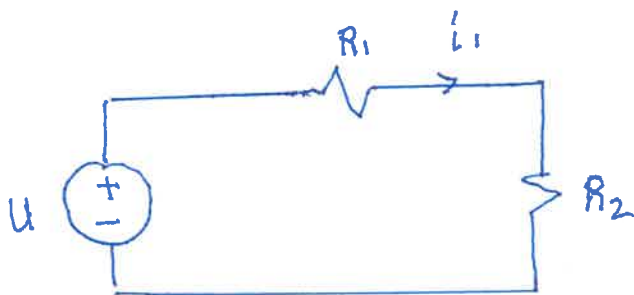

Lets relate i_1 to u . ($\exists R_1, R_2$)

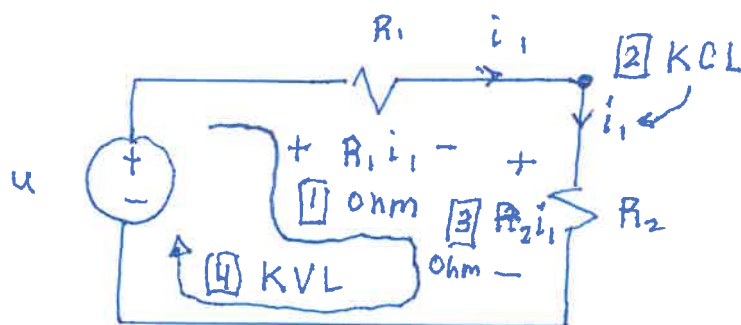
I shall label each step so that you can follow the step-by-step logic!



[4] KVL = $u = R_1 i_1 + R_2 i_1$
factor $i_1 \Rightarrow (R_1 + R_2) i_1$


$$\Rightarrow i_1 = \frac{u}{R_1 + R_2}$$

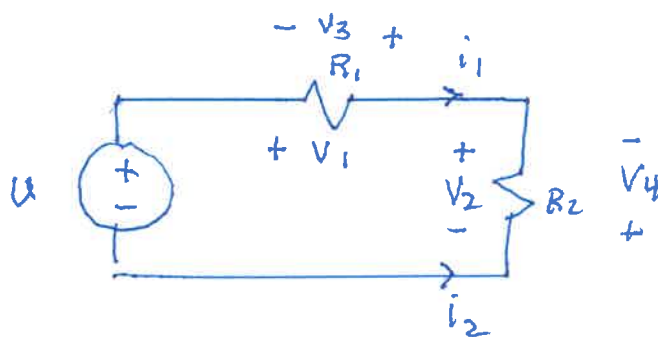Now that we have i_1 , let's find i_2 , $V_1, 2, 3, 4$ on the original circuit:



From KCL: $i_2 = -i_1 \Rightarrow i_2 = \frac{-u}{R_1 + R_2}$

Why?

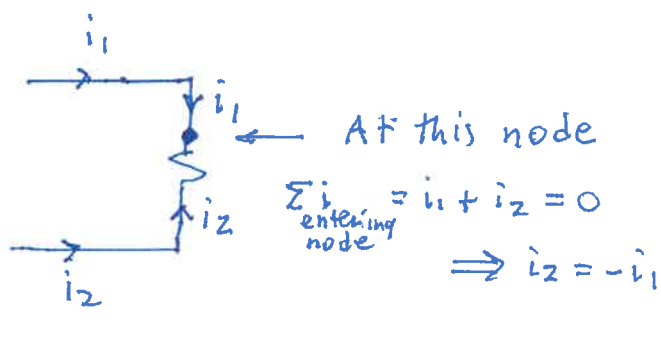

From the above:

$V_1 = R_1 i_1 \Rightarrow V_1 = \left(\frac{R_1}{R_1 + R_2} \right) u$


$V_2 = R_2 i_1 \Rightarrow V_2 = \left(\frac{R_2}{R_1 + R_2} \right) u$

Remember:
 These are referred to as the standard voltage divider formulae!
 Reasons matter!

KVL = $V_3 = -V_1 \Rightarrow V_3 = -\left(\frac{R_1}{R_1 + R_2} \right) u$
 $V_4 = -V_2$


$V_4 = -\left(\frac{R_2}{R_1 + R_2} \right) u$

2

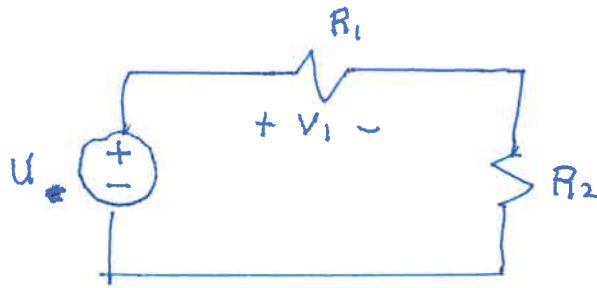Find V_1 first

Lets relate V_1 to u (R_1, R_2).

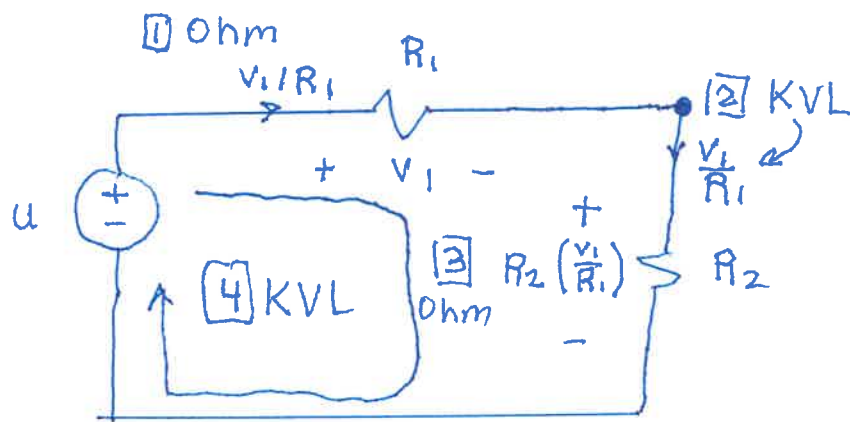I shall label each step so that you can follow the step-by-step logic!



Note:

Always Draw circuit "bigger" so that you can clearly label steps on the circuit!
 & see your work!

$$\boxed{4} \text{ KVL} = u = V_1 + R_2 \left(\frac{V_1}{R_1} \right)$$


$$\downarrow \text{factor out } V_1$$

$$= \left(1 + \frac{R_2}{R_1} \right) V_1$$

$$= \left(\frac{R_1 + R_2}{R_1} \right) V_1$$

$$\Rightarrow \boxed{V_1 = \left(\frac{R_1}{R_1 + R_2} \right) u}$$

Looking at the original circuit:

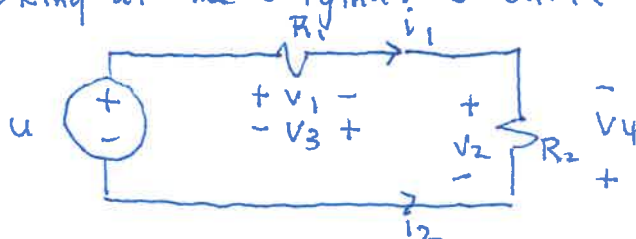

We have

$$\downarrow \text{ohm}$$

$$i_1 = \frac{V_1}{R_1}$$

$$\Rightarrow \boxed{i_1 = \frac{u}{R_1 + R_2}}$$

$$\text{KCL: } i_2 = -i_1 \Rightarrow$$

$$i_2 = \frac{-u}{R_1 + R_2}$$

$$\overset{\substack{\downarrow \text{ohm}}}{V_2 = R_2 i_1} \Rightarrow$$


$$V_2 = \left(\frac{R_2}{R_1 + R_2} \right) u$$

$$\text{KVL: } \begin{aligned} V_3 &= -V_1 \\ V_4 &= -V_2 \end{aligned} \Rightarrow$$

$$\begin{aligned} V_3 &= -\left(\frac{R_1}{R_1 + R_2} \right) u \\ V_4 &= -\left(\frac{R_2}{R_1 + R_2} \right) u \end{aligned}$$


Method 3

Find V_2 first

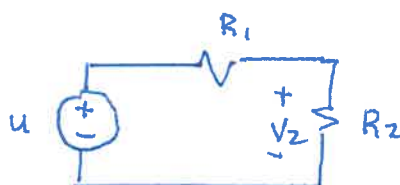

Let's relate V_2 to u (R_1, R_2).

I'll label my steps!

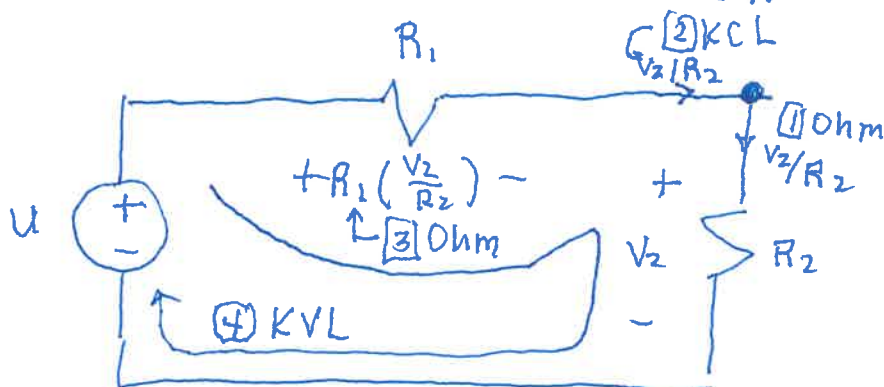

Note:


Always draw circuit "bigger" so that you can clearly label steps on the circuit & see your work!

$$\begin{aligned} \text{(4) KVL: } u &= R_1 \left(\frac{V_2}{R_2} \right) + V_2 \\ &\stackrel{\substack{\downarrow \text{factor out } V_2}}{=} \left(\frac{R_1}{R_2} + 1 \right) V_2 \end{aligned}$$

$$= \left(\frac{R_1 + R_2}{R_2} \right) V_2 \Rightarrow$$

$$V_2 = \left(\frac{R_2}{R_1 + R_2} \right) u$$

Looking at the original circuit:

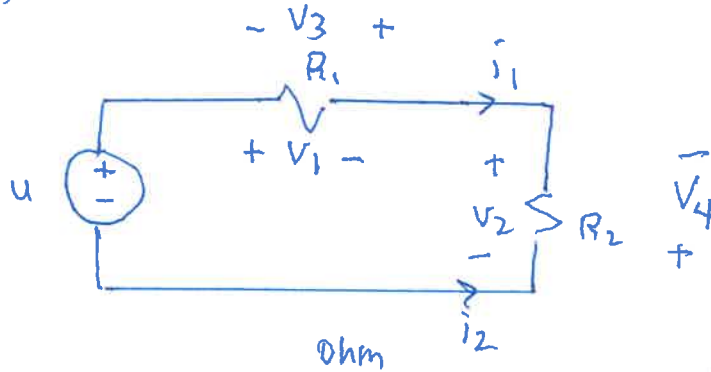

we have

$$i_1 \stackrel{\text{Ohm}}{=} \frac{V_2}{R_2} \Rightarrow$$

$$i_1 = \frac{u}{R_1 + R_2}$$

$$\text{KCL: } i_2 = -i_1 \Rightarrow$$

$$i_2 = \frac{-u}{R_1 + R_2}$$

$$V_1 \stackrel{\text{Ohm}}{=} R_1 i_1 \Rightarrow$$

$$V_1 = \left(\frac{R_1}{R_1 + R_2} \right) u$$

$$\text{KVL: } V_3 = -V_1$$

$$V_4 = -V_2$$

$$V_3 = - \left(\frac{R_1}{R_1 + R_2} \right) u$$

$$V_4 = - \left(\frac{R_2}{R_1 + R_2} \right) u$$

etc...