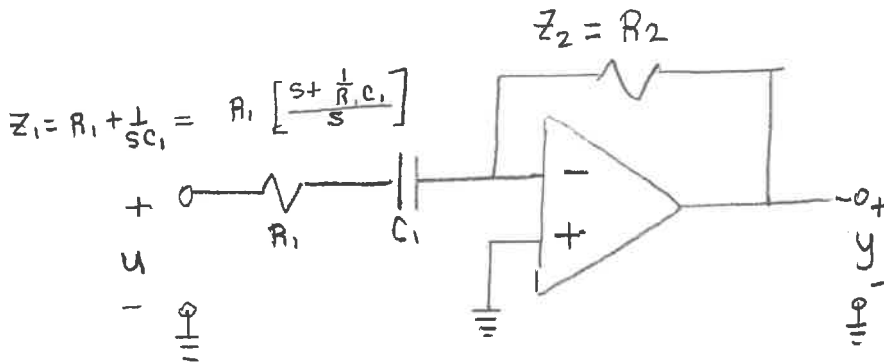


# Example 31

(HPF, LPF, BPF Via Op-Amp)

2040

## High Pass Filter (HPF)



Transfer function from u to y

$$H = \frac{y}{u} = -\left(\frac{Z_2}{Z_1}\right) = -\left[\frac{R_2}{R_1 \left[ \frac{s + \frac{1}{R_1 C_1}}{s} \right]}\right] \Rightarrow H(s) = -\left(\frac{R_2}{R_1}\right) \left[ \frac{s}{s + \frac{1}{R_1 C_1}} \right]$$

$$H(j\omega) = -\left(\frac{R_2}{R_1}\right) \left[ \frac{j\omega}{j\omega + \frac{1}{R_1 C_1}} \right]$$

$j\omega = \omega e^{j90^\circ}$

$\frac{1}{R_1 C_1}$

$\sqrt{\omega^2 + \left(\frac{1}{R_1 C_1}\right)^2}$

$\tan^{-1}\left(\frac{\omega}{\frac{1}{R_1 C_1}}\right)$

$\omega e^{j90^\circ}$

$\sqrt{\omega^2 + \left(\frac{1}{R_1 C_1}\right)^2} e^{j \tan^{-1}\left(\frac{\omega}{\frac{1}{R_1 C_1}}\right)}$

$= \left(\frac{R_2}{R_1}\right) e^{j180^\circ} \left[ \frac{\omega e^{j90^\circ}}{\sqrt{\omega^2 + \left(\frac{1}{R_1 C_1}\right)^2} e^{j \tan^{-1}\left(\frac{\omega}{\frac{1}{R_1 C_1}}\right)}} \right]$

$= \left(\frac{R_2}{R_1}\right) \omega \frac{e^{j(180+90 - \tan^{-1}(\frac{\omega}{\frac{1}{R_1 C_1}}))}}{\sqrt{\omega^2 + \left(\frac{1}{R_1 C_1}\right)^2}}$


Note:  
 $H \approx -R_2 C_1 s$  for small s  
 $H \approx -\frac{R_2}{R_1}$  for large s

Magnitude Response

$$|H(j\omega)| = \left(\frac{R_2}{R_1}\right) \left[ \frac{\omega}{\sqrt{\omega^2 + \left(\frac{1}{R_1 C_1}\right)^2}} \right]$$

$|H(j\infty)|$

$H$  is a High Pass Filter (HPF)

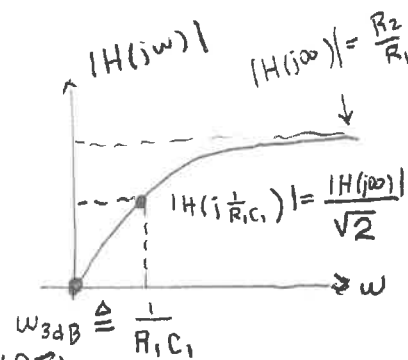


# Example 31

2050


$$\angle H(j\omega) = 270^\circ - \tan^{-1} \left( \frac{\omega}{\frac{1}{R_1 C_1}} \right)$$

Phase  
Response

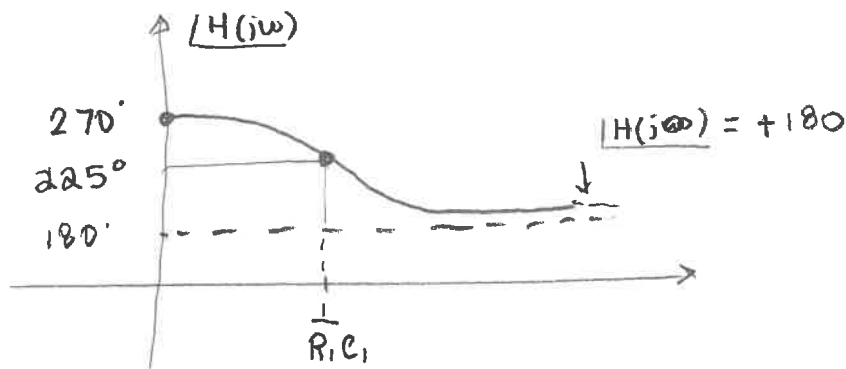

2

Low Pass Filter (LPF)

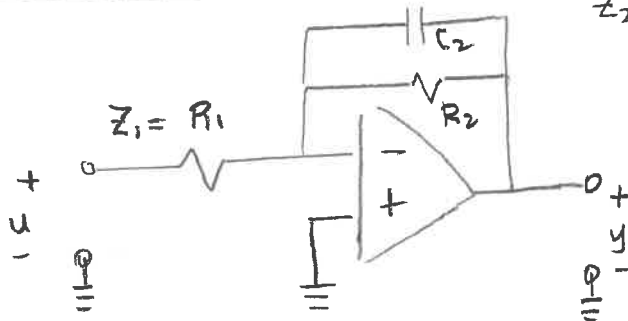

$$Z_2 = R_2 \parallel \frac{1}{sC_2} = \frac{\frac{R_2}{sC_2}}{R_2 + \frac{1}{sC_2}} = \frac{\frac{1}{C_2}}{s + \frac{1}{R_2 C_2}}$$

$$H = \frac{y}{u} = - \left( \frac{Z_2}{Z_1} \right) = - \left[ \frac{\frac{1}{C_2}}{s + \frac{1}{R_2 C_2}} \right] \frac{1}{R_1}$$

Transfer function from u to y

$$H(s) = - \left( \frac{R_2}{R_1} \right) \left[ \frac{\frac{1}{R_2 C_2}}{s + \frac{1}{R_2 C_2}} \right]$$

↑  
-H(0)

$$H(j\omega) = - \left( \frac{R_2}{R_1} \right) \left[ \frac{\frac{1}{R_2 C_2}}{j\omega + \frac{1}{R_2 C_2}} \right]$$

$$= \frac{\left( \frac{R_2}{R_1} \right) e^{j180^\circ} \left( \frac{1}{R_2 C_2} \right) e^{j0^\circ}}{\sqrt{\omega^2 + \left( \frac{1}{R_2 C_2} \right)^2} e^{j \tan^{-1} \left( \frac{\omega}{\frac{1}{R_2 C_2}} \right)}}$$


Note:  $H(s) \cong - \left( \frac{R_2}{R_1} \right)$   
for s small  
 $H(s) \cong - \frac{1}{R_1 C_2} \frac{1}{s}$   
for s large

# Example 31

2060

Magnitude Response


$$|H(j\omega)| = \left( \frac{R_2}{R_1} \right) \left[ \frac{\frac{1}{R_2 C_2}}{\sqrt{\omega^2 + \left( \frac{1}{R_2 C_2} \right)^2}} \right]$$

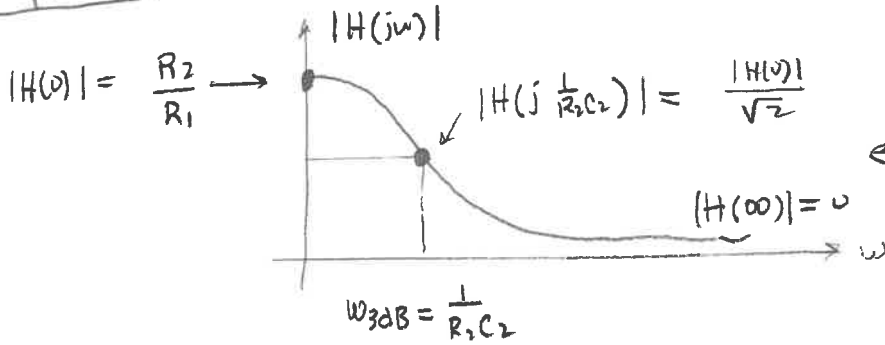

$\leftarrow H$  is a Low Pass Filter (LPF)


Phase Response
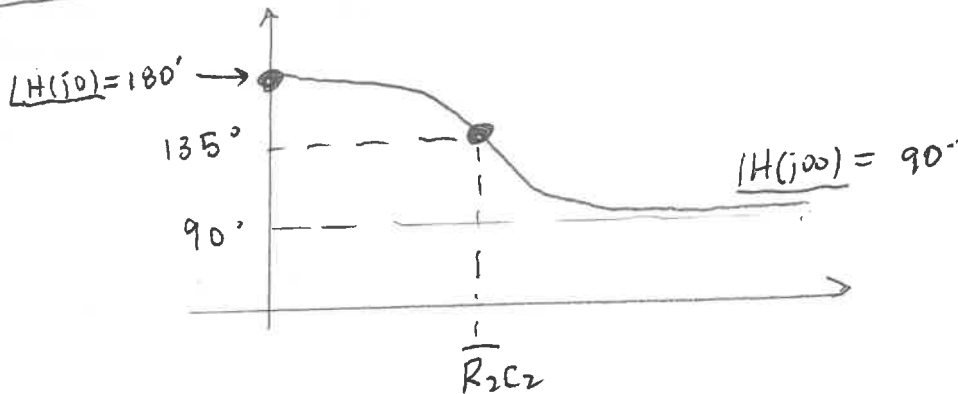
$$\angle H(j\omega) = 180^\circ - \tan^{-1} \left( \frac{\omega}{\frac{1}{R_2 C_2}} \right)$$



3 Band Pass Filter (BPF)

-HPF followed by a LPF

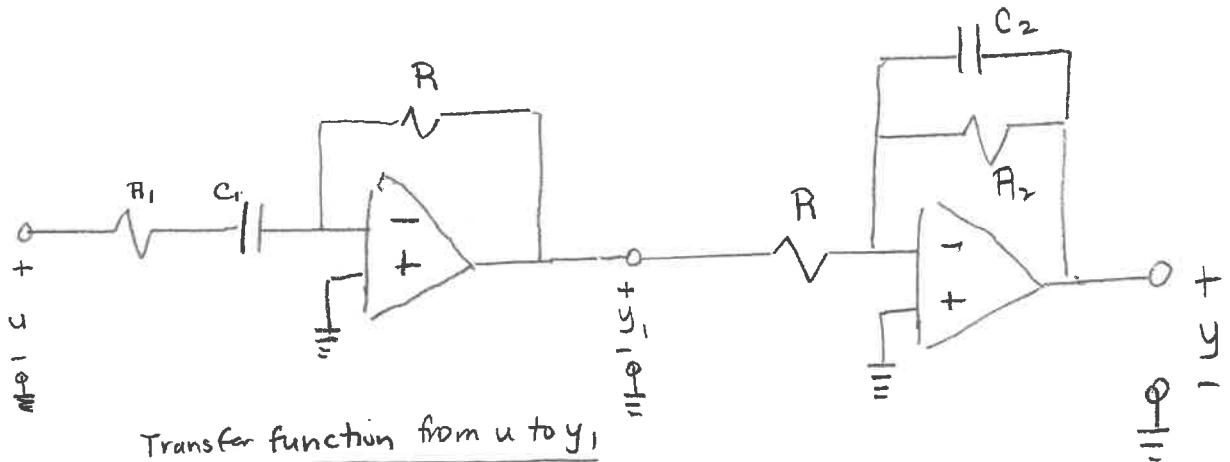

Transfer function from  $u$  to  $y_1$

$$y_1 = - \left( \frac{R}{R_1} \right) \left[ \frac{s}{s + \frac{1}{R_1 C_1}} \right] u$$

Assume:  $\frac{1}{R_1 C_1} \ll \frac{1}{R_2 C_2}$

$$y_2 = - \left( \frac{R_2}{R} \right) \left[ \frac{\frac{1}{R_2 C_2}}{s + \frac{1}{R_2 C_2}} \right] y_1 = \left( \frac{R_2}{R} \right) \left[ \frac{\frac{1}{R_2 C_2}}{s + \frac{1}{R_2 C_2}} \right] \left( \frac{R}{R_1} \right) \left[ \frac{s}{s + \frac{1}{R_1 C_1}} \right] u$$

Transfer function from  $y_1$  to  $y_2$


$$H(s) = \left[ \frac{s}{s + \frac{1}{R_1 C_1}} \right] \left( \frac{R_2}{R_1} \right) \left[ \frac{\frac{1}{R_2 C_2}}{s + \frac{1}{R_2 C_2}} \right]$$

$$H(j\omega) = \left[ \frac{j\omega}{j\omega + \frac{1}{R_1 C_1}} \right] \left( \frac{R_2}{R_1} \right) \left[ \frac{\frac{1}{R_2 C_2}}{j\omega + \frac{1}{R_2 C_2}} \right]$$

Transfer function from  $u$  to  $y$

Magnitude Response

$$|H(j\omega)| = \left[ \frac{\omega}{\sqrt{\omega^2 + \left( \frac{1}{R_1 C_1} \right)^2}} \right] \left( \frac{R_2}{R_1} \right) \left[ \frac{\frac{1}{R_2 C_2}}{\sqrt{\omega^2 + \left( \frac{1}{R_2 C_2} \right)^2}} \right]$$

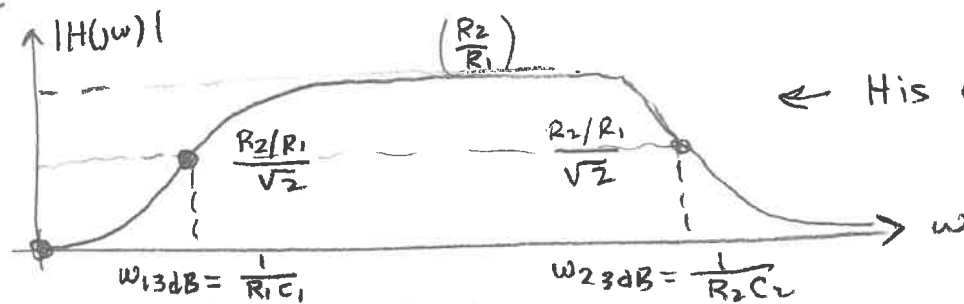

← This is a Band Pass Filter (BPF)


# Example 31

2080

Phase  
Response

$$\angle H(j\omega) = 90^\circ - \tan^{-1}\left(\frac{\omega}{\frac{1}{R_1 C_1}}\right) - \tan^{-1}\left(\frac{\omega}{\frac{1}{R_2 C_2}}\right)$$

$$\angle H(j0) = 90^\circ$$

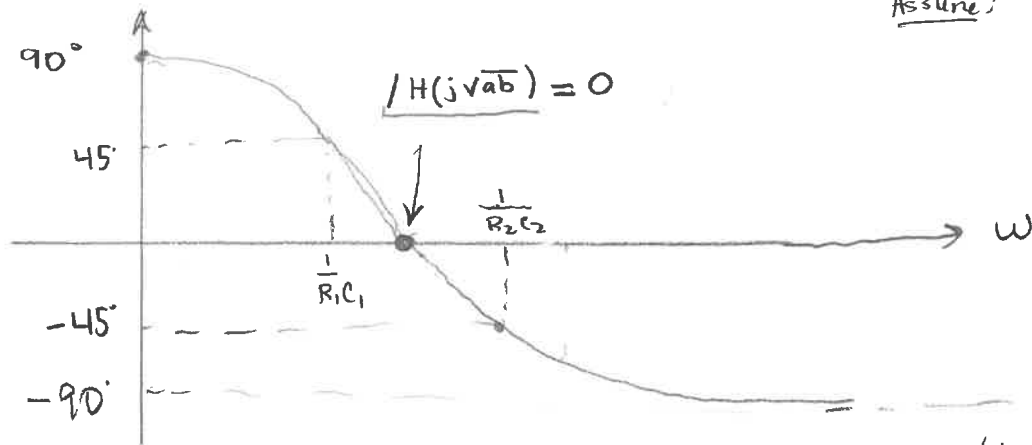

Assume:  $\frac{1}{R_1 C_1} \ll \frac{1}{R_2 C_2}$

$$\angle H(j\infty) = -90^\circ$$

Lets show  $\angle H(j\sqrt{ab}) = 0$

$$\text{Let } \theta(\omega) = \tan^{-1}\left(\frac{\omega}{a}\right) + \tan^{-1}\left(\frac{\omega}{b}\right)$$

$$\tan[\theta(\omega)] = \frac{\frac{\omega}{a} + \frac{\omega}{b}}{1 - \left(\frac{\omega^2}{ab}\right)} \Rightarrow$$

$$\tan(x+y) = \frac{\tan x + \tan y}{1 - \tan x \tan y}$$

$$\tan[\theta(\sqrt{ab})] = \frac{\sqrt{\frac{b}{a}} - \sqrt{\frac{a}{b}}}{1 - 1} = \frac{0}{0} = \infty$$

$$\Rightarrow \theta(\sqrt{ab}) = 90^\circ$$

$$\Rightarrow \angle H(j\sqrt{ab}) = 90 - 90 = 0^\circ$$



### Example 31

2090

Note:- The "Bode analyzer" software in the lab is designed to plot the

magnitude response  $|H(j\omega)|$   
= phase response  $\angle H(j\omega)$

versus frequency  $\omega$ .


Together,  
they are the  
frequency  
response  
of the  
system  $H$

Why are these important?

$|H(j\omega)|$  &  $\angle H(j\omega)$

are important because of  
the following

EXTREMELY IMPORTANT  
RESULT =

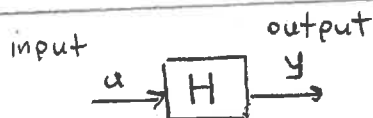

stable (all poles in LHP)  
i.e.  $\text{Re pole} < 0$

If

$$u(t) = A + B \sin(\omega_0 t + \Theta)$$

cos

then

$$y_{ss} = A H(0) + B |H(j\omega_0)| \sin(\omega_0 t + \Theta + \angle H(j\omega_0))$$

cos

↑  
steady state output

Problem 31

3000

For each of the following

- compute  $|H(j\omega)|$ ,  $\angle H(j\omega)$
- plot  $|H(j\omega)|$  &  $\angle H(j\omega)$  vs  $\omega$
- show how to construct  $H$  using op-amps & resistors.

$$[1] \quad H(s) = 100 \left[ \frac{s}{s+1} \right]$$

$$[2] \quad H(s) = 100 \left[ \frac{10^3}{s+10^3} \right]$$

$$[3] \quad H(s) = \left[ \frac{s}{s+1} \right] (100) \left[ \frac{10^3}{s+10^3} \right]$$