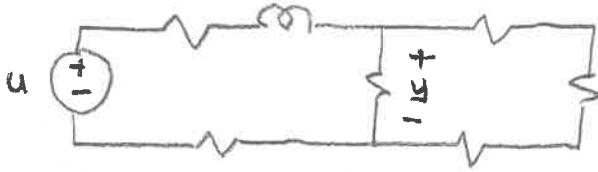


EXAM RULES

- 1) One 8.5" x 11" sheet permitted;
otherwise closed books, closed notes, open minds!
- 2) Scientific calculator is permitted; no computers and no phone!
- 3) **NO PHONES !!!**
Phones should not be visible at all!
A visible phone will result in a zero grade for the exam!
- 4) Write FULL NAME legibly on each page provided.
- 5) **PLEASE SHOW ALL WORK !!!**
This is essential to receive partial credit!
- 6) Please do not submit multiple answers. You must pick an answer!!
- 7) Write your solutions on the sheets provided.
No other paper/sheets/pages should be used!
- 8) Clearly label voltages and currents on the circuits provided.
- 9) Use the variables provided!
No additional variables should be used!
- 10) Unreadable work will receive NO CREDIT.
- 11) Please place important equations and answers within boxes as we have done in lecture.
- 12) Please be careful with your algebra, signs, etc.
- 13) Please turn in your solutions to me at the end of the period!
- 14) **PLEASE DO NOT CHEAT !!!**

Problem # 1

Determine H , diff. eq, t_s , y_{ss} , y , $\overset{\text{plot}}{|H(j\omega)|}$, $\angle H(j\omega)$
(All $R, L = 1$)




$$u = 11 + 11 \sin\left(\frac{1}{4}t\right)$$

Problem # 1

Problem # 2

Determine poles, t_s , $H_i(0)$, $H_i(\infty)$
($i=1,2$)

(All $R, L, C=1$)

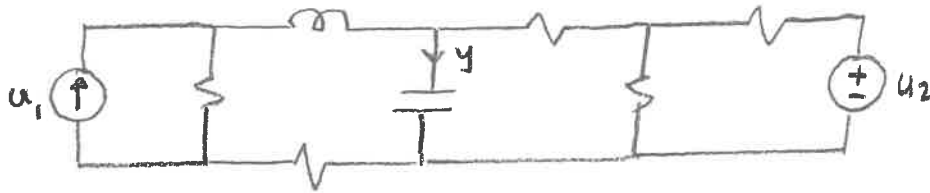


Problem #2

Problem # 3

Determine $H_{1,2}$, diff eq, t_s , y_{ss}

(All $R, L, C = 1$)

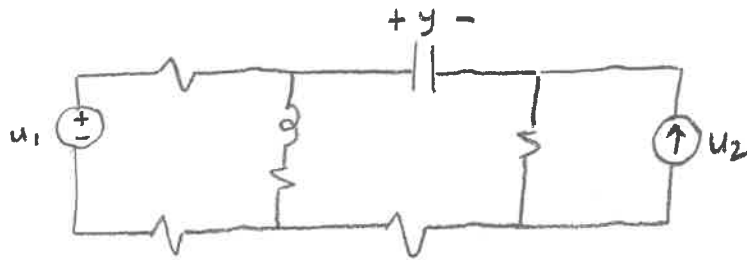

$$u_1 = 10 - \sin(t + 20^\circ)$$


$$u_2 = -3 + \cos(100t - 90^\circ)$$

Problem # 3

Problem #4

Determine H , diff eq, y , y_{ss}

(All $R, C=1$)

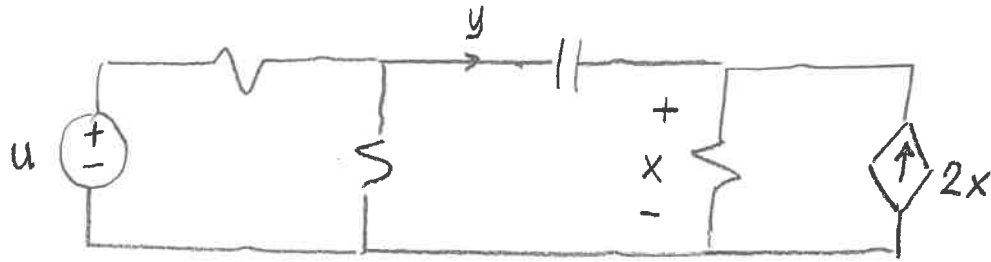

$$u = 4 + \sin 2t$$

Problem #4

Problem #5

Determine t_s , y_{ss} , y

$$H(s) = \frac{(s+0.01)(s^2+4)(s^2+64)}{(s+1)(s+2)(s^2+s+1)(s^2-4s+8)}$$

$$u = -10 + 2 \cos(0.01t - 45^\circ) + 3 \sin(2t + 20^\circ)$$

$$-4 \sin(8t - 24^\circ) + 5 \cos(100t + 90^\circ)$$

Note:-

Show how to compute all coefficients associated with constants, sinusoids, & instabilities in y


Problem # 5

Problem # 6

(All $R, L, C = 1$)

Determine an s-domain Thevenin equivalent at y

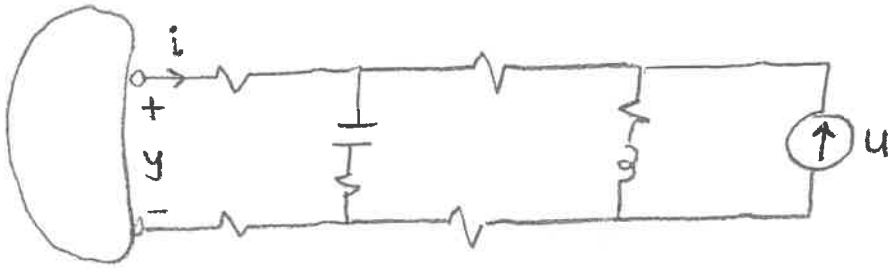(specify Z_{th} & V_{th} --- emphasize process ... not algebra!)



Problem # 6

Problem #7


Determine H , y_{ss} , t_s

Compute all coefficients in y_{ss} (approximately)!

Hint: poles are

$$-0.3522, -0.0239 \pm j0.8607$$

(all $R, L, C = 1$)

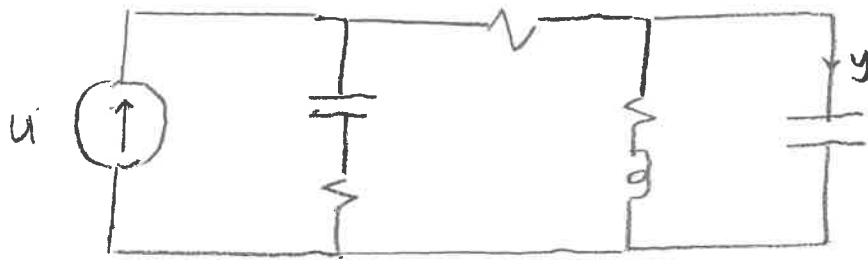


$$u = -7 + 100 \sin(0.01t - 90^\circ) - 2 \cos(100t - 5^\circ)$$

Problem # 7

Problem # 8

Determine & plot $|H(j\omega)| \approx \underline{|H(j\omega)|}$

(All $R, L, C = 1$)

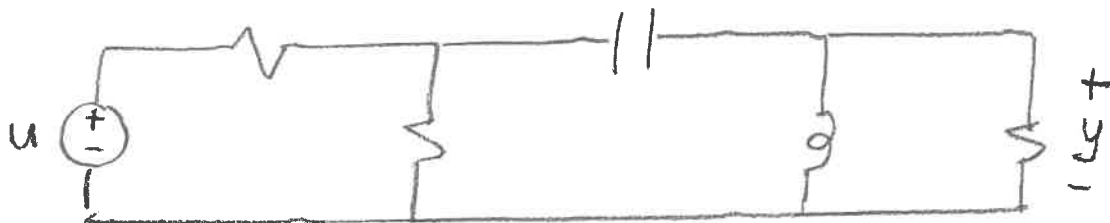


Problem # 8

Problem #1


Determine H , diff eq, t_s , y_{ss} , y , $|H(j\omega)|$, $\angle H(j\omega)$

(All $R, L = 1$)
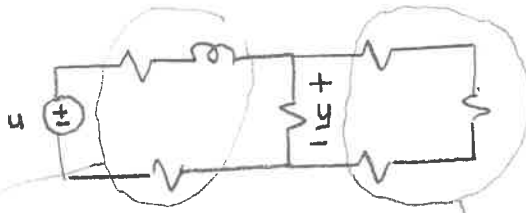
$$u(t) = 11 + 11 \sin\left(\frac{11}{4}t\right)$$



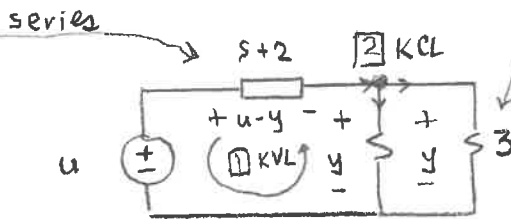Solution via Series combinations, KVL, KCL, Ohm



series \rightarrow \downarrow \rightarrow
[2] KCL =

$$\left(\frac{u-y}{s+2}\right) = (y) + \left(\frac{y}{s}\right)$$

$$\Rightarrow y \left[\frac{1}{s+2} + 1 + \frac{1}{s} \right] = \frac{u}{s+2}$$


$$\Rightarrow y \left[1 + \frac{4}{3}(s+2) \right] = u$$

$$\Rightarrow y \left[\frac{3}{4} + s + 2 \right] = \frac{3}{4}u$$

$$\Rightarrow H = \frac{y}{u} = \frac{\frac{3}{4}}{s + \frac{11}{4}}$$

$$H(j\omega) = \frac{\frac{3}{4}}{j\omega + \frac{11}{4}}$$


$$|H(j\omega)| = \frac{\frac{3}{4}}{\sqrt{\omega^2 + \left(\frac{11}{4}\right)^2}}$$

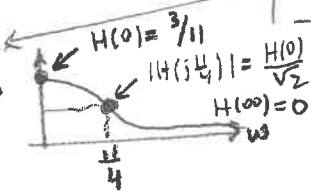

$$\dot{y} + \frac{11}{4}y = \frac{3}{4}u$$

$$\Phi = s + \frac{11}{4} = 0 \Rightarrow \text{pole at } s = -\frac{11}{4}$$
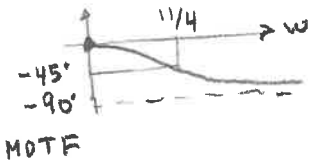
$$\angle H(j\omega) = \angle \text{top} - \angle \text{bottom} = 0 - \tan^{-1}\left(\frac{\omega}{11/4}\right)$$



pole in LHP \Rightarrow system stable

$$t_s = \frac{5}{|\text{pole}|} = \frac{5}{11/4} = \frac{20}{11} \text{ sec}$$

$$y_{ss} = 11 H(0) + 11 |H(j\frac{11}{4})| \sin\left(\frac{11}{4}t + \angle H(j\frac{11}{4})\right)$$

$$H(0) = \frac{3}{11} \quad H(j\frac{11}{4}) = \frac{\frac{3}{4}}{j\frac{11}{4} + \frac{11}{4}} = \frac{3/11}{1+j1} = \frac{3}{11\sqrt{2}} e^{j(-45^\circ)}$$

Find y

$$U(s) = \frac{11}{s} + 11 \left[\frac{\frac{11/4}{s^2 + (\frac{11}{4})^2}}{s} \right] = \frac{11(s^2 + (\frac{11}{4})^2) + 11(\frac{11}{4})s}{s(s^2 + (\frac{11}{4})^2)}$$

$$Y(s) = H(s)U(s) = \left(\frac{\frac{3}{4}}{s + \frac{11}{4}}\right) \left(\frac{\text{num}}{s(s^2 + (\frac{11}{4})^2)}\right) = \frac{A}{s} + \frac{B}{s + \frac{11}{4}} + \frac{C}{s - j\frac{11}{4}} + *$$

$$\Rightarrow y = A + B e^{-\frac{11}{4}t} + 2|C| \cos\left(\frac{11}{4}t + \angle C\right)$$

$$2|C| \sin\left(\frac{11}{4}t + \angle C + 90^\circ\right)$$



$$\Rightarrow A = \lim_{s \rightarrow 0} s Y(s) = 11 H(0) \quad B = \lim_{s \rightarrow -\frac{11}{4}} (s + \frac{11}{4}) Y(s)$$

$$C = \lim_{s \rightarrow j\frac{11}{4}} (s - j\frac{11}{4}) Y(s) = \frac{11 H(j\frac{11}{4})}{2} e^{j(\angle H(j\frac{11}{4}) - 90^\circ)}$$

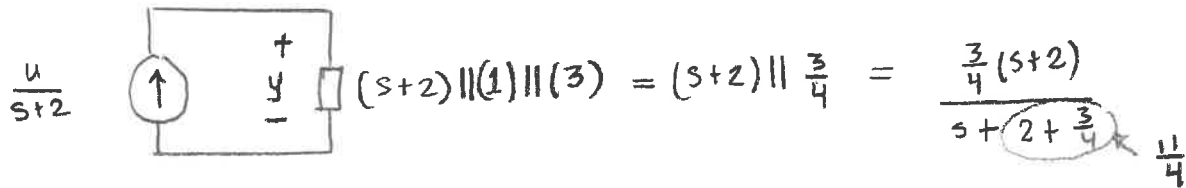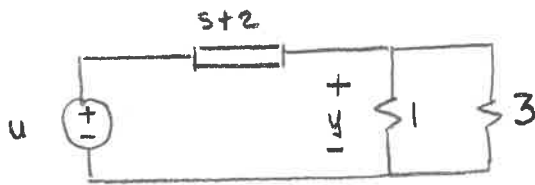Problem # 1

EEF 202 Fall 2024 Exam #2 Fri 12-6-24

Solution via series-parallel & source transf




$$\Rightarrow y = \left[\frac{\frac{3}{4}(s+2)}{s + \frac{11}{4}} \right] \frac{u}{s+2}$$

$$\Rightarrow H(s) = \frac{y}{u} = \frac{\frac{3}{4}}{s + \frac{11}{4}}$$

... just as before!


Pole Check (No KVL, KCL, Ohm)

Set $u=0$

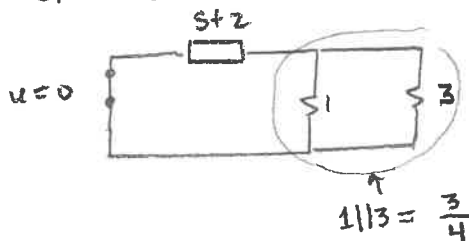


$$\begin{aligned} Z_1 &= s+2 + \frac{3}{4} \quad \text{(characteristic eq)} \\ &= s + \frac{11}{4} \\ &= 0 \Rightarrow \text{pole} = -\frac{11}{4} \checkmark \end{aligned}$$

Analysis at $s=0$

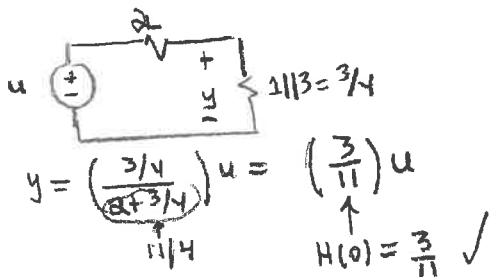


Analysis at $s=\infty$

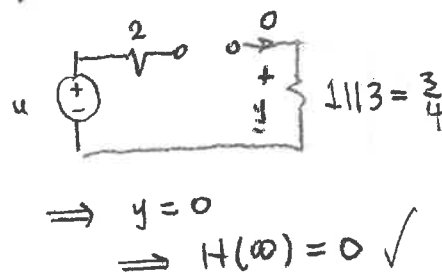

Problem #2


Determine poles, t_s , $H_1(s)$, $H_2(s)$

(All $R=L=C=1$)

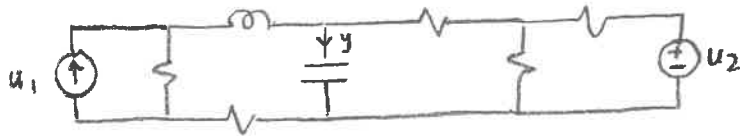

poles, t_s


Set $u_1 = 0$, $u_2 = 0$

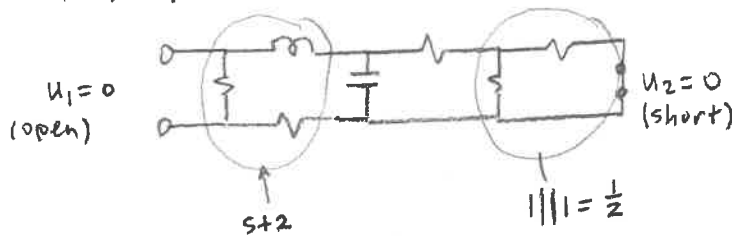

$$\Rightarrow (s+2) \parallel \frac{1}{2} = \frac{s+2}{s+2+\frac{1}{2}} = \frac{s+2}{s^2+2s+1}$$

Analysis at $s=0$

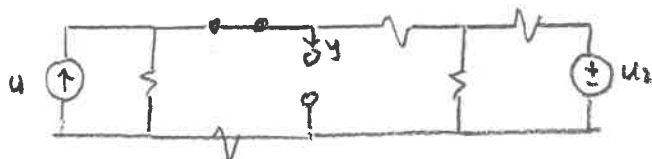$Z_L = sL = 0$ (short)
 $Z_C = \frac{1}{sC} = \infty$ (open)



$$\Rightarrow y = 0 = 0u_1 + 0u_2$$

$$\Rightarrow H_1(0) = H_2(0) = 0$$

$$Z = \frac{s+2}{s^2+2s+1} + \frac{3}{2}$$

$$= \frac{s+2 + \frac{3}{2}(s^2+2s+1)}{s^2+2s+1} = \frac{s^2 + \frac{8}{3}s + \frac{7}{3}}{s^2+2s+1}$$

$$= \frac{\frac{2}{3}s + \frac{4}{3} + s^2+2s+1}{s^2+2s+1}$$

$$\Phi = s^2 + \frac{8}{3}s + \frac{7}{3} = 0$$

$$s_{1,2} = \frac{-\frac{8}{3} \pm \sqrt{\frac{64}{9} - \frac{28}{3}}}{2(1)}$$

$$= -\frac{8}{6} \pm \sqrt{\frac{16}{9} - \frac{7}{3}} = -\frac{4}{3} \pm j\frac{\sqrt{5}}{3}$$


$$= -\frac{4}{3} \pm j\frac{\sqrt{5}}{3}$$

stable

$$t_s = \frac{5}{|\text{Re poles}|} = \frac{5}{\frac{4}{3}} = \frac{15}{4} \text{ sec}$$

Analysis at $s=\infty$

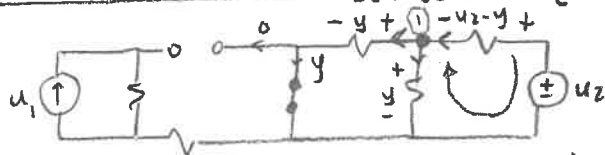$Z_L = sL = \infty$ (open)
 $Z_C = \frac{1}{sC} = 0$ (short)



u_1 has no impact on y !
(only u_2 does!)

$$\textcircled{1} \text{KCL} = u_2 - y = y + y$$

$$\Rightarrow 3y = u_2$$


$$\Rightarrow y = 0u_1 + \left(\frac{1}{3}\right)u_2$$

$$H_1(\infty) = 0 \quad H_2(\infty) = \frac{1}{3}$$

Problem #2

Solution via source transformations

(All $R, L, C = 1$)

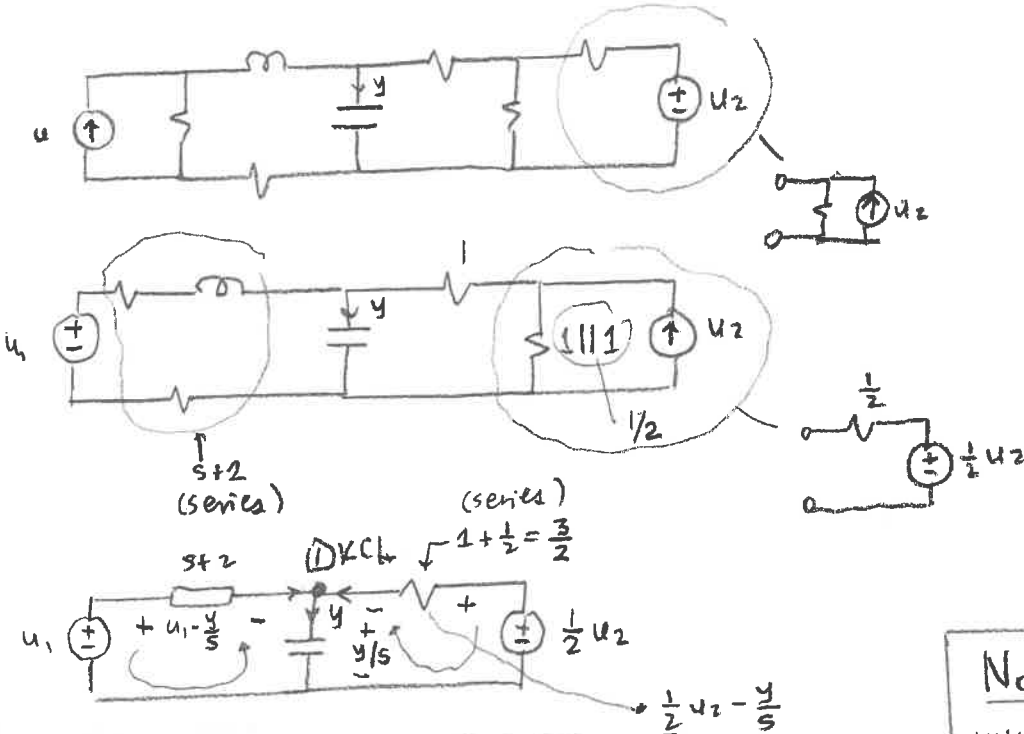

VERY IMPORTANT!

Note:

Without source transformations or some other trick (e.g. Thevenin equiv), we would NEED to INTRODUCE ANOTHER VARIABLE! (to solve the problem)

$$\textcircled{1} \text{ KCL} = \left(\frac{u_1 - \frac{y}{s}}{s+2} \right) + \left(\frac{\frac{1}{2}u_2 - \frac{y}{s}}{\frac{3}{2}} \right) = y$$

$$\Rightarrow y \left[\frac{1/s}{s+2} + \frac{2/3}{s} + 1 \right] = \frac{u_1}{s+2} + \frac{u_2}{3}$$

$$\Rightarrow y \left[1 + \frac{2}{3}(s+2) + s(s+2) \right] = s u_1 + \frac{1}{3}s(s+2)u_2$$

$$s^2 + (2 + \frac{2}{3})s + 1 + \frac{4}{3}$$

$$s^2 + \frac{8}{3}s + \frac{7}{3}$$

$$y = \left[\frac{s}{s^2 + \frac{8}{3}s + \frac{7}{3}} \right] u_1 + \left[\frac{\frac{1}{3}s(s+2)}{s^2 + \frac{8}{3}s + \frac{7}{3}} \right] u_2$$

$\uparrow H_1$ $\uparrow H_2$

Note: Same characteristic eq as before! --- $\Phi(s) = s^2 + \frac{8}{3}s + \frac{7}{3}$


$H_1(0) = H_2(0) = 0$ --- same as before!

$H_1(\infty) = 0$ $H_2(\infty) = \frac{1}{3}$ --- same as before!



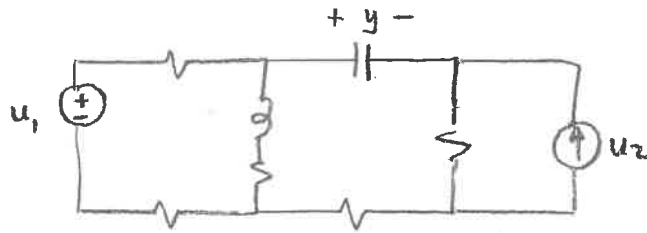Problem #3

Determine $H_{1,2}$, diff eq, ts, yss (All R, L, C=1)



$$u_1 = 10 \sin(t + 20^\circ)$$

$$u_2 = -3 + \cos(100t - 90^\circ)$$

solution:

Can 1st determine yss via MDTF!

(we know circuit will be stable since it consists of R, L, C & indep sources

... for a circuit to be unstable

it is necessary to have dependent sources !!!)

Necessary but NOT sufficient!

linearity (superposition)

$$y_{ss} = y_{1ss} + y_{2ss}$$



MDTF

$$y_{1ss} = 10 H_1(0) - |H_1(j1)| \sin(t + 20^\circ + \angle H_1(j1))$$

MDTF

$$y_{2ss} = -3 H_2(0) + |H_2(j100)| \cos(100t - 90^\circ + \angle H_2(j100))$$

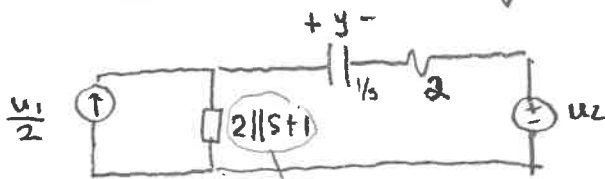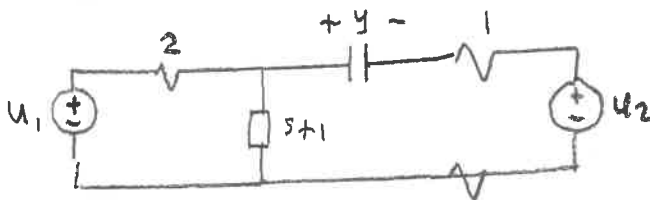solution via series-parallel & source transformations



$$\text{KVL} = \left(\frac{s+1}{s+3} \right) u_1 = \left[\frac{2(s+1)}{s+3} \right] sy + y + 2sy + u_2$$

$$\left(\frac{s+1}{s+3} \right) u_1 \Rightarrow y \left[\frac{2s(s+1)}{s+3} + 1 + 2s \right] = \left[\frac{s+1}{s+3} \right] u_1 - u_2$$

$$\Rightarrow y [2s(s+1) + s+3 + 2s^2 + 6s] = (s+1)u_1 - (s+3)u_2$$

$$4s^2 + 9s + 3 = 4 \left[s^2 + \frac{9}{4}s + \frac{3}{4} \right]$$

diff eq =

$$\ddot{y} + \frac{9}{4}\dot{y} + \frac{3}{4}y = \frac{1}{4}(\dot{u}_1 + u_1) - \frac{1}{4}(\dot{u}_2 + 3u_2)$$

$$y = \left[\frac{\frac{1}{4}(s+1)}{s^2 + \frac{9}{4}s + \frac{3}{4}} \right] u_1 + \left[\frac{-\frac{1}{4}(s+3)}{s^2 + \frac{9}{4}s + \frac{3}{4}} \right] u_2$$

H_1

H_2

517


Problem #3

poles
↓

$$\Phi = s^2 + \frac{9}{4}s + \frac{3}{4} = 0 \Rightarrow s_{1,2} = \frac{-\frac{9}{4} \pm \sqrt{\frac{81}{16} - 3}}{2}$$

$$= \frac{-\frac{9}{4} \pm \sqrt{\frac{81}{64} - \frac{3}{4}}}{2} = \frac{-\frac{9}{4} \pm \sqrt{\frac{81}{64} - \frac{48}{64}}}{2} = \frac{-\frac{9}{4} \pm \sqrt{\frac{33}{64}}}{2}$$
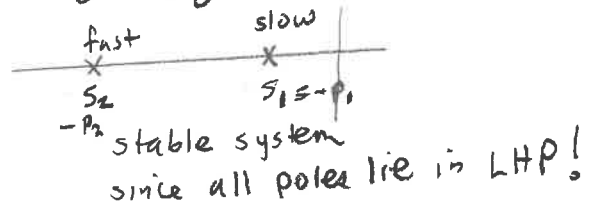
$$= \frac{-\frac{9}{4} \pm \frac{\sqrt{33}}{8}}{2} = -\frac{9}{8} \pm \frac{\sqrt{33}}{8}$$



$$t_s = \frac{5}{1.911} = \frac{5}{\frac{9}{8} - \frac{\sqrt{33}}{8}} = \frac{5}{\frac{9 - \sqrt{33}}{8}}$$

Gains for y_{1ss}, y_{2ss}

$$H_1 = \frac{\frac{1}{4}(s+1)}{s^2 + \frac{9}{4}s + \frac{3}{4}}$$

$$H_1(0) = \frac{1/4}{3/4} = \frac{1}{3}$$

$$H_1(j\omega) = \frac{\frac{1}{4}(j\omega+1)}{\frac{1}{4}\omega^2 + j\frac{9}{4}\omega + \frac{3}{4}} = \frac{\frac{1}{4}\sqrt{2}e^{j45^\circ}}{\frac{1}{4}\sqrt{9^2+1}e^{j(180-\tan^{-1}(9))}} = \frac{\sqrt{2}}{\sqrt{82}}e^{j(45^\circ-180+\tan^{-1}(9))}$$

Needed in y_{1ss}


$$H_2 = \frac{-\frac{1}{4}(s+3)}{s^2 + \frac{9}{4}s + \frac{3}{4}}$$

$$H_2(0) = \frac{-1/4}{3/4} = -\frac{1}{3}$$

$$H_2(j100) \approx \frac{-1/4}{s} \Big|_{s=100} e^{j90^\circ} = \frac{1}{100} e^{j90^\circ} = \frac{1}{400} e^{j(90^\circ)}$$

Needed in y_{2ss}

check poles = $s_1 + u_1 = 0, u_2 = 0$

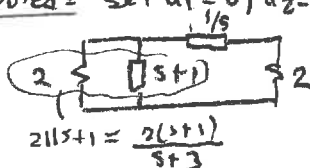

$$\Rightarrow Z = \frac{2(s+1)}{s+3} + \frac{1}{s} + 2 = \frac{2s^2+2s+s+3+2s^2+6s}{s(s+3)}$$

$$\Rightarrow \Phi = s^2 + \frac{9}{4}s + \frac{3}{4} \text{ (same as before!)} \\ \dots \text{hence same poles \& } t_s!$$


Problem #3

EEE202 Fall 2024 Exam #2 Fri 12-6-24

check gains =

Analysis at $s=0$

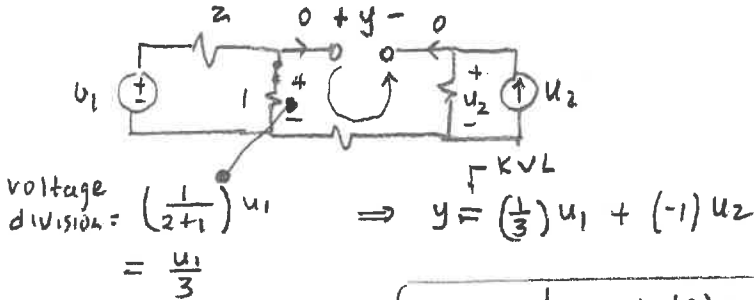$Z_L = sL = 0$ (short)
 $Z_C = \frac{1}{sC} = \infty$ (open)



$H_1(0) = \frac{1}{3} \quad H_2(0) = -1$ ← Gains Agree with

$$H_1 = \frac{\frac{1}{4}(s+1)}{s^2 + \frac{3}{4}s + \frac{3}{4}}$$

$$H_2 = \frac{-\frac{1}{4}(s+3)}{s^2 + \frac{3}{4}s + \frac{3}{4}}$$

Analysis at $s=\infty$

$Z_L = sL = \infty$ (open)
 $Z_C = \frac{1}{sC} = 0$ (short)

$\Rightarrow y = 0u_1 + 0u_2$

$H_1(\infty) = H_2(\infty) = 0$ ← Gains Agree with

Lets find form of y ... for the hell of it! 😊

$U_1 = \frac{10}{s} + \frac{\text{num } 1}{s(s^2+1)} \quad U_2 = \frac{-3}{s} + \frac{\text{num } 2}{s(s^2+104)}$

$Y = H_1 U_1 + H_2 U_2 = \left[\frac{\frac{1}{4}(s+1)}{(s+p_1)(s+p_2)} \right] \left[\frac{\text{num } 1}{s(s^2+1)} \right] + \left[\frac{-\frac{1}{4}(s+3)}{(s+p_1)(s+p_2)} \right] \left[\frac{\text{num } 2}{s(s^2+104)} \right]$

$= \frac{A}{s} + \frac{B}{s+p_1} + \frac{C}{s+p_2} + \frac{D}{s-j1} + \frac{E}{s} + \frac{F}{s+p_1} + \frac{G}{s+p_2} + \frac{H}{s-j100} + \dots$

$y = y_1 + y_2$

$y_1 = A + Be^{-p_1 t} + Ce^{-p_2 t} + 2|D| \cos(t + \angle D)$

$y_2 = E + Fe^{-p_1 t} + Ge^{-p_2 t} + 2|H| \cos(100t + \angle H)$

$-2|D| \cos(t + \angle D - 180^\circ) = -2|D| \sin(t + \angle D - 180^\circ + 90^\circ)$

y_{ss}

$A = \lim_{s \rightarrow 0} s Y_1(s) = 10 H_1(0)$

$D = \lim_{s \rightarrow j1} j(s-j1) Y_1(s) = \frac{|H_1(j1)|}{2} e^{j(20^\circ + |H_1(j1)| + 180 - 90^\circ)}$


$E = \lim_{s \rightarrow 0} s Y_2(s) = -3 H_2(0)$

$H = \lim_{s \rightarrow j100} (s-j100) Y_2(s) = \frac{|H_2(j100)|}{2} e^{j(-90^\circ + |H_2(j100)|)}$

Problem #4

Determine H , diff eq, y , y_{ss}


(All $R, C = 1$)

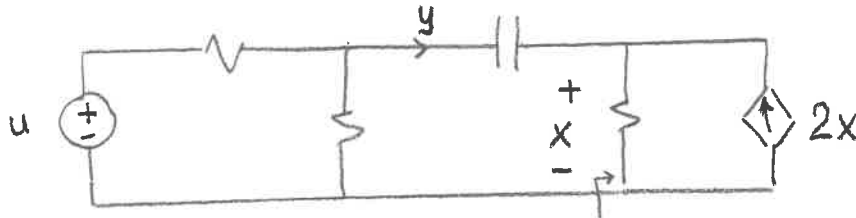



Hint: Find R_{th}

$u = 4 + \sin 2t$

solution using hint (finding R_{th})

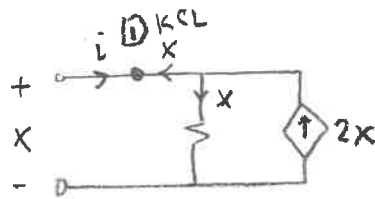

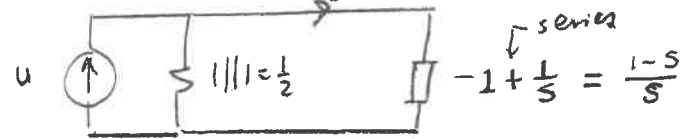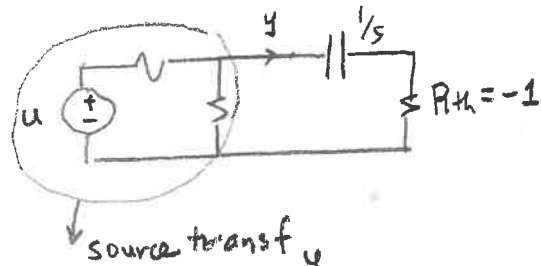① KCL: $i = -x$
 $x = -i \Rightarrow R_{th} = -1$



Current Division:

$$y = \left[\frac{\frac{1}{2}}{\frac{1}{2} + \frac{1-s}{s}} \right] u = \left[\frac{\frac{1}{2}s}{\frac{1}{2}s + 1 - s} \right] u$$

$$= \left[\frac{s}{2-s} \right] u$$

MOTF:

component of y that can be computed using MOTF

$H(0) = 0$

$$H(j2) = \frac{-j2}{j2-2} = \frac{2e^{j(-90^\circ)}}{2\sqrt{2}e^{j135^\circ}} = \frac{1}{\sqrt{2}}e^{j(-90-135^\circ)} = \frac{1}{\sqrt{2}}e^{j(-225^\circ)}$$

Note:

The following is also correct:

$$H(j2) = \frac{j1}{1-j1} = \frac{1e^{j90^\circ}}{\sqrt{2}e^{-j45^\circ}} = \frac{1}{\sqrt{2}}e^{j(90+45^\circ)} = \frac{1}{\sqrt{2}}e^{j135^\circ}$$

$H = \frac{y}{u} = \frac{-s}{s-2}$

$\hookrightarrow \dot{y} - 2y = -u$

$\Phi = s-2 = 0 \Rightarrow s=2$ pole in RHP \Rightarrow unstable system

$U(s) = \frac{4}{s} + \frac{2}{s^2+4} = \frac{4s^2+2s+16}{s(s^2+4)}$

... lets now find $y(t)$...

Problem #4

EEE 202 Fall 2024 Exam #2 Fri 12-6-24

$$Y(s) = H(s)U(s) = \left[\frac{-5}{s-2} \right] \left[\frac{\text{num}}{s(s^2+4)} \right] = \frac{A}{s} + \frac{B}{s-2} + \frac{C}{s-j2} + *$$

$$\Rightarrow y = A + B e^{2t} + 2|C| \cos(2t + \angle C)$$

y_{MOTF} \uparrow unstable y_{ss} $2|C| \sin(2t + \angle C + 90^\circ)$

$$A = \lim_{s \rightarrow 0} s Y(s) = 4 H(0)$$

$$C = \lim_{s \rightarrow j2} (s-j2) Y(s) = \frac{|H(j2)|}{2} e^{j(\angle H(j2) - 90^\circ)}$$

$$B = \lim_{s \rightarrow 2} (s-2) Y(s)$$


$$= -s \left[\frac{4s^2 + 2s + 16}{s(s^2+4)} \right] \Big|_{s=2}$$

$$= -2 \left[\frac{4(4) - 4 + 16}{(-2)(4+4)} \right]$$

$$= \frac{28}{8} = \frac{7}{2}$$

$$B = 3.5$$

Solution via KVL, KCL, Ohm

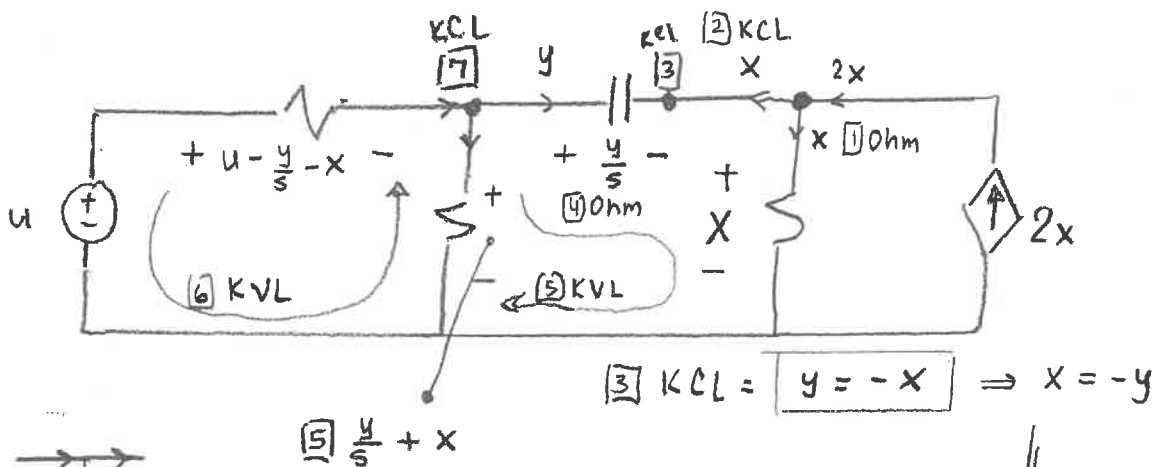

$$(7) \text{ KCL: } (u - \frac{y}{s} - x) = (\frac{y}{s} + x) + y$$

$$\Rightarrow u = \frac{y}{s} + \frac{x}{-y} + \frac{y}{s} + \frac{x}{-y} + y$$

$$= y \left[\frac{1}{s} - 1 + \frac{1}{s} - 1 + 1 \right]$$

$$= y \left[\frac{2}{s} - 1 \right]$$

$$= y \left[\frac{2-s}{s} \right]$$

$$\Rightarrow H = \frac{y}{u} = \frac{-s}{s-2}$$

917

as obtained earlier! 😊


Problem #4

EEE 202 Fall 2024 Exam #2

Fri 12-6-24

pole check: (use $R_{th} = -1$)

set $u = 0$

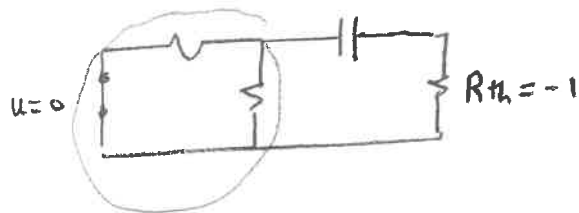


$$1 \parallel \frac{1}{s} \Rightarrow Z = \frac{1}{\frac{1}{2} + \frac{1}{s} - 1} = \frac{1}{\frac{1}{s} - \frac{1}{2}} = \frac{1 - \frac{1}{2}s}{s} = -\frac{1}{2} \frac{(s-2)}{s}$$

$\Rightarrow \Phi = s-2$
as we obtained earlier! 😊

Gain Checks: (I'll use $R_{th} = -1$)

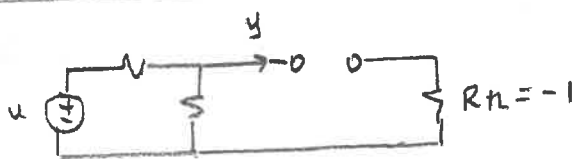
Analysis at $s=0$ $Z_C = \frac{1}{sC} = \infty$ (open)



$$\Rightarrow y = 0 = 0u$$

$\Rightarrow H(0) = 0 \leftarrow$ Agree with our $H(s) = \frac{-s}{s-2}$ 😊

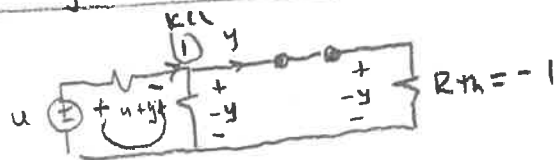Analysis at $s=\infty$ $Z_C = \frac{1}{sC} = 0$ (short)



$$\text{KCL: } u + y = (-y) + y$$

$$\Rightarrow y = -u$$

$\Rightarrow H(\infty) = -1 \leftarrow$ Agree with

— IT'S ALWAYS GOOD TO

PERFORM THE ABOVE CHECKS!

10/17


Problem #5

Determine t_s , y_{ss} , y

Note: Show how to
 Compute all coefficients
 associated with constants &
 sinusoids & instabilities in y

$$H(s) = \frac{(s+0.01)(s^2+4)(s^2+64)}{(s+1)(s+2)(s^2+s+1)(s^2-4s+8)}$$

solution:

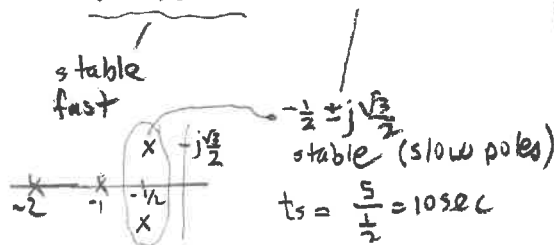

$$u = -10 + 2\cos(0.01t - 45^\circ) + 3\sin(2t + 20^\circ) - 4\sin(8t - 24^\circ) + 5\cos(100t + 90^\circ)$$

$2 \pm j2$
unstable!

component of y that can be computed using MOTF!

$$y_{\text{MOTF}} = -10H(0) + 2|H(j0.01)|\cos(0.01t - 45^\circ + \angle H(j0.01))$$

$$+ 3|H(j2)|\sin(2t + 20^\circ + \angle H(j2))$$

zero since
 $H(j2) = 0$

$$- 4|H(j8)|\sin(8t - 24^\circ + \angle H(j8))$$

zero since
 $H(j8) = 0$

$$+ 5|H(j100)|\cos(100t + 90^\circ + \angle H(j100))$$

$$H(0) = \frac{(0.01)(4)(64)}{(1)(2)(1)(8)}$$

$$H(j0.01) \cong \frac{(s+0.01)(4)(64)}{(1)(2)(1)(8)} \bigg|_{s=j0.01} = M(0.01)(1+j1)$$

$$= \underset{\uparrow}{0.01M\sqrt{2}} e^{j45^\circ}$$

\uparrow $|H(j0.01)|$ \quad $\angle H(j0.01)$

$H(j2) = H(j8) = 0$ as stated above

$$H(j100) \cong \frac{s^5}{s^6} \bigg|_{s=j100} = \frac{1}{s} \bigg|_{s=100e^{j90^\circ}} = \frac{1}{100e^{j90^\circ}} = \underset{\uparrow}{0.01} e^{j(-90^\circ)}$$

\uparrow $|H(j100)|$ \quad $\angle H(j100)$

... Now let's find y (the form of y !!!)

11	17
----	----

Problem # 5

EEE 202 Fall 2024 Exam #2

Fri 12-6-24

$$U(s) = \frac{-10}{s} + \frac{1}{s^2 + 10^{-4}} + \frac{1}{s^2 + 4} + \frac{1}{s^2 + 64} + \frac{1}{s^2 + 104}$$

$$= \frac{\text{num}}{s(s^2 + 10^{-4})(s^2 + 4)(s^2 + 64)(s^2 + 104)}$$

$$Y(s) = H(s)U(s) = \left[\frac{(s+0.01)(s^2+4)(s^2+64)}{(s+1)(s+2)(s^2+s+1)(s^2-4s+8)} \right] \left[\frac{\text{num}}{s(s^2+10^{-4})(s^2+4)(s^2+64)(s^2+104)} \right]$$

$$= \frac{A}{s} + \frac{B}{s+1} + \frac{C}{s+2} + \left(\frac{D}{s+\frac{1}{2}-j\frac{\sqrt{3}}{2}} + \frac{D^*}{s+\frac{1}{2}+j\frac{\sqrt{3}}{2}} \right) + \left(\frac{E}{s-2-j2} + \frac{E^*}{s-2+j2} \right) + \left(\frac{F}{s-j0.01} + \frac{F^*}{s+j0.01} \right) + \left(\frac{G}{s-j100} + \frac{G^*}{s+j100} \right)$$

$$\Rightarrow y = A + Be^{-t} + Ce^{-2t} + 2|D|e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t + \angle D\right) + 2|E|e^{2t} \cos(2t + \angle E) + 2|F| \cos(0.01t + \angle F) + 2|G| \cos(100t + \angle G)$$

stable, $t_s = \frac{s}{\frac{1}{2}} = 10 \text{ sec}$

unstable, $y_{ss}!$

Non-zero
components of y_{HOTE}
computed earlier!


$$A = \lim_{s \rightarrow 0} sY(s) = -10 H(0)$$

$$F = \lim_{s \rightarrow j0.01} (s-j0.01)Y(s) = |H(j0.01)| e^{j(-45^\circ + \angle H(j0.01))}$$

$$G = \lim_{s \rightarrow j100} (s-j100)Y(s) = \frac{5|H(j100)|}{2} e^{j(90^\circ + \angle H(j100))}$$




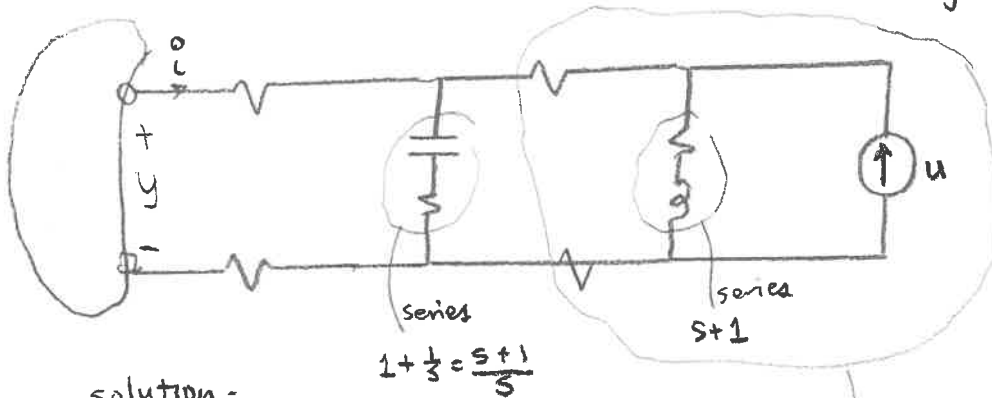
Problem # 6

Determine an s-domain Thevenin equivalent at y (All $R, L, C=1$)
(specify Z_{th} & V_{th} ... emphasize process
... not algebra!)



solution:

lets use source transformations:

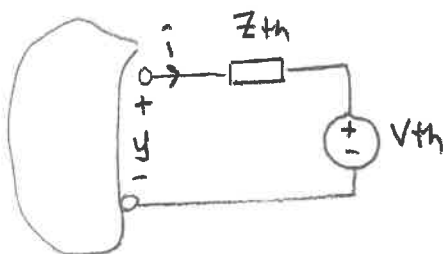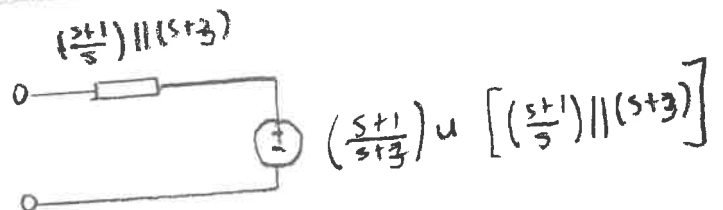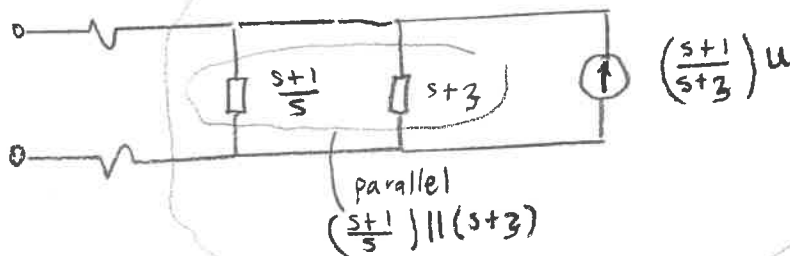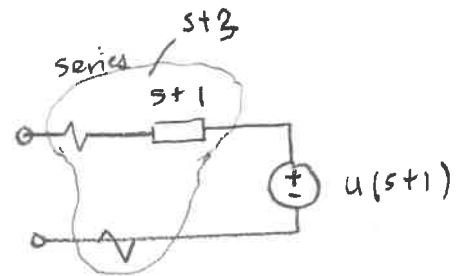

$$Z_{th} = 2 + \left[\left(\frac{s+1}{s} \right) || (s+3) \right]$$


$$V_{th} = \left[\left(\frac{s+1}{s} \right) || (s+3) \right] \left(\frac{s+1}{s} \right) u$$

Problem #7

Determine H , y_{ss} , t_s

Compute all coefficients in y_{ss} (approximately)!
(all $R, L, C = 1$)

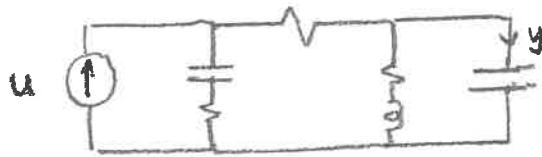Hint: poles = -0.3522
 $-0.8239 \pm j0.8607$



$$u = -7 + 100 \sin(0.01t - 90^\circ) - 2 \cos(100t - 5^\circ)$$


solution:

System is stable since it only has R, L, C & an indep source
(a dependent source is necessary (not sufficient) to get an unstable system!)


NOT F

$$\Rightarrow y_{ss} = -7 H(0) + 100 |H(j0.01)| \sin(0.01t - 90^\circ + \angle H(j0.01)) - 2 |H(j100)| \cos(100t - 5^\circ + \angle H(j100))$$

$$t_s = \frac{5}{|\text{slow pole}|} = \frac{5}{0.3522}$$

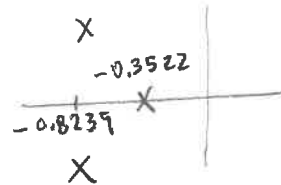


Let's find H via source transformations:

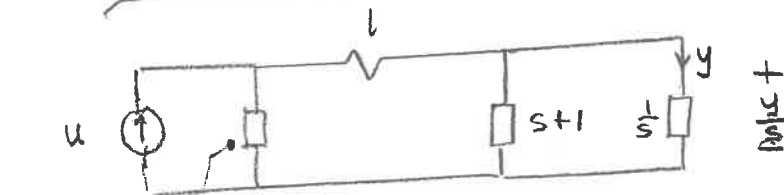

$$\frac{1}{s} + 1 = \frac{s+1}{s}$$

$$\frac{s+1}{s} + 1 = \frac{2s+1}{s}$$

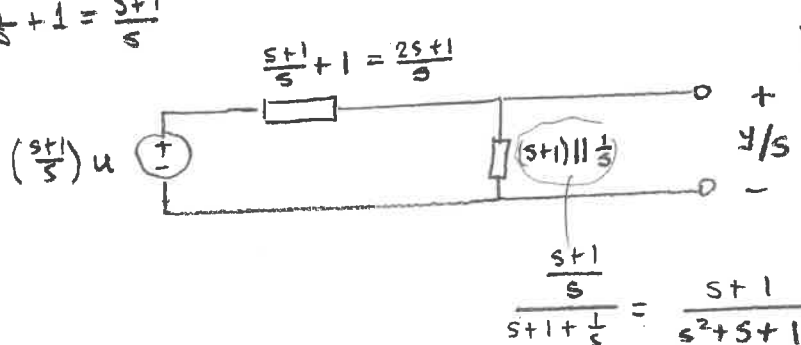

$$\frac{\frac{s+1}{s}}{\frac{s+1}{s} + \frac{1}{s}} = \frac{s+1}{s^2+s+1}$$

voltage division

$$= \left[\frac{\frac{s+1}{s^2+s+1}}{\left(\frac{2s+1}{s}\right) + \left(\frac{s+1}{s^2+s+1}\right)} \right] \left(\frac{s+1}{s}\right) u$$

$$= \left[\frac{s(s+1)}{(2s+1)(s^2+s+1) + s(s+1)} \right] \left(\frac{s+1}{s}\right) u$$

$$2s^3 + 2s^2 + 2s + s^2 + s + 1 + s^2 + s$$

$$2s^3 + 4s^2 + 4s + 1 = 2(s^3 + 2s^2 + 2s + \frac{1}{2})$$

$$\boxed{14 \mid 17}$$

$$\Rightarrow \frac{y}{s} = \left[\frac{\frac{1}{2} (s+1)^2}{s^3 + 2s^2 + 2s + \frac{1}{2}} \right] u$$

Problem #7

$$H = \frac{y}{u} = \frac{\frac{1}{2} s (s+1)^2}{s^3 + 2s^2 + 2s + \frac{1}{2}}$$

Note = roots are -0.3522
-0.8239 ± j0.8607

-via calculator or MATLAB!

Compute gain needed in yss

$$H(0) = 0$$

$$H(j0.01) \approx \frac{\frac{1}{2} s}{\frac{1}{2}} \bigg|_{s=j0.01} = 10^{-2} e^{j90^\circ}$$

$$\sim |H(j0.01)| \quad \sim \angle H(j0.01)$$

$$H(j100) \approx \frac{1}{2} = \frac{1}{2} e^{j0^\circ}$$

$$\sim |H(j100)|$$

Gain Checks on H =

Analysis at $s=0$

$Z_L = sL = 0$ (short)
 $Z_C = \frac{1}{sC} = \infty$ (open)




$$y=0 \Rightarrow H(0)=0$$

as expected! 😊

Analysis at $s=\infty$

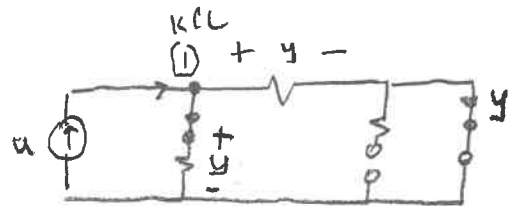$Z_L = sL = \infty$ (open)
 $Z_C = \frac{1}{sC} = 0$ (short)




$$KCL: u = y + y = 2y$$

$$\Rightarrow y = \frac{1}{2} u$$

$$\Rightarrow H(\infty) = \frac{1}{2}$$

as expected! 😊

Characteristic Eq Check: (set u=0)

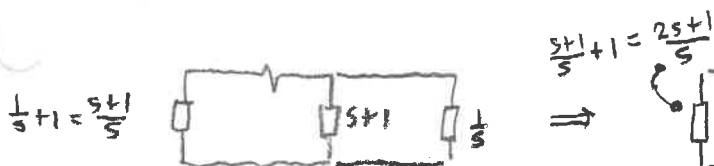

$$\frac{s+1}{s} + 1 = \frac{2s+1}{s}$$

$$\left(\frac{s+1}{s} \right) \parallel \left(\frac{1}{s} \right) = \frac{s+1}{s+1+\frac{1}{s}} = \frac{s+1}{s^2+s+1}$$

$$Z = \frac{2s+1}{s} + \frac{s+1}{s^2+s+1} = \frac{(2s+1)(s^2+s+1) + s(s+1)}{s(s^2+s+1)}$$


\Rightarrow Numerator yields Φ obtained earlier! 😊

15/17



Problem #8

Determine & plot $|H(j\omega)|$ & $\angle H(j\omega)$

(All $R, L, C = 1$)

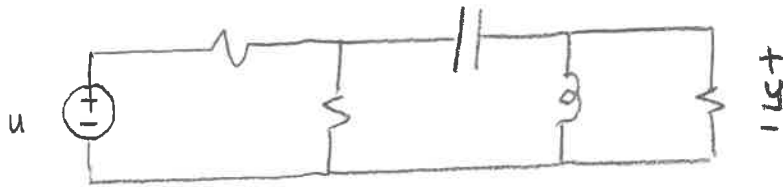

solution via source transformations =

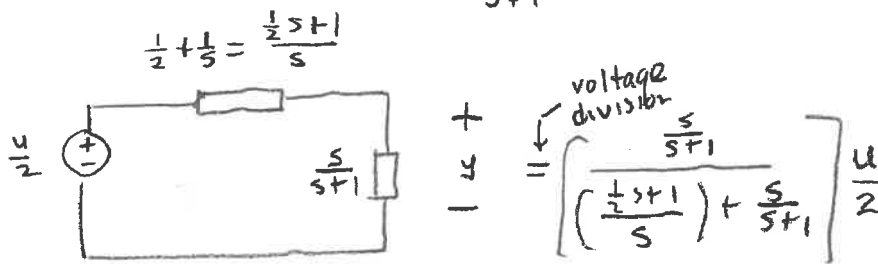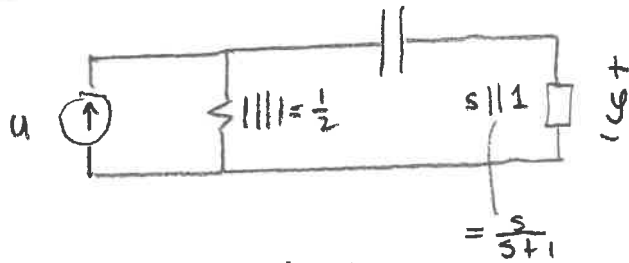

$$H = \frac{u_1}{u} = \frac{\frac{1}{2} s^2}{\left(\frac{1}{2}s + 1\right)(s+1) + s^2}$$



$$= \frac{\frac{1}{2} s^2}{\frac{1}{2} s^2 + \frac{1}{2} s + s + 1 + s^2}$$

$$= \frac{\frac{1}{2} s^2}{\frac{3}{2} s^2 + \frac{3}{2} s + 1}$$

$$= \frac{3}{2} \left[s^2 + s + \frac{2}{3} \right]$$

$$H = \frac{\frac{1}{3} s^2}{s^2 + s + \frac{2}{3}}$$

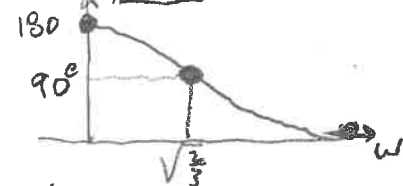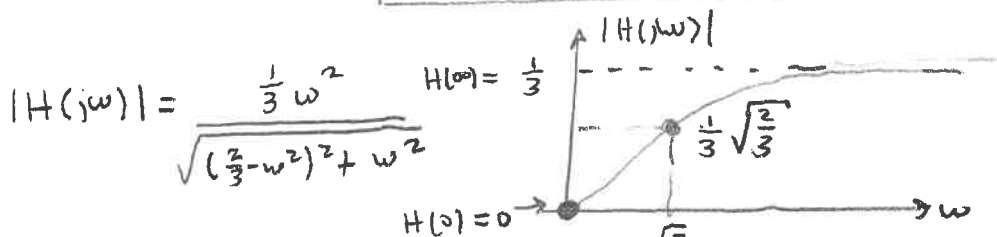
$$H(j\omega) = \frac{-\frac{1}{3} \omega^2}{\frac{2}{3} - \omega^2 + j\omega}$$



$$\angle H(j\omega) = \angle_{\text{top}} - \angle_{\text{bottom}} = 180 - \begin{cases} \tan^{-1}\left(\frac{\omega}{\frac{2}{3}-\omega^2}\right) & \omega \in [0, \sqrt{\frac{2}{3}}] \\ 180 - \tan^{-1}\left(\frac{\omega}{\omega^2-\frac{2}{3}}\right) & \omega \in [\sqrt{\frac{2}{3}}, \infty) \end{cases}$$

Problem #8

solution via KVL, KCL, Ohm

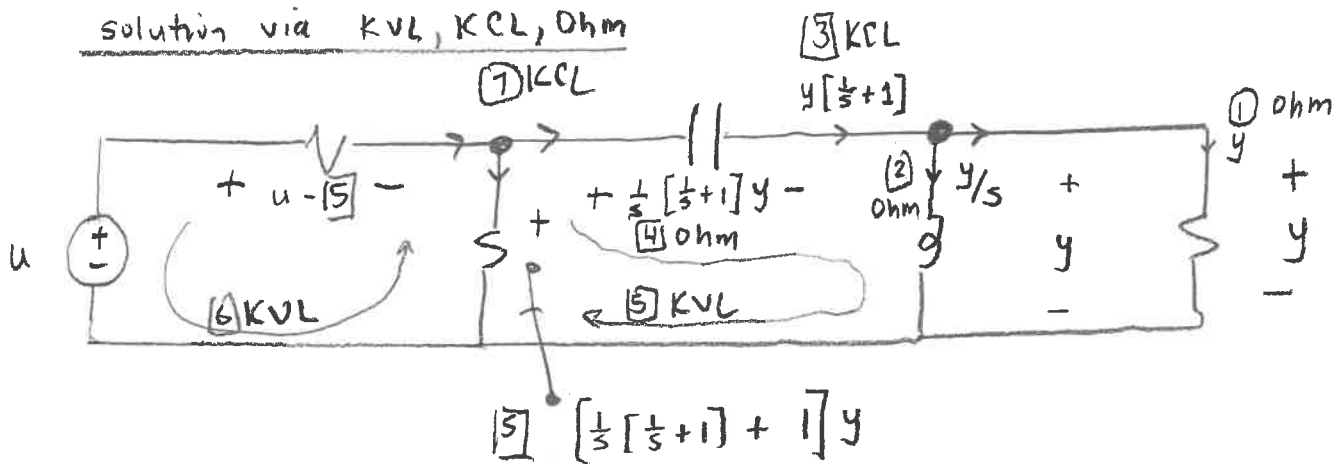

$$[7] \text{ KCL} = \left(\frac{u - [\frac{1}{s}(\frac{1}{s} + 1) + 1]y}{1} \right) = \left(\frac{\frac{1}{s}(\frac{1}{s} + 1) + 1}{1} y + y(\frac{1}{s} + 1) \right)$$

$$\Rightarrow y \left[\frac{1}{s}(\frac{1}{s} + 1) + 1 + \frac{1}{s}(\frac{1}{s} + 1) + 1 + \frac{1}{s} + 1 \right] = u$$

$$\Rightarrow y \left[\frac{2}{s^2} + \frac{3}{s} + 3 \right] = u$$

$$\Rightarrow y \left[2 + 3s + 3s^2 \right] = s^2 u$$

$3(s^2 + s + \frac{2}{3})$

$$\Rightarrow H = \frac{y}{u} = \frac{\frac{1}{3}s^2}{s^2 + s + \frac{2}{3}}$$

which agrees with what we obtained earlier 