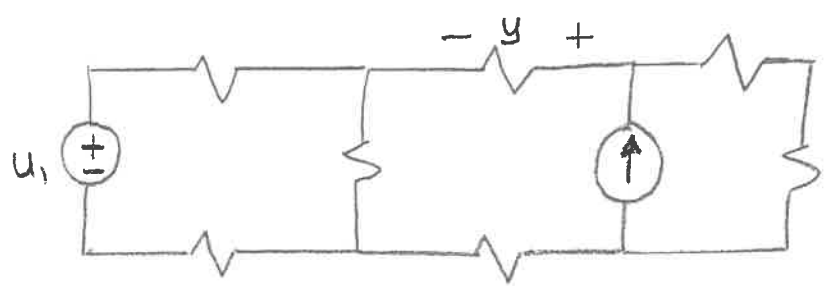


EXAM RULES

- 1) One 8.5" x 11" sheet permitted;
otherwise closed books, closed notes, open minds!
- 2) Scientific calculator is permitted; no computers and no phone!
- 3) **NO PHONES !!!**
Phones should not be visible at all!
A visible phone will result in a zero grade for the exam!
- 4) Write FULL NAME legibly on each page provided.
- 5) **PLEASE SHOW ALL WORK !!!**
This is essential to receive partial credit!
- 6) Please do not submit multiple answers. You must pick an answer!!
- 7) Write your solutions on the sheets provided.
No other paper/sheets/pages should be used!
- 8) Clearly label voltages and currents on the circuits provided.
- 9) Use the variables provided!
No additional variables should be used!
- 10) Unreadable work will receive NO CREDIT.
- 11) Please place important equations and answers within boxes as we have done in lecture.
- 12) Please be careful with your algebra, signs, etc.
- 13) Please turn in your solutions to me at the end of the period!
- 14) **PLEASE DO NOT CHEAT !!!**

Problem # 1

Relate y to u_1, u_2
(All $R=1$)




Problem # 2

Relate w_1, w_2, w_3, w_4 to u_1, u_2
(Just set up the equations!)

(Nodal Analysis)

3/8

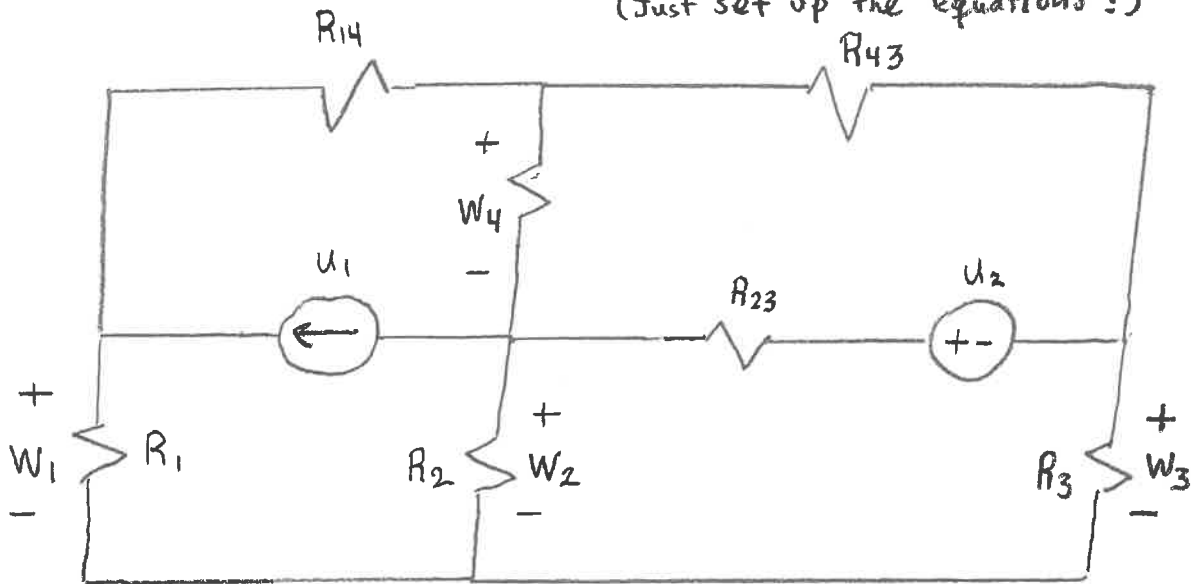


Problem #3

Relate I_1, I_2, I_3, I_4 to u_1, u_2, u_3, u_4
 (Just set up the equations!)

(Mesh Analysis)


4/8

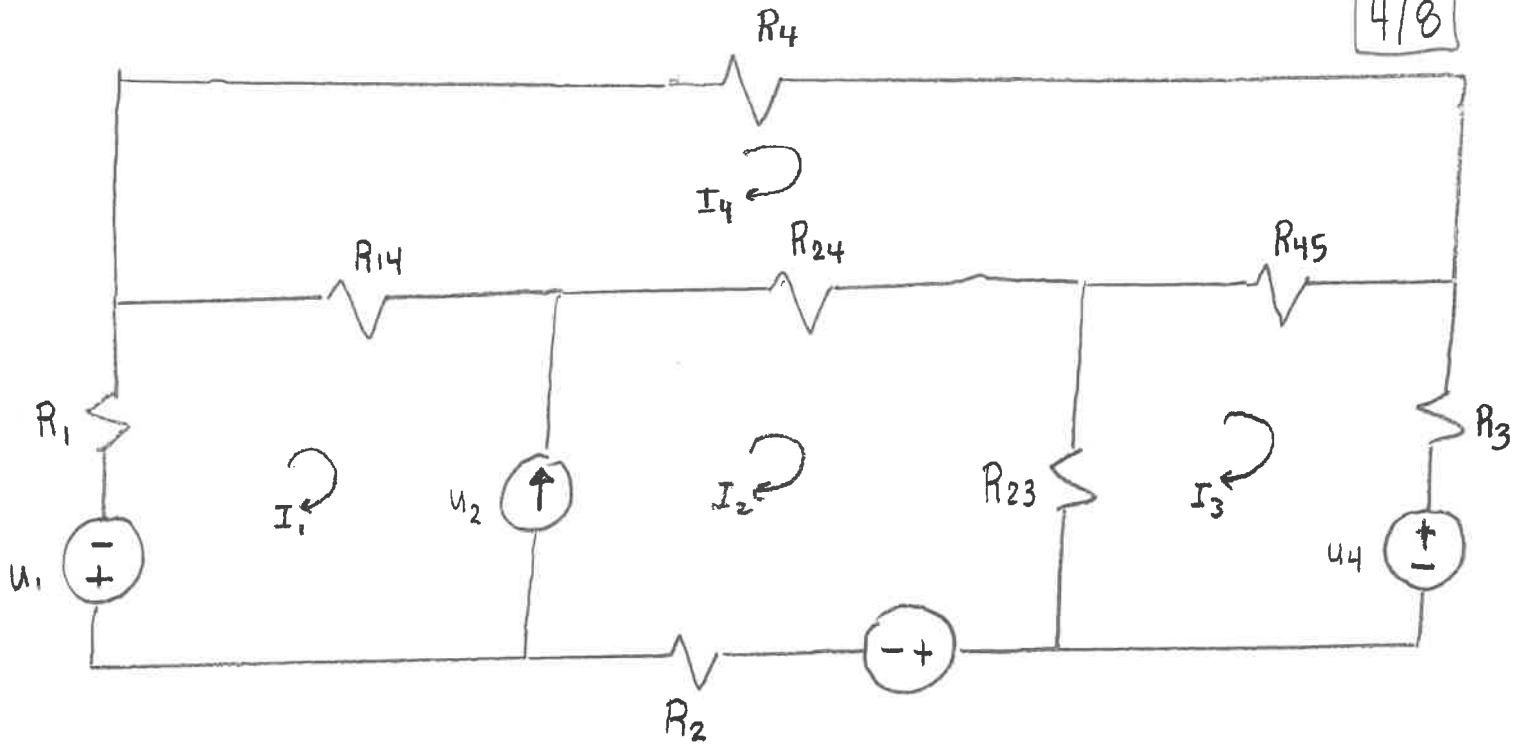

Problem #4

Find a Thevenin & Norton Equivalent at y
 (All $R=1$) ... Must specify R_{th} & V_{th}


(Thevenin -
 Norton
 at y)

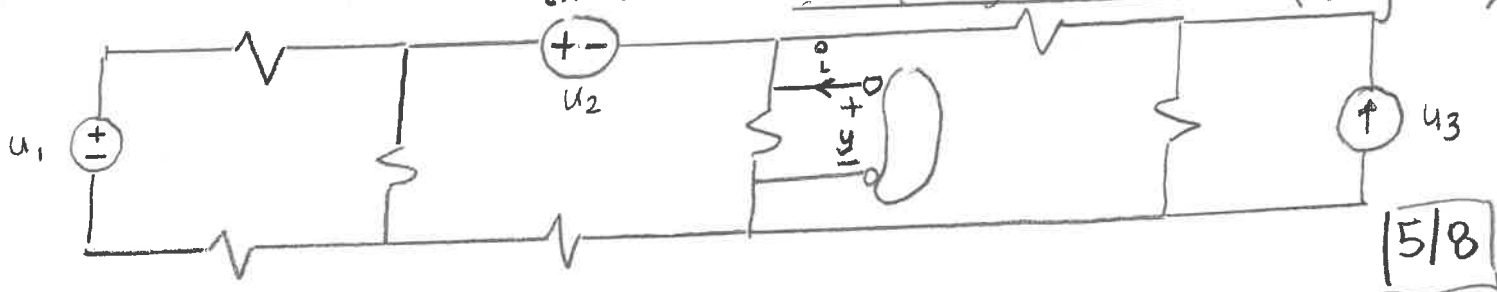

Problem # 5

Find a Thevenin & Norton Equivalent at y
(All $R=1$) ... Must specify R_{th} & V_{th}


(Thevenin-Norton
at y)

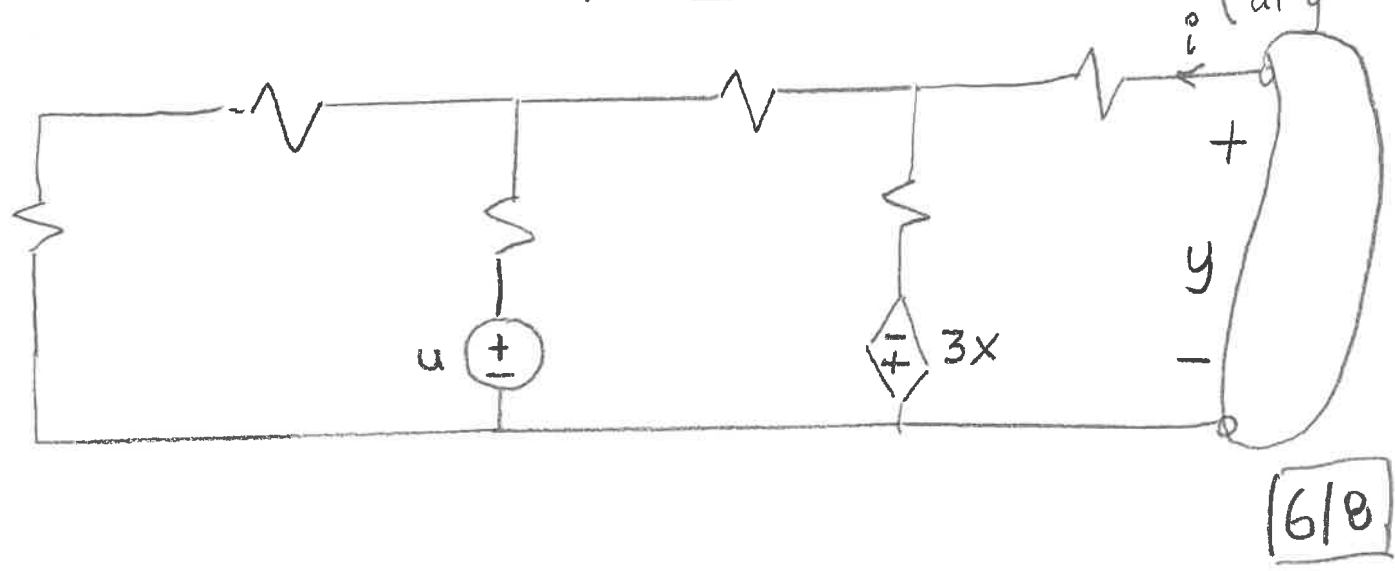

Problem # 6

Find a Thevenin & Norton Equivalent at y
(All $R=1$) ... must specify $R_{th} < V_{th}$

(Thevenin-
Norton
at y)

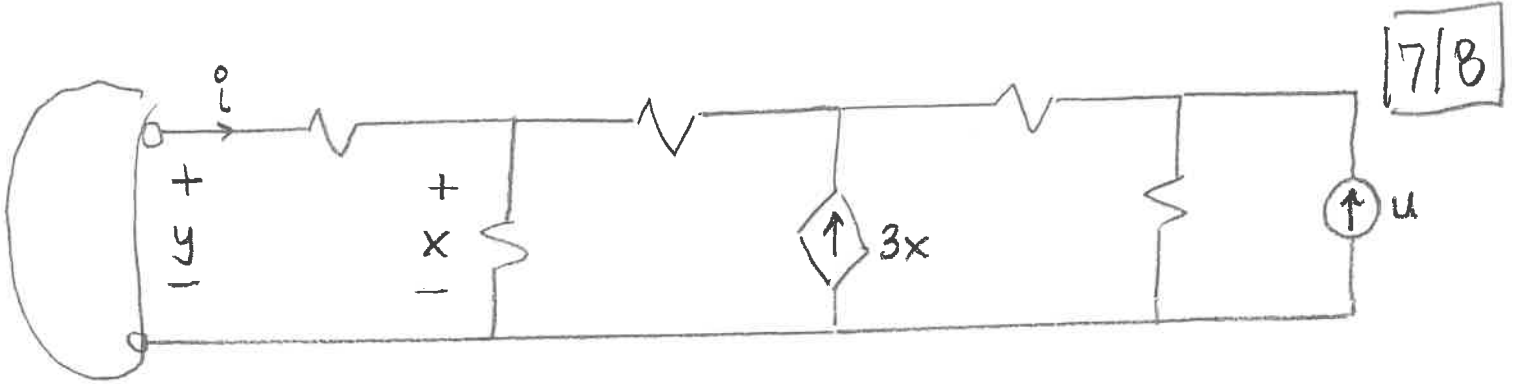


Problem #17

Relate y to u_1, u_2




(All $R=1$)

(Need
Another
Variable)

8/8

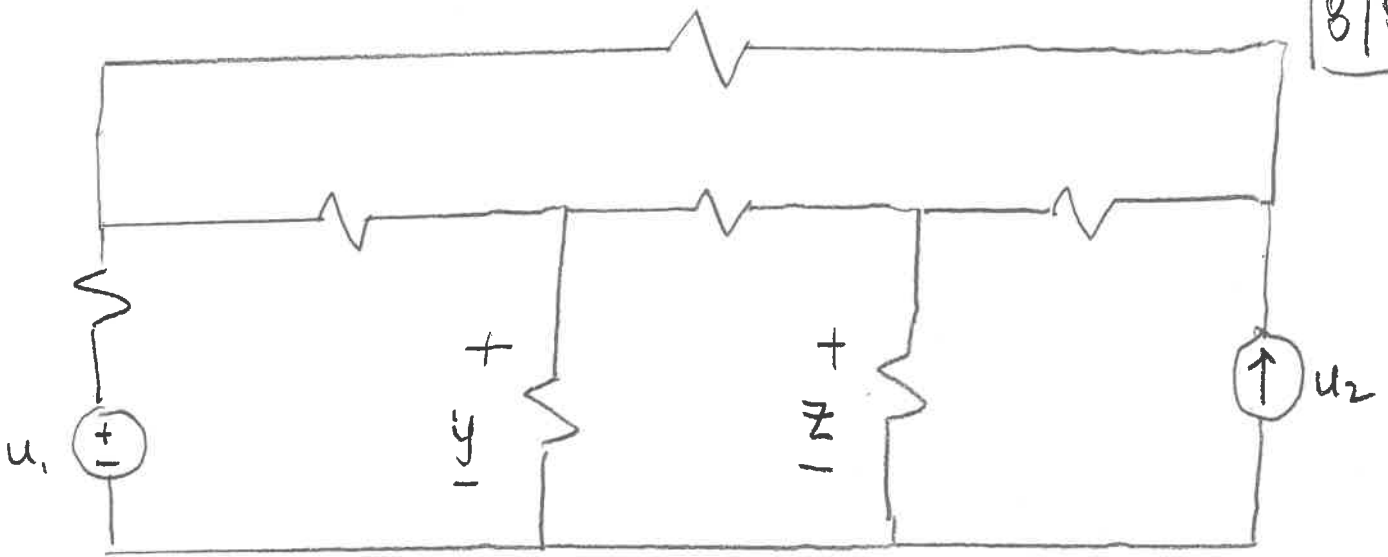

Problem 1

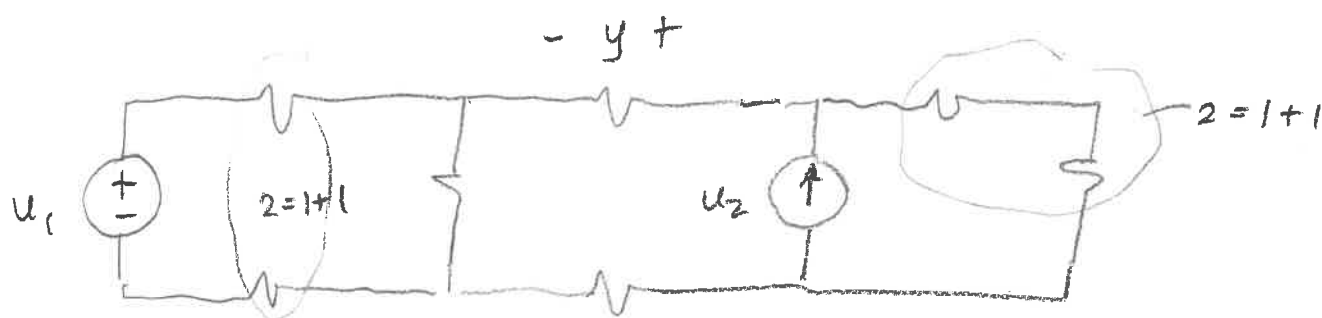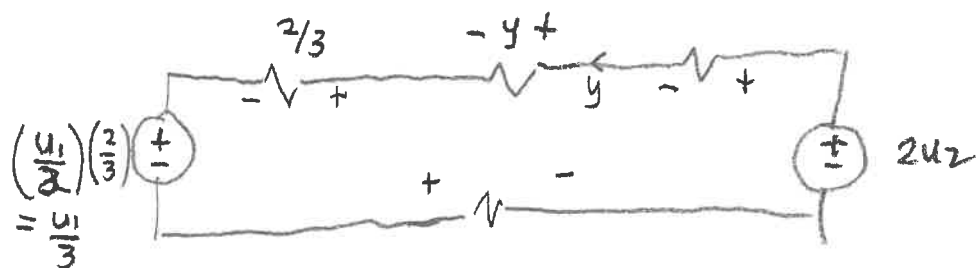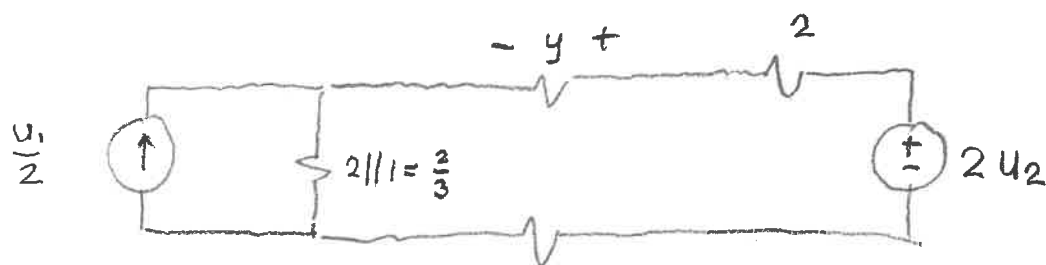Relate y to u_1, u_2 (All R 's = 1)a) sol via source transf

$$\frac{u_1}{3} = -\left(\frac{2}{3}\right)y - y - y + 2u_2 - y = -3\frac{2}{3}y + 2u_2$$

$$\frac{11}{3}y = -\frac{u_1}{3} + 2u_2$$


$$11y = -u_1 + 6u_2$$

$$y = -\left(\frac{1}{11}\right)u_1 + \left(\frac{6}{11}\right)u_2$$

Problem 1

2/13

[b] Sol via KVL, KCL, Ohm (All R's=1)

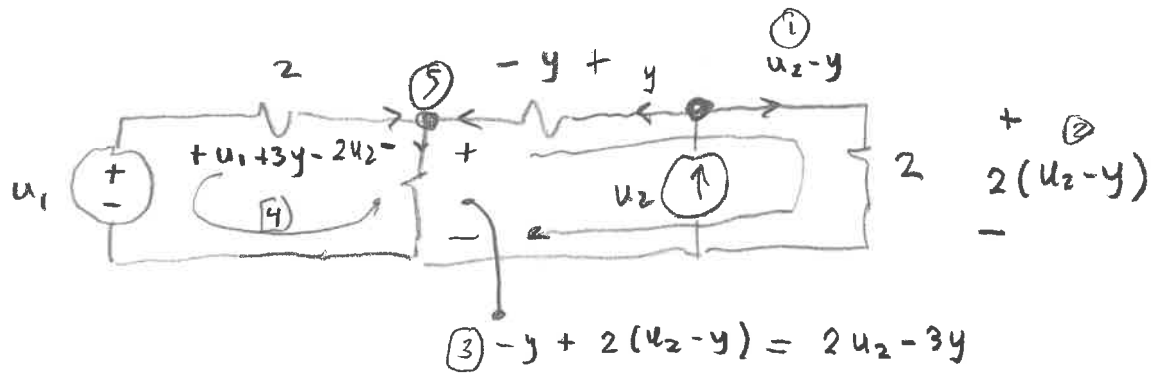

$$(5) \text{ KCL} = \underbrace{(u_1 + 3y - 2u_2)}_{\uparrow} + \underbrace{y}_{\leftarrow} = \underbrace{2u_2 - 3y}_{\downarrow}$$

$$u_1 + 3y - 2u_2 + 2y = 4u_2 - 6y$$


$$11y = -u_1 + 6u_2$$

$$y = -\left(\frac{1}{11}\right)u_1 + \left(\frac{6}{11}\right)u_2$$



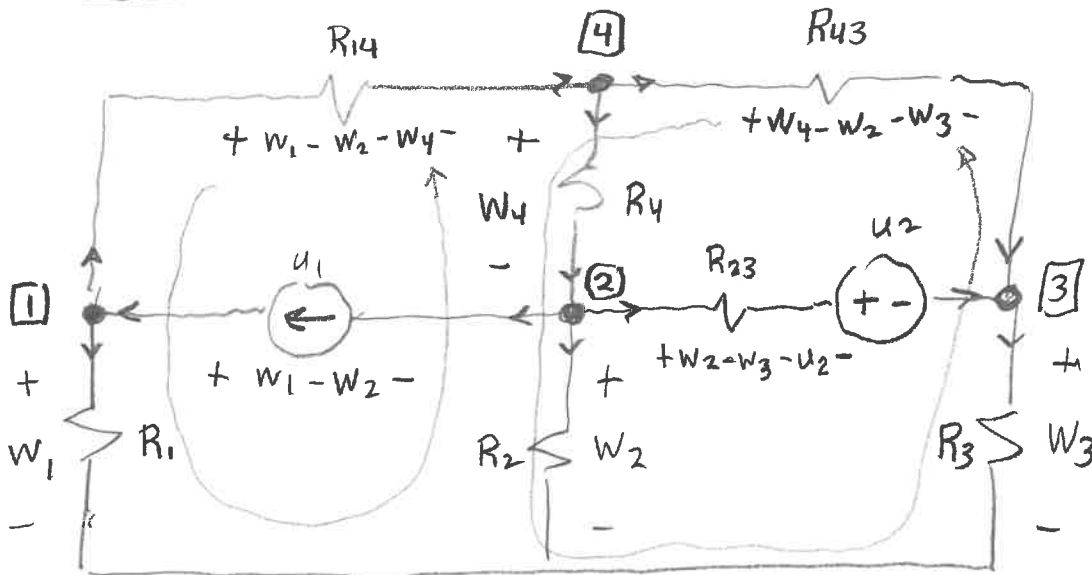Problem 2 (Nodal Analysis)

Relate $w_{1,2,3,4}$ to $u_{1,2}$ (Just set up the equations!)



① KCL =
$$u_1 = \left(\frac{w_1}{R_1} \right) + \left(\frac{w_1 - w_2 - w_4}{R_{14}} \right)$$

② KCL =
$$\left(\frac{w_4}{R_4} \right) = u_1 + \left(\frac{w_2}{R_2} \right) + \left(\frac{w_2 - w_3 - w_2}{R_{23}} \right)$$

③ KCL =
$$\left(\frac{w_2 - w_3 - u_2}{R_{23}} \right) + \left(\frac{w_4 - w_2 - w_3}{R_{43}} \right) = \left(\frac{w_3}{R_3} \right)$$

④ KCL =
$$\left(\frac{w_1 - w_2 - w_4}{R_{14}} \right) = \left(\frac{w_4}{R_4} \right) + \left(\frac{w_4 - w_2 - w_3}{R_{43}} \right)$$


\Rightarrow 4 eqs in 4 unknowns $w_{1,2,3,4}$!

Problem 3

(Mesh Analysis)

4/13

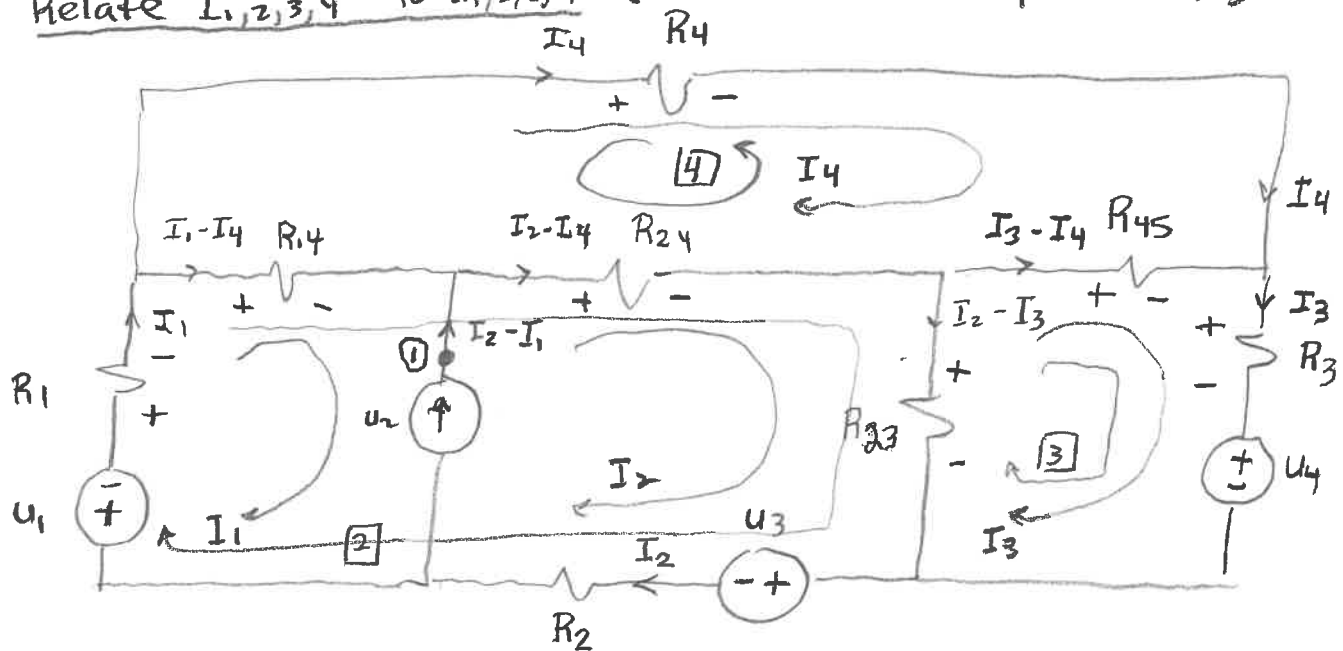Relate $I_{1,2,3,4}$ to $u_{1,2,3,4}$ (Just set up the equations!)



$$\textcircled{1} \text{ KCL} = I_2 - I_1 = u_2$$

$\textcircled{2}$ KVL

Bottom 2
left loops

$$-R_1 I_1 - u_1 = R_{14} (I_1 - I_4) + R_{24} (I_2 - I_4) + R_{23} (I_2 - I_3) + u_3 + R_2 I_2$$

$\textcircled{3}$ KVL =

bottom right
loop

$$R_{23} (I_2 - I_3) = R_{45} (I_3 - I_4) + R_3 I_3 + u_4$$

$\textcircled{4}$ KVL =

top loop

$$R_4 I_4 = R_{14} (I_1 - I_4) + R_{24} (I_2 - I_4) + R_{45} (I_3 - I_4)$$


\Rightarrow 4 eqs in 4 unknowns $I_{1,2,3,4}$

Problem 4

(Norton & Thevenin Equivalents)
(All R's = 1)


5/13

Exam 1
Fri 10-18-24


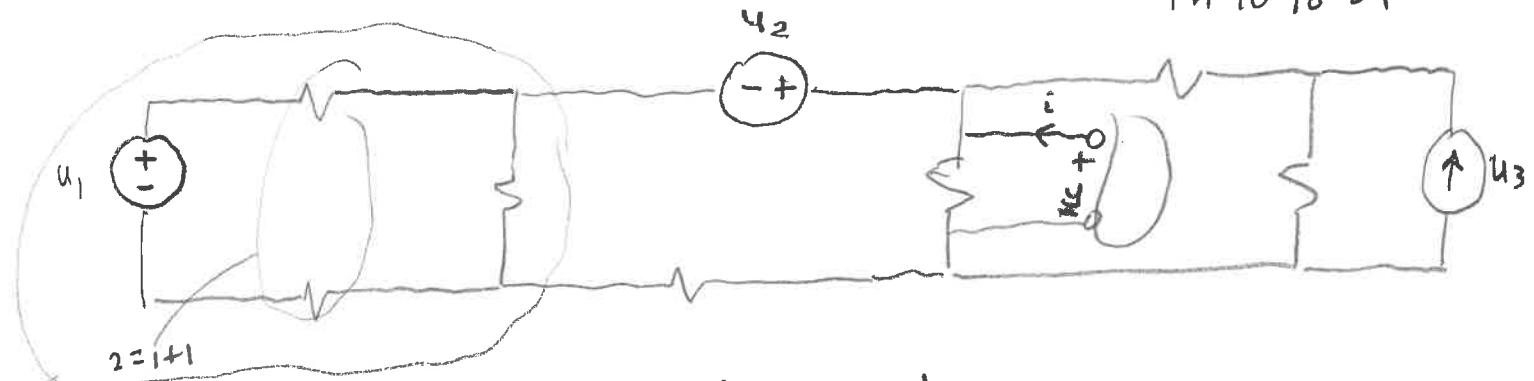


Find a Norton & Thevenin Equivalent at y


solution via source transformations

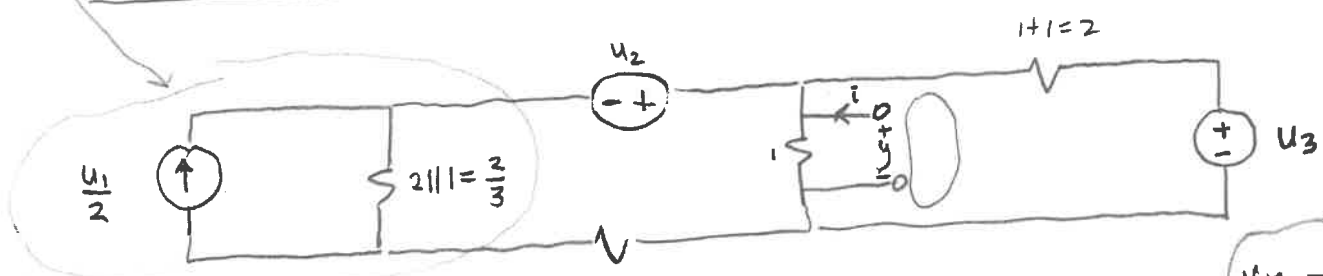

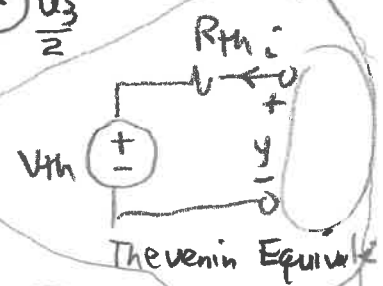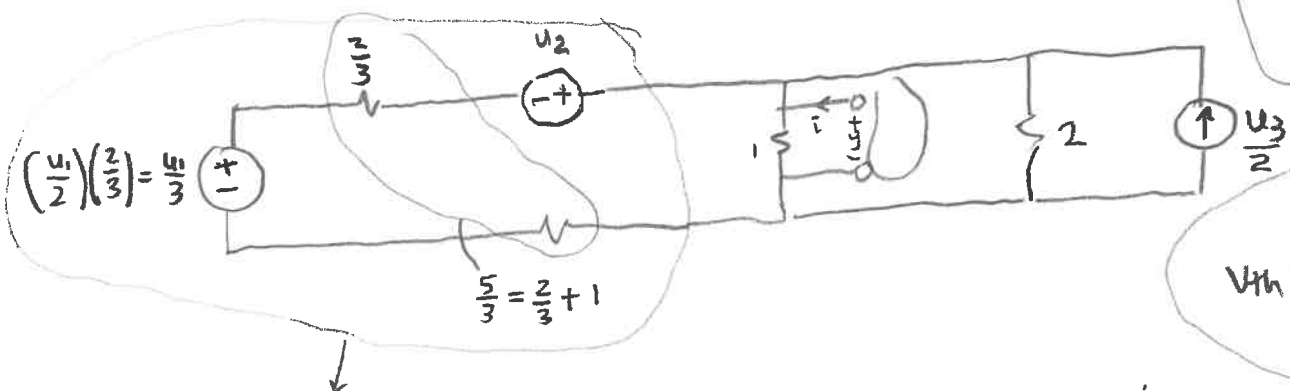
$$V_{th} = \left(\frac{2}{21}\right)u_1 + \left(\frac{6}{21}\right)u_2 + \left(\frac{5}{21}\right)u_3$$


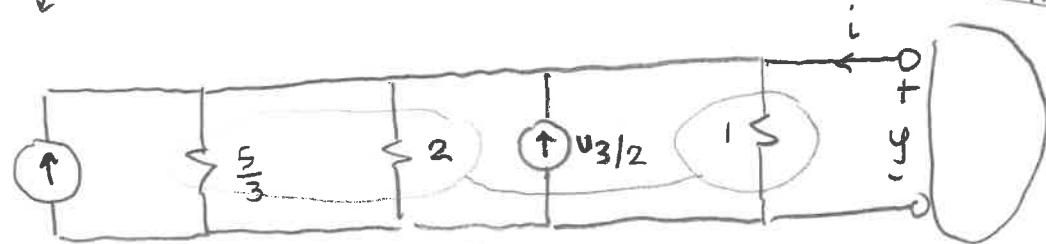
$$\begin{aligned} &\left(\frac{u_1}{3} + u_2\right) \\ &= \frac{u_1}{5} + \frac{3u_2}{5} \end{aligned}$$


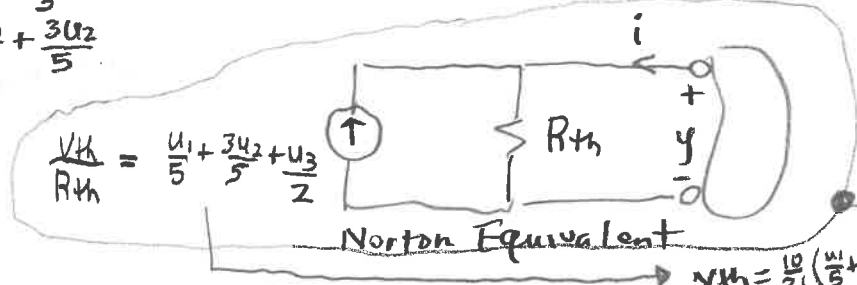
$$\begin{aligned} R_{th} &= \left(\frac{5}{3}\right) \parallel (2) \parallel (1) \\ &= \left(\frac{5}{3}\right) \parallel \left(\frac{2}{3}\right) = \left(\frac{5}{3}\right)\left(\frac{2}{3}\right) \\ &= \frac{10}{9} \end{aligned}$$



$$R_{th} = \frac{10}{21}$$


$$V_{th} = \frac{10}{21} \left(\frac{u_1}{5} + \frac{3u_2}{5} + \frac{u_3}{2} \right)$$

Problem 5





(Thevenin & Norton Equivalent)

6/13

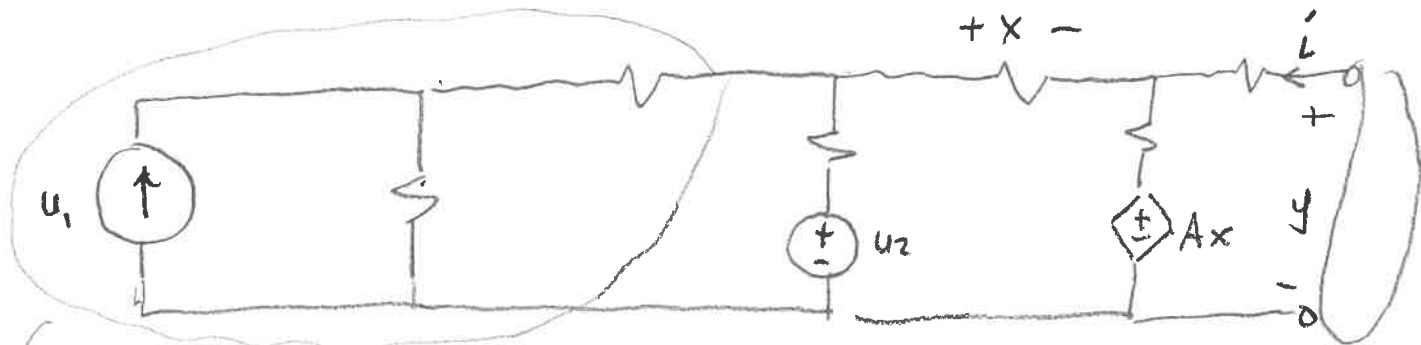Find Thevenin & Norton equivalent at y (All R 's = 1)





Solution using source transformation

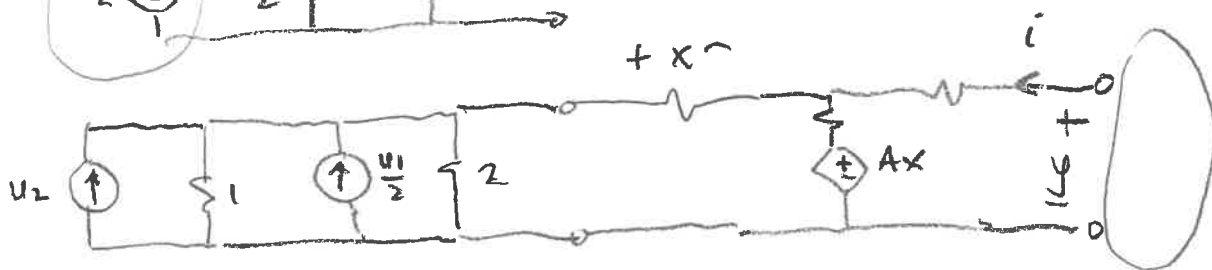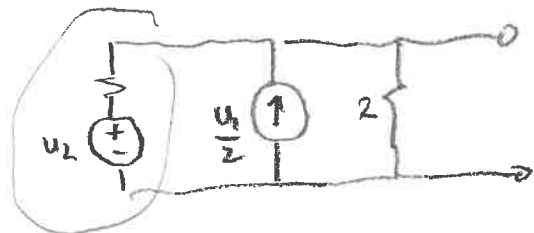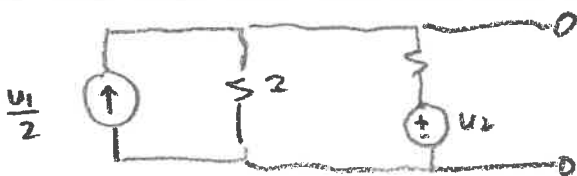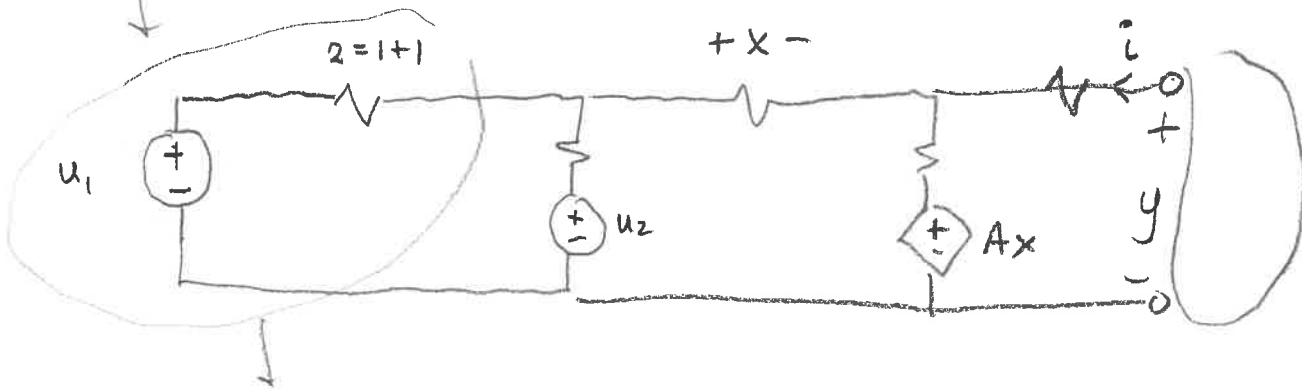

Problem 5

7/13

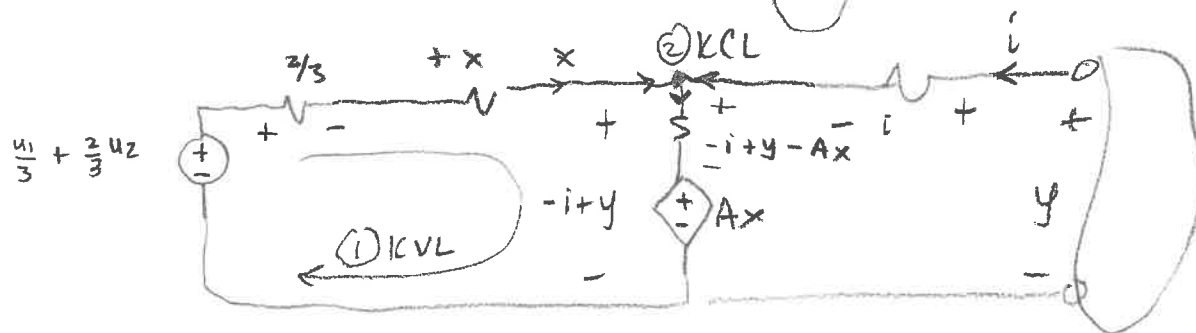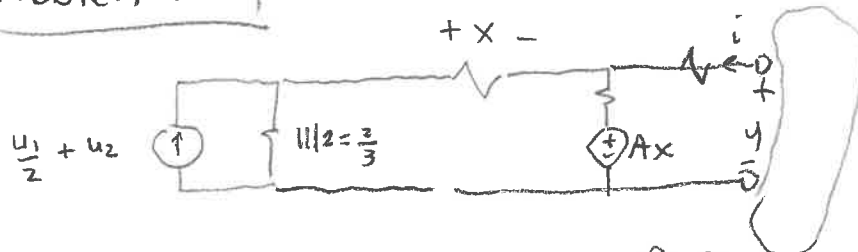

$$\textcircled{1} \text{KVL} = \frac{u_1}{3} + \frac{2u_2}{3} = \frac{2}{3}x + x + (-i + y)$$

$$\Rightarrow y = i - \frac{5}{3}x + \frac{u_1}{3} + \frac{2u_2}{3}$$

$$\Rightarrow x = \frac{3}{5} \left[i - y + \frac{u_1}{3} + \frac{2u_2}{3} \right]$$

$$\textcircled{2} \text{KCL} = x + i = -i + y - Ax$$

$$x = \frac{3}{5} (i - y) + \frac{u_1}{5} + \frac{2u_2}{5}$$

$$\Rightarrow y = 2i + (1+A)x$$

$$= 2i + (1+A) \left[\frac{3}{5} (i - y) + \frac{u_1}{5} + \frac{2u_2}{5} \right]$$

$$\Rightarrow y \left[1 + (1+A) \frac{3}{5} \right] = i \left[2 + (1+A) \frac{3}{5} \right] + \frac{(1+A)}{5} [u_1 + 2u_2]$$


$$\Rightarrow y \left[\frac{8}{5} + 3A \right] = i \left[\frac{13}{5} + 3A \right] + (1+A) [u_1 + 2u_2]$$

$$\Rightarrow y = \left[\frac{13+3A}{8+3A} \right] i + \left[\frac{1+A}{8+3A} \right] [u_1 + 2u_2]$$

Thov Equiv = R_{th}



Norton Equiv =

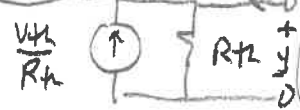

For $A = -3$ $R_{th} = \frac{13-9}{8-9} = \frac{4}{-1} = -4$







$$V_{th} = \left(\frac{1-3}{8-9} \right) (u_1 + 2u_2) = \left(\frac{-2}{-1} \right) (u_1 + 2u_2) = 2u_1 + 4u_2$$

Exam #1 Fri 10-18-24

Problem 5

8/13

Solve for $A = -3$

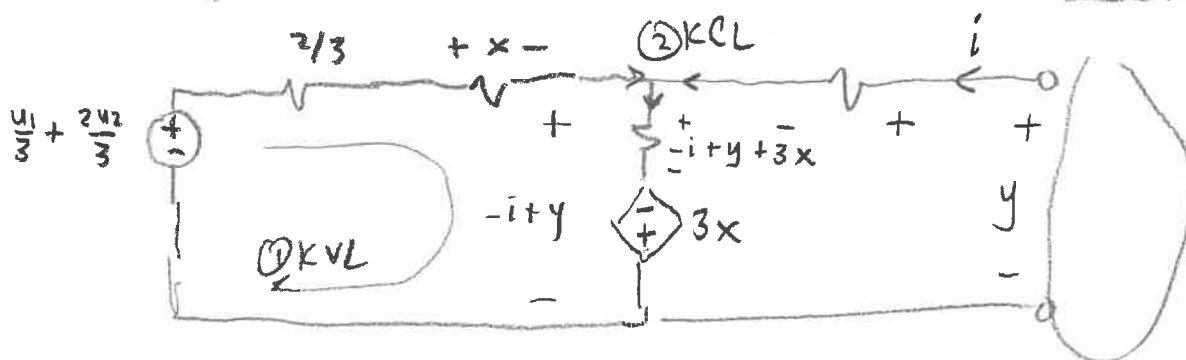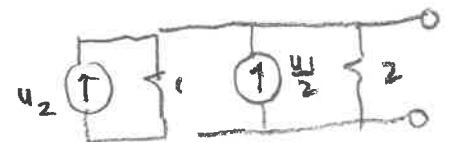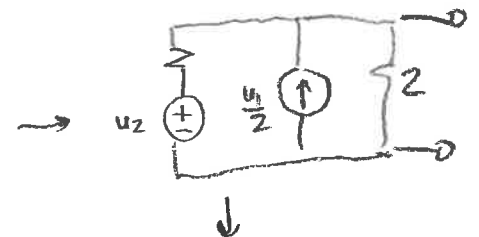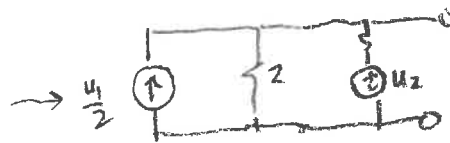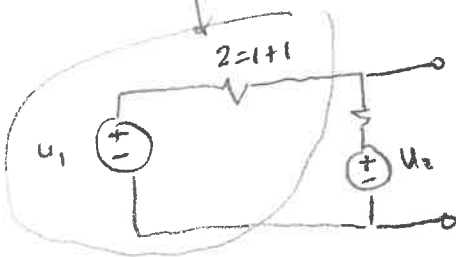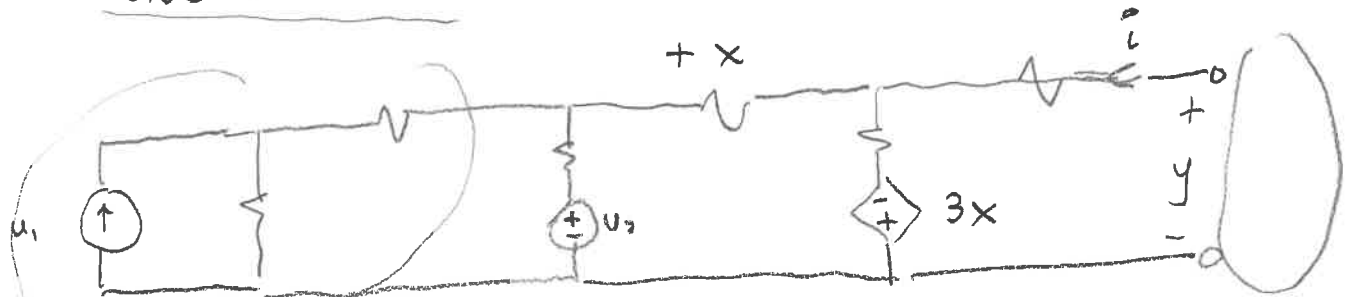

$$\textcircled{1} \text{KVL} = \frac{u_1}{3} + \frac{2u_2}{3} = \frac{2}{3}x + x + (-i + y) \Rightarrow \frac{5}{3}x = i - y + \frac{u_1}{3} + \frac{2u_2}{3}$$

$$\Rightarrow x = \frac{3}{5}(i - y) + \frac{u_1}{5} + \frac{2u_2}{5}$$

$$\textcircled{2} \text{KCL} = \vec{x} + \vec{i} = -i + y + 3x$$

$$\Rightarrow y = 2i - 2x = 2i - 2 \left[\frac{3}{5}(i - y) + \frac{u_1}{5} + \frac{2u_2}{5} \right]$$

Problem 5

9/13

$$\Rightarrow y \left[1 - 2 \left(\frac{3}{5} \right) \right] = i \left[2 - 2 \left(\frac{3}{5} \right) \right] - 2 \left[\frac{u_1}{5} + \frac{2u_2}{5} \right]$$

$$\Rightarrow y \left[\underbrace{5 - 6}_{-1} \right] = i \left[10 - 6 \right] - 2 \left[\frac{u_1}{5} + \frac{2u_2}{5} \right]$$


$$\Rightarrow \boxed{y = -4i + 2u_1 + 4u_2}$$

$$R_{th} = -4$$

$$V_{th} = 2u_1 + 4u_2$$

Final Circuit for Exam 1 (Fall 2024)

(set $u_1 = 0$)

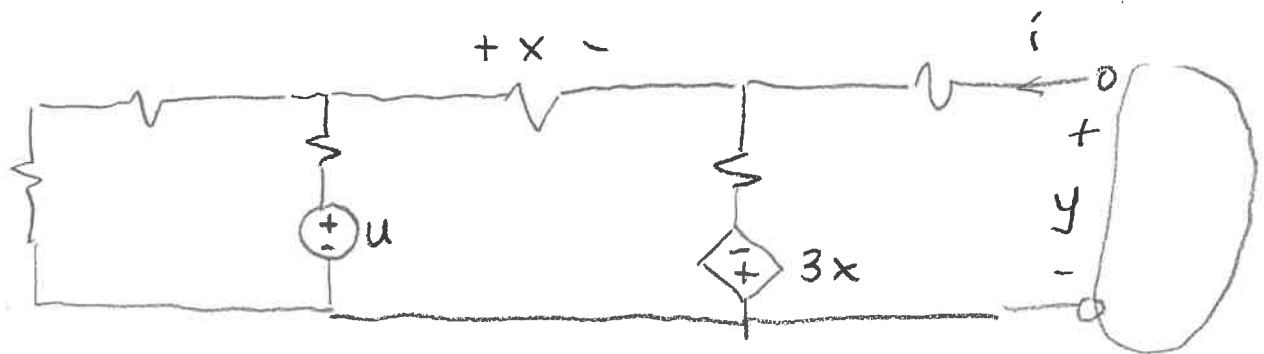

$$\begin{aligned} u_1 &= 0 \\ u_2 &= u \end{aligned} \Rightarrow$$



$$\boxed{y = -4i + 4u}$$

Problem 6

(Thevenin & Norton Equivalent)

10/13

Find Thevenin & Norton Eq at y

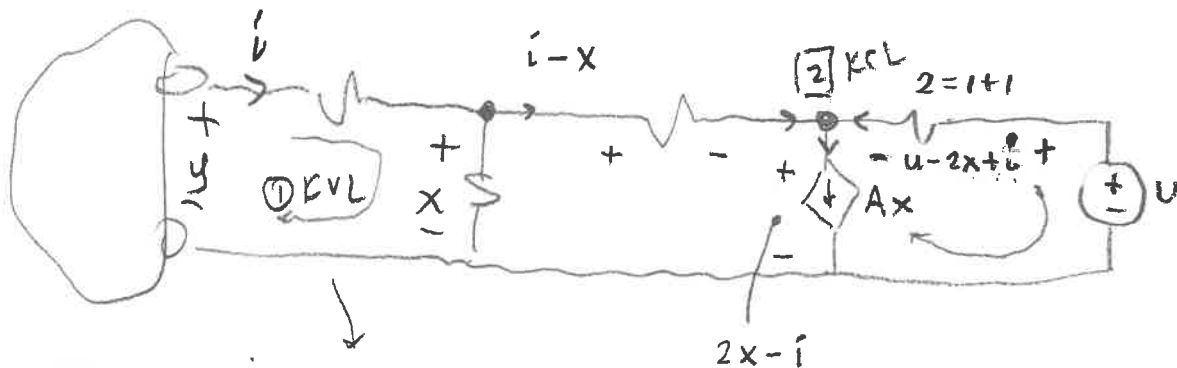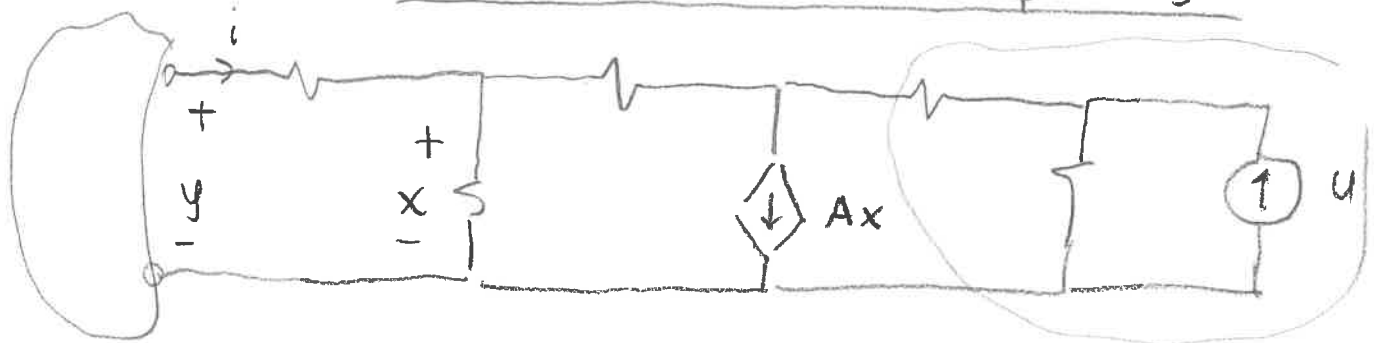

$$\textcircled{1} \text{ KVL} = \boxed{y = i + x}$$

$$x = y - i$$

$$\textcircled{2} \text{ KCL} = \rightarrow \downarrow \leftarrow$$

$$\boxed{(i - x) + \left(\frac{u - 2x + i}{2}\right) = Ax}$$


$$2i - 2x + u - 2x + i = 2Ax$$

$$3i + u = (4 + 2A)x$$


$$3i + u = (4 + 2A)[y - i]$$

$$(4 + 2A)y = i \left[\overset{7}{3 + 4 + 2A} \right] + u$$
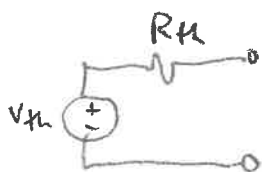
$$\boxed{y = \underbrace{\left[\frac{7 + 2A}{4 + 2A} \right]}_{R_{th}} i + \underbrace{\left[\frac{1}{4 + 2A} \right]}_{V_{th}} u}$$



Thevenin
Equiv

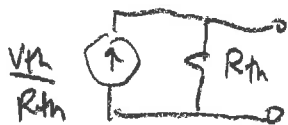

Norton
Equiv

$$A = -3 \quad R_{th} = \frac{7 - 6}{4 - 6} = -\frac{1}{2}$$


$$V_{th} = -\frac{1}{2}u$$

Problem 6

(Thevenin & Norton Equiv)

11/13

Final Cct for $A = -3$:

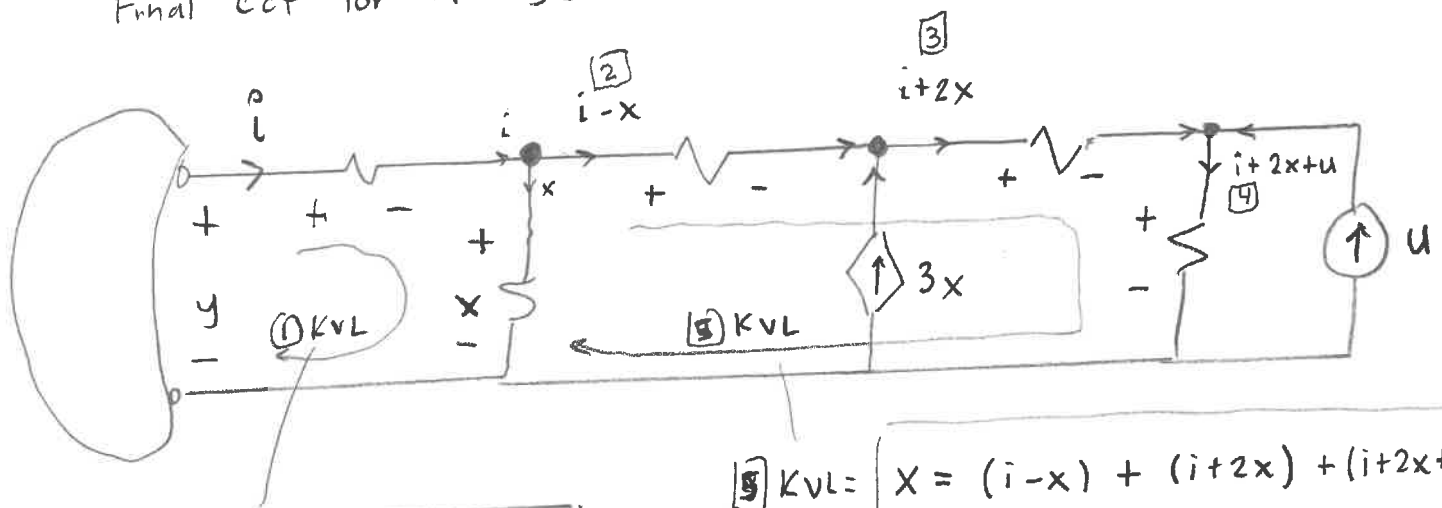

$$\textcircled{1} \text{ KVL: } y = i + x$$

$$\Rightarrow x = y - i$$

$$\textcircled{2} \text{ KVL: } x = (i - x) + (i + 2x) + (i + 2x + u)$$

$$\begin{aligned} 0 &= 3i + u + 2x \\ &= 3i + u + 2(y - i) \\ &= i + u + 2y \end{aligned}$$

$$\Rightarrow y = -\left(\frac{1}{2}\right)i + \left(-\frac{1}{2}\right)u$$

$$R_{th} = -\frac{1}{2}$$

$$V_{th} = -\left(\frac{1}{2}\right)u$$


Problem 7

(Need Additional Variable) (All $R's = 1$)

Relate

y to u_1, z

12/13

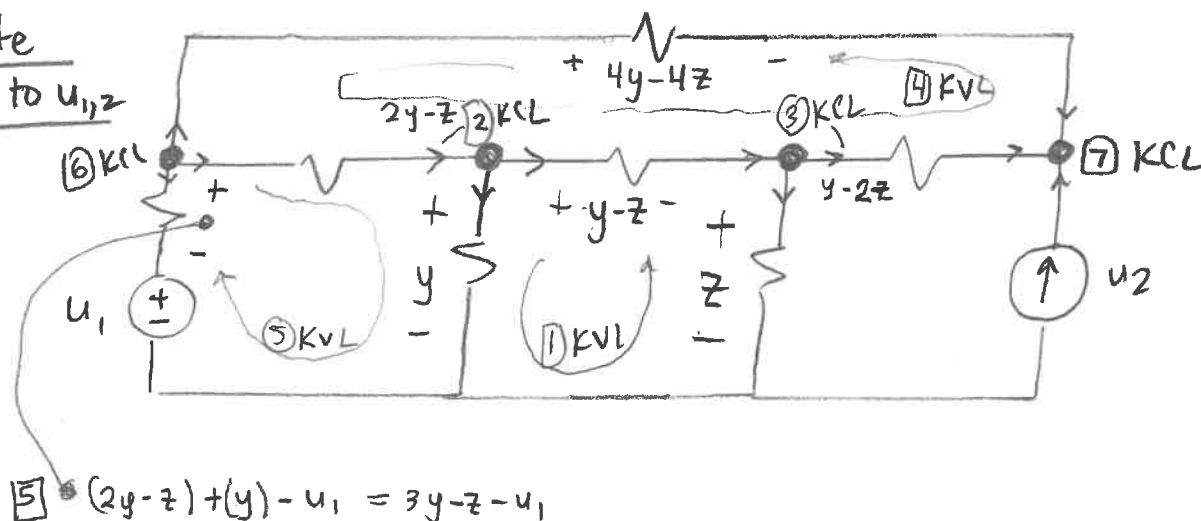

$$6 \text{ KCL} = (3y-z-u_1) + (2y-z) + (4y-4z) = 0$$

$$6z = 9y - u_1$$

$$7 \text{ KCL} = (y-2z) + (4y-4z) + u_2 = 0$$

$$6z = 5y + u_2$$

$$9y - u_1 = 5y + u_2$$

$$4y = u_1 + u_2$$

$$y = \frac{1}{4}u_1 + \frac{1}{4}u_2$$

$$6z = 9y - u_1 = \frac{9}{4}u_1 + \frac{9}{4}u_2 - u_1 = \frac{5}{4}u_1 + \frac{9}{4}u_2$$

$$z = \left(\frac{5}{24}\right)u_1 + \left(\frac{9}{24}\right)u_2$$

$$y = \left(\frac{6}{24}\right)u_1 + \left(\frac{6}{24}\right)u_2$$

$$y-z = \left(\frac{6}{24}\right)u_1 + \left(\frac{6}{24}\right)u_2 - \left(\frac{5}{24}\right)u_1 - \left(\frac{9}{24}\right)u_2 = \left(\frac{1}{24}\right)u_1 - \frac{3}{24}u_2$$

$$4(y-z) = \left(\frac{4}{24}\right)u_1 - \left(\frac{12}{24}\right)u_2$$

Problem 7

13/13


$$y - 2z = \left(\frac{6}{24}\right)u_1 + \left(\frac{6}{24}\right)u_2 - \left(\frac{10}{24}\right)u_1 - \left(\frac{18}{24}\right)u_2 = \left(\frac{-4}{24}\right)u_1 + \left(\frac{-12}{24}\right)u_2$$

$$2y - z = \left(\frac{12}{24}\right)u_1 + \left(\frac{12}{24}\right)u_2 - \left(\frac{5}{24}\right)u_1 - \left(\frac{9}{24}\right)u_2 = \left(\frac{7}{24}\right)u_1 + \left(\frac{3}{24}\right)u_2$$

$$3y - z - u_1 = \left(\frac{18}{24}\right)u_1 + \left(\frac{18}{24}\right)u_2 - \left(\frac{5}{24}\right)u_1 - \left(\frac{9}{24}\right)u_2 = \left(\frac{13}{24}\right)u_1 + \left(\frac{9}{24}\right)u_2 - u_1$$

$$-u_1 = \left(\frac{-11}{24}\right)u_1 + \left(\frac{9}{24}\right)u_2$$

Summary on Circuit:

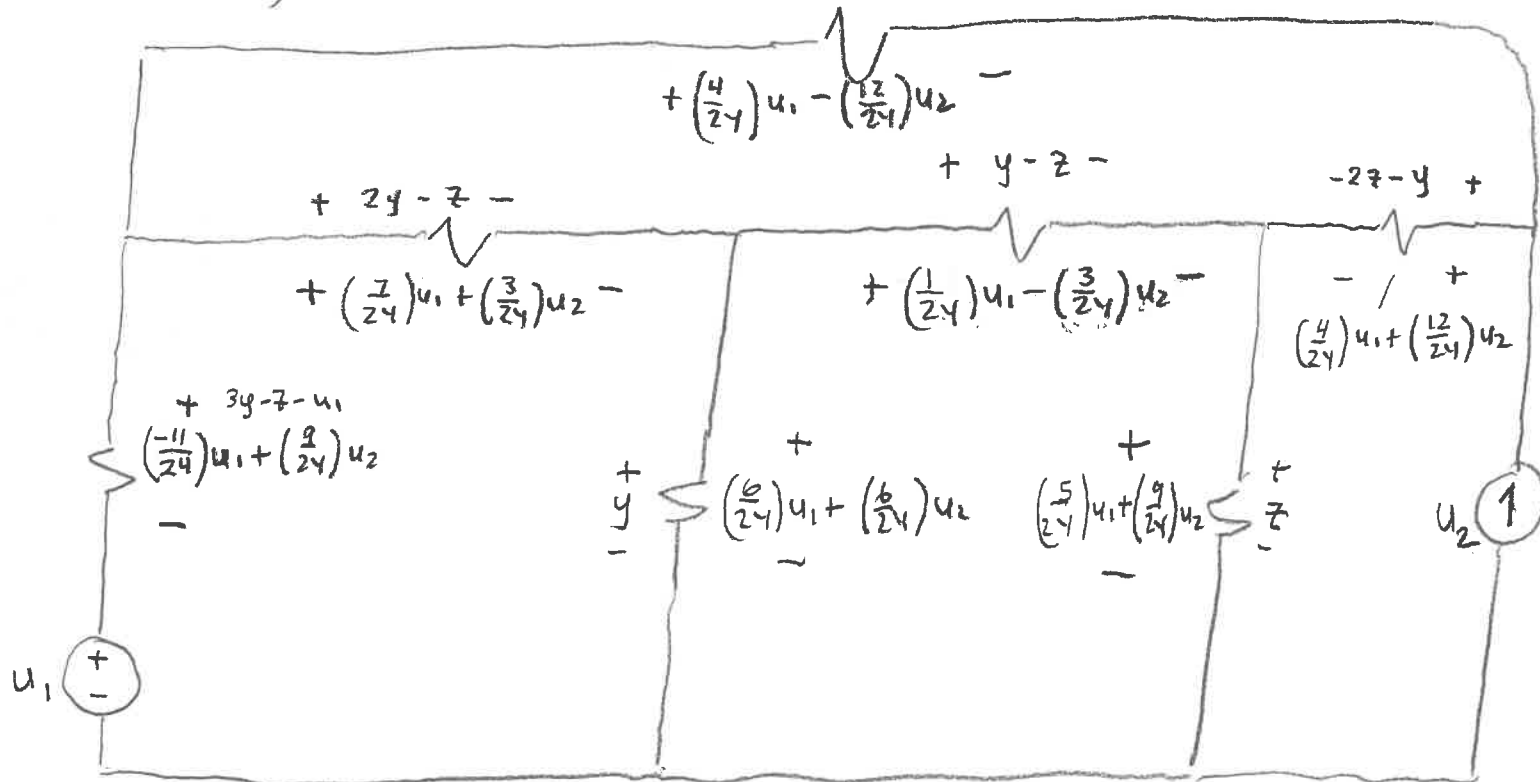

Note: KVL & KCL are satisfied everywhere!
(Ohm)

... consistent summary on the circuit
suggests that our solution for y & z
are correct!!!

