

Exam Rules

(As discussed in class & ^{"formally"} announced)

Exam #1

Fri 2/23/24


- 1 One $8\frac{1}{2}" \times 11"$ sheet permitted;
otherwise closed books, closed notes, closed phones,
open minds!
- 2 Calculator permitted (no computer!!; no phone!!!)
- 3 NO PHONES ! Phones should not be visible at all!
A visible phone will result in a zero
grade for the exam!
- 4 Write full name legibly on each page provided.
- 5 Please show all work. Write your solutions on the pages
provided. (No other pages should be used!)
- 6 Clearly label voltages and currents on circuits provided.
- 7 Use variables provided! (No additional variables!)
- 8 Unreadable work will receive no credit.
- 9 Please place important equations and answers within boxes.
- 10 Please turn in solutions to me at end of period!
- 11 PLEASE DO NOT CHEAT!!! 😐

Problem # 1

Relate y to u_1, u_2, u_3

(All $R=1$)


2/8

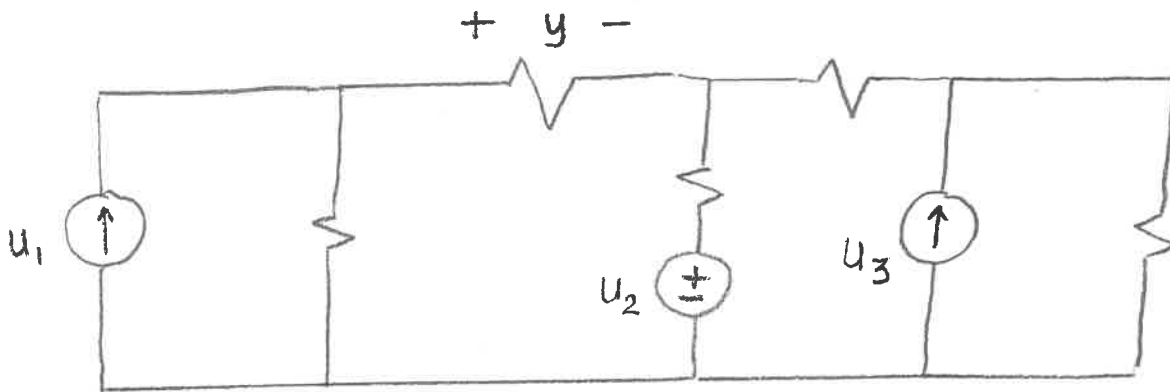

2/8

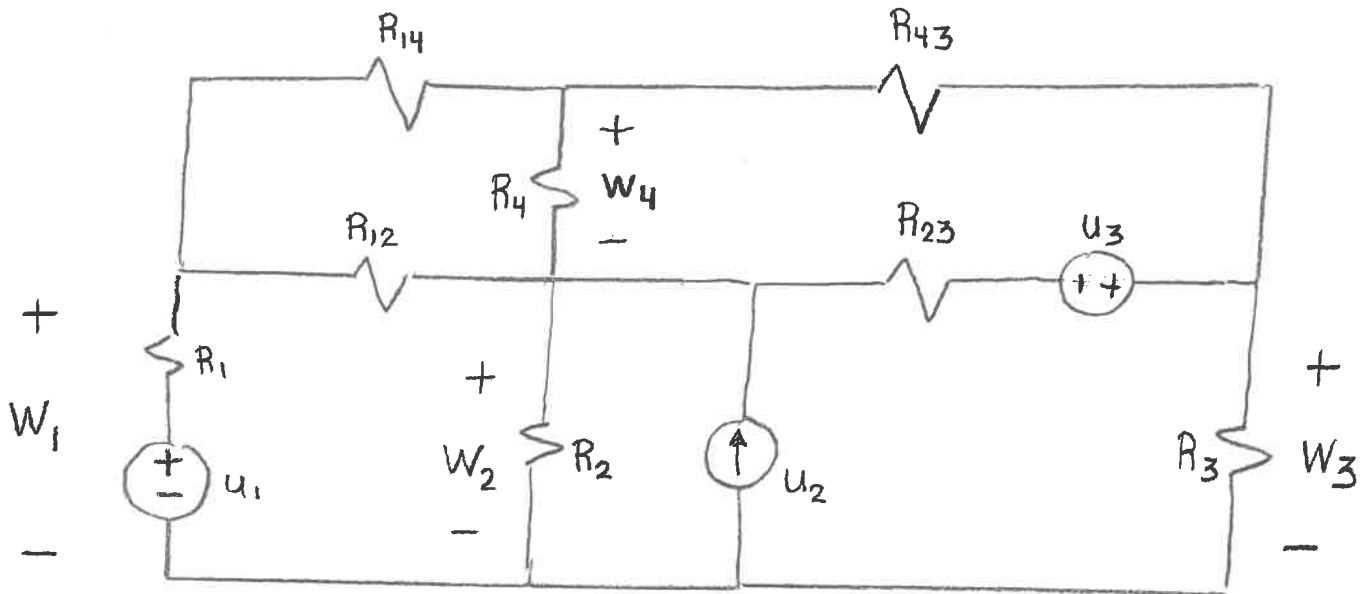
Problem # 2

Relate W_1, W_2, W_3, W_4 to u_1, u_2, u_3 (Nodal Analysis)



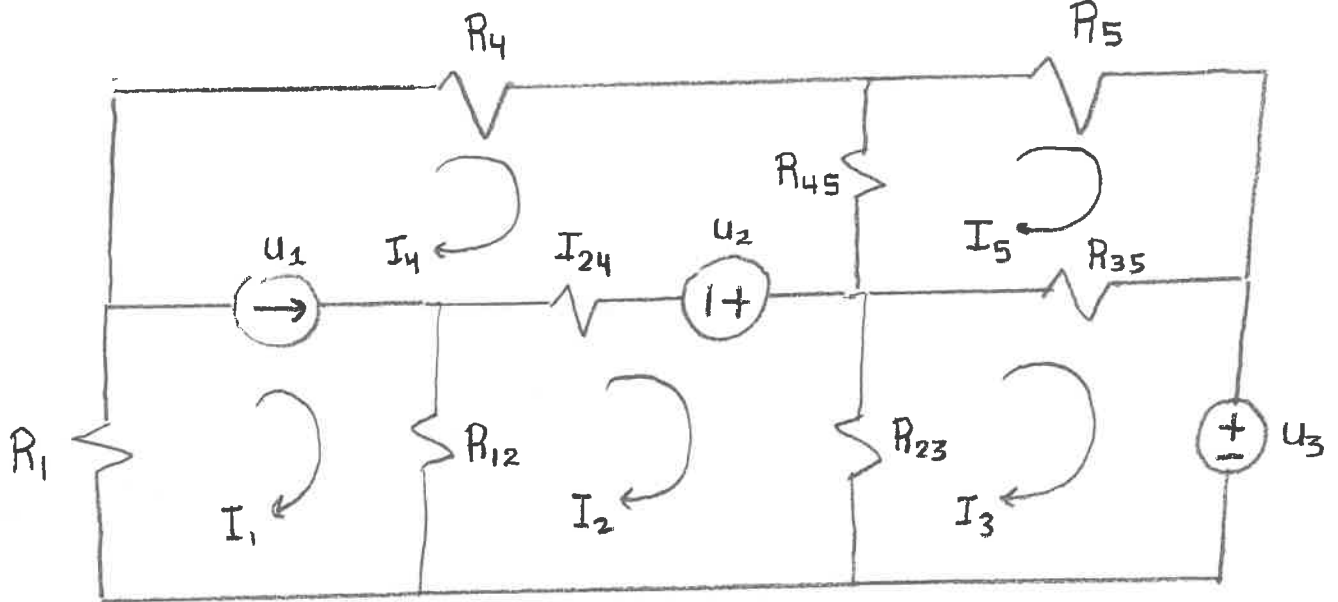Problem # 3

Relate I_1, I_2, I_3, I_4, I_5 to u_1, u_2, u_3 (Mesh Analysis)




Problem #4

Find a Thevenin equivalent at y

(Thevenin
Equivalent)

(All $R=1$)

(looking rightward)

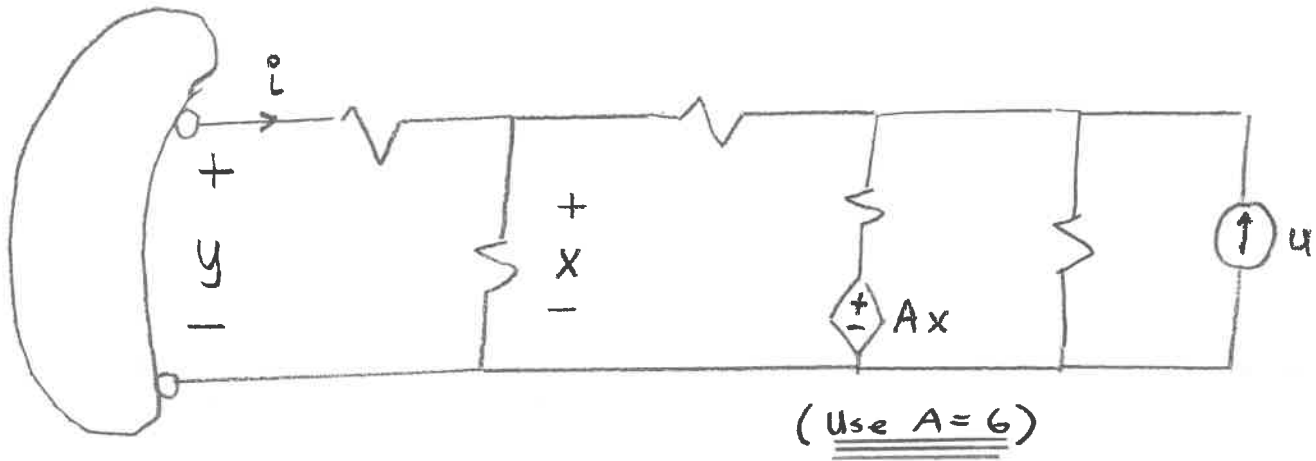


Problem # 5

Find a Thevenin equivalent at y

(Thevenin
Equivalent)


(All $R=1$)

(looking leftward)

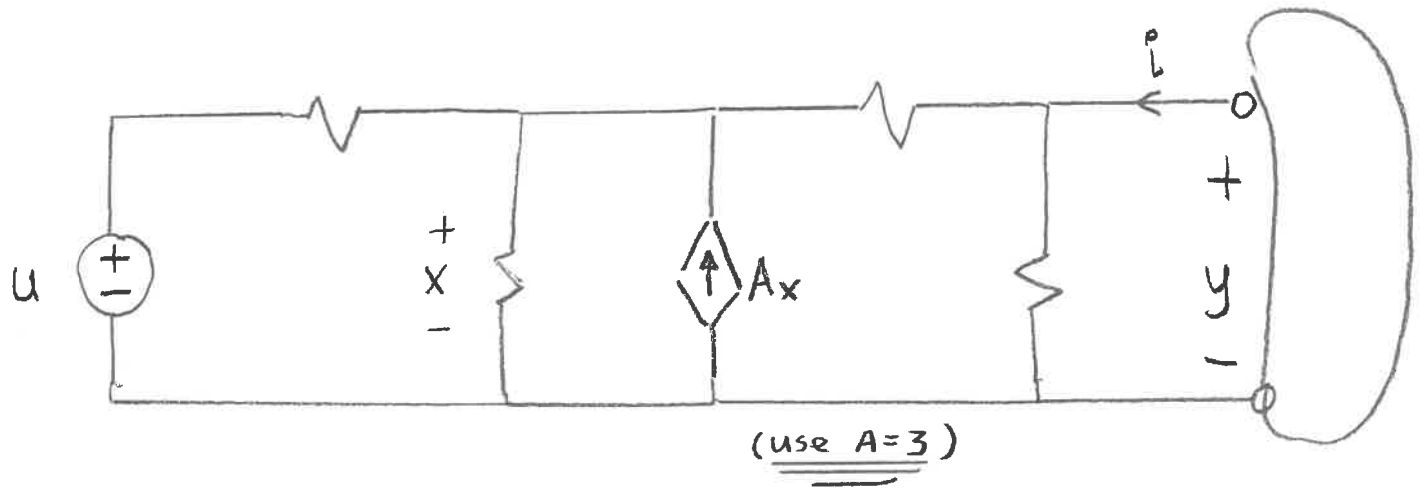

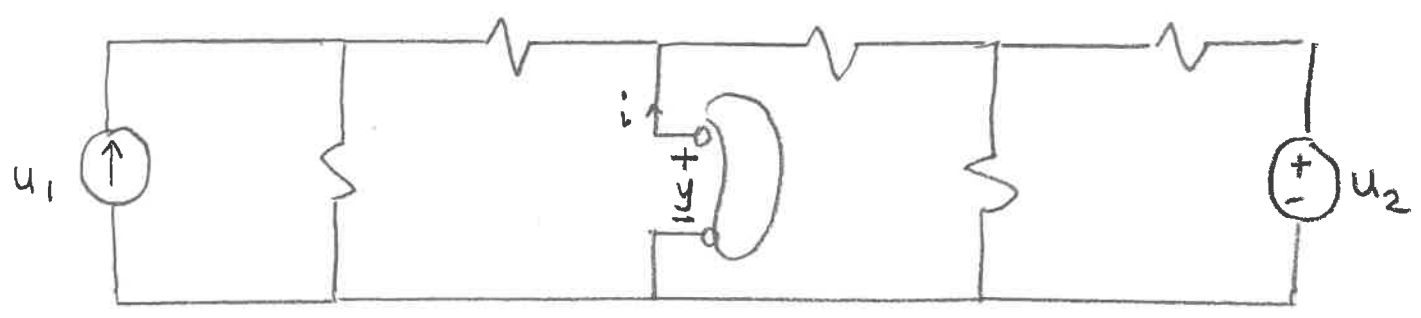Problem # 6

Find a Thevenin equivalent at y (Thevenin Equivalent)
(All $R=1$)




Problem #7

Relate y, z, u_1, u_2, u_3

(All $R=1$)

(Introduction
of
 z)

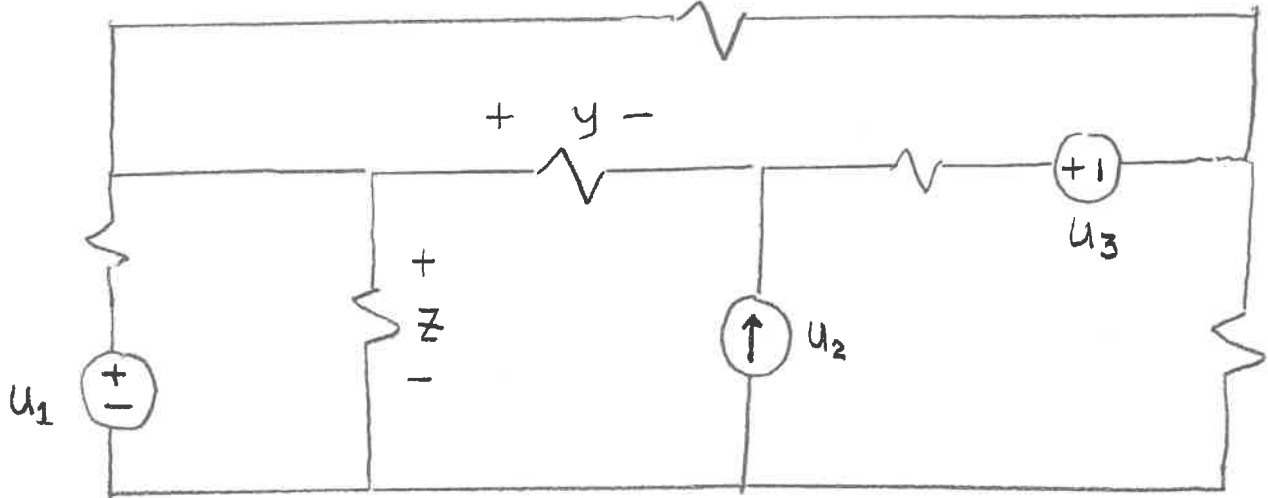

Solutions

to Exam #1

Fri 2/23/24

Dr. A.A. Rodriguez, copy right

(all rights reserved)


(19 pages follow)

=

Problem #1

Relate y to u_1, u_2, u_3 (All $R=1$)

1/19

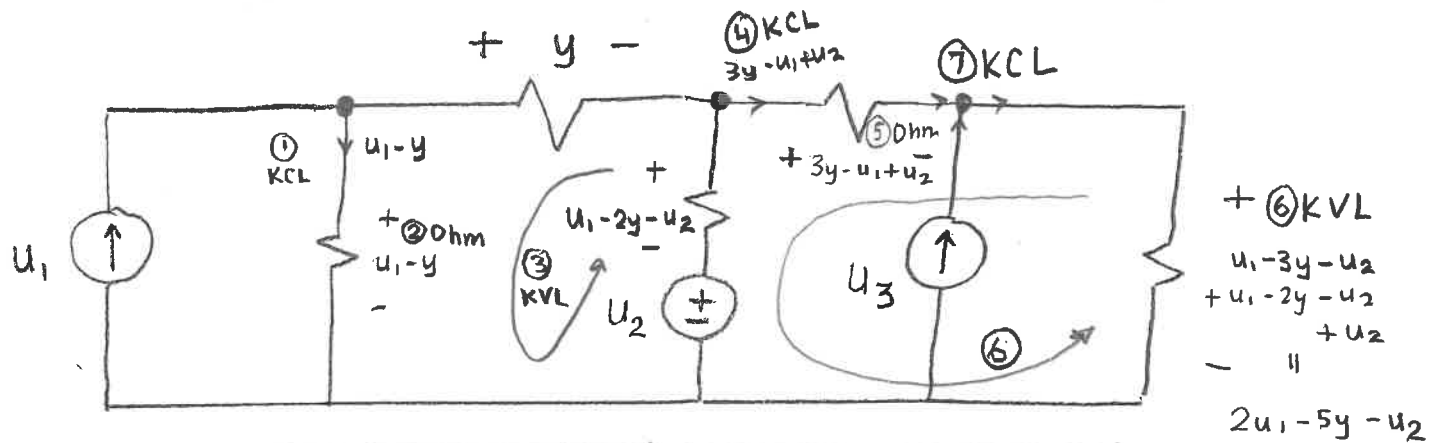

$$\textcircled{7} \text{ KCL} = \left(\frac{3y - u_1 + u_2}{1} \right) + u_3 = \left(\frac{2u_1 - 5y - u_2}{1} \right)$$



algebra

$$8y = 3u_1 - 2u_2 - u_3$$

$$\Rightarrow y = \left(\frac{3}{8} \right) u_1 + \left(-\frac{2}{8} \right) u_2 + \left(-\frac{1}{8} \right) u_3$$

Above was found via KVL, KCL, Ohm.

Now, let's solve via source transf:

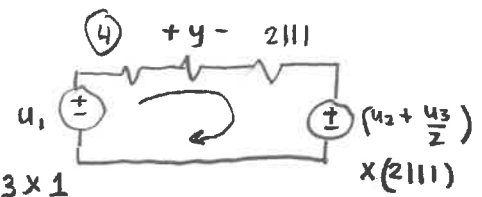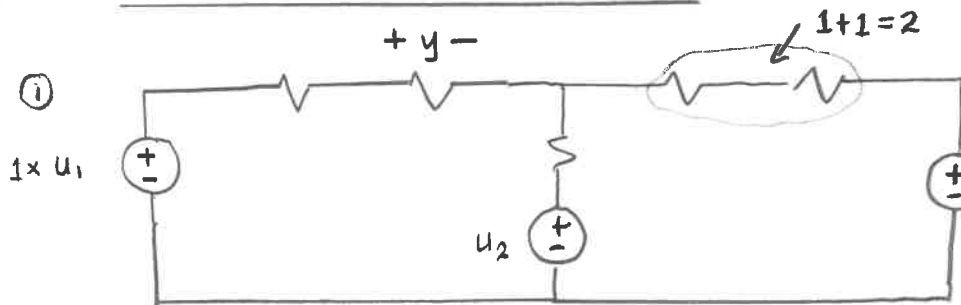

$$\textcircled{5} \text{ KVL} = u_1 = y + y + (2||1)y + (u_2 + \frac{u_3}{2})(2||1)$$

$$u_1 = y \left[1 + 1 + \frac{2}{3} \right] + \left[u_2 + \frac{u_3}{2} \right] \left(\frac{2}{3} \right)$$

$$3u_1 = y \left[3 + 3 + 2 \right] + \left(u_2 + \frac{u_3}{2} \right) (2)$$

$$8y = 3u_1 - 2u_2 - u_3$$

$$\Rightarrow y = \left(\frac{3}{8} \right) u_1 + \left(-\frac{2}{8} \right) u_2 + \left(-\frac{1}{8} \right) u_3$$


😊

✓✓✓

Problem # 2

Relate (W_1, W_2, W_3, W_4) to (U_1, U_2, U_3) (Nodal Analysis)

2/19/

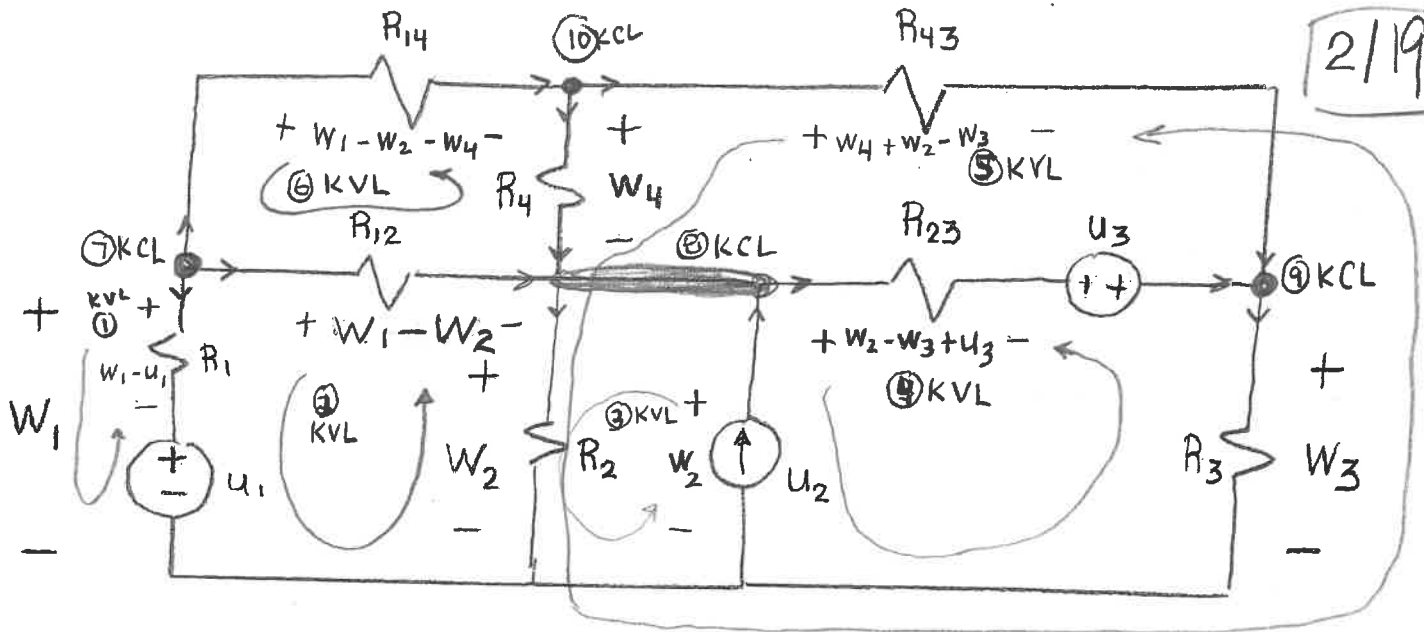
Need 4 eqs in 4 unknowns $W_1, 2, 3, 4$. $(\sum i_{\text{leaving}} = 0)$

⑦ KCL =



$$\left(\frac{W_1 - U_1}{R_1} \right) + \left(\frac{W_1 - W_2 - W_4}{R_{14}} \right) + \left(\frac{W_1 - W_2}{R_{12}} \right) = 0$$

⑧ KCL =

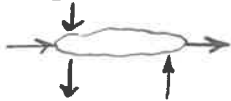

$$\left(\frac{W_1 - W_2}{R_{12}} \right) + \left(\frac{W_4}{R_4} \right) + (U_2) = \left(\frac{W_2}{R_2} \right) + \left(\frac{W_2 - W_3 + U_3}{R_{23}} \right)$$

⑨ KCL =



$$\left(\frac{W_2 - W_3 + U_3}{R_{23}} \right) + \left(\frac{W_4 + W_2 - W_3}{R_{43}} \right) = \left(\frac{W_3}{R_3} \right)$$

⑩ KCL =



$$\left(\frac{W_1 - W_2 - W_4}{R_{14}} \right) = \left(\frac{W_4}{R_4} \right) + \left(\frac{W_4 + W_2 - W_3}{R_{43}} \right)$$

Next, you'll want to put the above in matrix-vector form
 - a form that can be fed to your calculator or MATLAB...

Toward the desired matrix-form, we rewrite our 4 eqs as follows:

3/19

$$\left(\frac{1}{R_1} + \frac{1}{R_{14}} + \frac{1}{R_{12}}\right)w_1 - \left(\frac{1}{R_{14}} + \frac{1}{R_{12}}\right)w_2 + 0w_3 - \left(\frac{1}{R_{14}}\right)w_4 = \left(\frac{1}{R_1}\right)u_1$$

$$\left(\frac{1}{R_{12}}\right)w_1 - \left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{R_{23}}\right)w_2 + \left(\frac{1}{R_{23}}\right)w_3 + \left(\frac{1}{R_4}\right)w_4 = (-1)u_2 + \left(\frac{1}{R_{23}}\right)u_3$$

$$0w_1 + \left(\frac{1}{R_{23}} + \frac{1}{R_{43}}\right)w_2 - \left(\frac{1}{R_{23}} + \frac{1}{R_{43}} + \frac{1}{R_3}\right)w_3 + \left(\frac{1}{R_{43}}\right)w_4 = \left(\frac{-1}{R_{23}}\right)u_3$$

$$\left(\frac{1}{R_{14}}\right)w_1 - \left(\frac{1}{R_{14}} + \frac{1}{R_{43}}\right)w_2 + \left(\frac{1}{R_{43}}\right)w_3 - \left(\frac{1}{R_{14}} + \frac{1}{R_4} + \frac{1}{R_{43}}\right)w_4 = 0$$

From the above, we get:

$$\begin{aligned} & \begin{matrix} \downarrow A \end{matrix} \begin{bmatrix} \left(\frac{1}{R_1} + \frac{1}{R_{14}} + \frac{1}{R_{12}}\right) & -\left(\frac{1}{R_{14}} + \frac{1}{R_{12}}\right) & 0 & -\frac{1}{R_{14}} \\ \frac{1}{R_{12}} & -\left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{R_{23}}\right) & \frac{1}{R_{23}} & \frac{1}{R_4} \\ 0 & \left(\frac{1}{R_{23}} + \frac{1}{R_{43}}\right) & -\left(\frac{1}{R_{23}} + \frac{1}{R_{43}} + \frac{1}{R_3}\right) & \frac{1}{R_{43}} \\ \frac{1}{R_{14}} & -\left(\frac{1}{R_{14}} + \frac{1}{R_{43}}\right) & \left(\frac{1}{R_{43}}\right) & -\left(\frac{1}{R_{14}} + \frac{1}{R_4} + \frac{1}{R_{43}}\right) \end{bmatrix} \begin{matrix} \downarrow x \\ \begin{bmatrix} w_1 \\ w_2 \\ w_3 \\ w_4 \end{bmatrix} \end{matrix} \\ & = \begin{bmatrix} \frac{1}{R_1} \\ 0 \\ 0 \\ 0 \end{bmatrix} u_1 + \begin{bmatrix} 0 \\ -1 \\ 0 \\ 0 \end{bmatrix} u_2 + \begin{bmatrix} 0 \\ \frac{1}{R_{23}} \\ -\frac{1}{R_{23}} \\ 0 \end{bmatrix} u_3 \\ & \quad \uparrow b_1 \quad \quad \quad \uparrow b_2 \quad \quad \quad \uparrow -b_3 \end{aligned}$$

The above has the matrix-vector form =

$$Ax = b_1 u_1 + b_2 u_2 + b_3 u_3$$

4/19

If $\begin{cases} Ax_1 = b_1 \\ Ax_2 = b_2 \\ Ax_3 = b_3 \end{cases}$ $\leftarrow \begin{cases} \text{Feed } (A, b_i) \text{ to your calculator} \\ \text{or MATLAB to get the } x_i \end{cases}$

then the desired general solution is given by =

$$x = \begin{bmatrix} w_1 \\ w_2 \\ w_3 \\ w_4 \end{bmatrix} = x_1 u_1 + x_2 u_2 + x_3 u_3$$

Why?

$$\begin{aligned} Ax &= A(x_1 u_1 + x_2 u_2 + x_3 u_3) \\ &= (Ax_1)u_1 + (Ax_2)u_2 + (Ax_3)u_3 \\ &= b_1 u_1 + b_2 u_2 + b_3 u_3 \end{aligned}$$

Note:

For $R_i = 1$


$$A = \begin{bmatrix} 3 & -2 & 0 & -1 \\ 1 & -3 & 1 & 1 \\ 0 & 2 & -3 & 1 \\ 1 & -2 & 1 & -3 \end{bmatrix}$$

$$b_1 = \begin{bmatrix} 1 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$b_2 = \begin{bmatrix} 0 \\ -1 \\ 0 \\ 0 \end{bmatrix}$$

$$b_3 = \begin{bmatrix} 0 \\ 1 \\ -1 \\ 0 \end{bmatrix}$$

Problem # 3

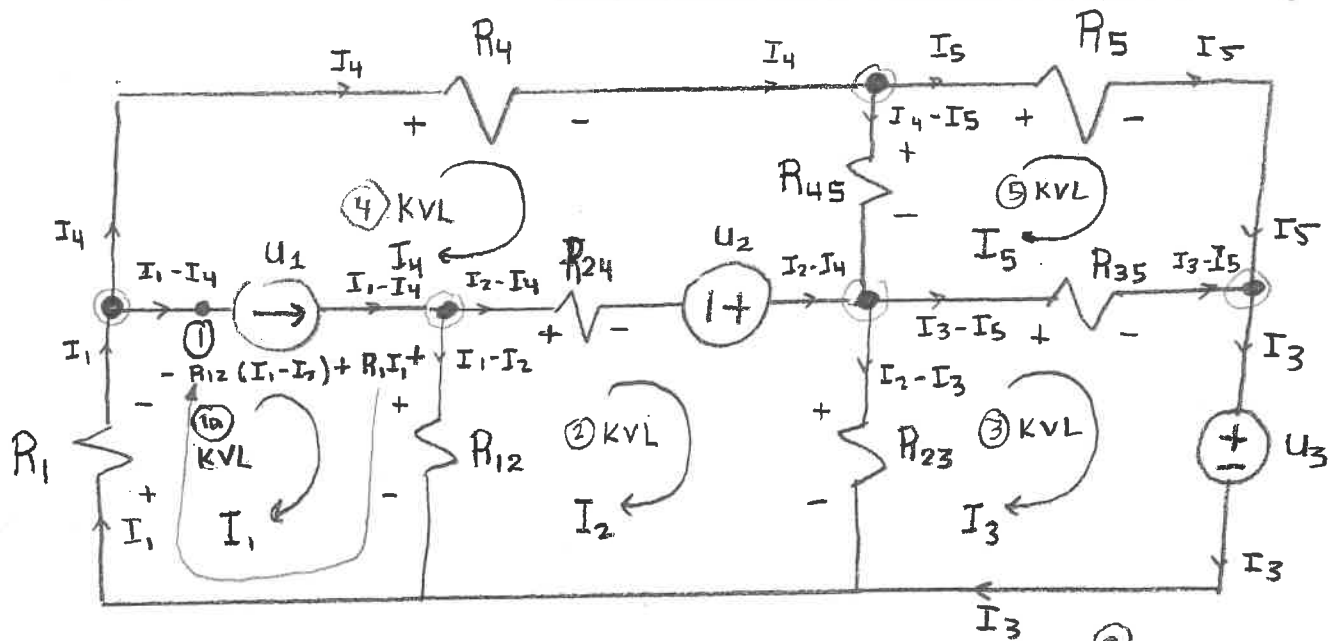Relate I_1, I_2, I_3, I_4, I_5 to U_1, U_2, U_3 (Mesh Analysis)

Note: KCL is satisfied at each of the 5 encircled nodes.
 We shall now get the required 5 eqs in the 5 unknowns I_1, I_2, I_3, I_4, I_5 .

5/19

$$\textcircled{1} \text{ KCL} = I_1 - I_4 = U_1$$

$$\textcircled{2} \text{ KVL} = R_{12}(I_1 - I_2) = R_{24}(I_2 - I_4) - U_2 + R_{23}(I_2 - I_3)$$

$$\textcircled{3} \text{ KVL} = R_{23}(I_2 - I_3) = R_{35}(I_3 - I_5) + U_3$$

$$\textcircled{4} \text{ KVL} = R_{45}(I_4 - I_5) + (-R_4 I_4) = U_2 - R_{24}(I_2 - I_4) + [R_1 I_1 + R_{12}(I_1 - I_2)]$$

$$\textcircled{5} \text{ KVL} = R_{45}(I_4 - I_5) = R_5 I_5 - R_{35}(I_3 - I_5)$$

Next, you'll want to put the above in matrix - vector form
 - a form that can be fed to your calculator or MATLAB...

The above eqs may be rewritten as follows:

6/19

$$(1) I_1 + 0(I_2) + 0 I_3 + (-1) I_4 = u_1$$

$$(R_{12}) I_1 - (R_{12} + R_{24} + R_{23}) I_2 + R_{23} I_3 + R_{24} I_4 = -u_2$$

$$0 I_1 + (R_{23}) I_2 - (R_{23} + R_{35}) I_3 + 0 I_4 + (R_{35}) I_5 = u_3$$

$$-(R_1 + R_{12}) I_1 + (R_{24} + R_{12}) I_2 + 0 I_3 - (R_4 + R_{24}) I_4 + R_{45} I_5 = u_2$$

$+ R_{45}$

$$0 I_1 + 0 I_2 + (R_{35}) I_3 + (R_{45}) I_4 - (R_{45} + R_5 + R_{35}) I_5 = 0$$

From the above, we get the desired matrix-vector form =

$$\begin{bmatrix}
 1 & 0 & 0 & -1 & 0 \\
 R_{12} & -(R_{12} + R_{24} + R_{23}) & R_{23} & R_{24} & 0 \\
 0 & R_{23} & -(R_{23} + R_{35}) & 0 & R_{35} \\
 -(R_1 + R_{12}) & (R_{24} + R_{12}) & 0 & -(R_4 + R_{24}) & R_{45} \\
 0 & 0 & R_{35} & R_{45} & -(R_{45} + R_5 + R_{35})
 \end{bmatrix}
 \begin{matrix}
 \downarrow A \\
 \\
 \\
 \\
 \nearrow
 \end{matrix}
 \begin{matrix}
 x \\
 \\
 \\
 \\
 \\
 \end{matrix}
 \begin{bmatrix}
 I_1 \\
 I_2 \\
 I_3 \\
 I_4 \\
 I_5
 \end{bmatrix}$$

$$= \begin{bmatrix} 1 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} u_1 + \begin{bmatrix} 0 \\ -1 \\ 0 \\ 1 \\ 0 \end{bmatrix} u_2 + \begin{bmatrix} 0 \\ 0 \\ 1 \\ 0 \\ 0 \end{bmatrix} u_3$$

$\uparrow b_1$
 $\uparrow b_2$
 $\uparrow b_3$

The above has the desired matrix-vector form

$$Ax = b_1 u_1 + b_2 u_2 + b_3 u_3$$

Given that we have

$$Ax = b_1 u_1 + b_2 u_2 + b_3 u_3$$

7/19

$$\text{If } \begin{cases} Ax_1 = b_1 \\ Ax_2 = b_2 \\ Ax_3 = b_3 \end{cases}$$

then the general solution is given by =

$$X = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{bmatrix} = x_1 u_1 + x_2 u_2 + x_3 u_3$$

Why?

$$\begin{aligned} Ax &= A(x_1 u_1 + x_2 u_2 + x_3 u_3) \\ &= (Ax_1) u_1 + (Ax_2) u_2 + (Ax_3) u_3 \\ &= b_1 u_1 + b_2 u_2 + b_3 u_3 \end{aligned}$$

Note=

For $R_i = 1$, $A = \begin{bmatrix} 1 & 0 & 0 & -1 & 0 \\ 1 & -3 & 1 & 1 & 0 \\ 0 & 1 & -2 & 0 & 1 \\ -2 & 2 & 0 & -3 & 1 \\ 0 & 0 & 1 & 1 & -3 \end{bmatrix}$

$$b_1 = \begin{bmatrix} 1 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad b_2 = \begin{bmatrix} 0 \\ -1 \\ 0 \\ 1 \\ 0 \end{bmatrix} \quad b_3 = \begin{bmatrix} 0 \\ 0 \\ 1 \\ 0 \\ 0 \end{bmatrix}$$


Problem # 4

Find a Thevenin equivalent at y

(Thevenin
Equivalent)


(All $R = 1$)

(looking rightward)

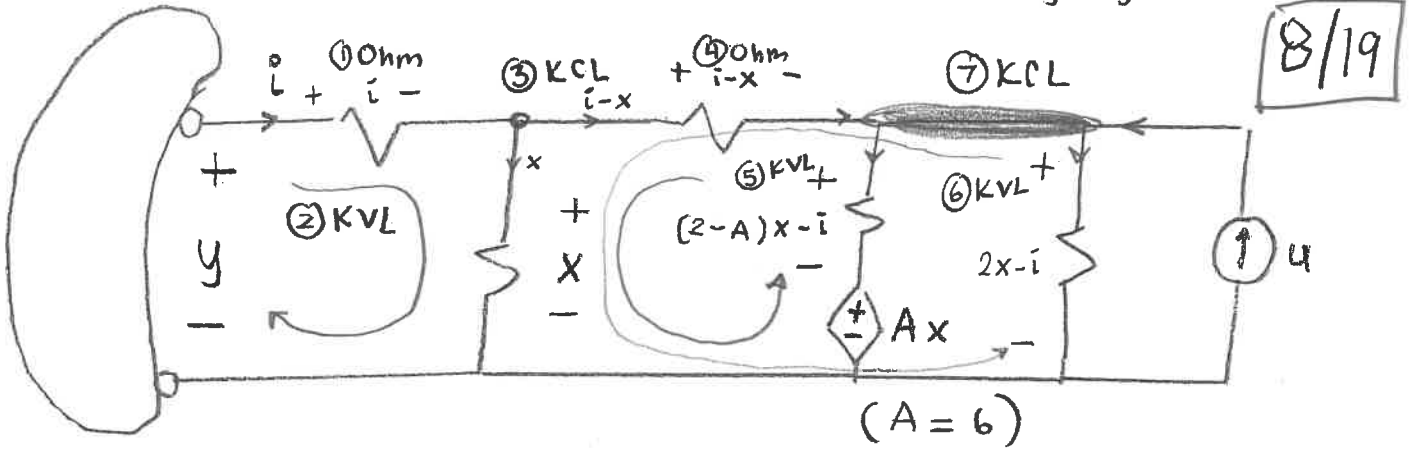

② KVL = $y = i + x \Rightarrow x = y - i$

⑦ KCL =



$$(i-x) + (u) = \left(\frac{(2-A)x-i}{1} \right) + \left(\frac{2x-i}{1} \right)$$

algebra $\Rightarrow 3i + u = \overset{\sqrt{1+2+2}}{(5-A)x} \xrightarrow{x=y-i}$
 $= (5-A)[y-i]$

$$\Rightarrow \left(\frac{3}{5-A}\right)i + \left(\frac{1}{5-A}\right)u = y - i$$

$$\Rightarrow y = \left[1 + \frac{3}{5-A} \right] i + \left[\frac{1}{5-A} \right] u$$

$$= \left[\frac{5-A+3}{5-A} \right] i + \left[\frac{1}{5-A} \right] u$$

$$y = \left[\frac{8-A}{5-A} \right] i + \left[\frac{1}{5-A} \right] u$$


$$R_{th} = \frac{8-A}{5-A}$$

$$V_{th} = \left(\frac{1}{5 - A} \right) u$$



Note: For $A=6$, $R_{th} = -2$ & $V_{th} = -u$ & $y = -2i - u$

Lets redo the above via source transf=


9/19

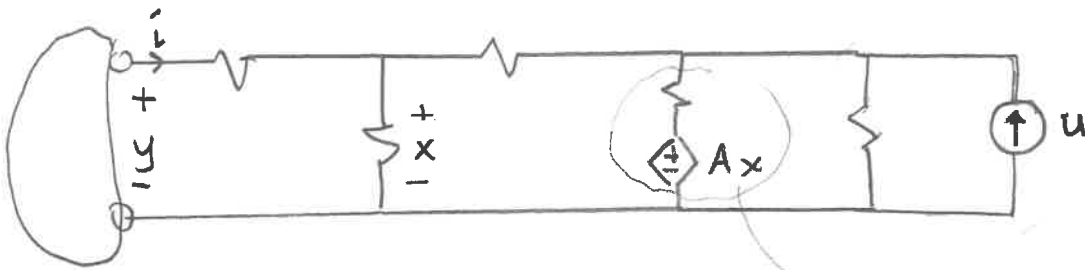

This can be rewritten as=

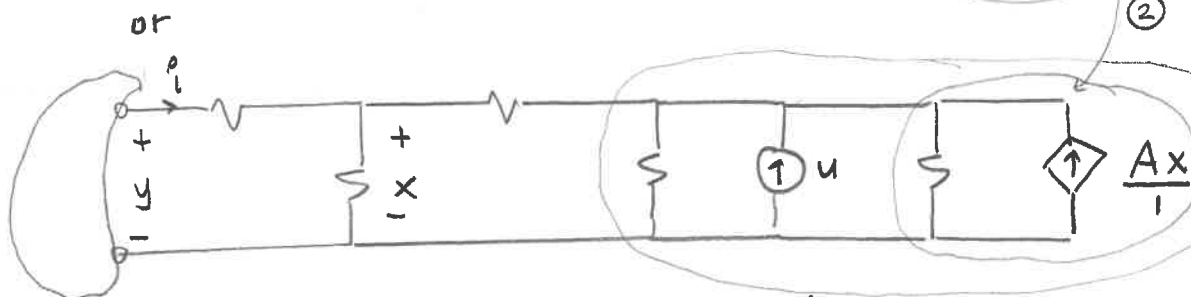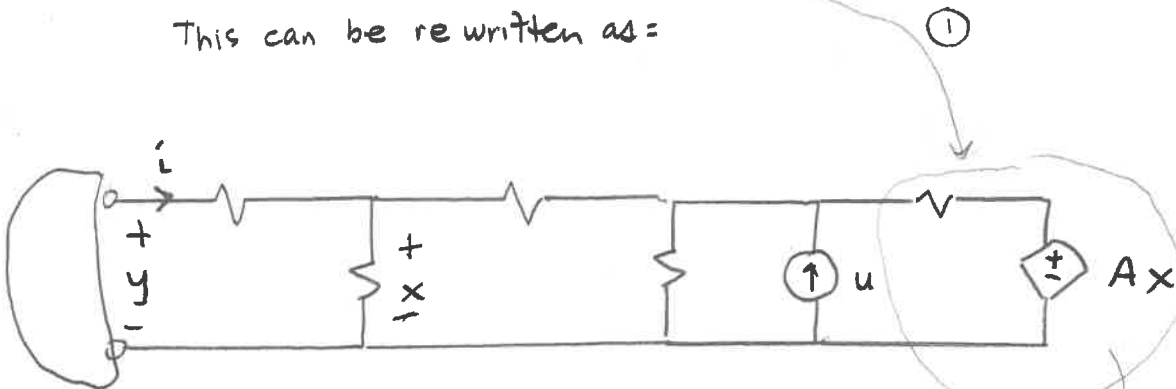

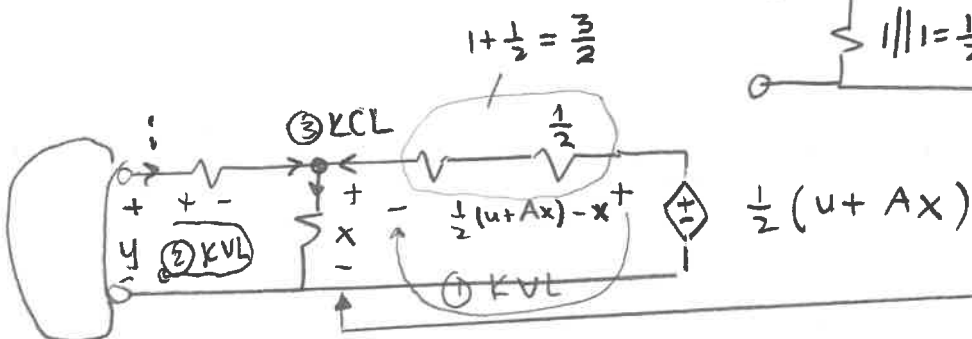Can do source transf on dependent sources so long as you do not destroy the dependant variable x !!!



② KVL: $y = i + x \Rightarrow x = y - i$

③ KCL: $i + \left(\frac{\frac{1}{2}(u + Ax) - x}{3/2} \right) = \left(\frac{x}{1} \right)$

algebra $3i + (u + Ax - 2x) = 3x$

Note that dependent variable x was NOT destroyed!

algebra

$$3i + u = (5-A)x$$

$$= (5-A)(y-i)$$

$$\Rightarrow y-i = \left[\frac{3}{5-A} \right] i + \left[\frac{1}{5-A} \right] u$$

$$y = \left[1 + \frac{3}{5-A} \right] i + \left[\frac{1}{5-A} \right] u$$

$$= \left[\frac{5-A+3}{5-A} \right] i + \left[\frac{1}{5-A} \right] u$$

$$y = \left[\frac{8-A}{5-A} \right] i + \left[\frac{1}{5-A} \right] u$$

$$R_{th} = \frac{8-A}{5-A} \stackrel{A=6}{=} -2$$


$$V_{th} = \left[\frac{1}{5-A} \right] u \stackrel{A=6}{=} -u$$

which is what we obtained earlier!




i.e. $y = -2i - u$ for $A = 6$

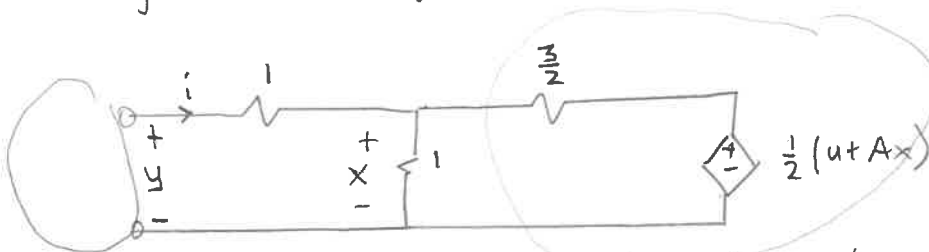
To get the above, we started with the following circuit (see previous page)



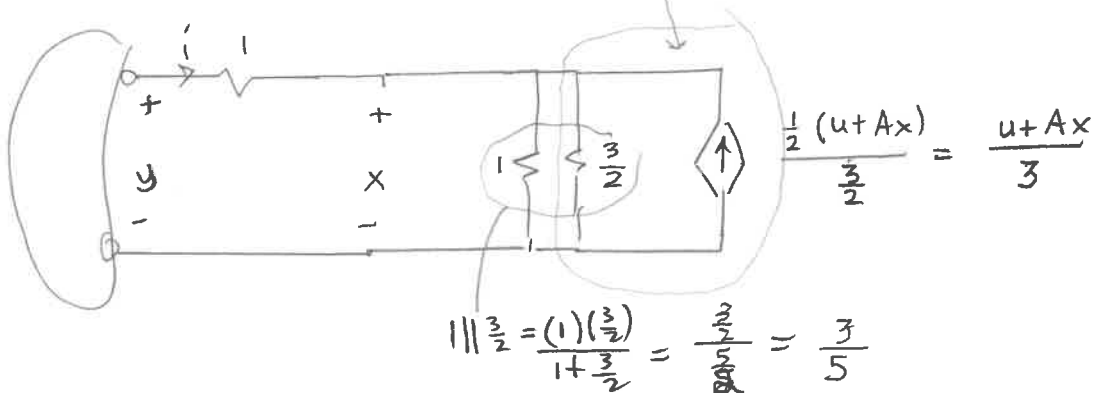
Rather than using KVL, KCL, Ohm's, let's do another source transformation:



11/19

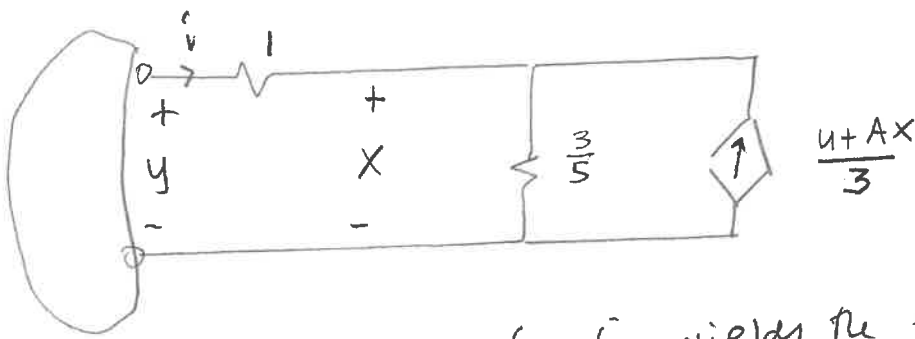

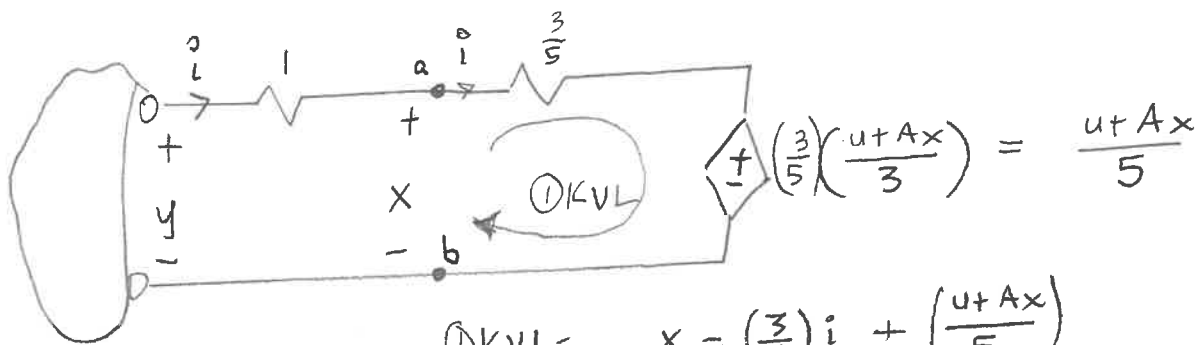One final transformation yields the following




$$\begin{aligned} \text{① KVL} = X &= \left(\frac{3}{5}\right)i + \left(\frac{u+Ax}{5}\right) \\ &= \left(\frac{3}{5}\right)i + \frac{u}{5} + \frac{A}{5}X \end{aligned}$$

$$\Rightarrow X\left(1 - \frac{A}{5}\right) = \left(\frac{3}{5}\right)i + \frac{u}{5}$$

$$\Rightarrow X(5-A) = 3i + u$$

$$\Rightarrow \boxed{X = \left(\frac{3}{5-A}\right)i + \left(\frac{1}{5-A}\right)u}$$

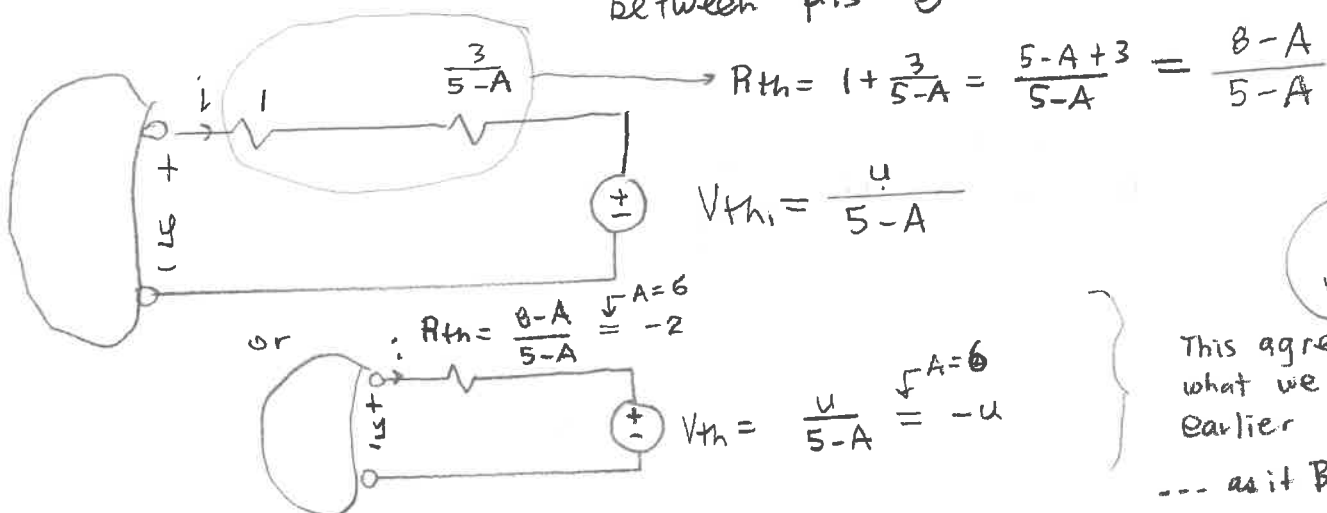↑
This gives us a thevenin equivalent
between pts a & b.



This agrees with
what we obtained
earlier
... as it BETTER!


12/19

Problem # 5

Find a Thevenin equivalent at y (Thevenin Equivalent)

(All R=1)

(looking leftward)

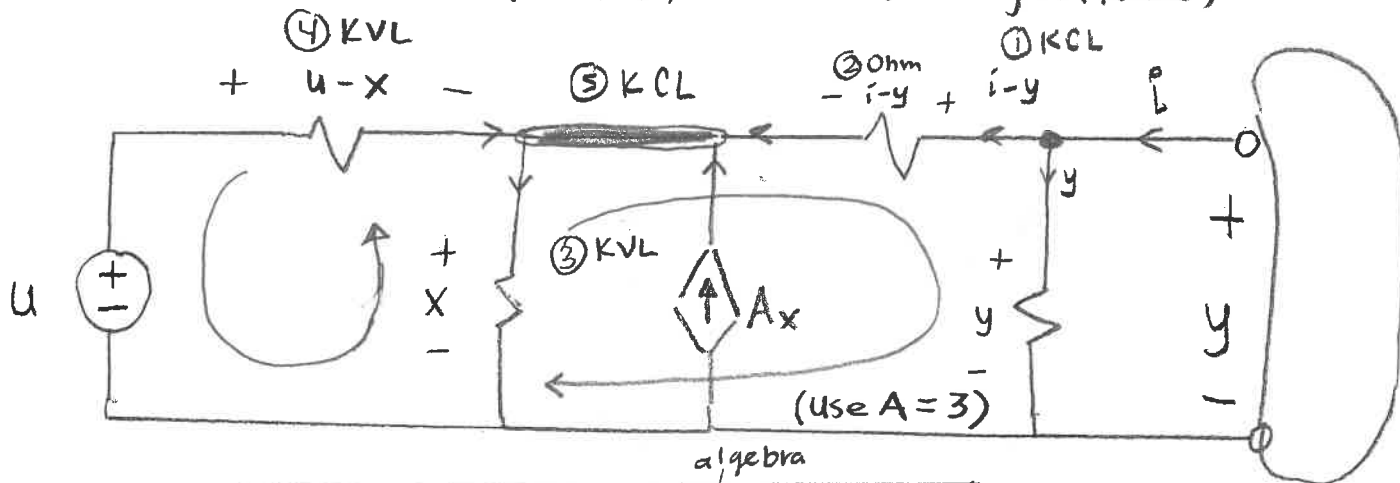

$$\textcircled{3} \text{ KVL} = \boxed{X = -[i-y] + y = -i + 2y}$$

⑤ KCL:

$$\boxed{\left(\frac{u-x}{1}\right) + (i-y) + (Ax) = \left(\frac{x}{1}\right)}$$

algebra

$$\Rightarrow u + i = x[2-A] + y$$

$$= (2y-i)(2-A) + y$$

algebra

$$\Rightarrow u + i[1 + 2-A] = y[2(2-A) + 1]$$

3-A 5-2A

$$\Rightarrow y = \left[\frac{3-A}{5-2A}\right]i + \left[\frac{1}{5-2A}\right]u$$

A=3

$$R_{th} = \frac{3-A}{5-2A} \stackrel{A=3}{=} 0$$

$$V_{th} = \left(\frac{1}{5-2A}\right)u \stackrel{A=3}{=} (-1)u$$

This means that

$$y = 0i - u = -u$$

for A=3

A=3

$$x = -i - 2u$$


Lets try to understand why we get $R_{th} = 0$ & $V_{th} = -u$ for $A=3$...

$$x = \left(\frac{1}{5-2A}\right)i + \left(\frac{2}{5-2A}\right)u$$

Problem # 5

13/19

Alternate approach via KVL, KCL, Ohm =

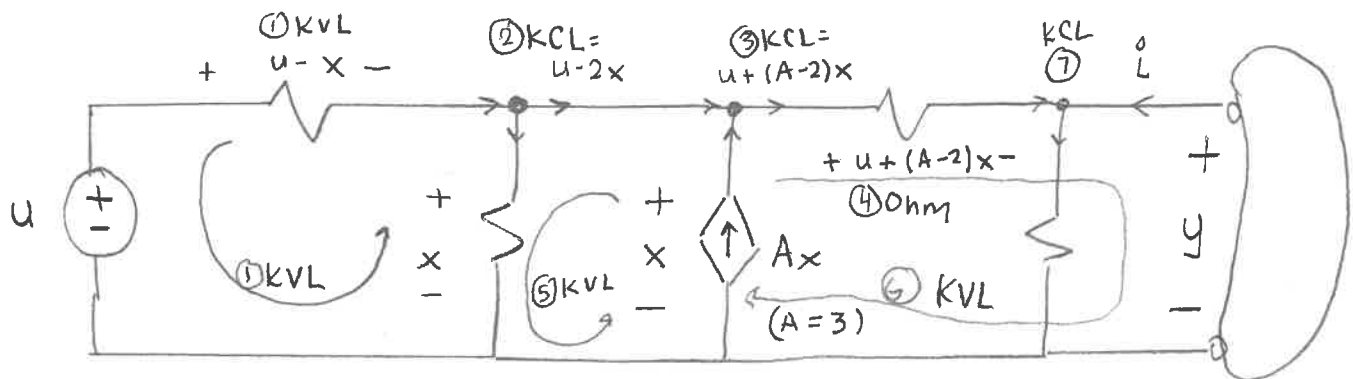

This is a quick way to get to $R_{th} = 0$ for $A=3$ but it doesn't really show us why!

$$\textcircled{6} \text{ KVL} = \boxed{x = u + (A-2)x + y}$$

$$\stackrel{A=3}{\Rightarrow} x = u + x + y \quad (x \text{ drops out of this eq for } A=3!!!)$$

$$\Rightarrow \boxed{y = -u} \Rightarrow \boxed{R_{th} = 0, V_{th} = -u}$$

Note: No additional eq^o is needed to relate y to u !

$$\textcircled{7} \text{ KCL} = \rightarrow \leftarrow \downarrow$$

$$\boxed{\left(\frac{u + (A-2)x}{1}\right) + \left(\frac{i}{1}\right) = \left(\frac{y}{1}\right)}$$

← This will be used to solve for x !

$$\Rightarrow y = i + u + (A-2)x$$

$$\stackrel{A=3}{\Rightarrow} y = i + u + x$$

$$\Rightarrow x = y - i - u = -u - i - u$$


$$\Rightarrow \boxed{x = -i - 2u}$$

Lets REALLY try to understand why we get $R_{th} = 0$!

$$\Rightarrow$$


Problem #5

14/19

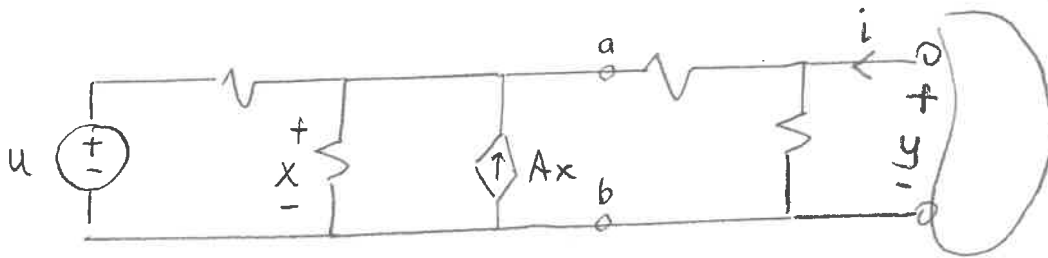


To REALLY understand why $R_{th} = 0$ for $A = 3$,
lets find a Thevenin equivalent at terminals ab looking leftward:

We have

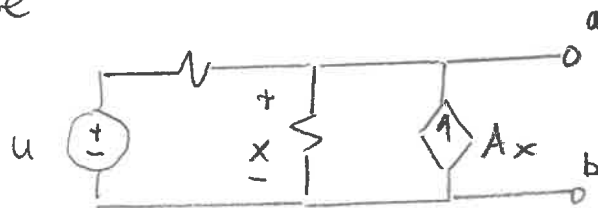

As source transf yields:

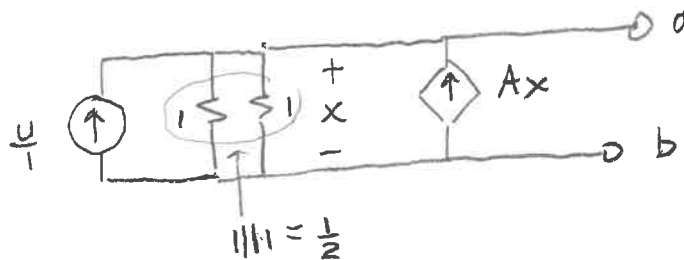

This can be rewritten as follows where w is the terminal current



Now lets relate x to $w =$

$$x = \frac{1}{2} (u + Ax + w) \quad \text{KCL}$$

$$= \frac{1}{2} u + \frac{1}{2} Ax + \frac{1}{2} w$$

$$2x = u + Ax + w$$

$$(2-A)x = w + u$$

$$x = \underbrace{\left(\frac{1}{2-A}\right)}_{R_{thab}} w + \underbrace{\left(\frac{1}{2-A}\right) u}_{V_{thab}}$$



Problem #5

15/19

from the above Thevenin equiv between a b looking leftward
we get

Note: $\frac{1}{2-A} = -1$ for $A=3$
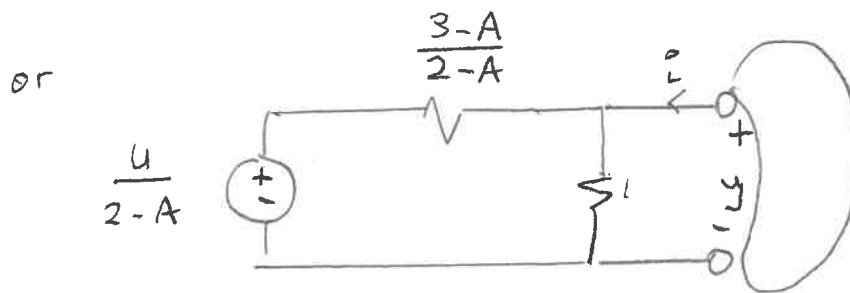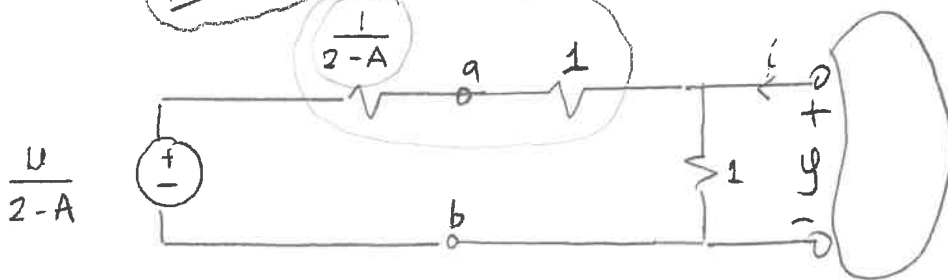
$$\frac{1}{2-A} + 1 = \frac{1+2-A}{2-A} = \frac{3-A}{2-A}$$



From this we now clearly see that


$$R_{th} = 1 \parallel \frac{3-A}{2-A}$$

BUT for $A=3$, this becomes


$$R_{th} = 1 \parallel 0 = 0!$$

One more source transf yields
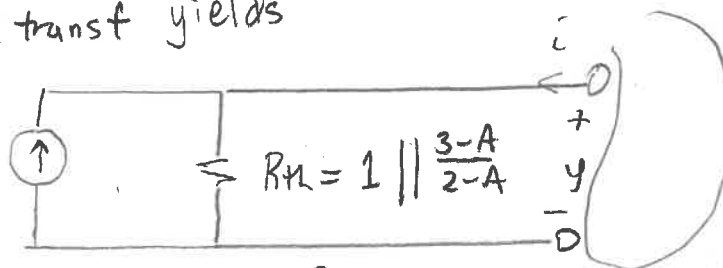
$$\left(\frac{u}{2-A}\right) \left(\frac{2-A}{3-A}\right) = \frac{u}{3-A}$$



or finally

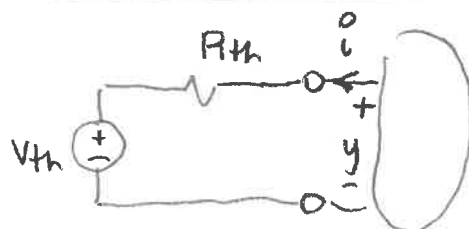

where

$$R_{th} = 1 \parallel \frac{3-A}{2-A}$$

after algebra $= \frac{3-A}{5-A}$


$$V_{th} = \frac{u}{5-A}$$

What we got
earlier!




For $A=3$, we specifically have the following=


16/19

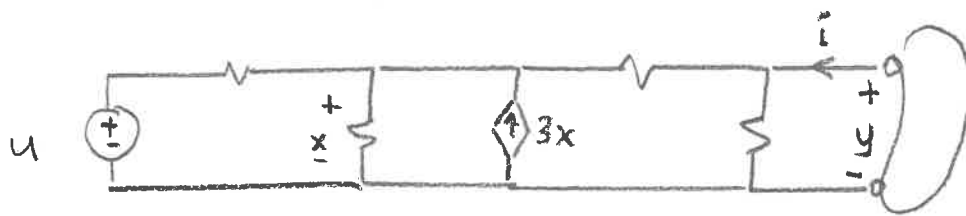

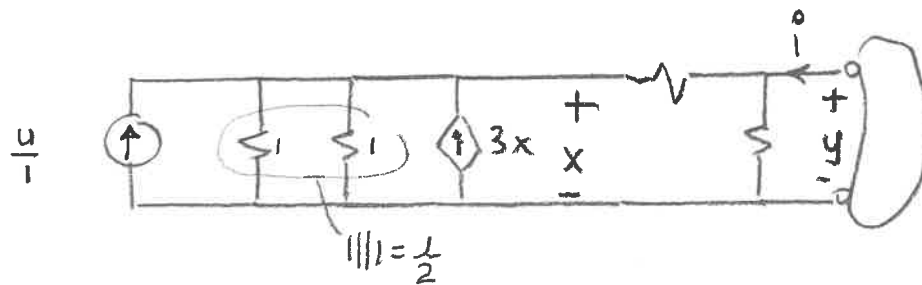Noting that voltage across $3x$ current is x , let's use source transform on the left side of the circuit:



This can be redrawn as:

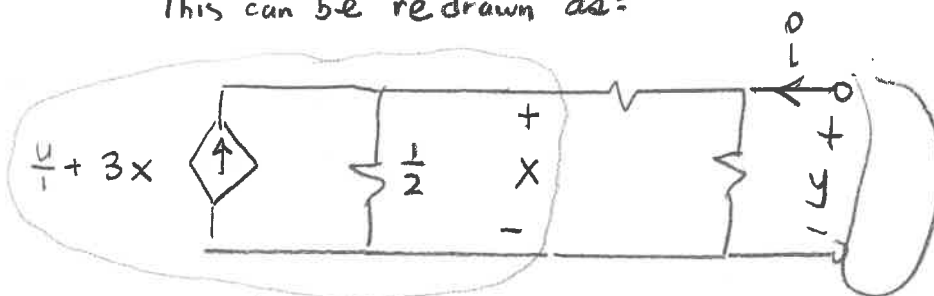

Let's find a Thevenin equiv. for this!

I (do not confuse I with i !!!)

$$\frac{u}{i} + 3x \quad \Rightarrow \quad x = \frac{1}{2} (I + \frac{u}{i} + 3x)$$


ohm KCL

$$= \frac{1}{2} I + \frac{1}{2} u + \frac{3}{2} x$$

$$\Rightarrow -\frac{1}{2} x = \frac{1}{2} I + \frac{1}{2} u$$

$$\Rightarrow x = -I - u$$
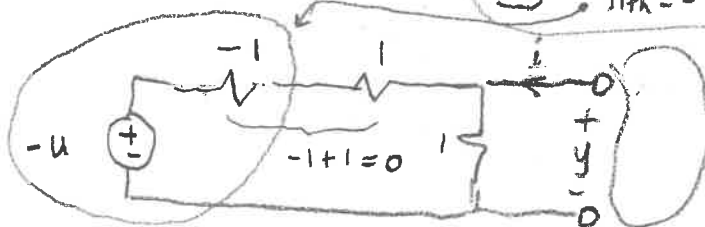
$$\Rightarrow R_{th} = -1 \quad V_{th} = -u$$



$$\Rightarrow y = 0i + (-u)$$


$$\Rightarrow y = -u$$

$$\Rightarrow R_{th} = 0 \quad V_{th} = -u$$

Problem # 6

Find a Thevenin equivalent at y (Thevenin
Equivalent y)(All $R=1$)





17/19

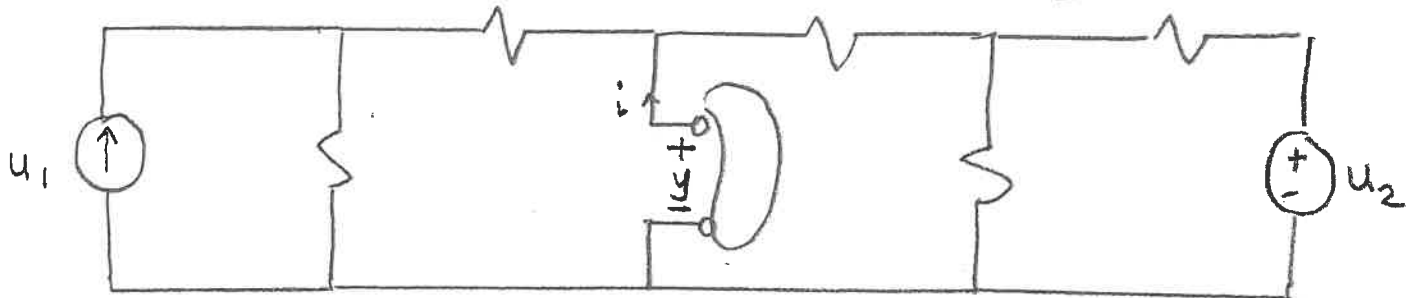


This is best done with source transformations:

Note:

Without source transf
you'll need to introduce
another variable z in
order to use KVL,
KCL, Ohm to propagate
(u, i) around the cct!

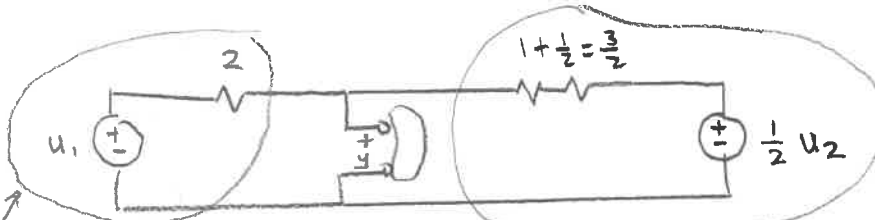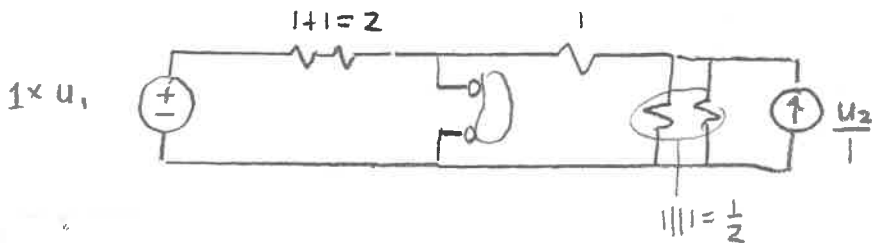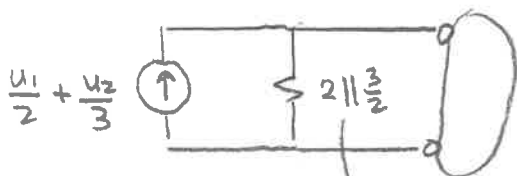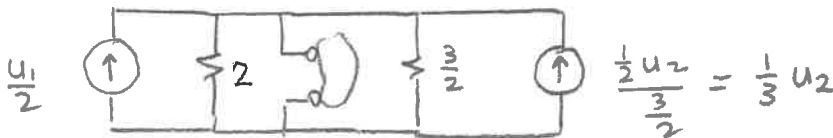Ther equiv u_1
looking leftwardsTher equiv u_2 looking rightwards
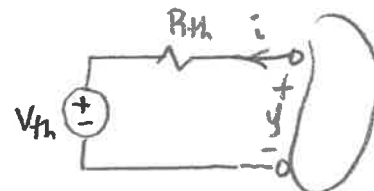
$$R_{th} = \frac{2(\frac{3}{2})}{\frac{4}{2} + \frac{3}{2}} = \frac{\frac{6}{2}}{\frac{7}{2}} = \frac{6}{7}$$



$$R_{th} = 6/7$$


$$V_{th} = \left(\frac{u_1}{2} + \frac{u_2}{3} \right) \frac{6}{7}$$

$$V_{th} = \frac{3}{7} u_1 + \frac{2}{7} u_2$$


Note: without source transf, we can introduce
another variable z \Rightarrow use KVL, KCL, Ohm --- lets do that --- \Rightarrow

Problem #6

18/19

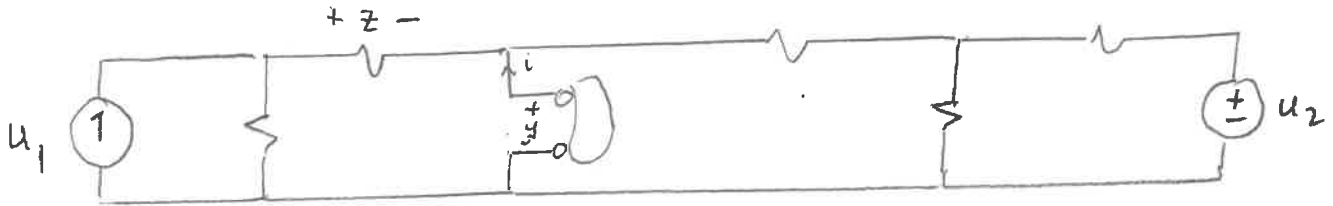Let's introduce $z =$ 

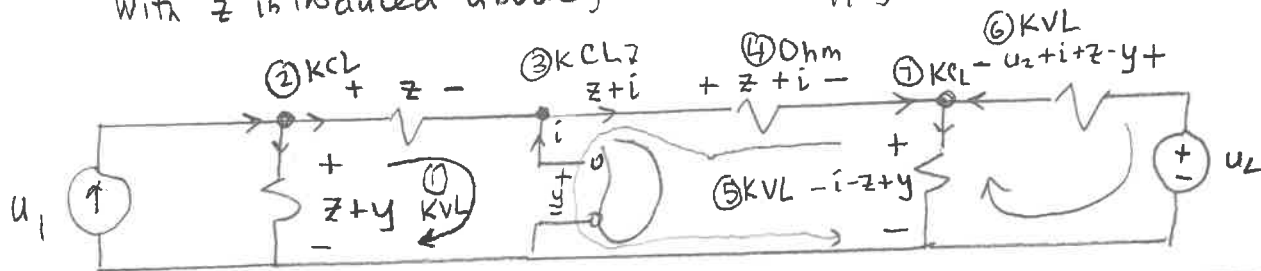With z introduced above, we can apply KVL, KCL, Ohm as follows:



$$\textcircled{2} \text{ KCL (Ohm)} = \begin{matrix} \rightarrow \\ u_1 = \left(\frac{z+y}{1} \right) + \left(\frac{z}{1} \right) \end{matrix}$$

$$\Rightarrow 2z = -u_1 - y$$

$$\downarrow$$

$$\stackrel{3x}{\Rightarrow} 6z = 3u_1 - 3y$$

$$\textcircled{7} \text{ KCL (Ohm)} = \begin{matrix} \rightarrow \\ \left(\frac{z+i}{1} \right) + \left(\frac{u_2+i+z-y}{1} \right) = \left(\frac{-i-z+y}{1} \right) \end{matrix}$$

$$\Rightarrow 3z = -3i + 2y - u_2$$

$$\stackrel{2x}{\Rightarrow} 6z = -6i + 4y - 2u_2$$

$$\Rightarrow 6z = 3u_1 - 3y = -6i + 4y - 2u_2$$

$$\Rightarrow 7y = 6i + 3u_1 + 2u_2$$

$$\Rightarrow y = \left(\frac{6}{7} \right) i + \left(\frac{3}{7} \right) u_1 + \left(\frac{2}{7} \right) u_2$$

$$R_m = \frac{6}{7}$$

$$v_{th} = \left(\frac{3}{7} \right) u_1 + \left(\frac{2}{7} \right) u_2$$



... just as we got earlier via
source transformations

Note:

while introducing z was not too bad, solving via source trans was much "cooler!"

$$(All R=1)+2y+u_2+u_3-$$


$$\xRightarrow{\text{algebra}} 2z + 3y = u_1 - u_2 - u_3 \Rightarrow z = \frac{u_1 - u_2 - u_3 - 3y}{2}$$

⑧ KCL

algebra $\Rightarrow z = 5y + 3u_2 + 2u_3$

$$y = \left(\frac{1}{13}\right)u_1 + \left(\frac{-7}{13}\right)u_2 + \left(\frac{-5}{13}\right)u_3$$

Exam #2

Fri 4-19-24

8 Problems (5+3)

(17 pages follow)


EXAM RULES

- 1) One 8.5" x 11" sheet permitted;
otherwise closed books, closed notes, open minds!
- 2) Scientific calculator is permitted; no computers and no phone!
- 3) **NO PHONES !!!**
Phones should not be visible at all!
A visible phone will result in a zero grade for the exam!
- 4) Write FULL NAME legibly on each page provided.
- 5) **PLEASE SHOW ALL WORK !!!**
This is essential to receive partial credit!
- 6) Please do not submit multiple answers. You must pick an answer!!
- 7) Write your solutions on the sheets provided.
No other paper/sheets/pages should be used!
- 8) Clearly label voltages and currents on the circuits provided.
- 9) Use the variables provided!
No additional variables should be used!
- 10) Unreadable work will receive NO CREDIT.
- 11) Please place important equations and answers within boxes as we have done in lecture.
- 12) Please be careful with your algebra, signs, etc.
- 13) Please turn in your solutions to me at the end of the period!
- 14) **PLEASE DO NOT CHEAT !!!**

Problem #1

Determine $H_{1,2}$, diff eq, t_s , y_{ss} , y


Compute $|H_i(j\omega)| < |H_i(j\omega)|$ (all $R=L=C=1$)

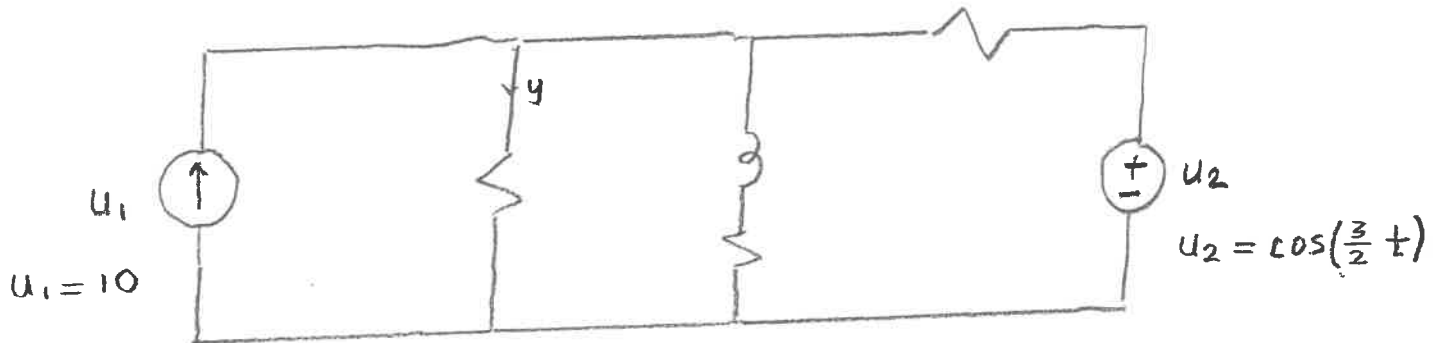

Problem # 1

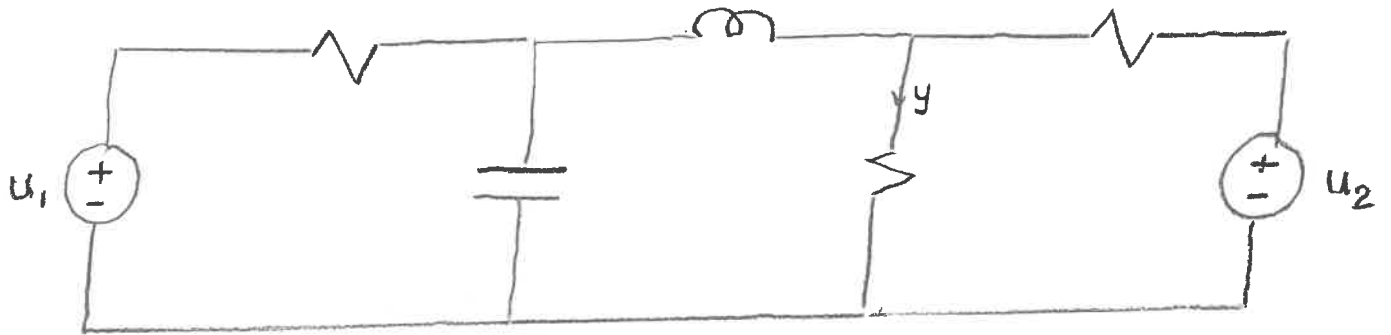Problem #2


Determine poles, t_s , $H_1(0)$, $H_2(0)$, $H_1(\infty)$, $H_2(\infty)$
(all $R=L=C=1$)



Problem #2

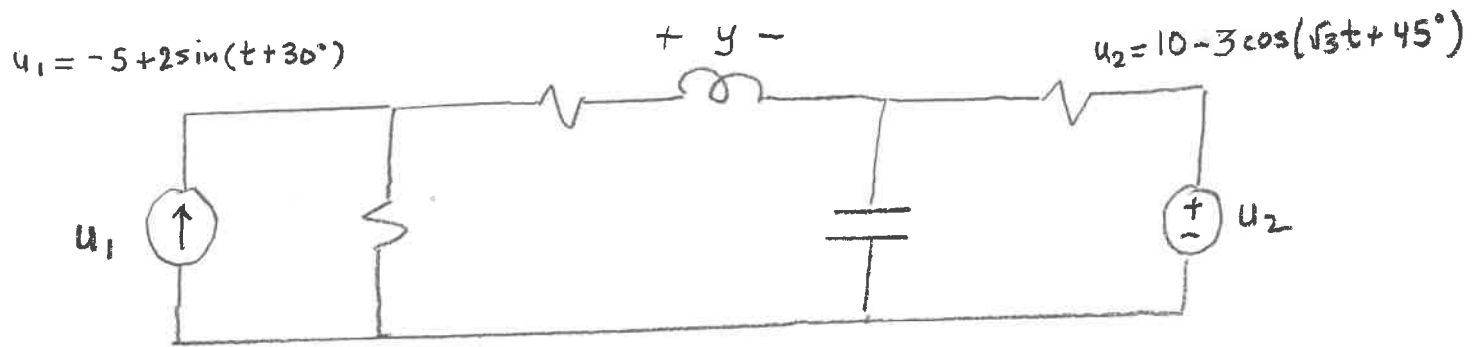Problem #3

Determine $H_{1,2}, t_s, \text{diff eq}, y_{ss}$ (all $R=L=C=1$)




Problem # 3

Problem #4

Determine H , diff eq, y , y_{ss} (all $R=L=C=1$)

Hint: Find R_{th}

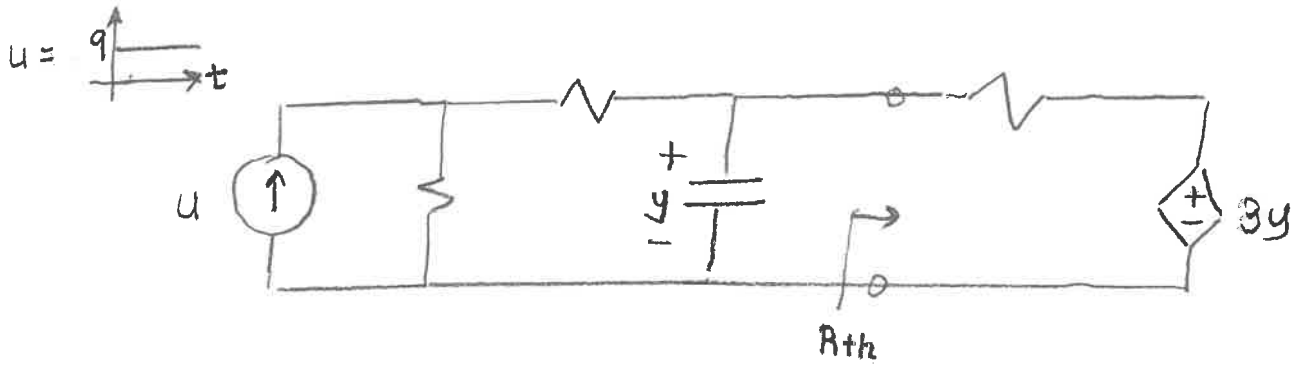

Problem #4

Problem #5

Determine t_s , y_{ss} , y

$$H(s) = \frac{s(s^2 + 1)}{(s+1)(s^2 - 6s + 25)(s^2 + 2s + 4)}$$

$$u(t) = 7 + 2 \sin(0.01t - 45^\circ) + 3 \cos(t + 30^\circ) + 4 \sin(100t + 135^\circ)$$

Note = Compute all coefficients associated with constants & sinusoids in y
Show how to compute coefficients associated with instabilities in y


Problem #5

Problem # 6

Determine an s-domain Thevenin equivalent at y

(Specify Z_{th} & V_{th})

(all $R=L=C=1$)

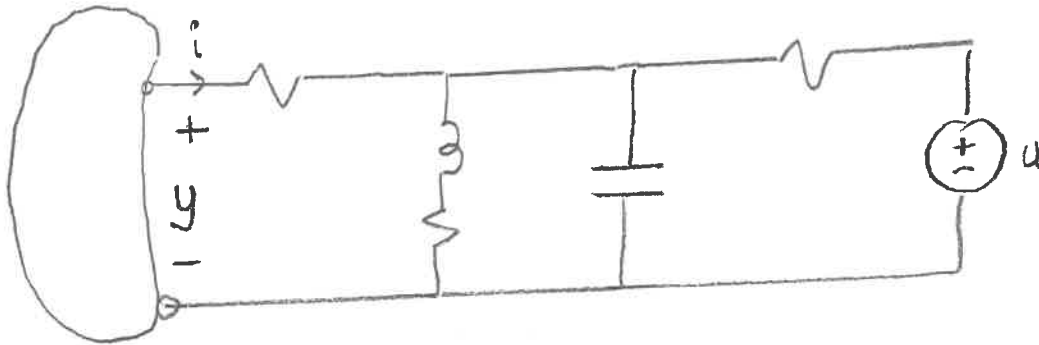

Problem # 6


Problem # 7

Determine H , y_{ss} , t_s

Compute all coefficients
in y_{ss} approximately!

Hint: poles = $\begin{cases} -0.3017 \pm j 1.0815 \\ -0.3966 \end{cases}$

(all $R=L=C=1$)

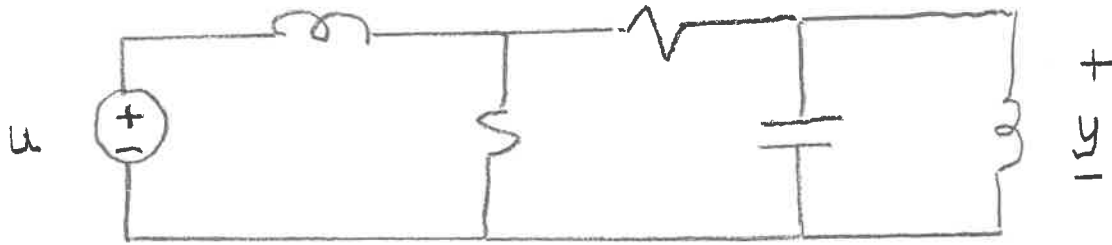


$$u(t) = 6 + 100 \sin(0.01t - 45^\circ) - 4 \cos(100t + 60^\circ)$$

Problem # 7

Problem # 8

Determine & plot $|H(j\omega)|$, $\angle H(j\omega)$

(all $R=L=C=1$)

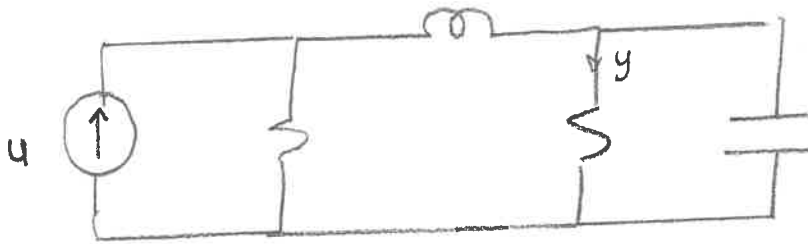

Problem # 8

Exam #2

Fri 4-19-24

Solutions

(21 pages total)


Problem #1

Determine $H_{1,2}$, diff eq, t_s , y_{ss} , y

2/21

Compute $|H_i(j\omega)| < |H_i(j\omega)|$

(all $R=L=C=1$)

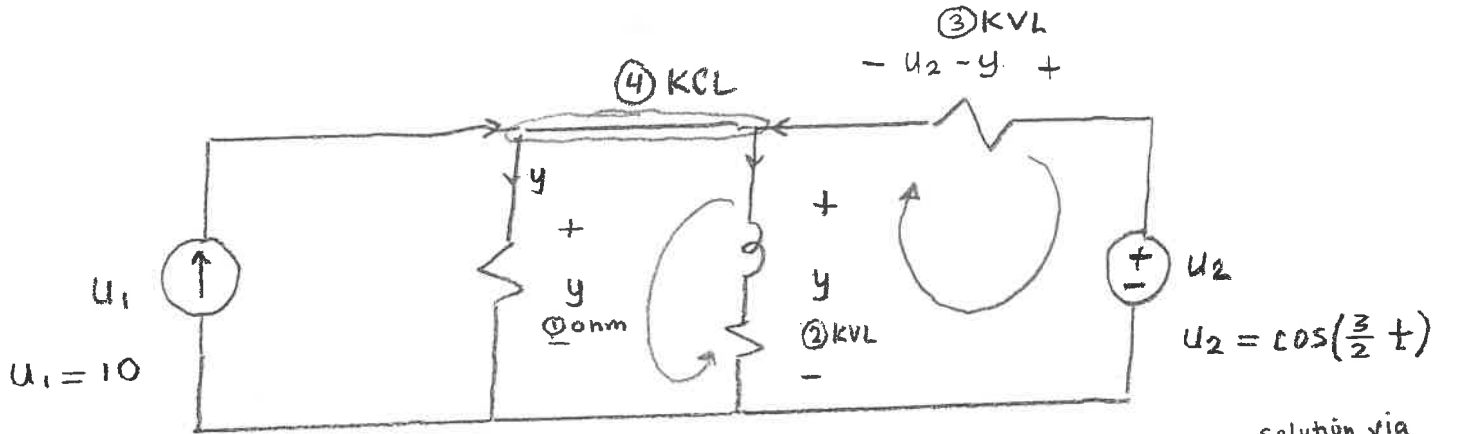

$$u_1 + \left(\frac{u_2 - y}{1}\right) = \left(\frac{y}{1}\right) + \left(\frac{y}{s+1}\right)$$

solution via Ohm, KVL, KCL

$$\Rightarrow u_1 + u_2 = y \left[1 + 1 + \frac{1}{s+1} \right]$$

$$\Rightarrow y \left[2s + 2 + 1 \right] = (s+1)(u_1 + u_2)$$

$$\Rightarrow y \left[s + \frac{3}{2} \right] = (s+1)(u_1 + u_2)$$

$$\Rightarrow y = \left[\frac{\frac{1}{2}(s+1)}{s + \frac{3}{2}} \right] (u_1 + u_2)$$

$$H_1 = H_2 = \frac{\frac{1}{2}(s+1)}{s + \frac{3}{2}}$$

$$|H_i(j\omega)| = \frac{\frac{1}{2}\sqrt{\omega^2 + 1}}{\sqrt{\omega^2 + \frac{9}{4}}}$$

$$\angle H_i(j\omega) = \tan^{-1}\left(\frac{\omega}{1}\right) - \tan^{-1}\left(\frac{\omega}{3/2}\right)$$

$$\Rightarrow \dot{y} + \frac{3}{2}y = \frac{1}{2}(\dot{u}_1 + \dot{u}_2) + \frac{1}{2}(u_1 + u_2)$$

$$t_s = \frac{5}{|\text{Re pole}|} = \frac{5}{\frac{3}{2}} = \frac{10}{3}$$

$$H(0) = \frac{1}{3}$$

$$y_{ss} = 10 H(0) + |H(j\frac{3}{2})| \cos(\frac{3}{2}t + \angle H(j\frac{3}{2}))$$

$$H(0) = \frac{1/2}{3/2} = \frac{1}{3}$$

$$H(j\frac{3}{2}) = \frac{\frac{1}{2}(j\frac{3}{2} + 1)}{j\frac{3}{2} + \frac{3}{2}}$$

$$|H(j\frac{3}{2})| = \frac{1}{2} \sqrt{\left(\frac{3}{2}\right)^2 + 1} = \frac{3}{2} \sqrt{2}$$

$$\angle H(j\frac{3}{2}) = \tan^{-1}\left(\frac{3/2}{1}\right) = 45^\circ$$

$$U = \frac{10}{s} + \frac{s}{s^2 + \frac{9}{4}} = \frac{10(s^2 + \frac{9}{4}) + s^2}{s(s^2 + \frac{9}{4})} = \frac{11s^2 + \frac{90}{4}}{s(s^2 + \frac{9}{4})}$$

$$Y = H U = \left[\frac{\frac{1}{2}(s+1)}{s + \frac{3}{2}} \right] \left[\frac{11s^2 + \frac{90}{4}}{s(s^2 + \frac{9}{4})} \right] = \frac{A}{s} + \frac{B}{s + \frac{3}{2}} + \left[\frac{C}{s - j\frac{3}{2}} + * \right]$$

$$\Rightarrow y = A + B e^{-\frac{3}{2}t} + 2|C| \cos(\frac{3}{2}t + \angle C)$$

decays to zero with $t_s = \frac{10}{3}$

$$A = \lim_{s \rightarrow 0} s Y = s H \left[\frac{10}{s} + \frac{s}{s^2 + \frac{9}{4}} \right] \Big|_{s=0} = 10 H(0) = 10 \left(\frac{1}{3} \right)$$

$$C = \lim_{s \rightarrow j\frac{3}{2}} (s - j\frac{3}{2}) Y = (s - j\frac{3}{2}) H \left[\frac{10}{s} + \frac{s}{(s - j\frac{3}{2})(s + j\frac{3}{2})} \right] \Big|_{s=j\frac{3}{2}}$$

Problem #1

3/21

$$C = H \left[\frac{10}{5} (s - j\frac{3}{2}) + \frac{s}{s + j\frac{3}{2}} \right] \Big|_{s = j\frac{3}{2}}$$

$$= H(j\frac{3}{2}) \left[0 + \frac{j^{3/2}}{2(j^{3/2})} \right]$$

$$= \frac{H(j\frac{3}{2})}{2}$$

$$= \frac{1}{2} |H(j\frac{3}{2})| e^{j \angle H(j\frac{3}{2})} \leftarrow \text{This also follows by equating}$$

$$2|C| \cos(\frac{3}{2}t + \angle C) = |H(j\frac{3}{2})| \cos(\frac{3}{2}t + \angle H(j\frac{3}{2}))$$


$$\Rightarrow |C| = \frac{|H(j\frac{3}{2})|}{2} \quad \angle C = \angle H(j\frac{3}{2})$$

$$B = \lim_{s \rightarrow -\frac{3}{2}} (s + \frac{3}{2}) Y = (s + \frac{3}{2}) \left[\frac{\frac{1}{2}(s+1)}{s + \frac{3}{2}} \right] \left[\frac{11s^2 + \frac{90}{4}}{s(s^2 + \frac{9}{4})} \right] \Big|_{s = -\frac{3}{2}}$$

$$= \frac{1}{2} (s+1) \left[\frac{11s^2 + \frac{90}{4}}{s(s^2 + \frac{9}{4})} \right] \Big|_{s = -\frac{3}{2}}$$

Note: A & C are the more important coefficients because they are associated with y_{ss} !

Alternate Solution:

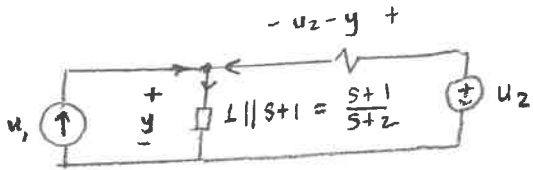

$$u_1 + (u_2 - y) = y \left(\frac{s+2}{s+1} \right)$$

$$(s+1)(u_1 + u_2) = y[s+2 + s+1]$$

$$= y[2s+3]$$

$$= y 2 \left[s + \frac{3}{2} \right]$$

$$\Rightarrow y = \left[\frac{\frac{1}{2}(s+1)}{s + \frac{3}{2}} \right] (u_1 + u_2)$$

as we obtained above!



Problem #1

4/21

It's Always Good
to Check !!!

check:

Find poles & ts (set $u_1 = u_2 = 0$)




$$\Rightarrow Z = s + 1 + \frac{1}{2} = s + \frac{3}{2} = 0$$

$$\Rightarrow \text{pole} = -3/2 \quad \checkmark \quad (\text{as obtained earlier})$$

$$ts = \frac{5}{|Re \text{ pole}|} = \frac{5}{3/2} = \frac{10}{3} \quad \checkmark \quad (\text{as obtained earlier})$$

Gains:

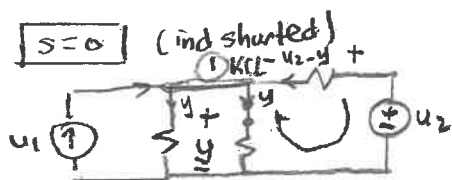


$$\textcircled{1} \text{KCL} = u_1 + \frac{(u_2 - y)}{1} = y + y$$

$$u_1 + u_2 = 3y \Rightarrow y = \frac{1}{3}(u_1 + u_2)$$

$$H_1(0) = H_2(0) = \frac{1}{3} \quad \checkmark$$

(agrees with H_i obtained earlier)

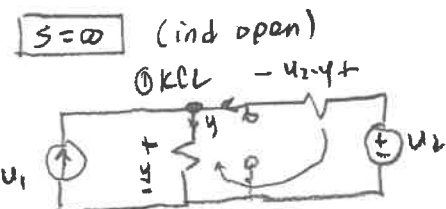

$$\textcircled{1} \text{KCL} = u_1 + \frac{(u_2 - y)}{1} = y \Rightarrow 2y = u_1 + u_2$$


$$\Rightarrow y = \frac{1}{2}(u_1 + u_2)$$


$$H_1(\infty) = H_2(\infty) = \frac{1}{2} \quad \checkmark$$

(agrees with H_i obtained earlier)



(all $R=L=C=1$)

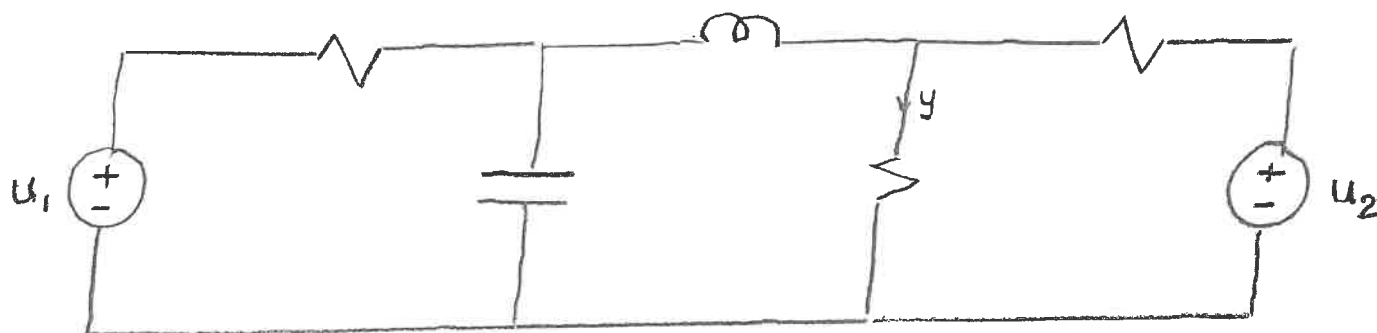


 $1 \parallel 1 = \frac{1}{2}$
 $10 \parallel \frac{1}{2} = \frac{10 \cdot \frac{1}{2}}{1 + \frac{1}{2}} = \frac{1}{5+1}$

$$\Rightarrow \frac{1}{s+1} \parallel \left(s + \frac{1}{2} \right) \Rightarrow Z = \frac{1}{\frac{1}{s+1} + s + \frac{1}{2}} = \frac{1 + (s + \frac{1}{2})(s+1)}{s+1} = \frac{s^2 + \frac{3}{2}s + \frac{3}{2}}{s+1}$$


$$\Rightarrow \Phi = s^2 + \frac{3}{2}s + \frac{3}{2} = 0$$

$$\Rightarrow s_{1,2} = -\frac{3}{2} \pm \sqrt{\left(\frac{3}{2}\right)^2 - 4\left(\frac{3}{2}\right)}$$


$$= -\frac{3}{4} \pm \sqrt{\frac{1}{4}\left(\frac{9}{4}\right) - \left(\frac{3}{2}\right)} = \frac{9}{16} - \frac{24}{16} = -\frac{15}{16}$$

$$= -\frac{3}{4} \pm j \frac{\sqrt{15}}{4}$$

$$\underline{\text{Find } t_s =} \quad \Rightarrow t_s = \frac{5}{|Re \text{ pole}|} = \frac{5}{\frac{3}{4}} = \frac{20}{3} \text{ sec}$$

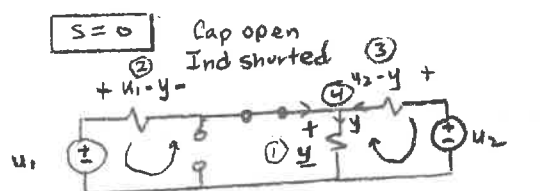
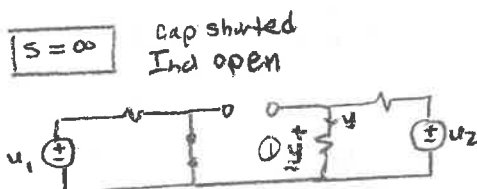
$$\begin{aligned} \textcircled{4} \text{KCL: } & \left(\frac{u_1 - y}{1} \right) + \left(\frac{u_2 - y}{1} \right) = \left(\frac{y}{1} \right) \\ \xrightarrow{y} & \Rightarrow u_1 + u_2 = 3y \\ & \Rightarrow y = \frac{1}{3} u_1 + \frac{1}{3} u_2 \\ & \Rightarrow H_1(0) = H_2(0) = \frac{1}{3} \end{aligned}$$



$$y = 0u_1 + \frac{1}{2}u_2 \quad (\text{by voltage division})$$


$$H_1(\infty) = 0 \quad H_2(\infty) = \frac{1}{2}$$

--- Now lets solve via KVL, KCL, Ohm ---
--- the long way ---

Problem #2


5/21

solution via source transformations =

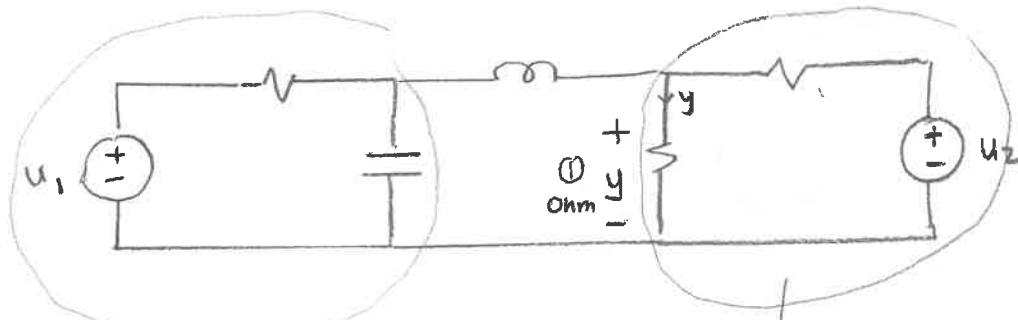



② source transf

③ source transf

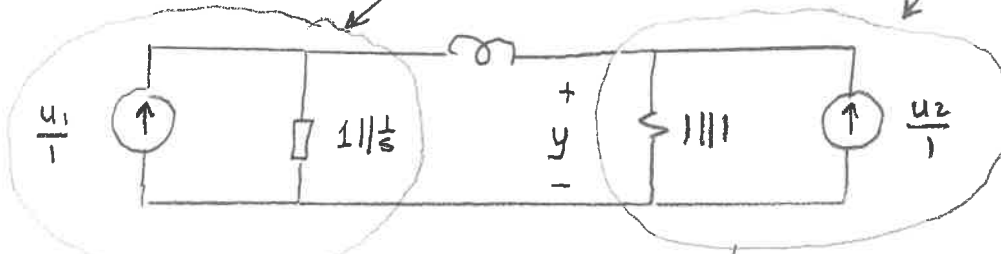

④ source transf

⑤ source transf

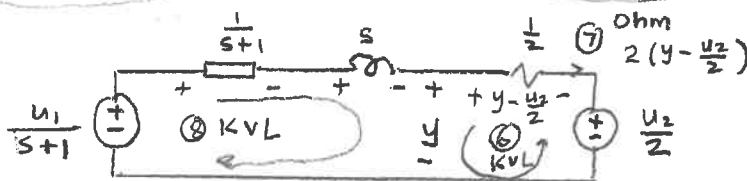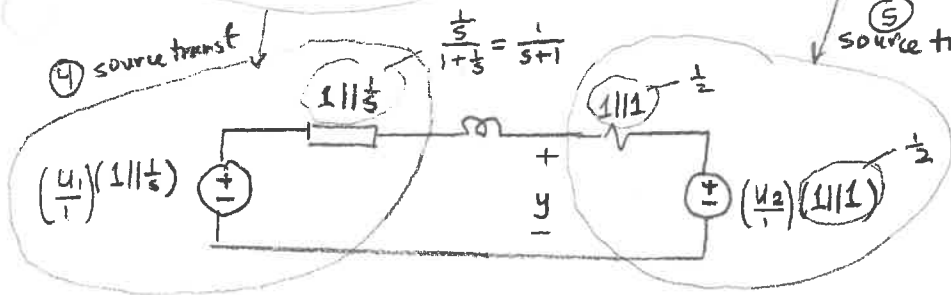

$$\textcircled{8} \text{ KVL} = \frac{u_1}{s+1} = \left[\frac{1}{s+1} + s \right] 2 \left(y - \frac{u_2}{2} \right) + y$$

$$= \left[\frac{1+s(s+1)}{s+1} \right] 2 \left(y - \frac{u_2}{2} \right) + y$$

$$u_1 = (s^2 + s + 1) 2 \left(y - \frac{u_2}{2} \right) + (s+1) y$$

$$\frac{1}{2} u_1 + \frac{1}{2} (s^2 + s + 1) u_2 = y \left[s^2 + s + 1 + \frac{1}{2} s + \frac{1}{2} \right] = y \left[s^2 + \frac{3}{2} s + \frac{3}{2} \right]$$

$$y = \left[\frac{\frac{1}{2}}{s^2 + \frac{3}{2} s + \frac{3}{2}} \right] u_1 + \left[\frac{\frac{1}{2} (s^2 + s + 1)}{s^2 + \frac{3}{2} s + \frac{3}{2}} \right] u_2$$

$\uparrow H_1$ $\uparrow H_2$

check = same Φ & hence poles & ts!

$$H_1(0) = H_2(0) = \frac{1}{3} \checkmark$$

$$H_1(\infty) = 0 \checkmark \quad H_2(\infty) = \frac{1}{2} \checkmark$$


80y!



Problem # 2

7/21

solution via straight KVL, KCL, Ohm =

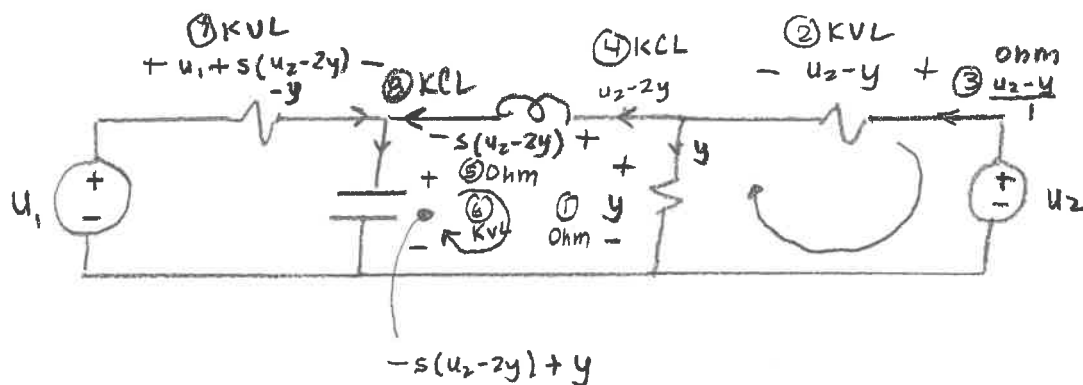

③ KCL =

$$\left(\frac{u_1 + s(u_2 - 2y) - y}{1} \right) + (u_2 - 2y) = s[y - s(u_2 - 2y)]$$

$$\Rightarrow u_1 + u_2 [s + 1 + s^2] = y [2s + 1 + 2 + s + 2s^2]$$

$$\Rightarrow u_1 + u_2 (s^2 + s + 1) = y [2s^2 + 3s + 3]$$

$$= y 2 \left[s^2 + \frac{3}{2}s + \frac{3}{2} \right]$$

$$\Rightarrow y = \left[\frac{\frac{1}{2}}{s^2 + 3s + 3} \right] u_1 + \left[\frac{\frac{1}{2}(s^2 + s + 1)}{s^2 + \frac{3}{2}s + \frac{3}{2}} \right] u_2$$


- which agrees with what we obtained earlier via source transformations!



Problem #3



Determine $H_{1,2}, t_s$, diff eq, y_{ss} (all $R=L=C=1$)

8/21

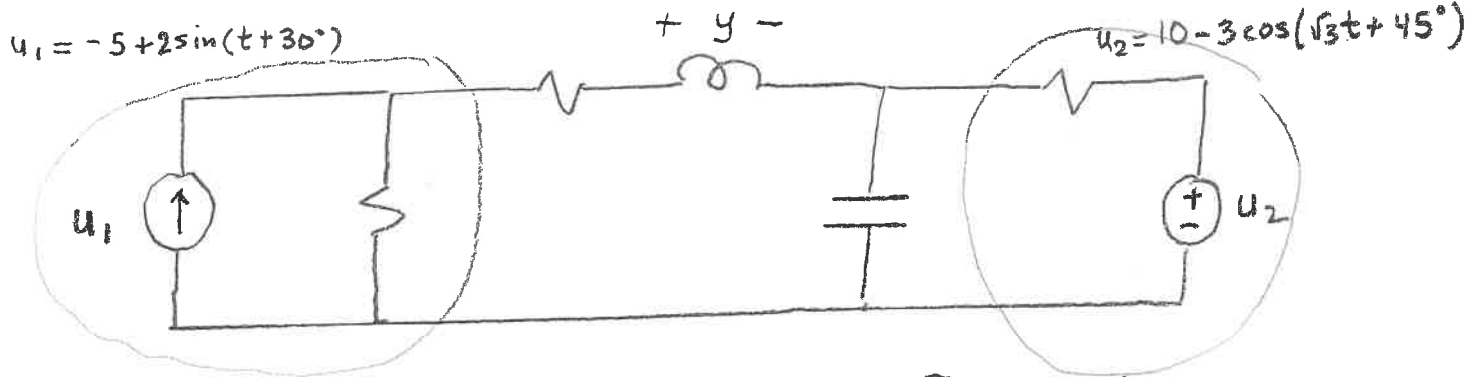

① source transf

② source transf

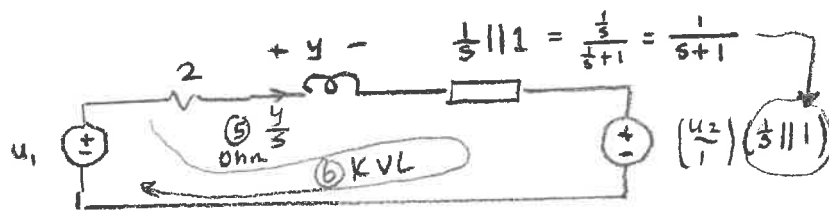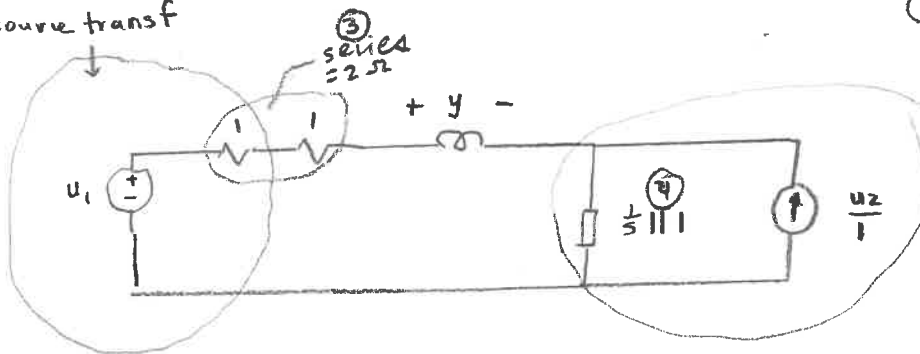

$$\textcircled{6} \text{ KVL: } u_1 = 2\left(\frac{y}{s}\right) + y + \left(\frac{1}{s+1}\right)\left(\frac{y}{s}\right) + \frac{u_2}{s+1}$$

$$\Rightarrow y \left[\frac{2}{s} + 1 + \frac{1}{s(s+1)} \right] = u_1 + \frac{u_2}{s+1}$$

$$\Rightarrow y [2(s+1) + s(s+1) + 1] = s(s+1) - s u_2$$

$$\Rightarrow y [s^2 + 3s + 3] = s(s+1) - s u_2$$

$$\Rightarrow y = \left[\frac{s(s+1)}{s^2 + 3s + 3} \right] u_1 + \left[\frac{-s}{s^2 + 3s + 3} \right] u_2$$

$$\Rightarrow \ddot{y} + 3\dot{y} + 3y = \ddot{u}_1 + \dot{u}_1 - \ddot{u}_2$$

$$\text{poles} = \frac{-3 \pm \sqrt{9 - 4(3)}}{2} = \frac{-3 \pm j\sqrt{3}}{2}$$

$$\Rightarrow t_s = \frac{5}{|\text{Re poles}|} = \frac{5}{\frac{3}{2}} = \frac{10}{3}$$

$$y_{ss} = y_{1ss} + y_{2ss}$$

$$y_{1ss} = -5 H_1(0) + 2 |H_1(j\omega)| \sin(t + 30^\circ + \angle H_1(j\omega))$$

Method of the Transfer function (MOTF)

$$H_1(0) = 0$$

$$H_1(j\omega) = \frac{j(1+j)}{3-j+j3} = \frac{j(1+j)}{2+j3}$$

$$= \frac{(1e^{j90^\circ})(\sqrt{2}e^{j45^\circ})}{\sqrt{4+9} e^{j \tan^{-1}(3/2)}}$$

Problem # 3

9/21

$$\Rightarrow H_1(j1) = \frac{(1)(\sqrt{2})}{\sqrt{4+9}} e^{j(90+45' - \tan^{-1}(3/2))}$$

\uparrow $|H_1(j1)|$

↓ MOTF

$$y_{2ss} = 10 H_2(0) - 3 |H_2(j\sqrt{3})| \cos(\sqrt{3}t + 45' + \angle H_2(j\sqrt{3}))$$


$$H_2 = \frac{-s}{s^2 + 3s + 3} \Rightarrow H_2(0) = 0$$

$$H_2(j\sqrt{3}) = \frac{-j\sqrt{3}}{-3 + j3\sqrt{3} + 3} = \frac{-j\sqrt{3}}{j3\sqrt{3}} = -\frac{1}{3}$$

$= \frac{1}{3} e^{j180^\circ}$

\uparrow $|H_2(j\sqrt{3})|$

solution via straight KVL, KCL, Ohm =

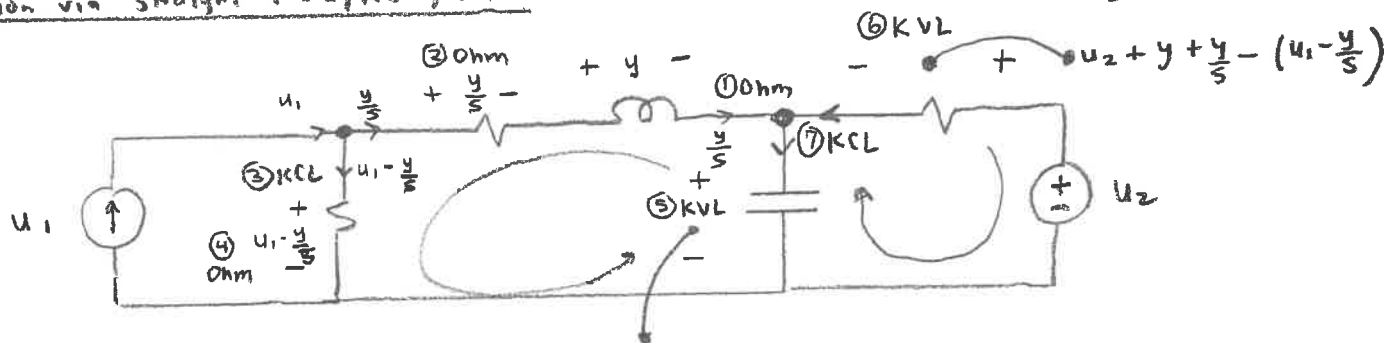

⑦ KCL =

$$\frac{y}{s} + \left(\frac{u_2 + y + \frac{y}{s} - (u_1 - \frac{y}{s})}{1} \right) = s \left[(u_1 - \frac{y}{s}) - y - \frac{y}{s} \right]$$

$$\Rightarrow y \left[\frac{1}{s} + 1 + \frac{1}{s} + \frac{1}{s} + 1 + s + 1 \right] = u_1 [1 + s] + u_2 [-1]$$

$$\Rightarrow y \left[\frac{3}{s} + s + 3 \right] = (s+1)u_1 - u_2$$

$$\Rightarrow y [s^2 + 3s + 3] = s(s+1)u_1 - s u_2$$

$$\Rightarrow y = \left[\frac{s(s+1)}{s^2 + 3s + 3} \right] u_1 + \left[\frac{-s}{s^2 + 3s + 3} \right] u_2$$

- which agreed with what we obtained earlier via source transf




Problem #3

It's Always Good to Check!

10/21

check:


Φ , poles? +s: set $u_1 = u_2 = 0$

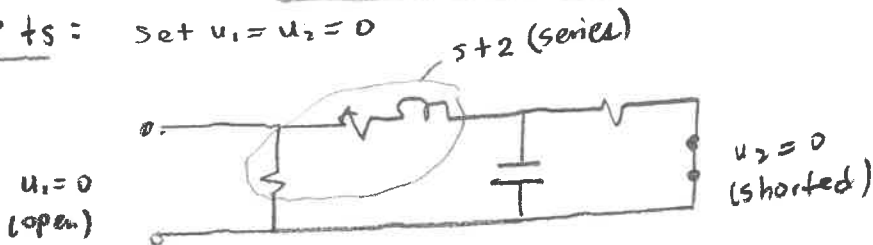

$$\boxed{1 || s+2 = \frac{s+2}{s+3}} \Rightarrow Z = \frac{s+2}{s+3} + \frac{1}{s} = \frac{s(s+2) + s+3}{s(s+3)} = \frac{s^2 + 3s + 3}{s(s+3)}$$

Gains:


$s=0$ (short ind, open cap)

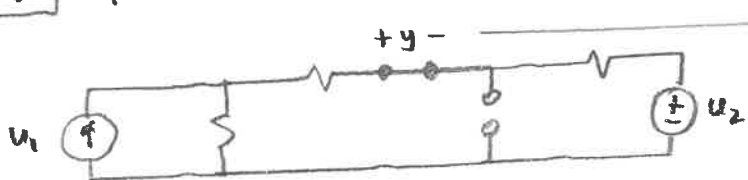

$\Phi = s^2 + 3s + 3$ as obtained earlier ✓
.. hence same poles + ts ✓

$\Rightarrow H_1(0) = H_2(0) = 0$ ✓
(agrees with H_i obtained earlier)

$s=\infty$ (open ind, short cap)

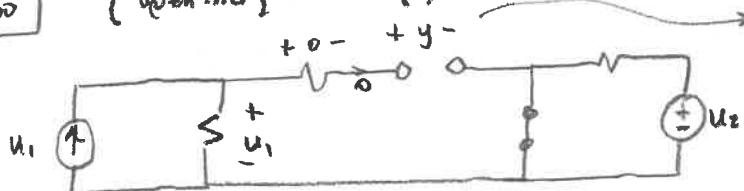

$y = u_1 \Rightarrow H_1(\infty) = 1$
 $H_2(\infty) = 0$ ✓
(agrees with H_i obtained earlier)




Problem #4

11/21

Determine H , diff eq, y , y_{ss} ($R=L=C=1$)

Hint: Find R_{th}


$$u = 9 \rightarrow t$$

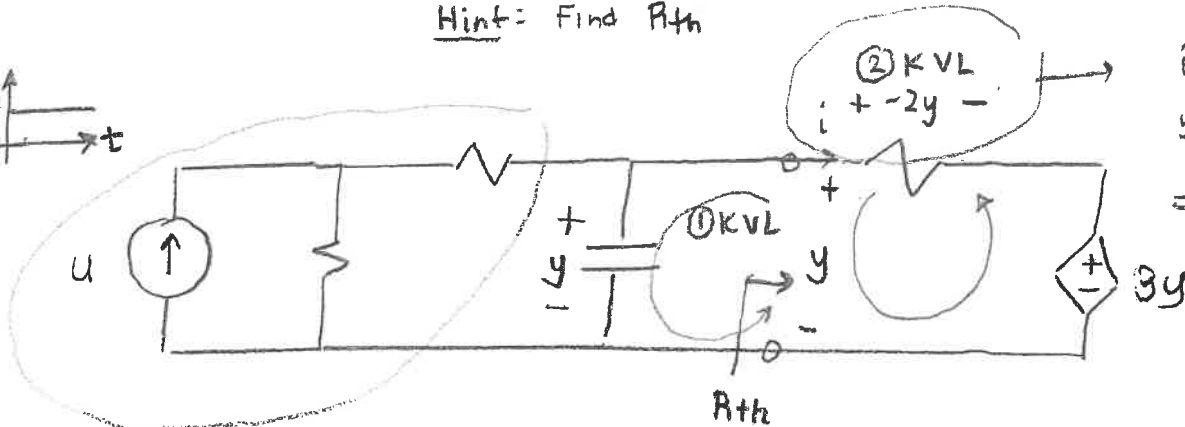

$$\begin{aligned} i &= -2y \\ y &= -\frac{1}{2}i \end{aligned}$$

$$\Rightarrow R_{th} = -\frac{1}{2}$$

source trans f:

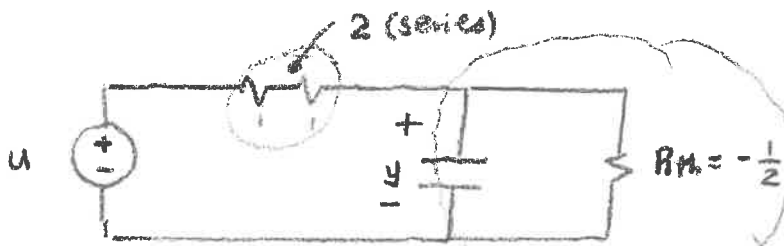

$$\begin{aligned} \frac{1}{s} \parallel (-\frac{1}{2}) &= \frac{-\frac{1}{2}}{\frac{1}{s} - \frac{1}{2}} = \frac{-\frac{1}{2}}{1 - \frac{1}{2}s} \\ &= \frac{-1}{2-s} \\ &= \frac{1}{s-2} \end{aligned}$$

voltage division

$$\begin{aligned} y &= \left[\frac{(\frac{1}{s-2})}{2 + (\frac{1}{s-2})} \right] u \\ &= \left[\frac{1}{2s-4+1} \right] u \\ &= \left[\frac{1}{2s-3} \right] u \\ &= \left[\frac{1/2}{s-3/2} \right] u \end{aligned}$$

$$Y = HU = \left[\frac{1/2}{s-3/2} \right] \left(\frac{9}{s} \right)$$

$$= \frac{A}{s} + \frac{B}{s-3/2}$$

$$y = A + B e^{\frac{3}{2}t} \leftarrow y_{ss}$$

expected from MOTF!


$$A = \lim_{s \rightarrow 0} sY = sH \frac{9}{s} \Big|_{s=0} = 9H(0) = 9 \left(\frac{1/2}{-3/2} \right) = 9 \left(-\frac{1}{3} \right) = -3$$

$$B = \lim_{s \rightarrow \frac{3}{2}} (s - \frac{3}{2})Y = (s - \frac{3}{2}) \left[\frac{1/2}{s - \frac{3}{2}} \right] \frac{9}{s} \Big|_{s=\frac{3}{2}} = \left(\frac{1}{2} \right) \left(\frac{9}{\frac{3}{2}} \right) = 3$$

Problem # 4

12/21

solution via straight KVL, KCL, Ohm =

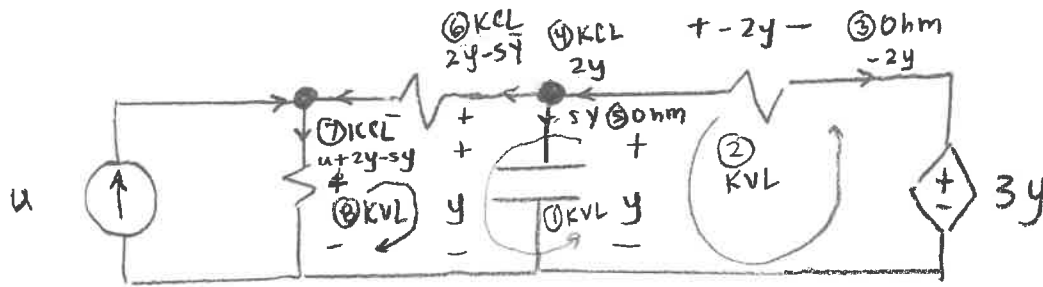

$$\textcircled{1} \text{ KVL} = 1(u + 2y - sy) = -[2y - sy] + y$$


$$\begin{aligned} \Rightarrow u &= y[-2 + s - 2 + s + 1] \\ &= y[2s - 3] \\ &= y 2[s - \frac{3}{2}] \end{aligned}$$

$$\Rightarrow y = \left[\frac{1/2}{s - 3/2} \right] u$$

\downarrow H ... agrees with what we got earlier via source transformations

check = - It's Always Good to Check!


Φ , poles, ts: set $u=0 \Rightarrow$

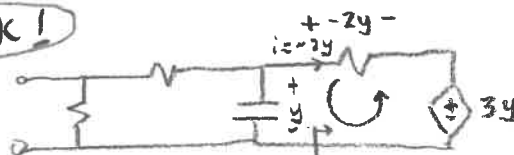

$2y = -i$
 $y = -\frac{1}{2}i \Rightarrow R_{th} = -1/2$ as obtained earlier!

$$\Rightarrow 1 + 1 = 2 \quad \Rightarrow \quad \frac{-1/2 \parallel 2}{= \frac{(-1/2)(2)}{-1/2 + 2} = \frac{-1}{3/2} = -\frac{2}{3}} \quad \Rightarrow \quad \frac{-2/3}{s} \quad \Rightarrow \quad \frac{-2/3}{s}$$


Gains:

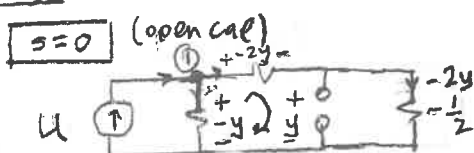

$$\begin{aligned} \textcircled{1} \text{ KCL} &= u_1 = (-y) + (-2y) = -3y \\ y &= -\frac{1}{3}u \quad H(0) = -\frac{1}{3} \checkmark \\ &\text{agrees with H obtained above!} \end{aligned}$$

$$\begin{aligned} Z &= -\frac{2}{3} + \frac{1}{s} = \frac{-\frac{2}{3}s + 1}{s} \\ &= -\frac{2}{3} \left[s - \frac{3}{2} \right] \end{aligned}$$

$s=\infty$ (short cap)

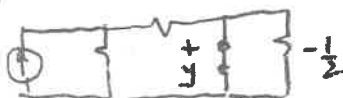

$$\Rightarrow y=0 \Rightarrow H(\infty)=0 \checkmark$$

agrees with H obtained above!

$\Phi = s - 3/2$ (as obtained above)
... hence same poles & ts \checkmark

Determine t_s , y_{ss} , y

$$\frac{-1+j\sqrt{3}}{x} + j\sqrt{3}$$

$$(s+1)(s^2-6s+25)(s^2+2s+4)$$

-1 stable $3 \pm j4$ (unstable)

$$u(t) = 7 + 2 \sin(0.01t - 45^\circ) + 3 \cos(t + 30^\circ)$$

Note: This dc term will not pass through H since $H(0) = 0$.

Note = Compute all coefficients associated with constants \rightarrow sinusoids in y
Show how to compute coefficients associated with instabilities in y

$$M \longleftrightarrow \frac{M}{S}$$

$$|M| \cos(\omega t + \frac{\pi}{3}) \leftrightarrow \frac{(|M| \cos \frac{\pi}{3})s + \omega_0 |M| \sin \frac{\pi}{3}}{s^2 + \omega_0^2}$$

dc & sinusoidal
components of
 y_{ss}

dominant growing (unstable) exponential sinusoid

$y_{ss} = |B| e^{3t} \cos(4t + \angle B)$

from partial fraction expansion below!

$+ 7|H(0)| + 2|H(j0.01)| \cos(0.01t - 135^\circ + \angle H(j0.01))$

zero since $H(0) = 0$

$+ 3|H(j1)| \cos(t + 30^\circ + \angle H(j1))$

zero since $H(j1) = 0$

$+ 4|H(j100)| \cos(100t + 45^\circ + \angle H(j100))$

from HDTF!

$135 - 90^\circ$

$$V = \frac{7}{5} + \left(\frac{2 \cos(-135^\circ) 5 + 0.012 \sin(-135^\circ)}{5^2 + 10^{-4}} \right) + \left(\frac{(3 \cos 30^\circ) 5 + (1) 3 \sin 30^\circ}{5^2 + 1} \right) + \left(\frac{4 \cos 45^\circ 5 + 100 (4 \sin 45^\circ)}{5^2 + 10^4} \right)$$



denominator is what is critical for forthcoming partial fraction expansion

$$Y = HU = \left[\frac{s(s^2+1)}{(s+1)(s^2-6s+25)(s^2+2s+4)} \right] \left[\frac{s(s^2+10^{-4})(s^2+1)(s^2+10^4)}{s(s^2+10^{-4})(s^2+1)(s^2+10^4)} \right]$$

Note = cancellation of s 's $\Rightarrow (s^2+1)$'s is expected since $H(0)=0 \Rightarrow H(j)=0$

$$= \frac{A}{s+1} + \left[\frac{B}{s-3-j4} + * \right] + \left[\frac{C}{s+1-j\sqrt{3}} + * \right] + \left[\frac{D}{s-j0.01} + * \right] + \left[\frac{E}{s-j100} + * \right]$$

$$y(t) = Ae^{-t} + 2|B|e^{3t}\cos(4t + \angle B) + 2|C|e^{-t}\cos(\sqrt{3}t + \angle C) + 2|D|\cos(0.01t + \angle D) + 2|E|\cos(100t + \angle E)$$

decaying stable exp growing unstable exp sinusoid decaying stable exp sinusoid  

exp sin usoid

There are just $2 |H(j0.01)| \cos(0.01t - 135^\circ + \underbrace{\angle H(j0.01)}_{\text{from MTF above}})$
+ $4 |H(j100)| \cos(100t + 45^\circ + \underbrace{\angle H(j100)}_{\text{from MTF above}})$

Problem # 5

14/21

Lets compute the important coefficients:

$$B = \lim_{s \rightarrow 3+j4} (s-3-j4) Y = \left[\frac{1}{(s+1)(s-3+j4)(s^2+2s+4)} \right] \left[\frac{\text{some numerator}}{(s^2+10^{-4})(s^2+10^4)} \right] \bigg|_{s=3+j4}$$

- to calculate B one would need to find the "some numerator" & then plug in $s=3+j4$ above to get B
--- can use MATLAB!

From \odot , it follows that

$$D = \frac{2|H(j0.01)|}{2} e^{j[-135^\circ + \angle H(j0.01)]}$$

$$E = \frac{4|H(j100)|}{2} e^{j[45^\circ + \angle H(j100)]}$$

Note: The above can also be obtained from the following standard partial fraction expansion coefficient formulae for D & E:

$$D = \lim_{s \rightarrow j0.01} (s-j0.01) Y(s)$$

$$E = \lim_{s \rightarrow j100} (s-j100) Y(s)$$

A & C are less important because they are associated with decaying (stable) exponentials --- but they can be computed using the following formulae for A & C:

$$A = \lim_{s \rightarrow -1} (s+1) Y(s)$$




$$C = \lim_{s \rightarrow -1+j\sqrt{3}} (s+1-j\sqrt{3}) Y(s)$$

Problem #6

15/21

Determine an s-domain Thevenin equivalent at y
(Specify Z_{th} & V_{th})

(all $R=L=C=1$)

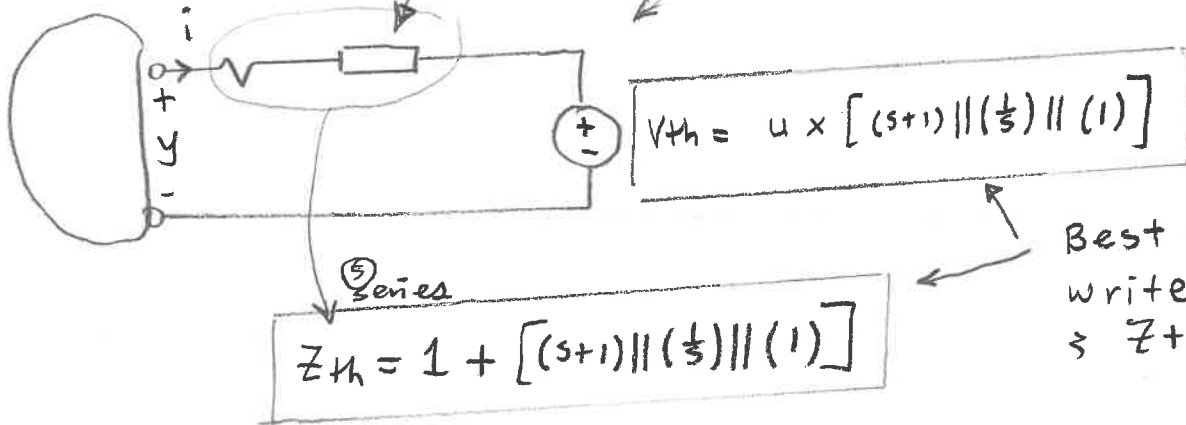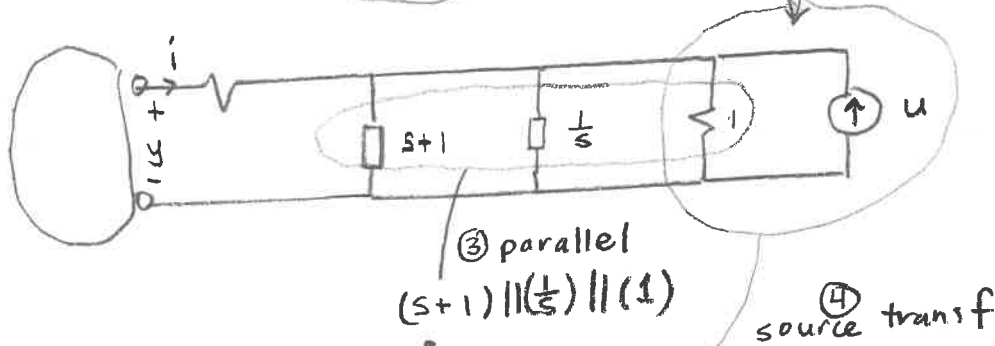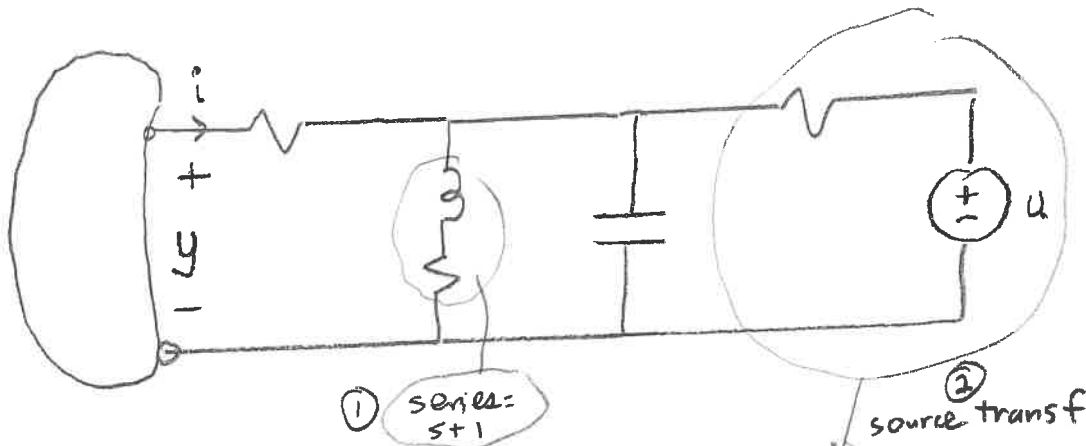

Best way to write V_{th} & Z_{th} !!!

Note: $(s+1) || (\frac{1}{s}) || (1) = (s+1) || \left[\frac{(\frac{1}{s})(1)}{\frac{1}{s} + 1} \right]$

$= (s+1) || \left[\frac{1}{s+1} \right]$

$= \frac{(s+1)(\frac{1}{s+1})}{s+1 + \frac{1}{s+1}}$

$= \frac{s+1}{(s+1)^2 + 1} = \frac{s+1}{s^2 + 2s + 2}$

This is like a check !!!

Note:

At dc ($s=0$), $Z_{th} = 1 + [(0+1) || \infty || 1]$

$= 1 + [1 || 1]$

$= 1 + \frac{1}{2}$

$= 3/2$

For $s=\infty$, $Z_{th} = 1 + [\infty || 0 || 1]$


$= 1 + 0$

$= 1$

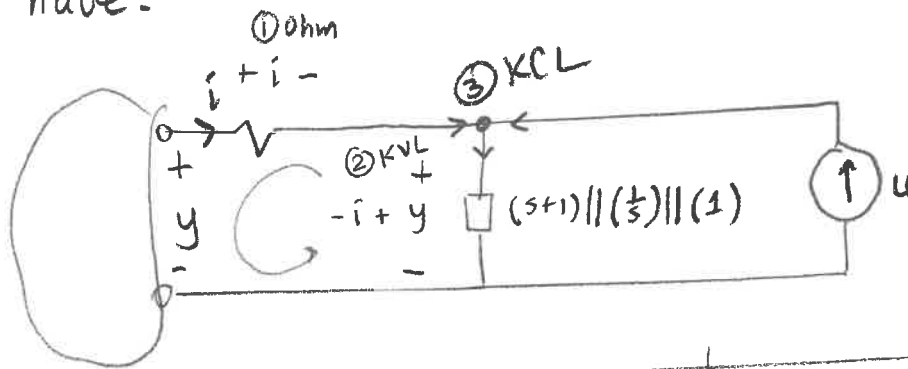Problem # 6

16/21

From our 2nd cut $\textcircled{\#}$; it follows that we have:



$\textcircled{3} \text{ KCL} =$



$$i + u = \frac{-i + y}{(s+1) \parallel (\frac{1}{s}) \parallel (1)}$$

$$\Rightarrow (i + u) [(s+1) \parallel (\frac{1}{s}) \parallel (1)] = -i + y$$

$$\Rightarrow y = [1 + (s+1) \parallel (\frac{1}{s}) \parallel (1)] i + [(s+1) \parallel (\frac{1}{s}) \parallel (1)] u$$

$$Z_{th} = 1 + (s+1) \parallel (\frac{1}{s}) \parallel (1)$$

$$V_{th} = [(s+1) \parallel (\frac{1}{s}) \parallel (1)] u$$

- as we got earlier via source transformations - -



17/21

Problem # 7

Determine H , y_{ss} , t_s


Compute all coefficients in y_{ss} approximately!

(all $R=L=C=1$)

all stable

Hint: poles = $\{-0.3017 \pm j 1.0815\}$
 $\{-0.3966\}$

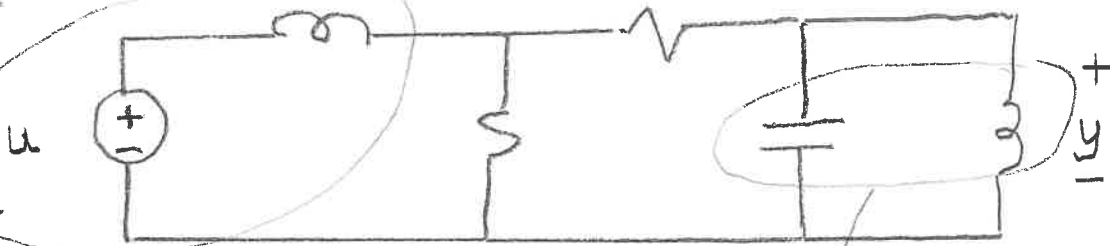Note: we can use MOTF to write expression for y_{ss} before analyzing circuit




$$t_s = \frac{5}{|Re \text{ slowest pole}|} = \frac{5}{0.3017}$$


$$u(t) = 6 + 100 \sin(0.01t - 45^\circ) - 4 \cos(100t + 60^\circ)$$

$$y_{ss} = 6 H(0) + 100 |H(j0.01)| \sin(0.01t - 45^\circ + \angle H(j0.01)) - 4 |H(j100)| \cos(100t + 60^\circ + \angle H(j100))$$
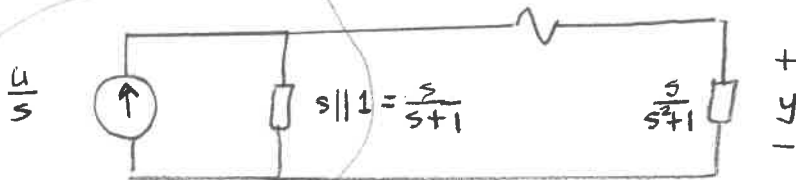
$$\text{① Source trans f from MOTF! (stable system) ② parallel } = \frac{1}{\frac{1}{s} + s} = \frac{s}{s^2 + 1}$$



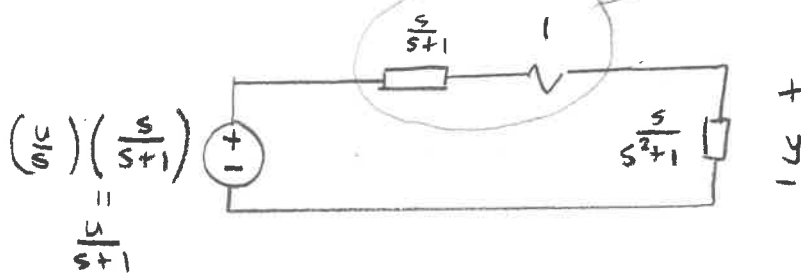③ source trans f series $1 + \frac{s}{s+1} = \frac{s+1+s}{s+1} = \frac{2s+1}{s+1}$



By voltage division:

multip top & bottom by $(s+1)(s^2+1)$:

$$y = \left[\frac{\frac{s}{s^2+1}}{\frac{2s+1}{s+1} + \frac{s}{s^2+1}} \right] \frac{u}{s+1}$$

$$= \left[\frac{s(s+1)}{(2s+1)(s^2+1) + s(s+1)} \right] \frac{u}{s+1}$$

$$= \left[\frac{\frac{1}{2} s}{s^3 + s^2 + \frac{3}{2} s + \frac{1}{2}} \right] u$$

\uparrow
 H

$$\frac{s^2 + 1}{2s + 1} \cdot \frac{s^2 + 1}{2s^3 + 2s} = \frac{s^2 + 1}{2s^3 + s^2 + 2s + 1}$$

$$\frac{s^2 + 1}{2s^3 + 2s^2 + 3s + 1} = 2 \left[s^3 + s^2 + \frac{3}{2} s + \frac{1}{2} \right]$$

Problem #7

18/21

MOTF (stable system)

$$y_{ss} = 6H(0) + 100 |H(j0.01)| \sin(0.01t - 45^\circ + \angle H(j0.01)) - 4 |H(j100)| \cos(100t + 60^\circ + \angle H(j100))$$

$$H(s) = \left[\frac{\frac{1}{2}s}{s^3 + s^2 + \frac{3}{2}s + \frac{1}{2}} \right]$$

$H(0) = 0$ — y_{ss} will have no constant (dc) component in it!

H looks like a differentiator at low freq's

$$H(s) \approx \frac{\frac{1}{2}s}{\frac{1}{2}}$$

$$= s$$

$$\Rightarrow H(j0.01) \approx j0.01 = 0.01 e^{j90^\circ}$$

$$\frac{|H(j0.01)|}{|H(j0.01)|} \approx 0.01$$

$$\angle H(j0.01) \approx 90^\circ$$

$$H(s) \approx \frac{\frac{1}{2}s}{s^3}$$

$$= \frac{1/2}{s^2}$$

↑

H looks like a double integrator at high freq's

$$\Rightarrow H(j100) \approx \frac{1/2}{(j100)^2} = \frac{1/2}{10^4 e^{j180^\circ}}$$

$$= \frac{1/2}{10^4} e^{-j180^\circ}$$

$$= \left(\frac{1}{2}\right) 10^{-4} e^{-j180^\circ}$$

$$|H(j100)| \approx \frac{1}{2} 10^{-4}$$

$$\angle H(j100) \approx -180^\circ$$

Problem #7


19/21

It's Always Good to Check!

check =

Φ , poles, ts = set $u=0$

$\Rightarrow u=0$
(short)

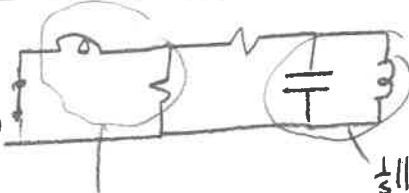

$$s||1 = \frac{s}{s+1}$$

$$\frac{1}{s}||s = \frac{(\frac{1}{s})s}{\frac{1}{s}+s} = \frac{1}{1+s} = \frac{s}{s^2+1}$$

\Rightarrow




$$\begin{aligned} Z &= \frac{s}{s+1} + 1 + \frac{s}{s^2+1} \\ &= \frac{s(s^2+1) + (s+1)(s^2+1) + s(s+1)}{(s+1)(s^2+1)} \\ &= \frac{s^3+s + s^3+s+s^2+1 + s^2+s}{(s+1)(s^2+1)} \\ &= \frac{2s^3 + 2s^2 + 3s + 1}{(s+1)(s^2+1)} \\ &= \frac{2[s^3 + s^2 + \frac{3}{2}s + \frac{1}{2}]}{(s+1)(s^2+1)} \end{aligned}$$

$\Phi = s^3 + s^2 + \frac{3}{2}s + \frac{1}{2}$ as obtained earlier! ✓
 \Rightarrow hence same poles & ts ✓

Gain =

$s=0$


(short inds, open cap)

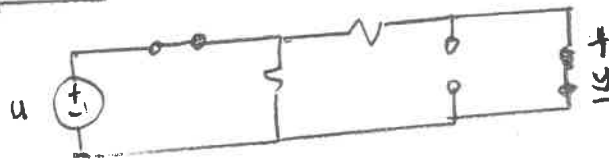

$\Rightarrow y=0 \Rightarrow H(0)=0$ (agrees with Φ obtained earlier) ✓

$s=\infty$

(open inds, short cap)

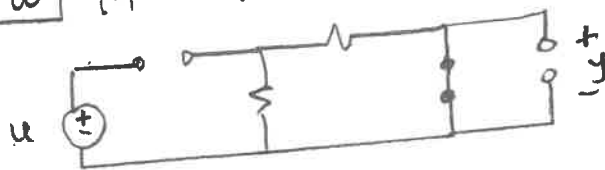

$\Rightarrow y=0 \Rightarrow H(\infty)=0$ (agrees with Φ obtained earlier) ✓




Problem # 8

Determine & plot $|H(j\omega)|$, $\angle H(j\omega)$

20/21

(all $R=L=C=1$)

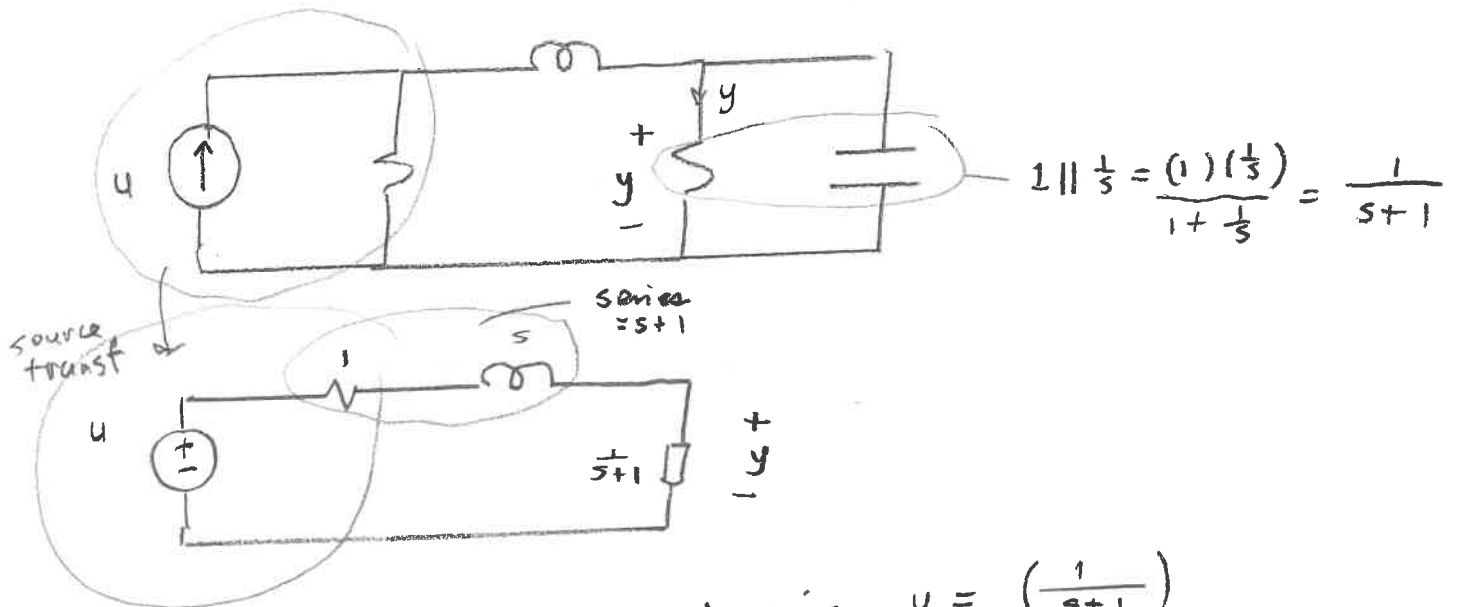

\Rightarrow By voltage division $H = \frac{y}{u} = \frac{(\frac{1}{s+1})}{s+1 + \frac{1}{s+1}}$

$= \frac{1}{(s+1)^2 + 1}$

$H(s) = \frac{1}{s^2 + 2s + 2}$

$H(j\omega) = \frac{1}{2 - \omega^2 + j2\omega}$

$|H(j\omega)| = \frac{1}{\sqrt{(2 - \omega^2)^2 + 4\omega^2}}$

Note: This is what I use to plot $|H(j\omega)|$ & $\angle H(j\omega)$


$H(0) = \frac{1}{2} = \frac{1}{2} e^{j0^\circ}$

$H(j\sqrt{2}) = \frac{1}{j\sqrt{2}} = \frac{1}{\sqrt{2}} e^{-j90^\circ}$

$H(s) \xrightarrow{s \text{ large}} \frac{1}{s^2}$

$|H(j\infty)| = 0 \quad \angle H(j\infty) = -180^\circ$

Visualize Denominator:


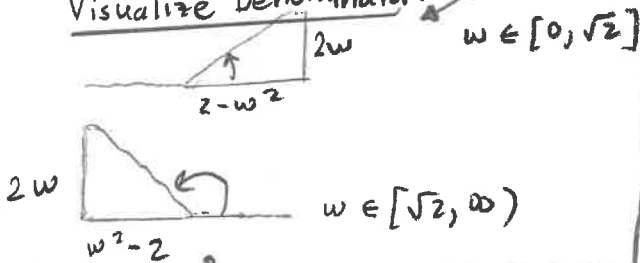


$\angle H(j\omega) = \begin{cases} -\tan^{-1}(\frac{2\omega}{2 - \omega^2}) & \omega \in [0, \sqrt{2}] \\ -[180^\circ - \tan^{-1}(\frac{2\omega}{\omega^2 - 2})] & \omega \in [\sqrt{2}, \infty) \end{cases}$

$H(0) = \frac{1}{2} \rightarrow$

$|H(j\sqrt{2})| = \frac{1}{2\sqrt{2}}$

$|H(j\infty)| = 0$

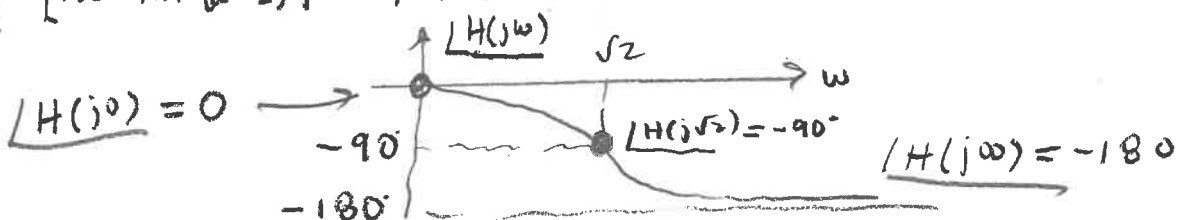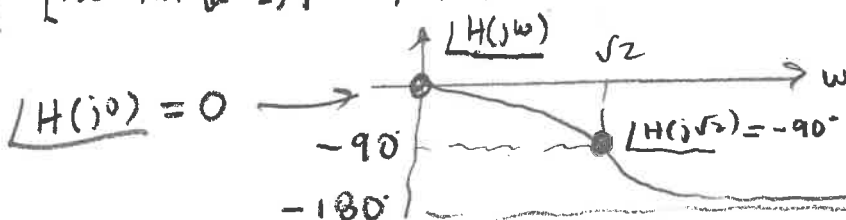


Problem # 8

21/21


It's Always Good to Check $\frac{1}{s+1}$ (series)

Check:

Φ , poles, $t_s =$ set $u=0 \Rightarrow$

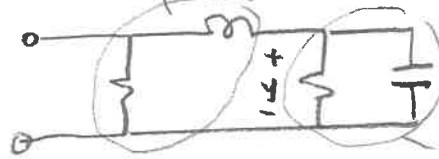

$$||| \frac{1}{s} = \frac{\frac{1}{s}}{1 + \frac{1}{s}} = \frac{1}{s+1}$$

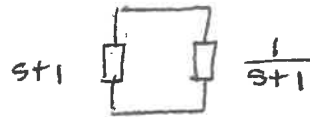

$$Z = s+1 + \frac{1}{s+1} = \frac{(s+1)^2 + 1}{s+1} = \frac{s^2 + 2s + 2}{s+1}$$


$\Rightarrow \Phi = s^2 + 2s + 2$ (agrees with what was obtained earlier!)

\Rightarrow hence same poles, t_s ! ✓

Gains:

$s=0$

(short ind, open cap)

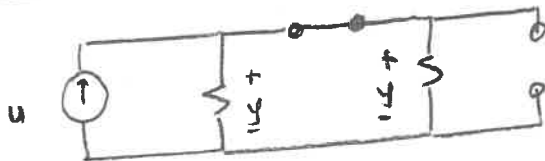


KCL

$$u = 2y \Rightarrow y = \frac{1}{2}u \Rightarrow H(0) = \frac{1}{2}$$

agrees with H obtained earlier!

$s=\infty$

(open ind, short cap)

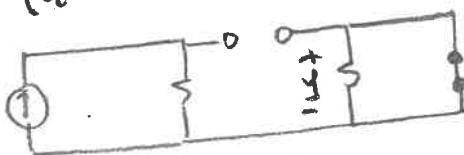

KVL

$$y = 0 \Rightarrow H(\infty) = 0$$

agrees with H obtained earlier!



EEE202

Final Exam

Fri 4-26-24

8 Problems (5+3)

(17 pages follow)

EXAM RULES


- 1) One 8.5" x 11" sheet permitted;
otherwise closed books, closed notes, open minds!
- 2) Scientific calculator is permitted; no computers and no phone!
- 3) **NO PHONES !!!**
Phones should not be visible at all!
A visible phone will result in a zero grade for the exam!
- 4) Write FULL NAME legibly on each page provided.
- 5) **PLEASE SHOW ALL WORK !!!**
This is essential to receive partial credit!
- 6) Please do not submit multiple answers. You must pick an answer!!
- 7) Write your solutions on the sheets provided.
No other paper/sheets/pages should be used!
- 8) Clearly label voltages and currents on the circuits provided.
- 9) Use the variables provided!
No additional variables should be used!
- 10) Unreadable work will receive NO CREDIT.
- 11) Please place important equations and answers within boxes as we have done in lecture.
- 12) Please be careful with your algebra, signs, etc.
- 13) Please turn in your solutions to me at the end of the period!
- 14) **PLEASE DO NOT CHEAT !!!**

Problem #1

Determine $H_{1,2}$, diff eq, t_s , y_{ss} , y_e

Compute $|H_i(j\omega)| \rightarrow \angle H_i(j\omega)$, ($i=1,2$),

(all $R=L=C=1$)

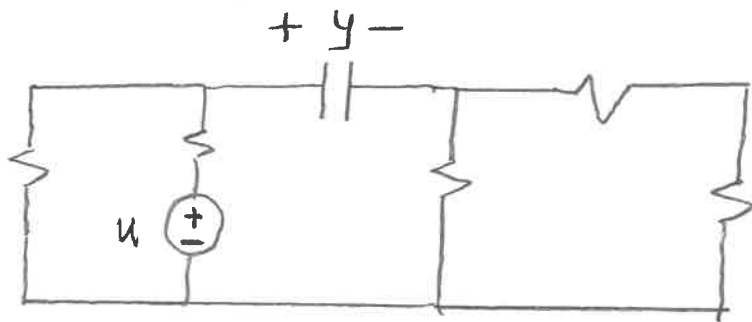


$$u = 10 - 7 \cos\left(\frac{1}{2}t + 45^\circ\right)$$

Problem # 1

Problem # 2

Determine poles, t_s , $H_1(0)$, $H_2(0)$, $H_1(\infty)$, $H_2(\infty)$.


(all $R=L=C=1$)

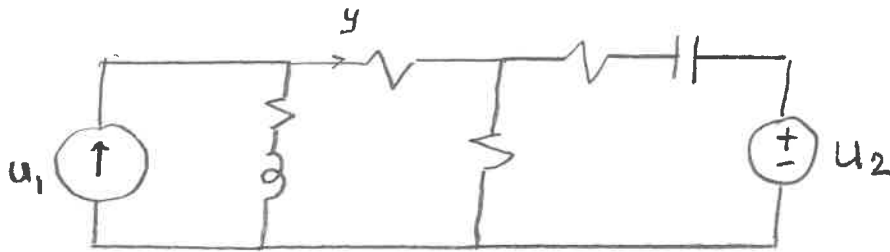

Problem #2

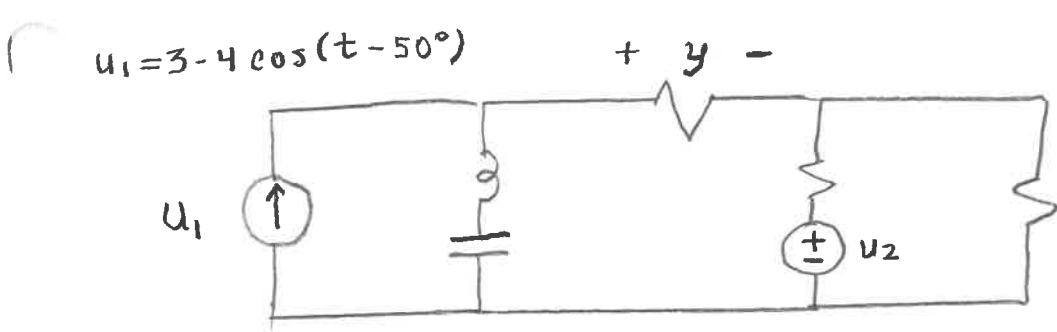Problem #3

Determine $H_{1,2}$, t_s , diff eq, y_{ss} (all $R=L=C=1$)




Problem # 3

Problem # 4

Determine H , diff eq, y , y_{ss} (all $R=L=C=1$)

$$u(t) = 10 + \cos t$$

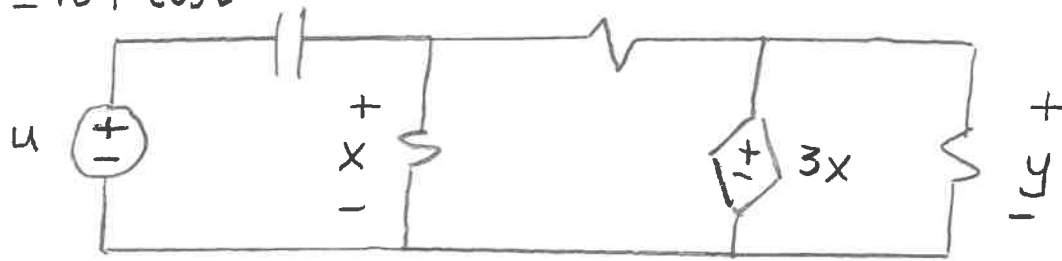

Problem # 4

Problem # 5

Determine t_s , y_{ss} , y

$$H(s) = \frac{(s+0.01)(s^2 + s + 1)}{(s+2)(s^2 + 8s + 25)(s^2 - 2s + 4)}$$

$$u = -5 - 6 \cos(0.01t - 45^\circ) + 7 \sin(100t + 60^\circ)$$


Note: compute all coefficients associated with constants & sinusoids in y .
show how to compute coefficients associated with instabilities in y .

Problem # 5

Problem #6

Determine an s-domain Thevenin equivalent at y
(specify Z_{th} & V_{th} !)

(all $R=L=C=1$)

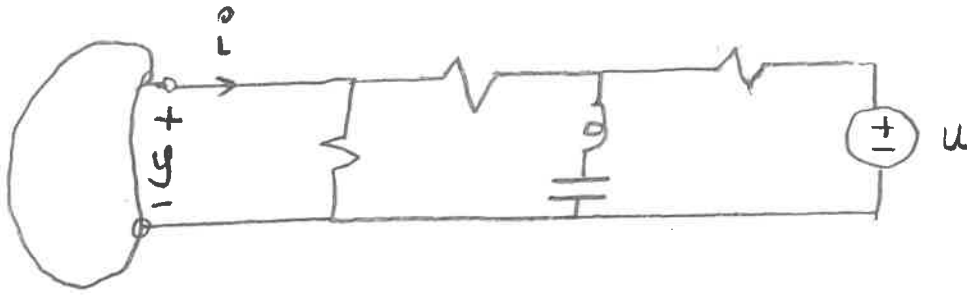


Problem # 6

Problem #7

Determine H , y_{ss} , t_s .

Compute all coefficients in y_{ss} approximately!

(all $R=L=C=1$)

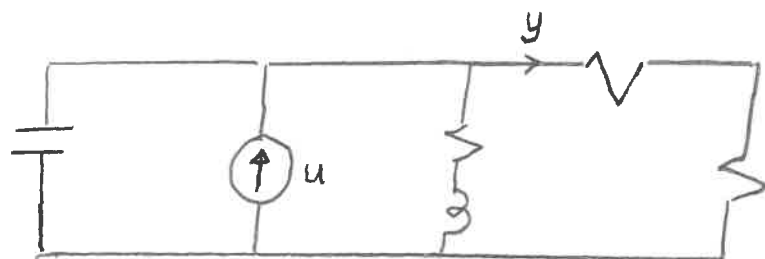


$$u = -7 - 8 \cos(\sqrt{\frac{3}{2}} t - 30^\circ) - 9 \sin(100t + 53^\circ)$$

Problem # 7

Problem # 8

Determine & plot $|H(j\omega)| \approx \underline{|H(j\omega)|}$

(all $R=L=C=1$)

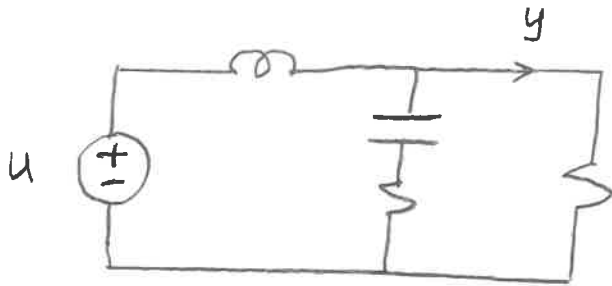

Problem # 8

EEE 202
Final Exam

Fri 4-26-24

Solutions


(pages 10-200)
follow

(20 pages follow)

Problem # 1

Determine $H_{1,2}$, diff eq, t_s , y_{ss} , y .

Compute $|H_i(j\omega)| \approx |H_i(j\omega)|$ ($i=1,2$).

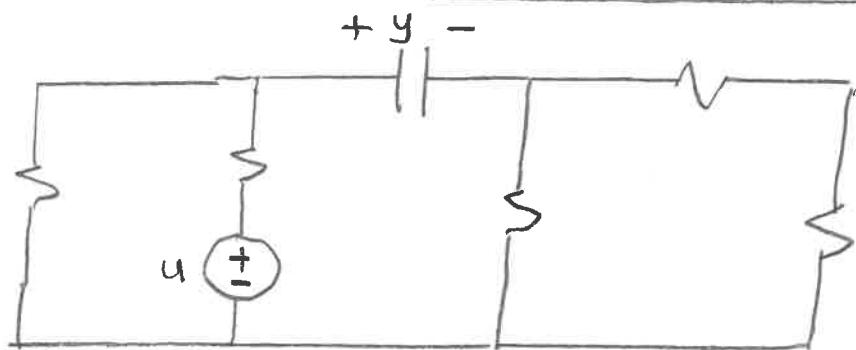

(all $R=L=C=1$)


$$u = 10 - 7 \cos\left(\frac{6}{7}t + 45^\circ\right)$$

solution:


(Note: Above circuit will be stable since it only has R's & C's)

MOTF

$$y_{ss} = 10 H(0) - 7 |H(j\frac{6}{7})| \cos\left(\frac{6}{7}t + 45^\circ + \angle H(j\frac{6}{7})\right)$$

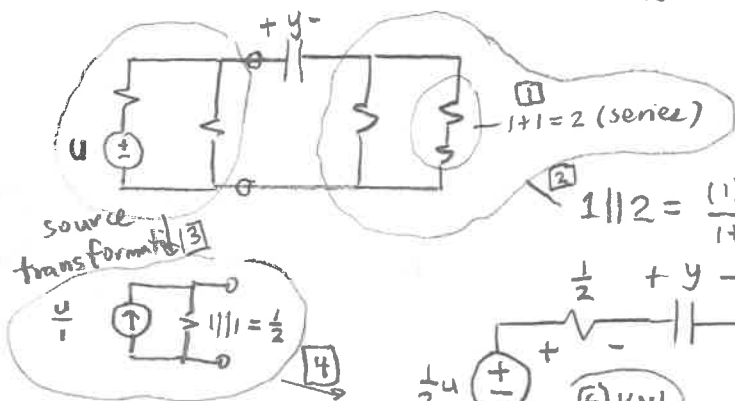
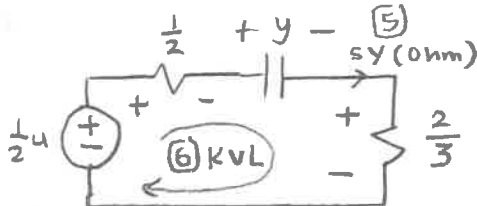
$$1 \parallel 2 = \frac{(1)(2)}{1+2} = \frac{2}{3} \text{ (parallel)}$$



⑥ KVL:

$$\begin{aligned} \frac{1}{2}u &= \frac{1}{2}sy + y + \frac{2}{3}sy \\ &= y \left[\frac{1}{2}s + 1 + \frac{2}{3}s \right] \\ &= y \left[\frac{7}{6}s + 1 \right] \\ &= y \frac{7}{6} \left[s + \frac{6}{7} \right] \end{aligned}$$

$$H(j\omega) = \frac{\frac{3}{7}}{\frac{6}{7} + j\omega}$$

$$y = \left[\frac{\frac{3}{7}}{s + \frac{6}{7}} \right] u$$

$$\begin{aligned} H(0) &= \frac{3}{6} = \frac{1}{2} \\ H(j\frac{6}{7}) &= \frac{\frac{3}{7}}{\frac{6}{7}(1+j1)} = \frac{\frac{1}{2}}{\sqrt{2}e^{j45^\circ}} = \frac{1}{2\sqrt{2}}e^{-j45^\circ} \end{aligned}$$

$$|H(j\omega)| = \frac{\frac{3}{7}}{\sqrt{\omega^2 + \left(\frac{6}{7}\right)^2}}$$

$$\begin{aligned} y + \frac{6}{7}y &= \frac{3}{7}u \quad |H(j\frac{6}{7})| \angle H(j\frac{6}{7}) = -45^\circ \\ t_s &= \frac{5}{|Re pole|} = \frac{5}{1 - \frac{6}{7}} = \frac{35}{6} \text{ sec} \end{aligned}$$

$$\angle H(j\omega) = \angle_{top} - \angle_{bottom} = 0 - \tan^{-1}\left(\frac{\omega}{6/7}\right)$$

Problem # 1

Recall =

$$M \leftrightarrow \frac{M}{s}$$

$$|M| \cos(\omega_0 t + \angle M) \leftrightarrow |M| \left[\frac{\cos \angle M s - \omega_0 \sin \angle M}{s^2 + \omega_0^2} \right]$$

$\frac{1}{\sqrt{2}}$

$$u(t) = 10 - 7 \cos\left(\frac{6}{7}t + 45^\circ\right) \leftrightarrow U(s) = \frac{10}{s} - 7 \left[\frac{\cos 45^\circ s - \frac{6}{7} \sin 45^\circ}{s^2 + \left(\frac{6}{7}\right)^2} \right]$$

$$= \frac{\text{some numerator}}{s(s^2 + \left(\frac{6}{7}\right)^2)} \leftarrow \begin{array}{l} \text{you do} \\ \text{algebra} \\ \text{at home!} \end{array}$$

$$Y = H U = \left[\frac{\frac{3}{7}}{s + \frac{6}{7}} \right] \frac{\text{Some numerator}}{s(s^2 + \left(\frac{6}{7}\right)^2)} = \frac{A}{s} + \frac{B}{s + \frac{6}{7}} + \left[\frac{C}{s - j\frac{6}{7}} + * \right]$$

$$\Rightarrow y = A + B e^{-\frac{6}{7}t} + 2|C| \cos\left(\frac{6}{7}t + \angle C\right)$$


y_{ss} - computed earlier!

$$\Rightarrow A = \lim_{s \rightarrow 0} s Y = s H(s) \frac{10}{s} \Big|_{s=0}$$

$$= 10 \times H(0) \quad \left[\begin{array}{l} \text{agrees with} \\ \text{MOTF!!!} \end{array} \right]$$

$$= 10 \left(\frac{1}{2} \right)$$

Enough for
an exam

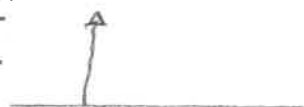

$$C = \lim_{s \rightarrow j\frac{6}{7}} (s - j\frac{6}{7}) Y(s)$$

$$B \text{ can be found via: } B = \lim_{s \rightarrow -\frac{6}{7}} (s + \frac{6}{7}) Y(s)$$

Lets find C:

$$C = \lim_{s \rightarrow j\frac{6}{7}} (s - j\frac{6}{7}) Y(s) = (s - j\frac{6}{7}) H(s) \left[\frac{10}{s} - \frac{7}{\sqrt{2}} \left[\frac{s - \frac{6}{7}}{s^2 + \left(\frac{6}{7}\right)^2} \right] \right] \Big|_{s=j\frac{6}{7}}$$

$$= H(s) \left[-\left(\frac{1}{\sqrt{2}}\right) \left(\frac{s - \frac{6}{7}}{s + j\frac{6}{7}} \right) \right] \Big|_{s=j\frac{6}{7}}$$

$$= \ominus \frac{7}{\sqrt{2}} H(j\frac{6}{7}) \frac{j\frac{6}{7} - \frac{6}{7}}{j^2 \left(\frac{6}{7}\right)^2}$$

$$= \left(1 e^{j180^\circ} \right) \frac{7}{\sqrt{2}} H(j\frac{6}{7})$$

$$\begin{array}{l} \cancel{\sqrt{2} e^{j135^\circ}} \quad \begin{array}{c} \sqrt{2} \quad 135^\circ \\ 45^\circ \end{array} \\ \frac{-1+j1}{j2} = 2 e^{j90^\circ} \quad \frac{2}{j2} \end{array}$$

Problem #1


$$\begin{aligned}
 C &= 1 e^{j180^\circ} \cdot \frac{7}{\sqrt{2}} |H(j\frac{6}{7})| e^{j/H(j\frac{6}{7})} \cdot \frac{\sqrt{2} e^{j135^\circ}}{2 e^{j90^\circ}} \\
 &= \frac{7}{2} |H(j\frac{6}{7})| e^{j[\underbrace{H(j\frac{6}{7})}_{\uparrow 45^\circ} + 135^\circ - 90^\circ + 180^\circ]}
 \end{aligned}$$

From the above $A \approx C$, we get the following for y_{ss} :

$$\begin{aligned}
 y_{ss} &= A + 2|C| \cos(\frac{6}{7}t + \angle C) \\
 &= 10 H(0) + 2\left(\frac{7}{2}\right) |H(j\frac{6}{7})| \cos(\frac{6}{7}t + 45^\circ + \underbrace{H(j\frac{6}{7})}_{+180^\circ}) \\
 &\stackrel{\updownarrow}{=} 10 H(0) - 7 |H(j\frac{6}{7})| \cos(\frac{6}{7}t + 45^\circ + \underbrace{H(j\frac{6}{7})}_{+180^\circ})
 \end{aligned}$$



used $\cos(x \pm 180^\circ) = -\cos x$

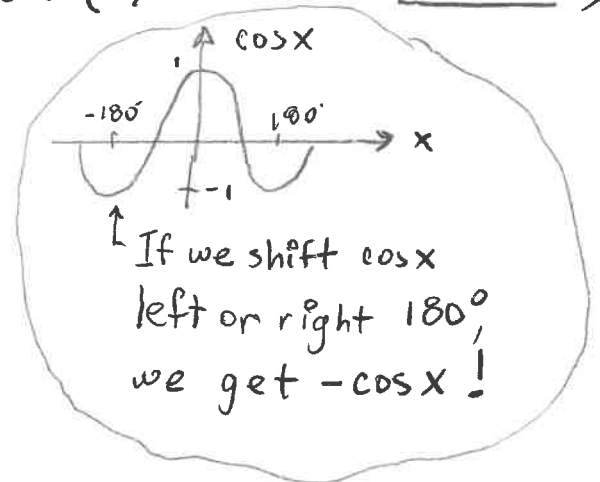This y_{ss} is precisely what was written above - 1st line; exploiting MOTF!



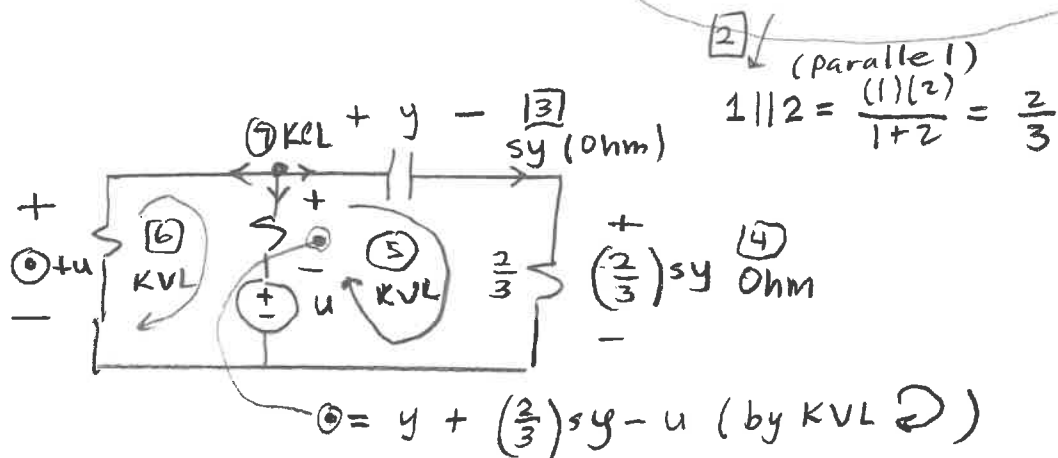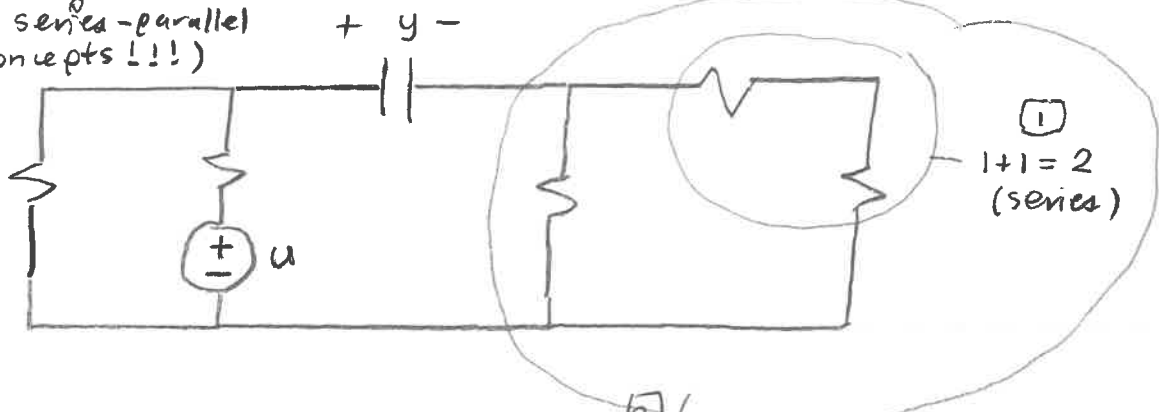Problem # 1

Lets derive H without source transformations:
(I will use series-parallel concepts!!!)



(7) KCL

$$\left[\frac{[1 + \frac{2}{3}s]y - u + u}{1} \right] + \left[\frac{[1 + \frac{2}{3}s]y - u}{1} \right] + sy = 0$$

$$\Rightarrow y \left[1 + \frac{2}{3}s + 1 + \frac{2}{3}s + s \right] = u$$

$$\Rightarrow y \frac{7}{3} \left[s + \frac{6}{7} \right] = u$$

$$\Rightarrow y = \left[\frac{\frac{3}{7}}{s + \frac{6}{7}} \right] u$$


H which is what we obtained earlier

40/280

... what if we don't use source transformations
or series-parallel concepts--- then what do we do? ...

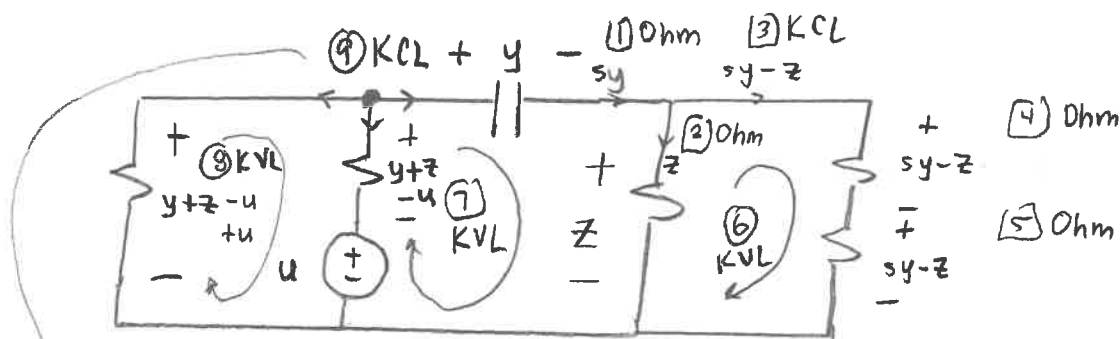Problem # 1

If we don't use source transformations or series-parallel concepts, then we are forced to introduce a variable z as follows:



$$\textcircled{6} \text{ KVL: } z = (s y - z) + (s y - z)$$

$$\Rightarrow 3z = 2s y$$

$$\Rightarrow z = \frac{2}{3} s y$$

$$\textcircled{9} \text{ KCL:}$$

$$\left(\frac{y+z}{1} \right) + \left(\frac{y+z-u}{1} \right) + (s y) = 0$$

using our 2 eqs in 2 unknowns (y, z)

$$y + \frac{2}{3} s y + y + \frac{2}{3} s y - u + s y = 0$$

$$\Rightarrow y \left[\underbrace{1 + \frac{2}{3} s + 1 + \frac{2}{3} s + s}_{\frac{7}{3} s + 2} \right] = u$$

$$\Rightarrow y \frac{7}{3} \left[s + \frac{6}{7} \right] = u$$

$$\Rightarrow y = \left[\frac{\frac{3}{7}}{s + \frac{6}{7}} \right] u$$

H - agrees with what we got earlier





... lets do a characteristic eq. & gain check ---

Problem # 1

It is always good to perform "CHECKS!"

Φ Check: Set $u = 0$

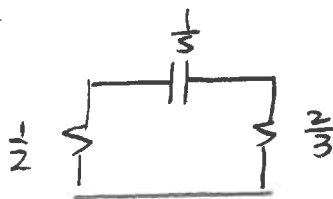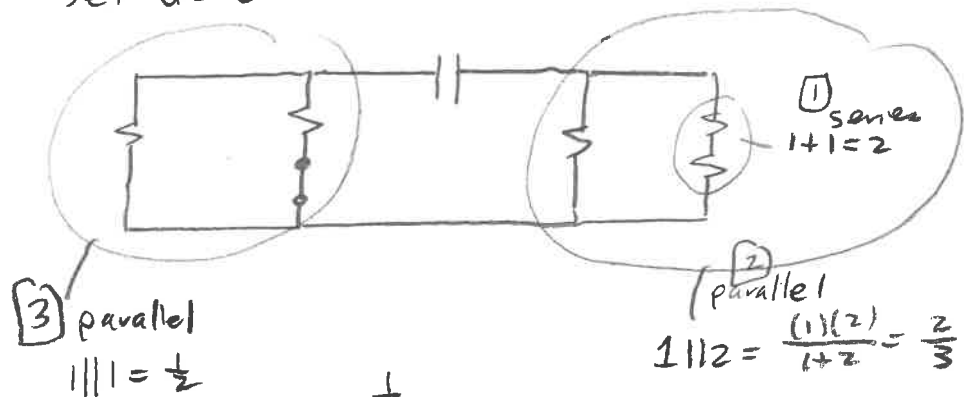

$$\begin{aligned} Z &= \frac{1}{2} + \frac{2}{3} + \frac{1}{s} \\ &= \frac{3+4}{6} + \frac{1}{s} \\ &= \frac{7}{6} + \frac{1}{s} \\ &= \frac{7s+1}{s} \\ &= \frac{7}{6} \left[s + \frac{6}{7} \right] \end{aligned}$$


$$\Rightarrow \Phi = s + \frac{6}{7}$$

which agrees with what we got earlier!

Gain Checks:

Be Careful:
 $y \neq 0$ for $s=0$

$s=0$ (cap open)

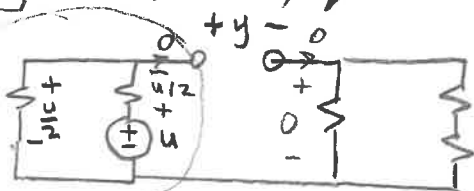

voltage divider

$$\Rightarrow y \equiv -\frac{u}{2} + u - 0 = \frac{1}{2}u \rightarrow H(0) = \frac{1}{2}$$

$s=\infty$ (Cap shorted)

$$\Rightarrow y = 0$$


$$\Rightarrow H(\infty) = 0$$

These gains agree with $H = \frac{3/7}{s+6/7}$

Problem #2

Determine poles, t_s , $H_1(0)$, $H_2(0)$, $H_1(\infty)$, $H_2(\infty)$.

(all $R=L=C=1$)

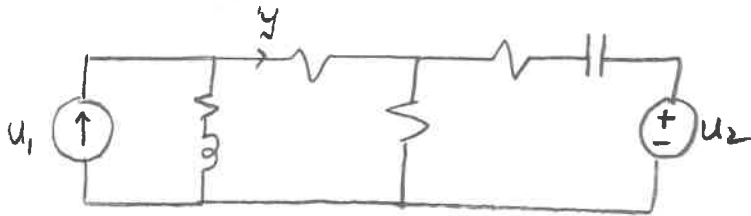

Φ , poles, t_s : set $u_1=0$ (open) & $u_2=0$ (shorted)

$$\Rightarrow s+1 \parallel \frac{s+1}{s} = \frac{(1)(\frac{s+1}{s})}{1 + \frac{s+1}{s}} = \frac{s+1}{s+s+1} = \frac{s+1}{2s+1}$$

$$\Rightarrow Z = (s+1) + (1) + \left(\frac{s+1}{2s+1} \right)$$

$$= s+2 + \left(\frac{s+1}{2s+1} \right)$$

$$= \frac{(s+2)(2s+1) + s+1}{2s+1}$$

$$= \frac{2s^2 + s + 4s + 2 + s + 1}{2s+1}$$

$$= \frac{2s^2 + 6s + 3}{2s+1}$$

$$= 2 \left[\frac{s^2 + 3s + \frac{3}{2}}{2s+1} \right]$$

$$\Rightarrow \Phi = s^2 + 3s + \frac{3}{2} = 0 \quad \text{Characteristic polynomial}$$

$$\Rightarrow \text{poles} = \frac{-3 \pm \sqrt{9-6}}{2} = \frac{-3 \pm \sqrt{3}}{2}$$

$$= \frac{-3+\sqrt{3}}{2}, \frac{-3-\sqrt{3}}{2}$$

$$= -\sigma_1, -\sigma_2$$

fast pole \uparrow $-\sigma_2$ $-\sigma_1$ \uparrow slow pole $\Rightarrow t_s = \frac{5}{\sigma_1} = \frac{5}{\frac{3-\sqrt{3}}{2}}$

70/280

Problem # 2


$$\Rightarrow t_s = \frac{10}{3 - \sqrt{3}}$$

Gains

$$Z_L = sL = 0$$

$$Z_C = \frac{1}{sC} = \infty$$

$s = 0$ (Ind shorted, Cap open)

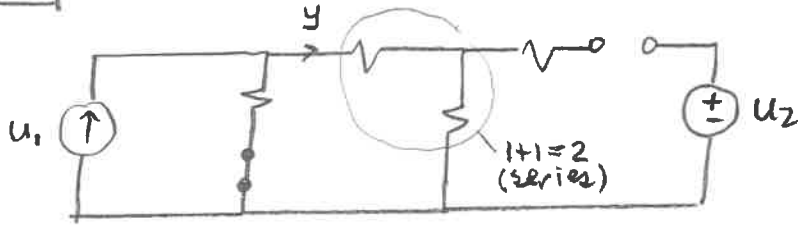

KCL

$$\Rightarrow u_1 = \left(\frac{2y}{1} \right) + (y)$$

$$= 3y$$

$$\Rightarrow y = \frac{1}{3} u_1 + 0 u_2$$

$$H_1(0) = \frac{1}{3} \quad H_2(0) = 0$$

$$Z_L = sL = \infty$$

$$Z_C = \frac{1}{sC} = 0$$

$s = \infty$ (Ind open, Cap shorted)



$$\Rightarrow y = u_1$$





$$= (1) u_1 + (0) u_2$$

$$H_1(\infty) = 1 \quad H_2(\infty) = 0$$

Now lets do all of the above using our
bread & butter KVL, KCL, Ohm ----
or clever circuit analysis

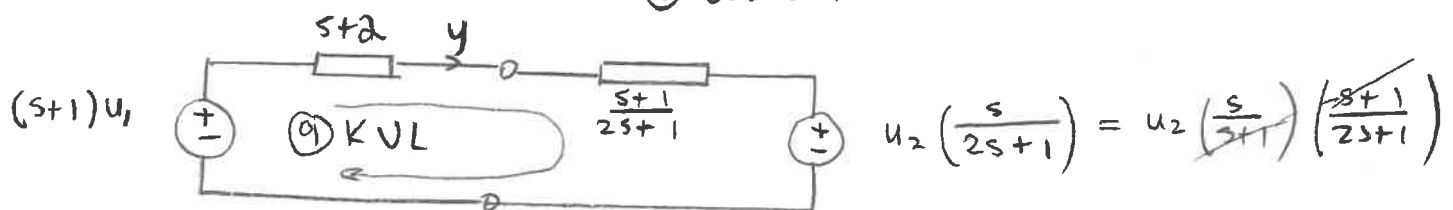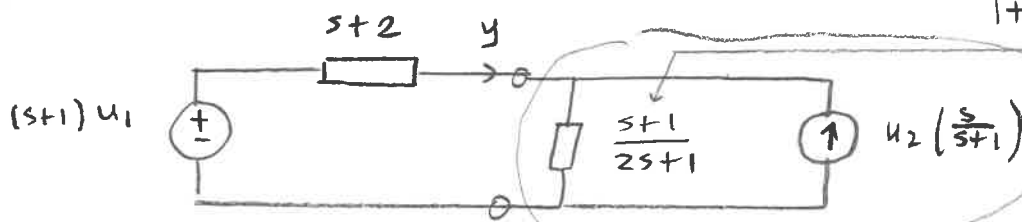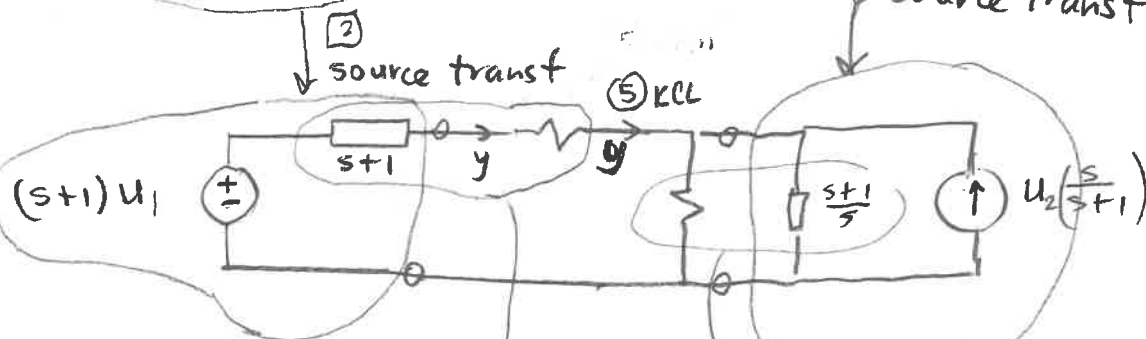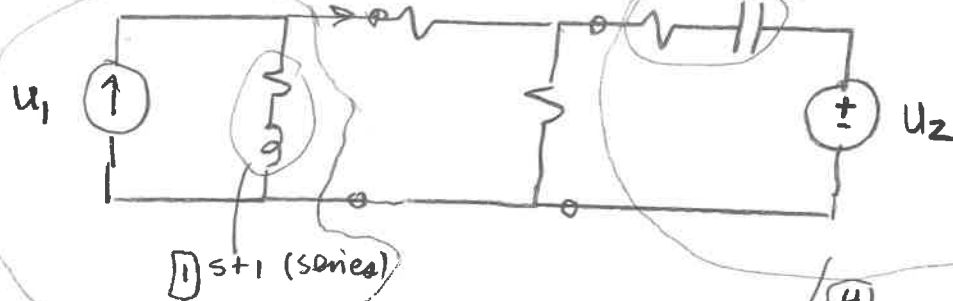Problem #2

1st some clever circuit analysis: (3) series $1 + \frac{1}{s} = \frac{s+1}{s}$



$$(9) \text{ KVL: } (s+1)u_1 = (s+2)y + \left(\frac{s+1}{2s+1}\right)y + u_2\left(\frac{s}{2s+1}\right)$$

$$\xRightarrow{\text{algebra}} y \left[s+2 + \frac{s+1}{2s+1} \right] = (s+1)u_1 + \left(\frac{-s}{2s+1}\right)u_2$$

$$\Rightarrow y \left[(s+2)(2s+1) + s+1 \right] = (s+1)(2s+1)u_1 + (-s)u_2$$

$$2s^2 + s + 4s + 2$$

Problem # 2

$$\Rightarrow y [2s^2 + s + 4s + 2 + s + 1] = (s+1)(2s+1)u_1 + (-s)u_2$$

$$\Rightarrow y [2s^2 + 6s + 2] = (s+1)(2s+1)u_1 + (-s)u_2$$

$$= 2 \left(s^2 + 3s + \frac{3}{2} \right)$$

$$\Rightarrow y = \left[\frac{\frac{1}{2}(s+1)(2s+1)}{s^2 + 3s + \frac{3}{2}} \right] u_1 + \left[\frac{-s}{s^2 + 3s + \frac{3}{2}} \right] u_2$$

\uparrow
 H_1

\uparrow
 H_2

Note: $\Phi = s^2 + 3s + \frac{3}{2}$ as obtained earlier!

$$H_1(0) = \frac{(\frac{1}{2})(1)(1)}{\frac{3}{2}} = \frac{1}{3}$$

$$H_2(0) = 0 \quad " \quad " \quad " !$$

$$H_1(\infty) = \left(\frac{1}{2}\right)(2) = 1$$


$$H_2(\infty) = 0 \quad " \quad " \quad " !$$



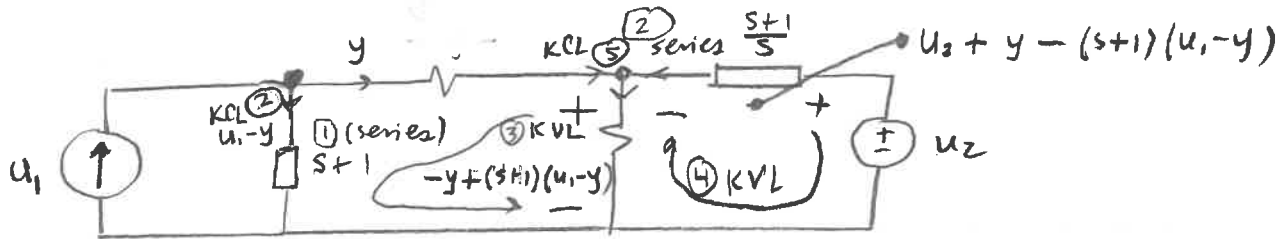Problem # 2

Now lets not be clever.

Lets just use KVL, KCL, Ohm (+ series concepts) =



$$\textcircled{5} \text{ KCL } \rightarrow \left(y \right) + \left[u_2 + y - (s+1)(u_1 - y) \right] \frac{s}{s+1} = \left(\frac{-y + (s+1)(u_1 - y)}{1} \right)$$

$$\Rightarrow y \left[1 + \frac{s}{s+1} + s + 1 + s+1 \right] = u_1 [s+1 + s] - u_2 \left[\frac{s}{s+1} \right]$$

$$\Rightarrow y \left[\frac{s}{s+1} + 2s+3 \right] = u_1 [2s+1] - u_2 \left[\frac{s}{s+1} \right]$$

$$\Rightarrow y \left[s + (2s+3)(s+1) \right] = u_1 (s+1)(2s+1) - s u_2$$


$$\Rightarrow y \left[2s^2 + 6s + 3 \right] = (s+1)(2s+1)u_1 + (-s)u_2$$

$$\Rightarrow y = \left[\frac{(s+1)(s+\frac{1}{2})}{s^2 + 3s + \frac{3}{2}} \right] u_1 + \left[\frac{-\frac{1}{2}s}{s^2 + 3s + \frac{3}{2}} \right] u_2$$

which agrees with what we obtained earlier!



Problem #3

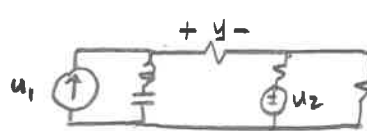

Determine $H_{1,2}$, t_s , diff eq, y_{ss}

(all $R=L=C=1$)

Since our circuit consists of R 's, L 's, C 's & indep sources, we know the circuit must be stable (i.e. all poles in left half s -plane = $\text{Re } s < 0$)

Given this, it follows that

$$y_{ss} = y_{1ss} + y_{2ss}$$

Recall:

$$u_1 = 3 - 4 \cos(t - 50^\circ)$$


$$u_2 = -8 - 2 \sin(t + 30^\circ) + 200 \cos(100t + 95^\circ)$$

↓ MOTF


$$y_{1ss} = 3 H_1(0) - 4 |H_1(j1)| \cos(t - 50^\circ + \angle H_1(j1))$$

$$y_{2ss} = -8 H_2(0) - 2 |H_2(j1)| \sin(t + 30^\circ + \angle H_2(j1)) + 200 |H_2(j100)| \cos(100t + 95^\circ + \angle H_2(j100))$$

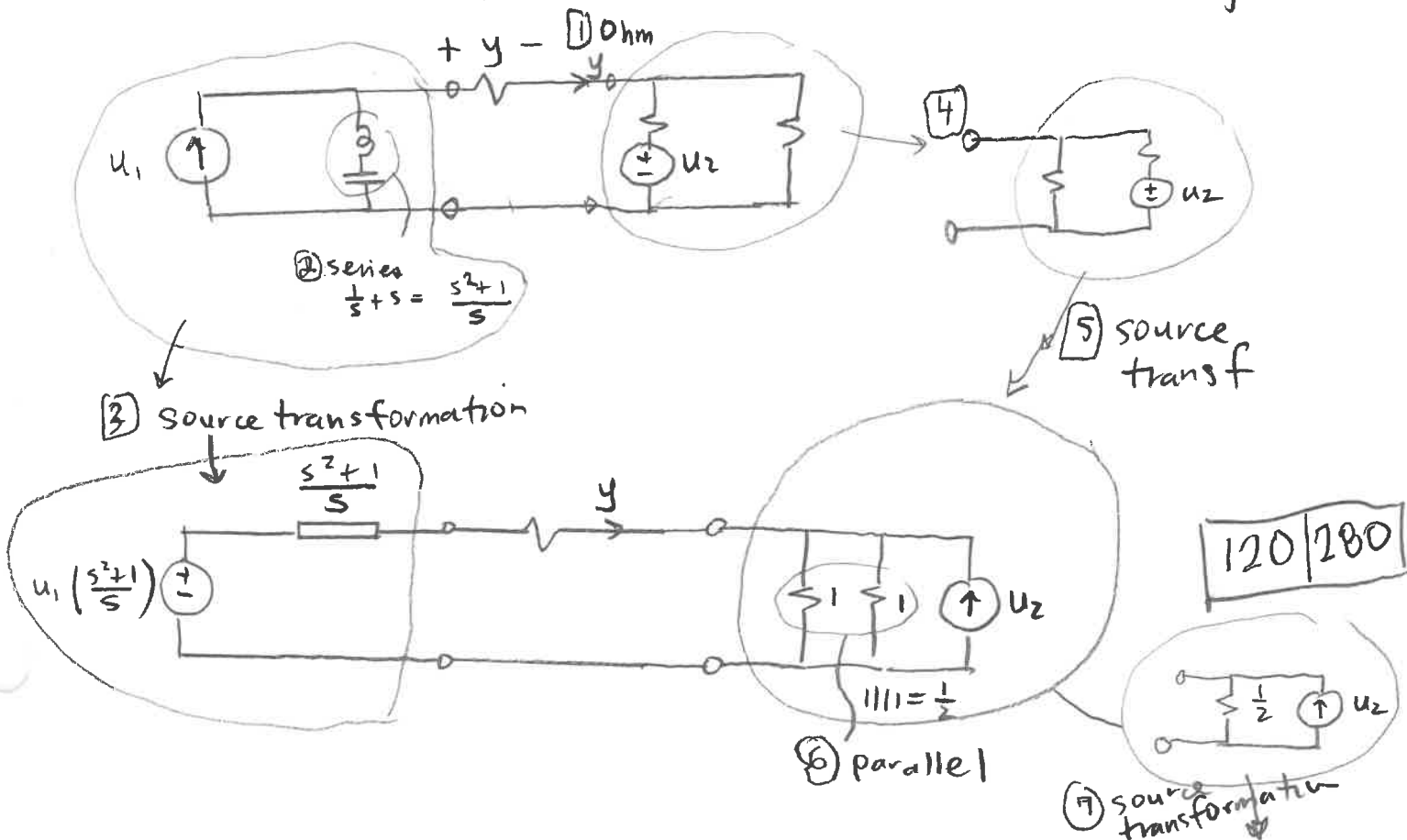Now let's find $H_{1,2}$... 1st by some "slightly clever" circuit analysis ...



Problem # 3

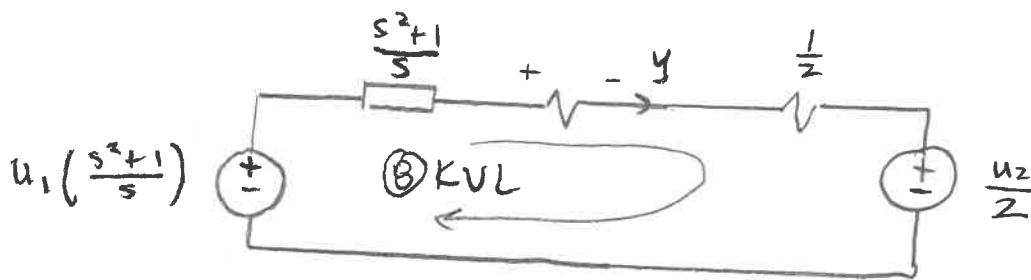

$$\textcircled{8} \text{ KVL} = u_1 \left(\frac{s^2+1}{s} \right) = \left(\frac{s^2+1}{s} \right) y + y + \frac{1}{2} y + \frac{u_2}{2}$$

$$\Rightarrow y \left[\frac{s^2+1}{s} + \left(1 + \frac{1}{2} \right) \right] = \left[\frac{s^2+1}{s} \right] u_1 + \left[-\frac{1}{2} \right] u_2$$

$$\Rightarrow y \left[s^2 + 1 + \frac{3}{2} s \right] = [s^2 + 1] u_1 + \left[-\frac{1}{2} s \right] u_2$$

$$\Rightarrow y = \left[\frac{s^2+1}{s^2 + \frac{3}{2}s + 1} \right] u_1 + \left[\frac{-\frac{1}{2}s}{s^2 + \frac{3}{2}s + 1} \right] u_2$$

$$\Rightarrow \ddot{y} + \frac{3}{2} \dot{y} + y = \ddot{u}_1 + \dot{u}_1 - \frac{1}{2} \dot{u}_2$$

$$\Rightarrow \Phi = s^2 + \frac{3}{2}s + 1 = 0 \quad (\text{characteristic polynomial})$$

$$\Rightarrow \text{poles} = \frac{-\frac{3}{2} \pm \sqrt{\left(\frac{9}{4} - 4(1) \right) - \frac{16}{4}}}{2} = \frac{-\frac{3}{2} \pm j\frac{\sqrt{7}}{2}}{2}$$

$$\Rightarrow t_s = \frac{5}{|\text{Re poles}|}$$

$$= \frac{5}{\frac{3}{4}} = \frac{20}{3} \text{ sec}$$

Gains Needed in yss:

$$H_1(0) = 1 \quad H_1(j1) = 0 \leftarrow \text{since } H_1 \text{ has zero at } \pm j1$$


$$H_2(0) = 0 \leftarrow \text{since } H_2 \text{ has a zero at } s=0$$

$$H_2(j1) = \frac{-\frac{1}{2} j^1}{-1 + j\frac{3}{2} + 1} = \frac{-j\frac{1}{2}}{j\frac{3}{2}} = -1 = \textcircled{1} e^{j180^\circ} \quad |H_2(j1)| = \boxed{130/280}$$

$$H_2(j100) \approx \frac{-\frac{1}{2}s}{s^2} = \frac{-\frac{1}{2}}{s} \Big|_{s=j100} = \frac{\frac{1}{2} e^{j180}}{100 e^{j90}} = \frac{1}{200} e^{j90^\circ} \quad |H_2(j100)| = \boxed{130/280}$$

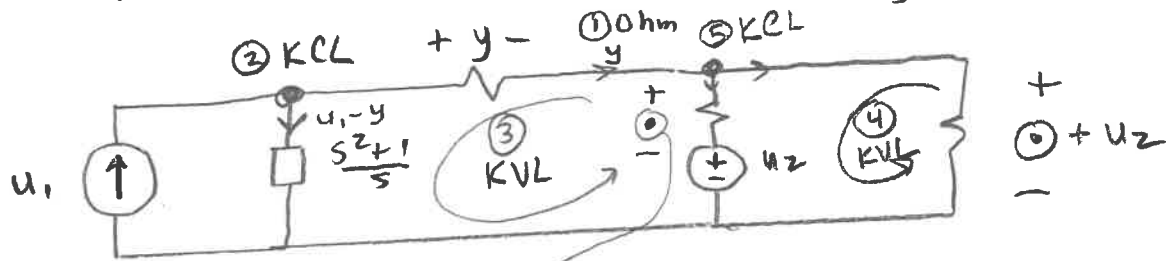Problem #3

Now let's just use straight KVL, KCL, Ohm =
(with ind & cap in series: $z_{lc} = \frac{1}{s} + s = \frac{s^2+1}{s}$)



$$\textcircled{3} = -y + \left(\frac{s^2+1}{s}\right)(u_1-y) - u_2$$

$$\textcircled{5} \text{ KCL} = \begin{array}{c} \rightarrow \quad \rightarrow \\ \downarrow \end{array}$$

$$(y) = \left(\frac{-y + \left(\frac{s^2+1}{s}\right)(u_1-y) - u_2}{1} \right) + \left(\frac{-y + \left(\frac{s^2+1}{s}\right)(u_1-y) - u_2}{1} \right)$$

$$\Rightarrow y \left[\underbrace{1+1}_{\text{circled}} + \frac{s^2+1}{s} + \underbrace{1}_{\text{circled}} + \frac{s^2+1}{s} \right] = \left[\frac{s^2+1}{s} + \frac{s^2+1}{s} \right] u_1 - u_2$$

$$\Rightarrow y \left[2\left(\frac{s^2+1}{s}\right) + 3 \right] = \left[2\left(\frac{s^2+1}{s}\right) \right] u_1 - u_2$$

$$\Rightarrow y \left[\underbrace{2s^2+2+3s}_{2(s^2+\frac{3}{2}s+1)} \right] = \left[2(s^2+1) \right] u_1 - s u_2$$

$$\Rightarrow y = \underbrace{\left[\frac{s^2+1}{s^2+\frac{3}{2}s+1} \right]}_{H_1} u_1 + \underbrace{\left[\frac{-\frac{1}{2}s}{s^2+\frac{3}{2}s+1} \right]}_{H_2} u_2$$

- this agrees with what we obtained earlier!




140 | 280

Problem # 3

It's Always Good to perform CHECKS!

Lets now do a characteristic polynomial & gain check!

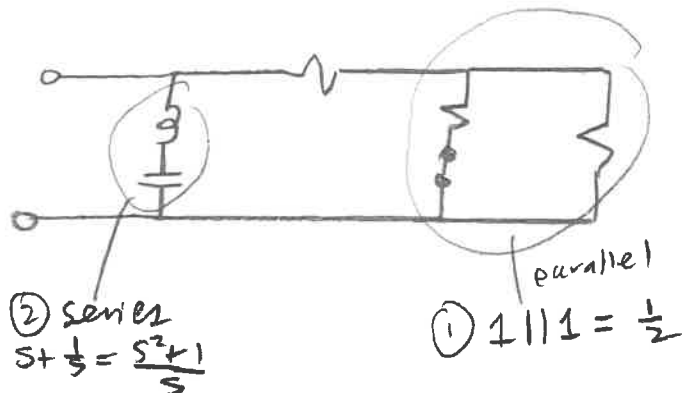Φ check = set $u_1 = 0$ (open)
 $u_2 = 0$ (short)



$$\Rightarrow Z = \frac{s^2 + 1}{s} + 1 + \frac{1}{2}$$

$$= \frac{s^2 + 1}{s} + \frac{3}{2}$$

$$= \frac{s^2 + 1 + \frac{3}{2}s}{s}$$

$$\Rightarrow \Phi = s^2 + \frac{3}{2}s + 1$$


just as we got earlier! ✓

Gain Checks:

$s = 0$ (short ind, open cap)

$s = \infty$ (open ind, short cap)

either way, we have u_1

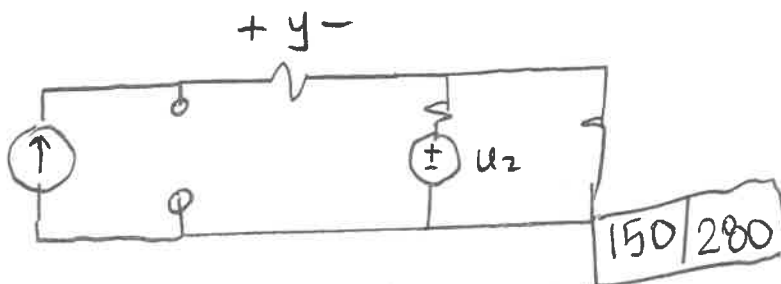

$$\Rightarrow \begin{matrix} H_1(0) = H_1(\infty) = 1 \\ H_2(0) = H_2(\infty) = 0 \end{matrix}$$


\Rightarrow these agree with $H_{1,2}$ obtained earlier!

oo
o
o

Problem # 4

Determine H , diff eq, y , y_{ss}

(all $R=L=C=1$)

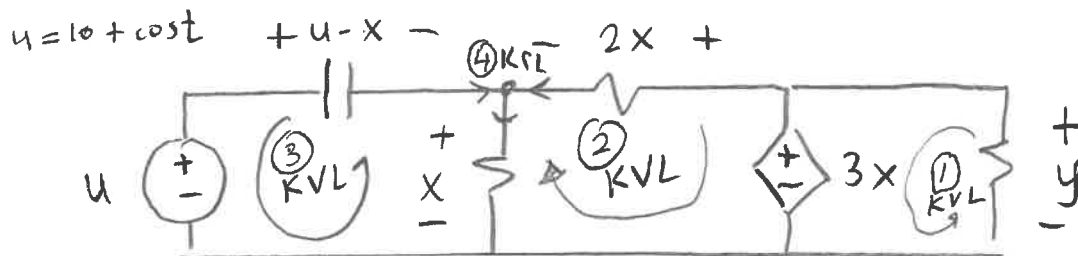

1st note that $y = 3x$ (by KVL)

④ KCL =

$$[s(u-x)] + \left[\frac{2x}{1} \right] = \left[\frac{x}{1} \right]$$

or $x = \frac{1}{3}y$

2 eqs in 2 unknowns (y, x)

but it is easy to get rid of x since $x = \frac{1}{3}y$

$$\Rightarrow su = x[s - 2 + 1]$$

$$= x[s - 1]$$

$$= \frac{1}{3}y[s - 1]$$


$$\Rightarrow y = \left[\frac{3s}{s-1} \right] u$$

$$H \Rightarrow \dot{y} - y = 3\dot{u}$$

Note that $H(0) = 0$!
since H has a zero at $s=0$

why? At dc, cap is open & u has no impact on y

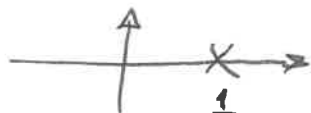Note: system H is unstable with a pole in the RHP (right half s -plane) at $s=1$



$$u = 10 + \cos t$$

$$\bar{U} = \frac{10}{s} + \frac{s}{s^2+1} = \frac{10(s^2+1) + s^2}{s(s^2+1)} = \frac{11s^2 + 10}{s(s^2+1)}$$

Problem #4

$$Y = HU = \left[\frac{3s}{s-1} \right] \left[\frac{11s^2 + 10}{s(s^2 + 1)} \right]$$

$$= \left[\frac{3}{s-1} \right] \left[\frac{11s^2 + 10}{s^2 + 1} \right]$$

\uparrow
 $(s-j1)(s+j1)$

$$= \frac{A}{s-1} + \left[\frac{B}{s-j1} + \frac{C}{s+j1} \right]$$

$$y = A e^t + 2|B| \cos(t + \angle B) = y_{ss}$$

unstable
growing
exponential
(dominant in
steady state!)

$y_{ss} \approx A e^t$
after a sufficiently
long time

since nothing in
y goes away
as $t \rightarrow \infty$!

from MOTF

this must equal

$$|H(j1)| \cos(t + \angle H(j1))$$

due to sinusoidal
component of u

$$u_{\text{sinusoid}} = \cos t$$

$$A = \lim_{s \rightarrow 1} (s-1) Y$$

$$= \cancel{(s-1)} \left[\frac{3s}{\cancel{s-1}} \right] \left[\frac{11s^2 + 10}{s(s^2 + 1)} \right] \Big|_{s=1}$$

$$= 3(1) \frac{[11 + 10]}{(1)(1+1)}$$

$$= 3 \frac{(21)}{2}$$

$$\Rightarrow B = \frac{|H(j1)|}{2} e^{j \angle H(j1)}$$

$$H(j1) = \frac{3j1}{j1-1} = \frac{j3}{-1+j1}$$

$$= \frac{3 e^{j90^\circ}}{\sqrt{2} e^{j135^\circ}}$$

$$= \frac{3}{\sqrt{2}} e^{j(90-135^\circ)} = \frac{3}{\sqrt{2}} e^{-j45^\circ}$$

Note: Since $u = 10 + \cos t$

from MOTF

From MOTF \Rightarrow Partial fraction Expansion (PFE)
concepts we know

$$y_{ss} = (10 H(0) + |H(j1)| \cos(t + \angle H(j1))) + A e^t$$

zero since $H(0) = 0$ [since H has a zero at $s=0$]


170/280

Problem #4

Lets do a gain check for $s = \infty$:

$$\sqrt{Z_C = \frac{1}{sC} = 0}$$

$s = \infty$ (Cap is shorted)

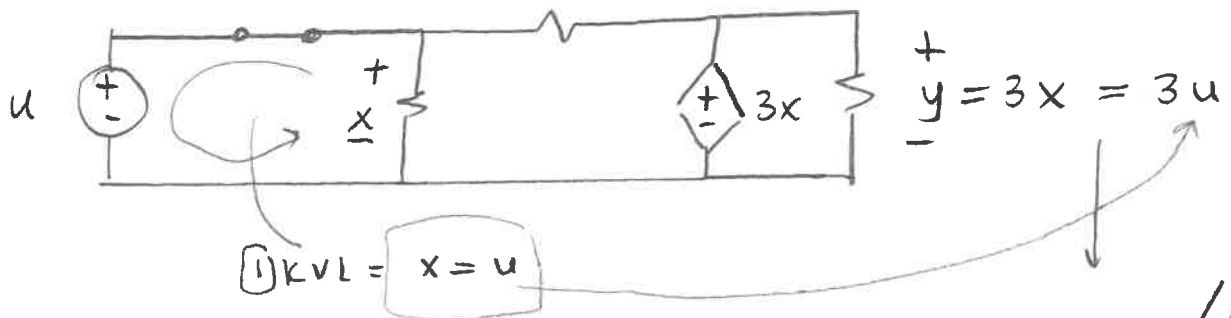

$$H(\infty) = 3$$



- this agrees with

$$H = \frac{3s}{s-1}$$

obtained earlier!

Lets do a characteristic eq check:

Set $u = 0$

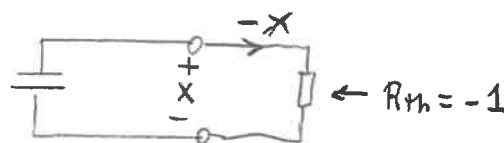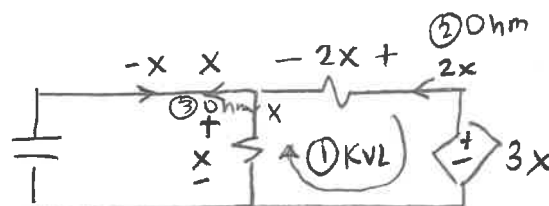

$$Z = \frac{1}{s} - 1 = \frac{1-s}{s} = -\left[\frac{s-1}{s}\right]$$

$$\Rightarrow \Phi = s - 1$$

as obtained earlier!

Note:

It is always good to perform "Checks"!




Problem # 5

Determine t_s , y_{ss} , y

$$H(s) = \frac{(s+0.01)(s^2+s+1)}{(s+2)(s^2+8s+25)(s^2-2s+4)}$$

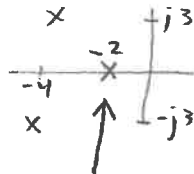poles: -2 (stable), $-4 \pm j3$ (stable), $1 \pm j\sqrt{3}$ (unstable)



slow pole at $s = -2 \Rightarrow t_s = \frac{5}{|-2|} = \frac{5}{2} = 2.5 \text{ sec}$

$$u = -5 - 6 \cos(0.01t - 45^\circ) + 7 \sin(100t + 60^\circ)$$

From MTF

$$y_{ss} = -5 H(0) - 6 |H(j0.01)| \cos(0.01t - 45^\circ + \angle H(j0.01)) + 7 |H(j100)| \sin(100t + 60^\circ + \angle H(j100))$$

+ growing exponential sinusoidal instability $2 |D| e^t \cos(\sqrt{3}t + \angle D)$

from partial fraction expansion ideas

$$H(0) = \frac{(0.01)(1)}{(2)(25)(4)}$$

dominant in steady state

$$H(j0.01) \approx \frac{(j0.01 + 0.01)(1)}{(2)(25)(4)} = \frac{(1)(0.01)}{(2)(25)(4)}$$

$$\sqrt{2} e^{j45^\circ} (1+j1)$$

$$= \frac{(1)(0.01)\sqrt{2}}{(2)(25)(4)}$$

$$e^{j45^\circ}$$

$$H(j100) \approx \frac{s^3}{s^5} = \frac{1}{s^2} \Big|_{s=j100} = \frac{1}{(100e^{j90^\circ})^2} = 10^{-4} e^{-j180^\circ}$$

$$|H(j100)| \approx 10^{-4}$$

$$\angle H(j100) \approx -2(90) = -180^\circ$$

Now lets find y --

190/280

Problem # 5

$$u = -5 - 6 \cos(0.01t - 45^\circ) + 7 \sin(100t + 60^\circ)$$

$$\Downarrow$$

$$U = -\frac{5}{s} - \frac{Us + \square}{s^2 + 10^{-4}} + \frac{Us + \square}{s^2 + 10^4}$$

$$= \frac{\text{some numerator}}{s(s^2 + 10^{-4})(s^2 + 10^4)} \leftarrow \text{you do this algebra at home!}$$

$$Y = HU = \left[\frac{(s+0.01)(s^2+s+1)}{(s+2)(s^2+8s+25)(s^2-2s+4)} \right] \left[\frac{\text{some numerator}}{s(s^2+10^{-4})(s^2+10^4)} \right]$$

$$= \frac{A}{s} + \frac{B}{s+2} + \left[\frac{C}{s+4-j3} + \frac{C^*}{s+4+j3} \right] + \left[\frac{D}{s-j0.01} + \frac{D^*}{s+j0.01} \right] + \left[\frac{E}{s-j100} + \frac{E^*}{s+j100} \right]$$

$$y = \underbrace{A}_{-5H(0)} + Be^{-2t} + 2|C|e^{-4t}\cos(\beta t + \angle C) + 2|D|e^t\cos(\sqrt{3}t + \angle D)$$

$$+ 2|E|\cos(0.01t + \angle E) + 2|F|\cos(100t + \angle F)$$

growing instability (dominates) yss

These 3 terms are in yss (along with instability)

The 3 terms were found earlier using MOTF!

$$\Rightarrow A = \lim_{s \rightarrow 0} sY = \cancel{s} H\left(\frac{-5}{s}\right) \Big|_{s=0} = -5H(0)$$

$$D = \lim_{s \rightarrow 1+j\sqrt{3}} (s-1-j\sqrt{3})Y$$

$$E = \lim_{s \rightarrow j0.01} (s-j0.01)Y$$

$$F = \lim_{s \rightarrow j100} (s-j100)Y$$

$$-6|H(j0.01)|\cos(0.01t - 45^\circ + \angle H(j0.01)) + 7|H(j100)|\sin(100t + 60^\circ - \angle H(j100))$$

$$= \left(6|H(j0.01)|\cos(0.01t - 45^\circ + \angle H(j0.01) - 180^\circ) + 7|H(j100)|\cos(100t + 60^\circ - \angle H(j100) - 90^\circ) \right)$$


From these $E = \frac{6|H(j0.01)|}{2} e^{j(-45^\circ + \angle H(j0.01) - 180^\circ)}$

$$F = \frac{7|H(j100)|}{2} e^{j(60^\circ - \angle H(j100) - 90^\circ)}$$


200 280

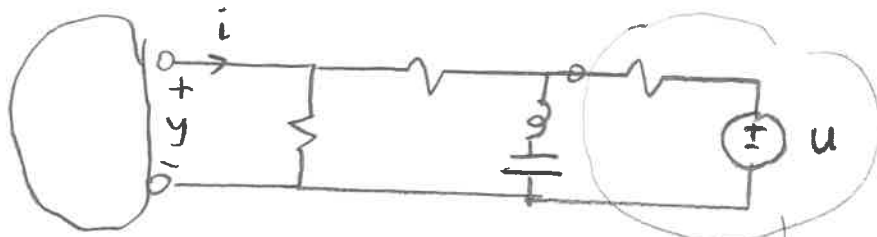Problem # 6

Determine an s-domain Thevenin equivalent at y- (specify: Z_{th} & V_{th} !) (all $R=L=C=1$)




source transformation

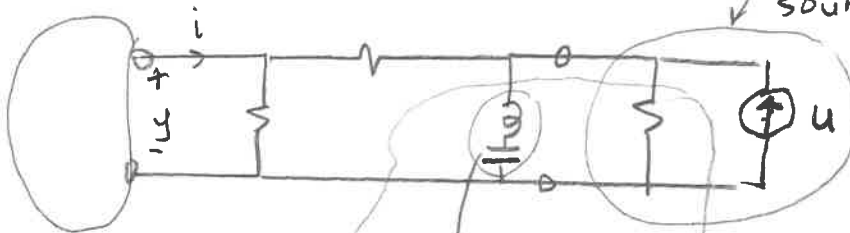

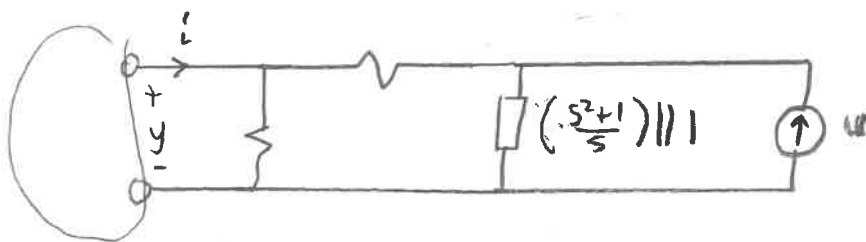
(2) series $s + \frac{1}{s} = \frac{s^2 + 1}{s}$

$$\left(\frac{s^2+1}{s}\right) \parallel 1 = \frac{\left(\frac{s^2+1}{s}\right)(1)}{\frac{s^2+1}{s} + 1} = \frac{s^2+1}{s^2+s+1}$$



$$1 + \left(\frac{s^2+1}{s}\right) \parallel 1 = 1 + \frac{s^2+1}{s^2+s+1} = \frac{s^2+s+1+s^2+1}{s^2+s+1} = \frac{2s^2+s+2}{s^2+s+1}$$
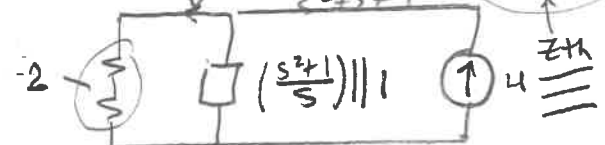
$$\Rightarrow Z_{th} = 1 \parallel \left[1 + \left(\frac{s^2+1}{s}\right) \parallel 1 \right] = 1 \parallel \frac{2s^2+s+2}{s^2+s+1} = \frac{2s^2+s+2}{s^2+s+1 + \frac{2s^2+s+2}{s^2+s+1}} = \frac{2s^2+s+2}{3s^2+2s+3}$$



$V_{th} = u \parallel i = 0$

current division


$$V_{th} = \left[\frac{\left(\frac{s^2+1}{s}\right) \parallel 1}{2 + \left(\frac{s^2+1}{s}\right) \parallel 1} \right] u$$

$$= \left[\frac{\frac{s^2+1}{s^2+s+1}}{2 + \frac{s^2+1}{s^2+s+1}} \right] u = \left[\frac{s^2+1}{2s^2+2s+2+s^2+1} \right] u = \left[\frac{s^2+1}{3s^2+2s+3} \right] u$$

210/280

Problem #6

Solution via KVL, KCL, Ohm:

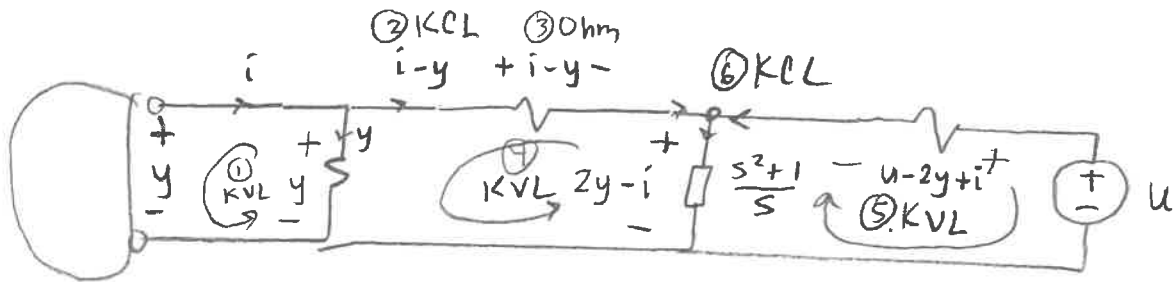

$$\textcircled{6} \text{KCL} = \left[(i-y) + \left(\frac{u-2y+i}{1} \right) \right] = (2y-i) \left(\frac{s}{s^2+1} \right)$$

$$\Rightarrow i \left[1 + 1 + \frac{s}{s^2+1} \right] + u = y \left[\quad \right]$$

$$\left[1 + 2 + \frac{2s}{s^2+1} \right]$$

$$\Rightarrow y \left[3 + \frac{2s}{s^2+1} \right] = \left[2 + \frac{s}{s^2+1} \right] i + u$$

$$\Rightarrow y [3s^2+3+2s] = [2s^2+2+s] i + (s^2+1)u$$

$$\Rightarrow y = \left[\frac{2s^2+s+2}{3s^2+2s+3} \right] i + \left[\frac{s^2+1}{3s^2+2s+3} \right] u$$

Z_{th}

V_{th}

Z_{th} & V_{th} here agree with that obtained on previous page




Problem #7

Determine H , y_{ss} , t_s

Compute all coefficients in y_{ss} approximately!



(all $R=L=C=1$)

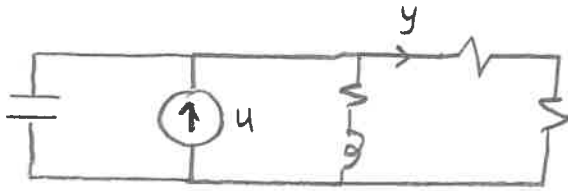

$$u = -7 - 8 \cos(\sqrt{\frac{3}{2}}t - 30^\circ) - 9 \sin(100t + 53^\circ)$$

solution: since ckt is stable \Rightarrow

$$y_{ss} = -7H(0) - 8|H(j\sqrt{\frac{3}{2}})|\cos(\sqrt{\frac{3}{2}}t - 30^\circ + \angle H(j\sqrt{\frac{3}{2}})) - 9|H(j100)|\sin(100t + 53^\circ + \angle H(j100))$$

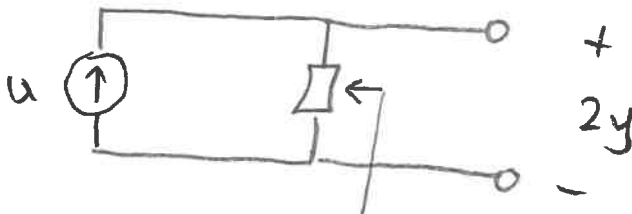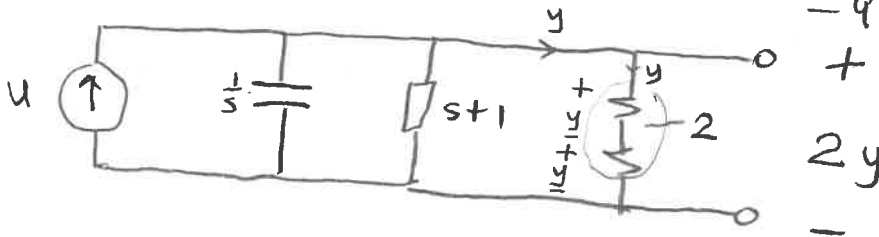

$$Z = (\frac{1}{s}) \parallel (s+1) \parallel (2)$$

Ohm \Rightarrow

$$2y = Zu = \left[\left(\frac{1}{s} \right) \parallel (s+1) \parallel (2) \right] u$$

$$y = \frac{1}{2} \left[\left(\frac{1}{s} \right) \parallel (s+1) \parallel 2 \right] u$$

H

$$H = \frac{\frac{1}{2}(s+1)}{s^2 + \frac{3}{2}s + \frac{3}{2}}$$

gains needed in $y_{ss} =$

$$H(0) = \frac{(\frac{1}{2})(1)}{(\frac{3}{2})} = \frac{1}{3}$$

$$H(j\sqrt{\frac{3}{2}}) = \frac{\frac{1}{2}(j\sqrt{\frac{3}{2}}+1)}{-\frac{3}{2} + j\frac{3}{2}\sqrt{\frac{3}{2}} + \frac{3}{2}} = \frac{\frac{1}{2}(1+j\sqrt{\frac{3}{2}})}{j\frac{3}{2}\sqrt{\frac{3}{2}}}$$

$$\frac{1}{s} \parallel (s+1) = \frac{\frac{s+1}{s}}{\frac{1}{s} + s+1} = \frac{s+1}{s^2+s+1}$$

$$\left[\frac{1}{s} \parallel (s+1) \right] \parallel 2 = \frac{2 \left[\frac{s+1}{s^2+s+1} \right]}{2 + \frac{s+1}{s^2+s+1}}$$

$$= \frac{2(s+1)}{2s^2 + 3s + 3}$$

$$= \frac{2(s+1)}{2[s^2 + \frac{3}{2}s + \frac{3}{2}]}$$

230/280

Note: $H(0) = 1/3$
 $H(\infty) = 0$

Problem # 7

$$H(j\sqrt{\frac{3}{2}}) = \frac{\frac{1}{2} (1 + j\sqrt{\frac{3}{2}})}{j \frac{3}{2} \sqrt{\frac{3}{2}}}$$

$$= \frac{\frac{1}{2} \sqrt{1 + \frac{3}{2}}}{\frac{3}{2} \sqrt{\frac{3}{2}}} e^{j \left(\tan^{-1} \left(\frac{\sqrt{\frac{3}{2}}}{1} \right) - 90^\circ \right)}$$

\uparrow
 $|H(j\sqrt{\frac{3}{2}})|$

$$H(j100) \cong \frac{\frac{1}{2} s}{s^2} = \frac{\frac{1}{2}}{s} \Big|_{s=j100} = \frac{1/2}{100 e^{j90^\circ}} = \frac{1}{200} e^{-j90^\circ}$$

$$|H(j100)| \cong \frac{1}{200}$$

$$\angle H(j100) \cong -90^\circ$$

Now lets get Φ , poles, t_s =

$$\Phi = s^2 + \frac{3}{2}s + \frac{3}{2} = 0$$

$$\Rightarrow \text{poles} = \frac{-\frac{3}{2} \pm \sqrt{\frac{9}{4} - 6}}{2} = \frac{-\frac{3}{2} \pm \sqrt{\frac{9}{4} - \frac{24}{4}}}{2} = \frac{-\frac{3}{2} \pm \sqrt{\frac{-15}{4}}}{2}$$

$$= -\frac{3}{4} \pm j \frac{\sqrt{15}}{4}$$

$$\Rightarrow t_s = \frac{5}{|\text{Re poles}|} = \frac{5}{\frac{3}{4}} = \frac{20}{3}$$


240/280

Lets do a characteristic poly & gain check ...

Problem # 7


It's always good to perform CHECKS!

I Check: Set $u=0$

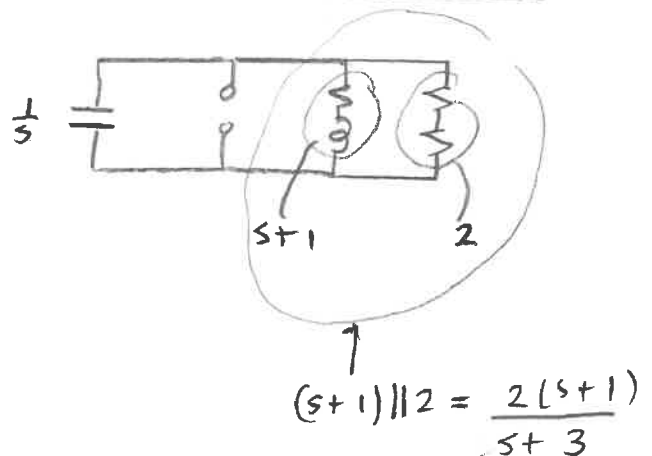

Gain Checks:-


$s=0$ (Cap open, Ind shorted)

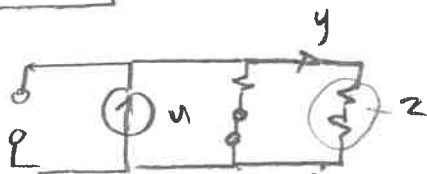

current division
 $y = \left(\frac{1}{1+2} \right) u = \frac{1}{3} u$

$\Rightarrow H(0) = \frac{1}{3}$

$s=\infty$ (Cap shorted, Ind open)

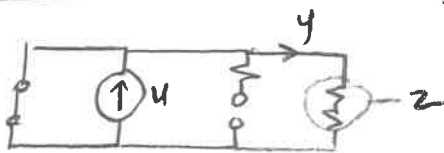

$\Rightarrow y=0$

$\Rightarrow H(\infty) = 0$

$$\Rightarrow Z = \frac{1}{s} + \frac{2(s+1)}{s+3}$$

$$= \frac{s+3 + 2(s+1)s}{s(s+3)}$$


$$= \frac{s+3 + 2s^2 + 2s}{s(s+3)}$$

$$= \frac{2s^2 + 3s + 3}{s(s+3)}$$

$$= 2 \left[\frac{s^2 + \frac{3}{2}s + \frac{3}{2}}{s(s+3)} \right]$$

$\Rightarrow \Phi = s^2 + \frac{3}{2}s + \frac{3}{2}$


all agree with what we got earlier!

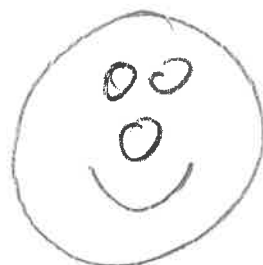

Problem # 8

Determine & plot $|H(j\omega)|$ & $\angle H(j\omega)$

(all $R=L=C=1$)

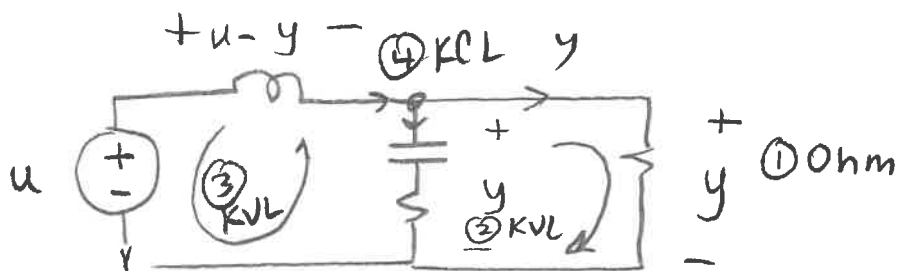

$$\textcircled{4} \text{ KCL} = \left(\frac{u-y}{s} \right) = \left(\frac{y}{\frac{1}{s} + 1} \right) + (y)$$

$$\frac{u}{s} = y \left[\frac{1}{s} + \frac{s}{s+1} + 1 \right]$$

$$(s+1)u = y \left[s+1 + s^2 + \frac{s(s+1)}{s^2+s} \right]$$

$$= y \left[2s^2 + 2s + 1 \right]$$

$$= y 2 \left[s^2 + s + \frac{1}{2} \right]$$

$$y = \left[\frac{\frac{1}{2} (s+1)}{s^2 + s + \frac{1}{2}} \right] u$$

$\uparrow H$

$$H(j\omega) = \frac{\frac{1}{2} (1+j\omega)}{\frac{1}{2} - \omega^2 + j\omega}$$

$\triangle \omega$
 $\frac{1}{2} - \omega^2$
 ω
 $\omega \in [0, \frac{1}{\sqrt{2}}]$
 $\omega \in [\frac{1}{\sqrt{2}}, \infty)$

$$|H(j\omega)| = \frac{\frac{1}{2} \sqrt{1+\omega^2}}{\sqrt{(\frac{1}{2} - \omega^2)^2 + \omega^2}}$$

$$\angle H(j\omega) = \tan^{-1}\left(\frac{\omega}{1}\right) - \begin{cases} \tan^{-1}\left(\frac{\omega}{\frac{1}{2}-\omega^2}\right) & \omega \in [0, \frac{1}{\sqrt{2}}] \\ 180 - \tan^{-1}\left(\frac{\omega}{\omega^2-\frac{1}{2}}\right) & \omega \in [\frac{1}{\sqrt{2}}, \infty) \end{cases}$$

260/280

Problem # 8

Note =

From $H(s) = \frac{\frac{1}{2}(s+1)}{s^2 + s + \frac{1}{2}}$

$$H(0) = 1 = 1e^{j0^\circ}$$



$$H(s) \stackrel{\text{large}}{\approx} \frac{\frac{1}{2}s}{s^2} = \frac{\frac{1}{2}}{s} \Rightarrow \begin{aligned} |H(j\infty)| &= 0 \\ \angle H(j\infty) &= -90^\circ \end{aligned}$$

$$\begin{aligned} H(j\sqrt{\frac{1}{2}}) &= \frac{\frac{1}{2}(1+j\sqrt{\frac{1}{2}})}{-\frac{1}{2} + j\sqrt{\frac{1}{2}} + \frac{1}{2}} \\ &= \frac{\frac{1}{2}(1+j\sqrt{\frac{1}{2}})}{j\sqrt{\frac{1}{2}}} \end{aligned}$$

$$= \left(\frac{\frac{1}{2} \sqrt{1+\frac{1}{2}}}{\sqrt{\frac{1}{2}}} \right) e^{j \left(\tan^{-1}\left(\frac{\sqrt{\frac{1}{2}}}{1}\right) - 90^\circ \right)}$$


$$\underline{|H(j\sqrt{\frac{1}{2}})|}$$

$$\begin{aligned} |H(j\sqrt{\frac{1}{2}})| &= \frac{1}{2} \sqrt{2+1} \\ &= \frac{\sqrt{3}}{2} \end{aligned}$$

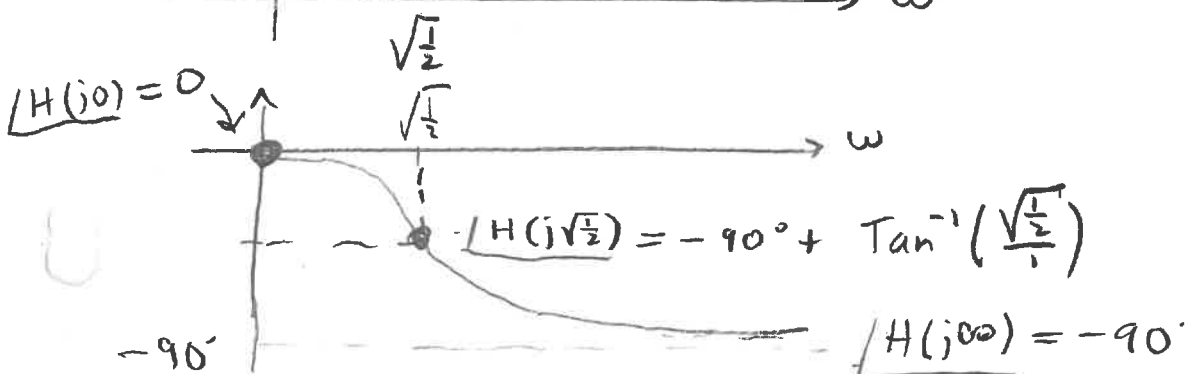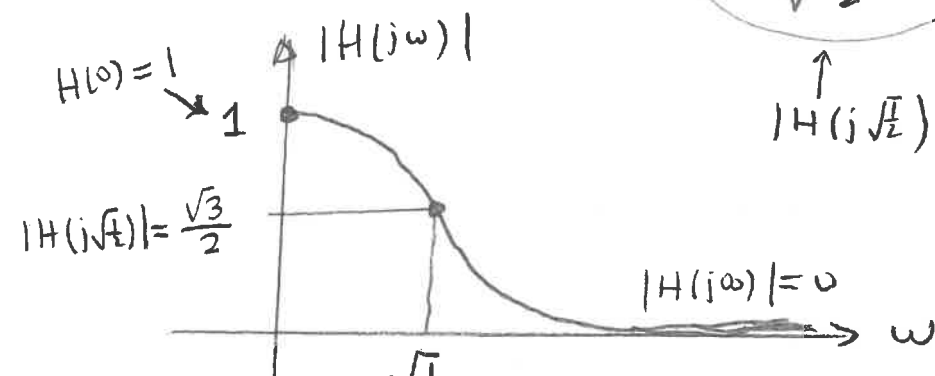

Problem # 8

Φ Check: Set $u=0$

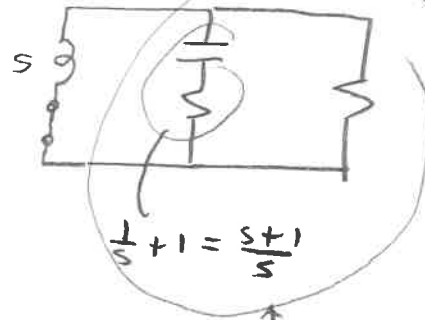

$$\frac{1}{s} + 1 = \frac{s+1}{s}$$

$$\left(\frac{s+1}{s}\right) \parallel 1 = \frac{\frac{s+1}{s}}{\frac{s+1}{s} + 1} = \frac{s+1}{2s+1}$$

$$\Rightarrow Z = s + \frac{s+1}{2s+1}$$

$$= \frac{2s^2 + s + s + 1}{2s+1}$$


$$= \frac{2s^2 + 2s + 1}{2s+1}$$

$$= 2 \left[\frac{s^2 + s + \frac{1}{2}}{2s+1} \right]$$

$$\Rightarrow \Phi = s^2 + s + \frac{1}{2}$$

Gain Checks:


$S=0$ (Ind shorted, cap open)

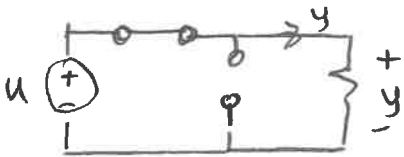

$$y = u$$

$$H(0) = 1$$

$S=\infty$ (Ind open, cap open)

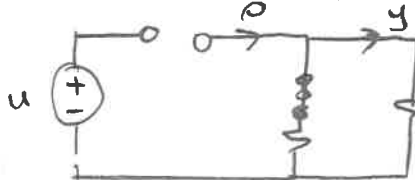

$$\Rightarrow y = 0$$

$$\Rightarrow H(\infty) = 0$$

All these agree with

$$H = \frac{\frac{1}{2}(s+1)}{s^2 + s + \frac{1}{2}}$$

obtained earlier!



280/280